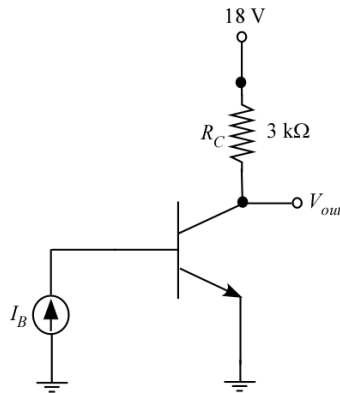


1 Given that the BJT in the figure below has a value of $\beta = 150$, find the output voltage, including dc and ac components, when

(a) $I_B = (20 + 10 \sin \omega t) \mu\text{A}$

(b) $I_B = (40 + 10 \sin \omega t) \mu\text{A}$

Compare the ac output voltages in (a) and (b), and explain any differences.



2 The short-circuit ac current gain from base to collector is defined as

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad \text{with } V_{CE} \text{ constant}$$

Taking ΔI_B as $10 \mu\text{A}$, use the characteristics of the figure below to evaluate b at $V_{CE} = +10 \text{ V}$ and

(a) $I_C = 1 \text{ mA}$

(b) $I_C = 2 \text{ mA}$

(c) $I_C = 3 \text{ mA}$

(d) $I_C = 4 \text{ mA}$

