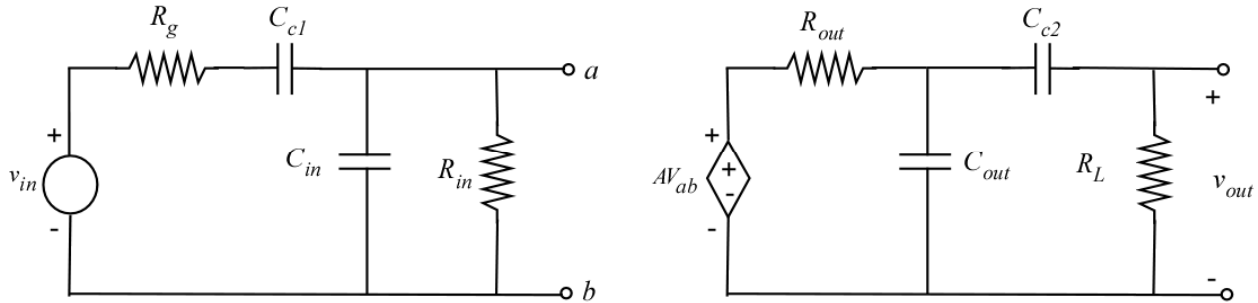


1. Write the frequency-dependent expression for voltage gain for the amplifier shown below at higher frequencies. Assume the following element values are used: $R_g = 200 \Omega$, $R_{in} = 12 \text{ k}\Omega$, $R_{out} = 3 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $C_{c1} = 5 \mu\text{F}$, $C_{c2} = 1 \mu\text{F}$, $C_{in} = 200 \text{ pF}$, and $C_{out} = 40 \text{ pF}$. The value of A is 160 V/V.



2. Plot the asymptotic frequency magnitude response for the gain

$$A = 42 \frac{3.2 + j \frac{f}{15}}{3.8 + j 0.00024 f}$$

3. Plot the asymptotic frequency magnitude response for the gain

$$A = 12 \frac{5 + j \frac{f}{10}}{\left(8 + j \frac{f}{45}\right) \left(2 + j \frac{f}{50,000}\right)}$$

4. Write the expression for voltage as a function of frequency for the response plotted in the figure. Calculate the upper 3-dB frequency.

