

# ECE 342

# Electronic Circuits

## Lecture 2


## Large and Small Signal Circuits

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jesa@Illinois.edu
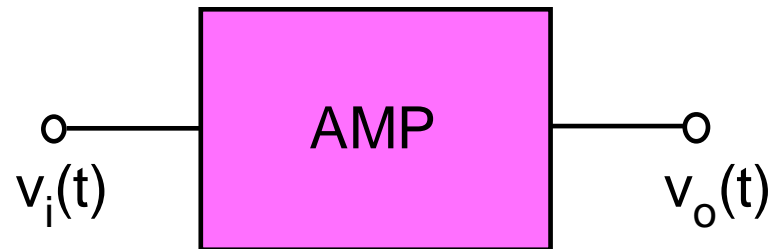
# Amplifiers

- **Definitions**

- Used to increase the amplitude of an input signal to a desired level
- This is a fundamental signal processing function
- Must be linear (free of distortion) – Shape of signal preserved



$v_o(t) = Av_i(t)$ , where  $A$  is the voltage gain

Voltage Gain:  $A_v = \frac{v_o}{v_i}$

Power Gain:  $A_p = \frac{\text{Load Power } (P_L)}{\text{Input Power } (P_I)}$

# Amplifiers

$$A_p = \frac{v_o i_o}{v_I i_I}$$

$$\text{Current Gain: } A_i = \frac{i_o}{i_i}$$

$$\text{Note: } A_p = A_v A_i$$

## Expressing gain in dB (decibels)


$$\text{Voltage gain in dB} = 20 \log |A_v|$$

$$\text{Current gain in dB} = 20 \log |A_i|$$

$$\text{Power gain in dB} = 10 \log |A_p|$$
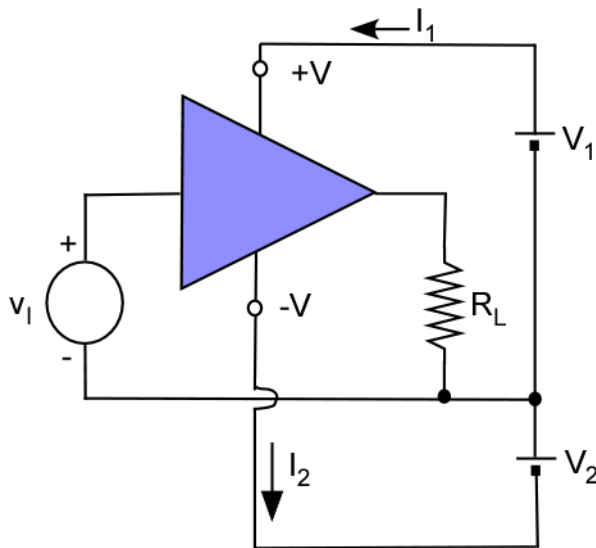
# Amplifiers

Since output associated with the signal is larger than the input signal, power must come from DC supply



$$P_{DC} = V_1 I_1 + V_2 I_2$$

$$P_{DC} + P_I = P_L + P_{dissipated}$$

$$\eta = \frac{P_L}{P_{DC}} \times 100 = \text{Power Efficiency}$$

# Problem

An amplifier has  $\pm 10$  V power supplies and an input current of 0.1 mA (sine wave) input voltage 1 V peak-to-peak and an output voltage with a peak of 9V. The load impedance is 1 k $\Omega$  and the amp draws 9.5 mA from each power supply. Determine:

- the voltage gain
- the current gain
- the power gain
- the power drawn from supplies
- the power dissipated and  $\eta$

$$A_v = \frac{V_o}{V_i} = \frac{9}{1} = 9$$

$$A_{v-dB} = 20 \log |A_v| = 20 \log |9| = 19.1 \text{ dB}$$

$$\hat{I}_o = \frac{9}{1 \text{ k}\Omega} = 9 \text{ mA}$$

The current gain is

$$A_i = \frac{\hat{I}_o}{\hat{I}_i} = \frac{9}{0.1} = 90$$

# Problem

$$A_{i-dB} = 20 \log 90 = 39.1 \text{ dB}$$

$$\text{Power at Load} = P_L = V_{o-rms} I_{o-rms} = \frac{9}{\sqrt{2}} \frac{9}{\sqrt{2}} = 40.5 \text{ mW}$$

$$\text{Power at input} = P_I = V_{I-rms} I_{I-rms} = \frac{1}{\sqrt{2}} \frac{0.1}{\sqrt{2}} = 0.05 \text{ mW}$$

$$A_p = \frac{P_d}{P_I} = \frac{40.5}{0.05} = 810$$

$$A_{p-dB} = 10 \log 810 = 29.1 \text{ dB}$$

$$P_{dc} = 10 \times 9.5 + 10 \times 9.5 = 190 \text{ mW}$$


$$P_{dissipated} = P_{dc} + P_I - P_L$$

$$P_{dissipated} = 190 - 0.05 - 4.05 = 149.6 \text{ mW}$$

$$\eta = \frac{P_L}{P_{dc}} \times 100 = 21.3\%$$
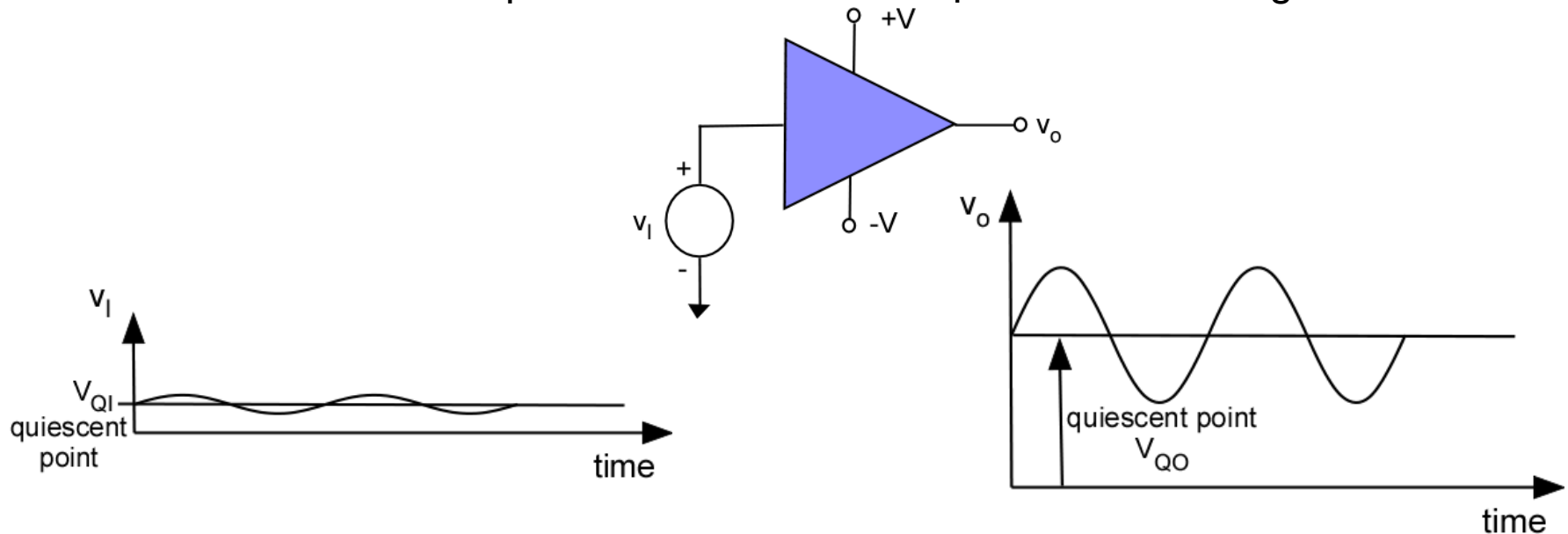
# Biassing of Amp

Bias will provide quiescent points for input and output about which variations will take place. Bias maintain amplifier in active region.



$$V_I(t) = V_{QI} + v_I(t)$$


$$V_o(t) = V_{QO} + v_o(t)$$

$$v_o(t) = A_v v_I(t)$$

$$A_v = \left. \frac{dv_o}{dv_I} \right|_{at Q}$$

**Amplifier characteristics are determined by bias point**

# Voltage Amplifier

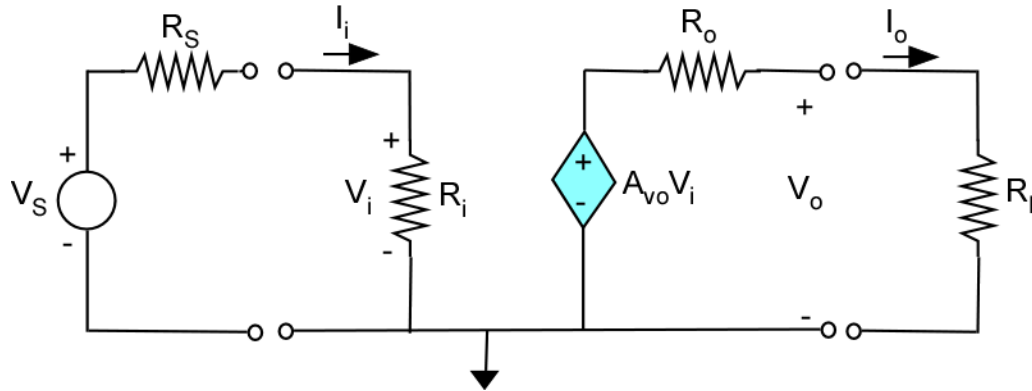

$$\text{Voltage gain is: } \frac{v_o}{v_i} = A_v = \frac{A_{vo} R_L}{R_L + R_o}$$

$$\text{Input } v_i = v_s \frac{R_i}{R_i + R_s}$$

$$v_o = \frac{A_{vo} v_i R_L}{R_L + R_o}$$


Want  $R_i$  large (so  $v_i \approx v_s$ )  
 (actually want  $R_i \gg R_s$ ) ideal  
 $R_i = \infty$

Want  $R_o$  small (as small as possible) to achieve maximum gain  $\rightarrow$  ideal  $R_o = 0$

$$\text{Overall gain: } \frac{v_o}{v_s} = A_{vo} \frac{R_i}{R_i + R_s} \cdot \frac{R_L}{R_L + R_o}$$



# Voltage Amplifier

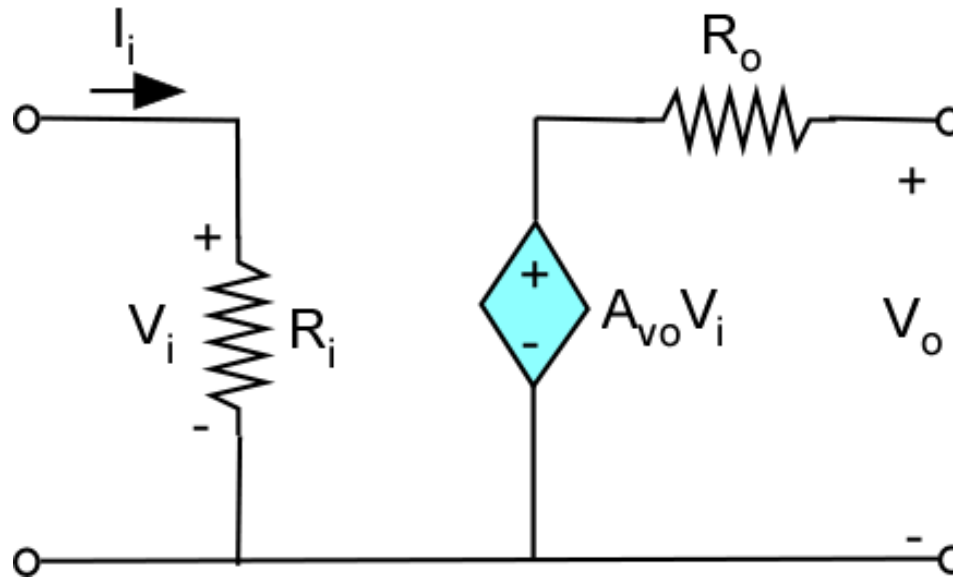


$$\text{Open Circuit Voltage Gain: } A_{vo} = \left. \frac{v_o}{v_i} \right|_{i_o=0}$$

$$\text{ideal: } R_i = \infty$$

$$R_o = 0$$

# Current Amplifier

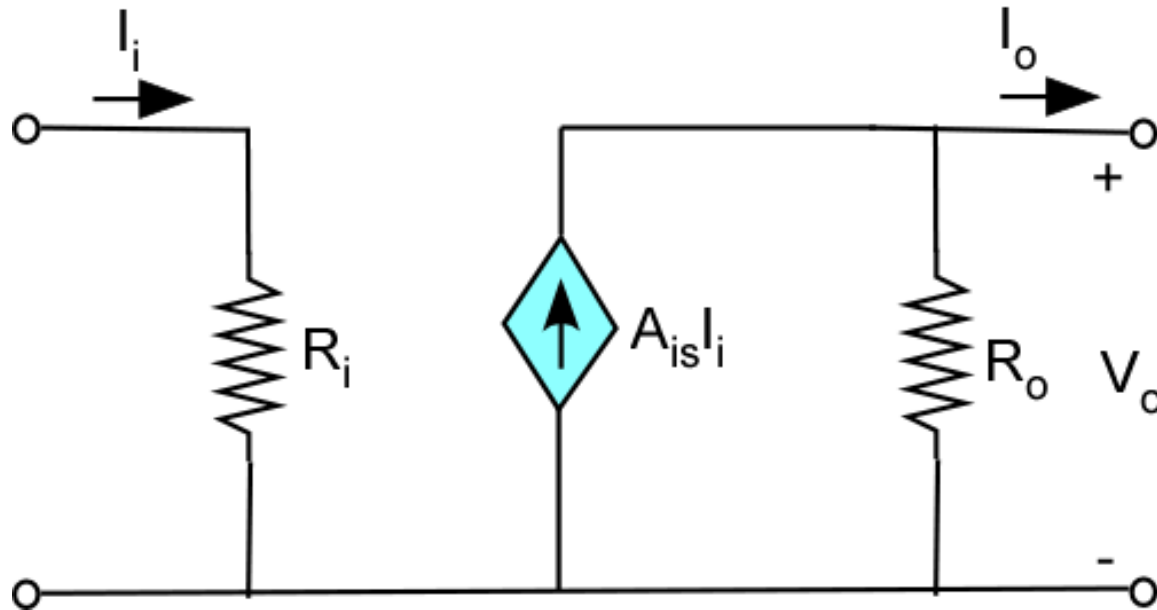


$$\text{Short Circuit Current Gain: } A_{is} = \left. \frac{i_o}{i_i} \right|_{i_o=0}$$

$$\text{ideal : } R_i = 0$$


$$R_o = \infty$$

# Transconductance Amplifier

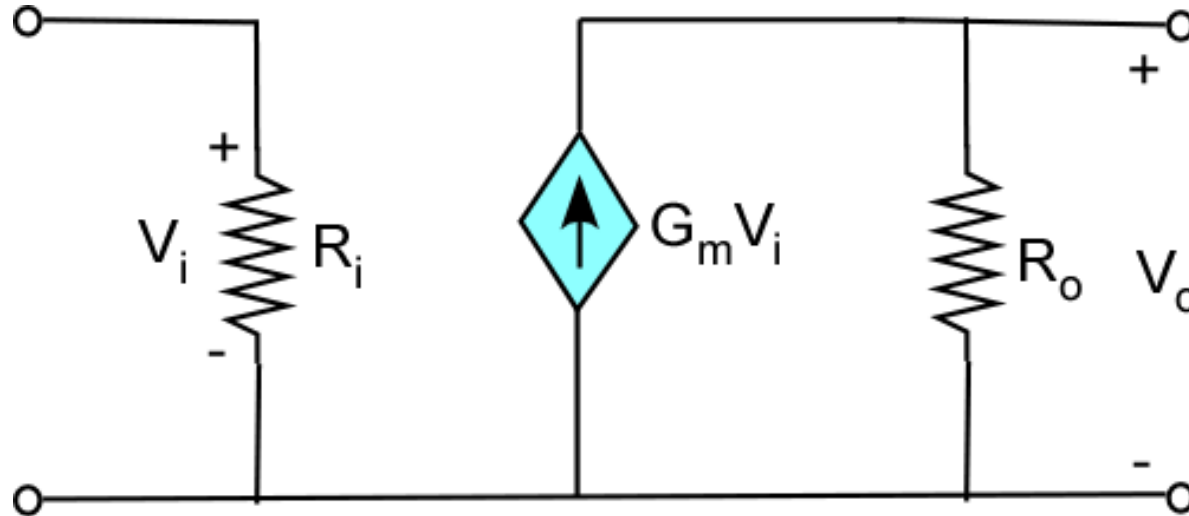

Short Circuit Transconductance:  $G_m = \frac{i_o}{v_i}$   
*ideal* :  $R_i = \infty$   
 $R_o = \infty$

# Transresistance Amplifier

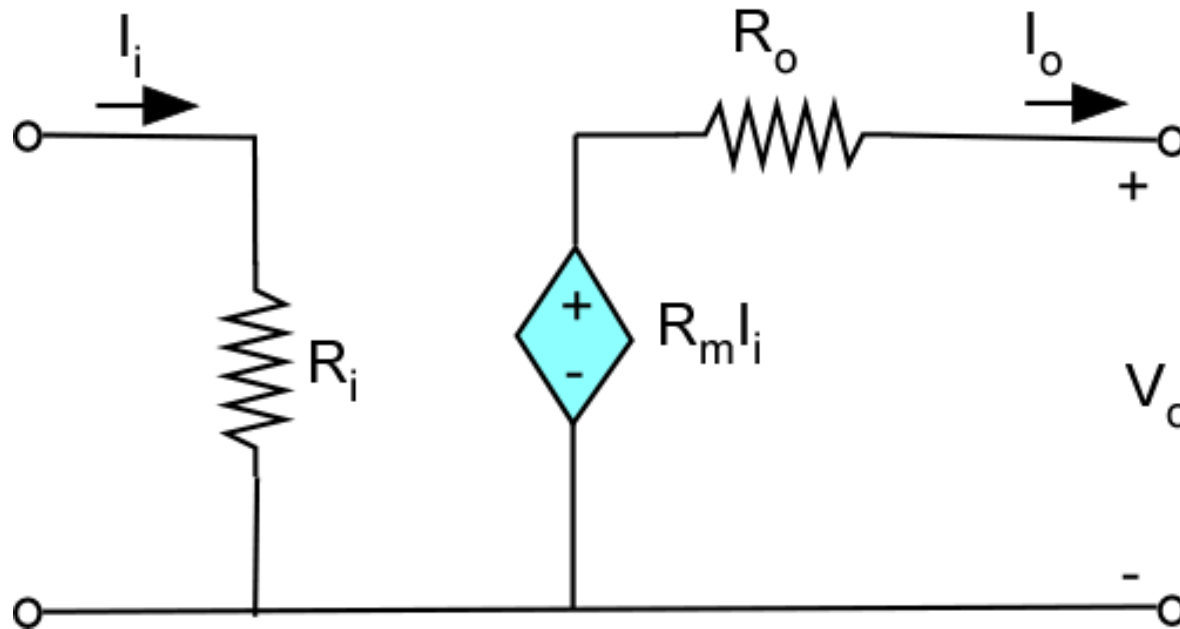

Open Circuit Transresistance:  $R_m = \frac{v_o}{i_i}$

*ideal* :  $R_i = 0$

$R_o = 0$

# Small-Signal Model

- **What is a small-signal incremental model?**
  - Equivalent circuit that only accounts for signal level fluctuations about the DC bias operating points
  - Fluctuations are assumed to be small enough so as not to drive the devices out of the proper range of operation
  - Assumed to be linear
  - Derives from superposition principle