

ECE 342

Electronic Circuits

Lecture 5


Diode Applications

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

Diodes as Voltage Regulators

- **Objective**

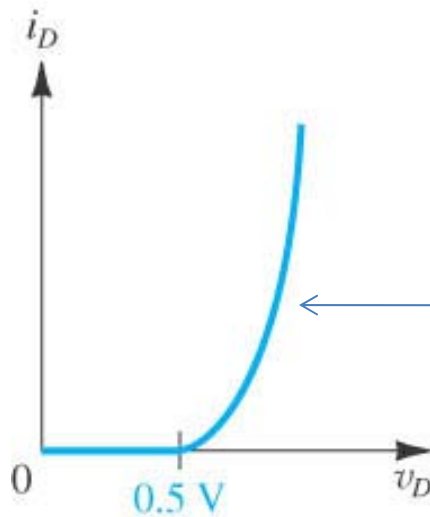- Provide constant dc voltage between output terminals
- Load current changes
- Dc power supply changes
- Take advantage of diode I-V exponential behavior



**Big change in current
correlates to small
change in voltage**

Voltage Regulator - Example

Assume $n=2$ and calculate % change caused by a $\pm 10\%$ change in power-supply voltage (a) with no load (b) with $1\text{-k}\Omega$ load

Nominal value of current is:

$$I = \frac{10 - 2.1}{1} = 7.9 \text{ mA}$$

Incremental resistance for each diode:


$$r_d = \frac{nV_T}{I} = \frac{2 \times 25}{7.9} = 6.3 \Omega$$

Resistance for all 3 diodes:

$$r = 3r_d = 18.9 \Omega$$

Voltage change
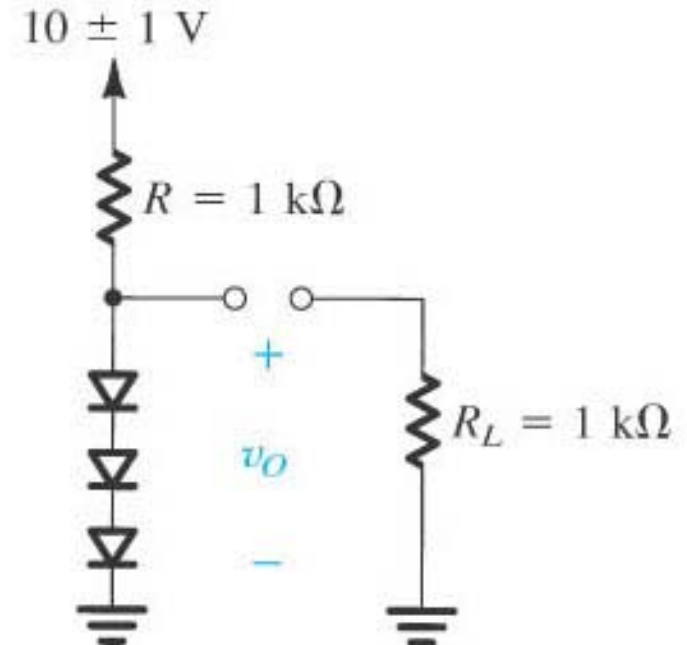
$$\Delta v_o = 2 \frac{r}{r + R} = 2 \frac{0.0189}{0.0189 + 1} = 37.1 \text{ mV} \rightarrow \pm 18.5 \text{ mV} \rightarrow \pm 0.9\%$$




Voltage Regulator – Example (con't)






When $1\text{k}\Omega$ load is connected, it draws a current of 2.1 mA resulting in a decrease in voltage across the 3 diodes given by

$$\Delta v_o = -2.1 \times r$$
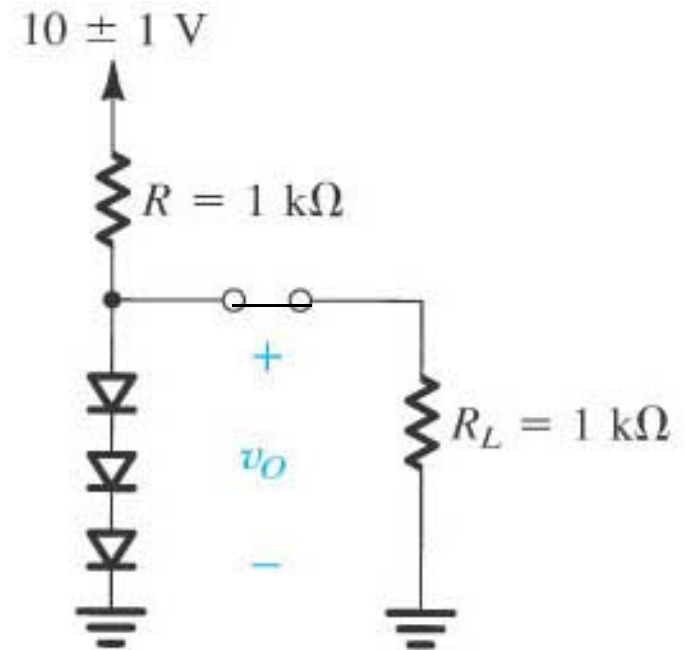
$$\Delta v_o = -2.1 \times 18.9 = -39.7\text{ mV}$$




Diode as Rectifier

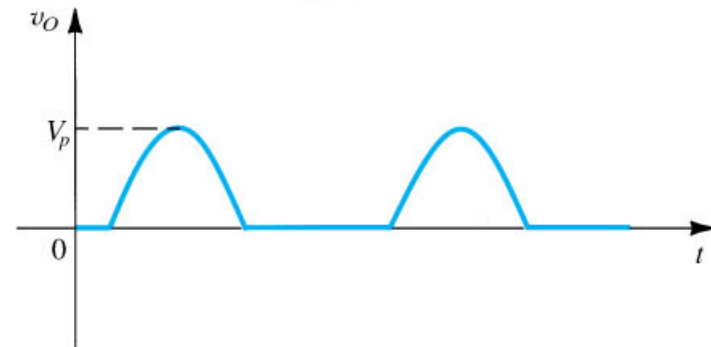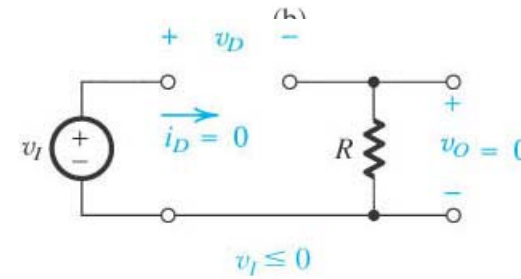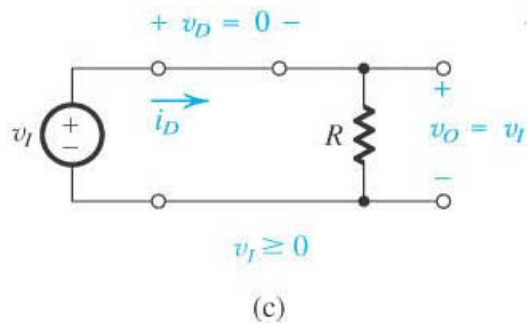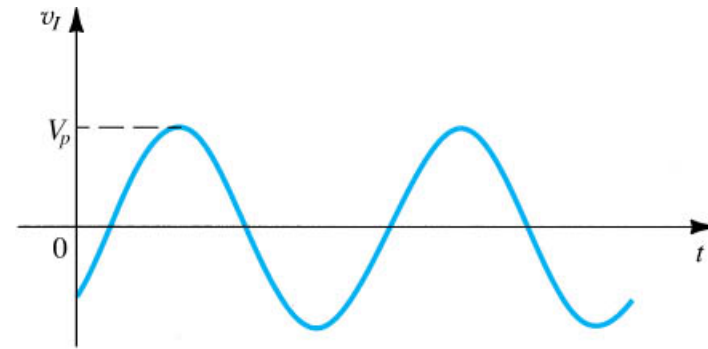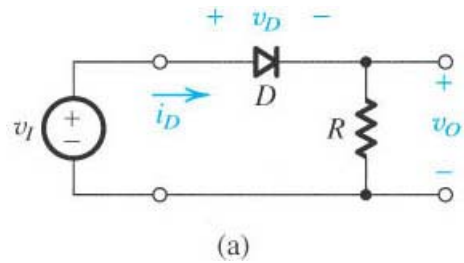

(e)

While applied source alternates in polarity and has zero average value, output voltage is unidirectional and has a finite average value or a *dc component*

Diode as Rectifier

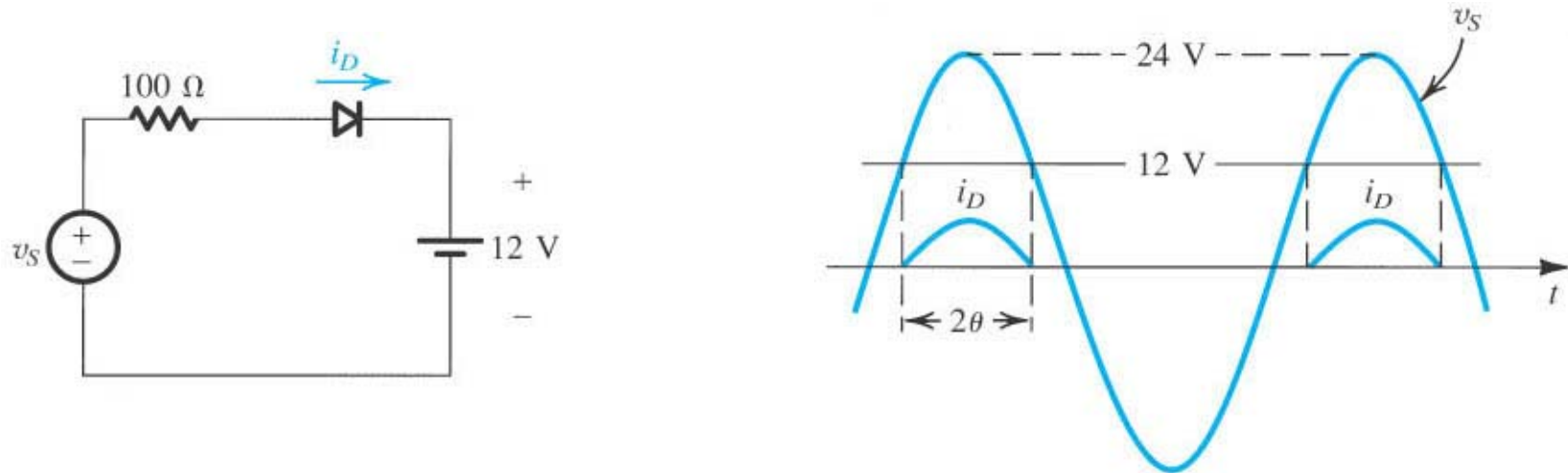

v_s is a sinusoid with 24-V peak amplitude. The diode conducts when v_s exceeds 12 V. The conduction angle is 2θ where θ is given by


$$24 \cos \theta = 12 \Rightarrow \theta = 60^\circ$$

The conduction angle is 120° , or one-third of a cycle. The peak value of the diode current is given by


$$I_d = \frac{24 - 12}{100} = 0.12\text{ A}$$

The maximum reverse voltage across the diode occurs when v_s is at its negative peak: $24 + 12 = 36\text{ V}$


Half-Wave Rectifier

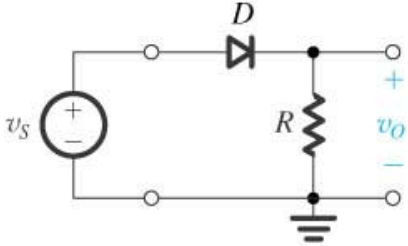


(a)

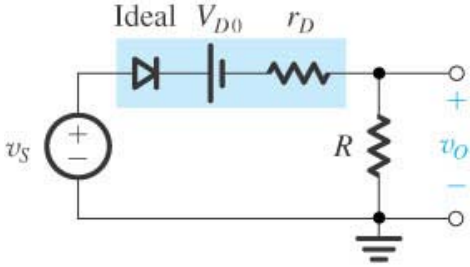


(b)

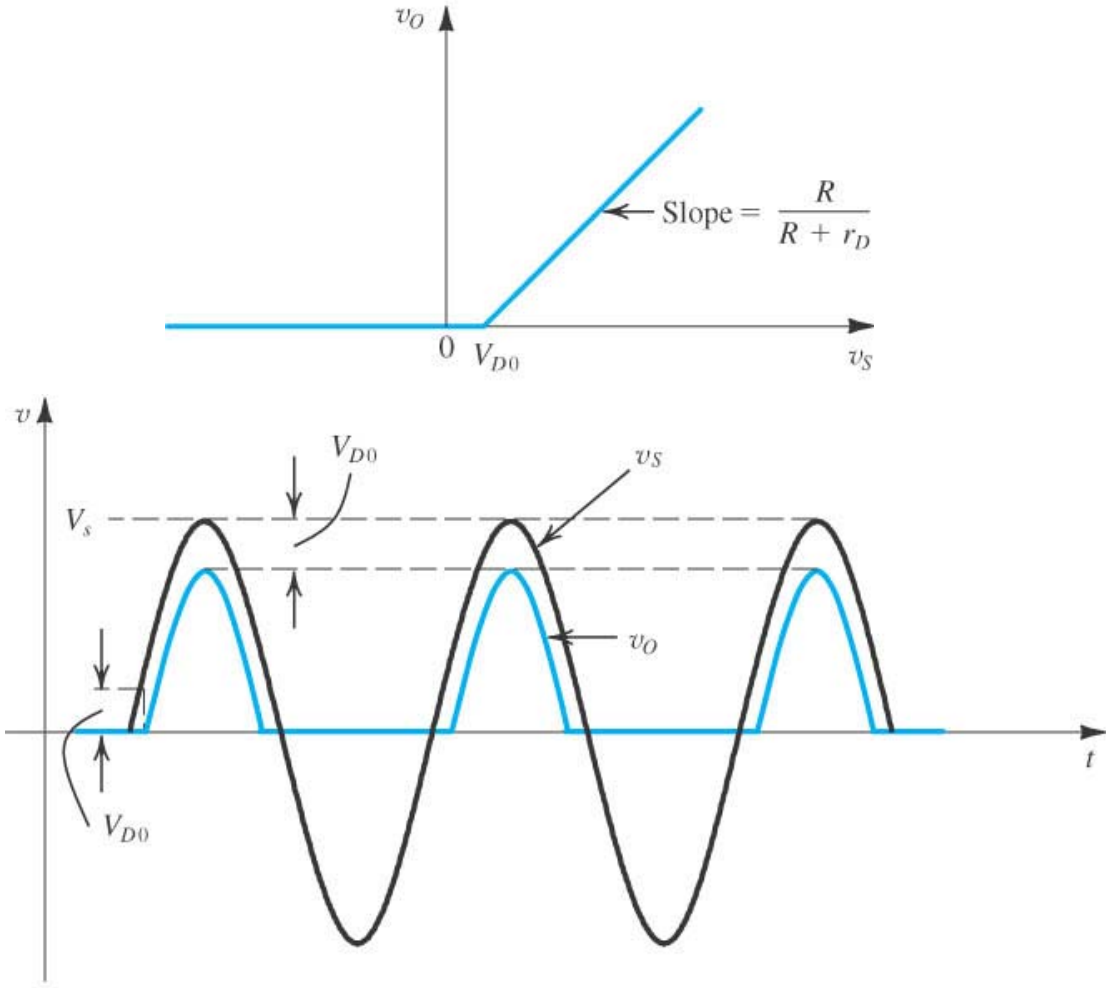


(d)

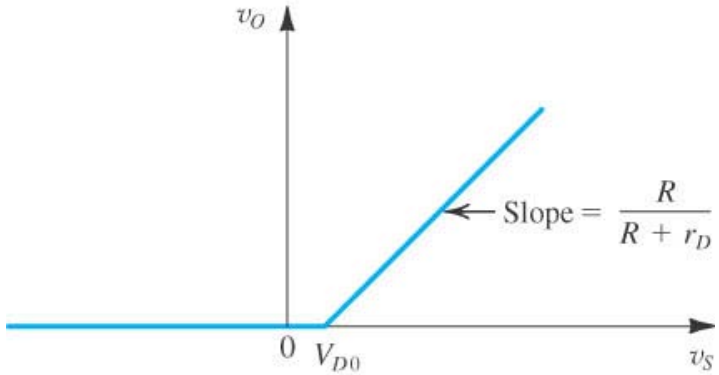


Full-Wave Rectifier

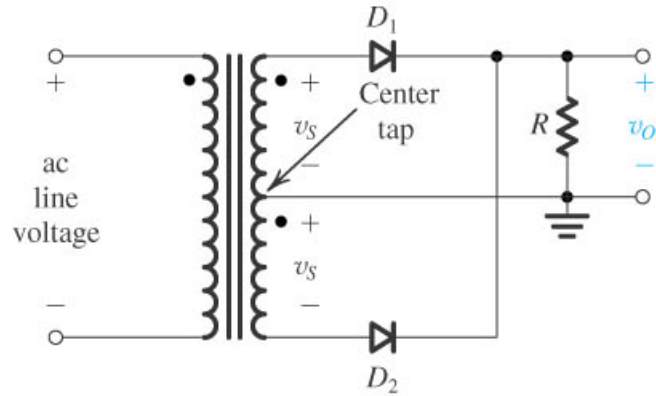

(a)

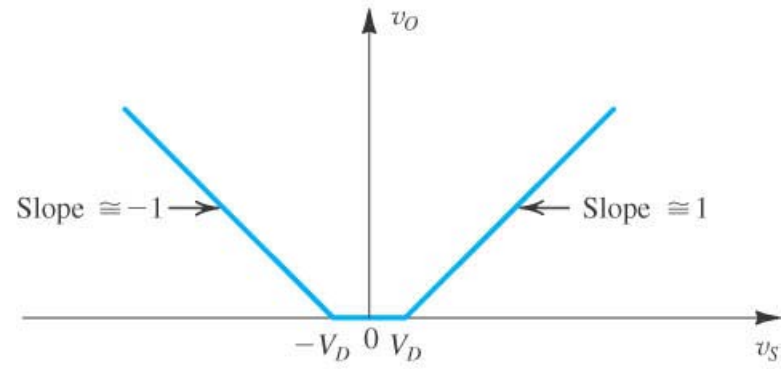


(b)

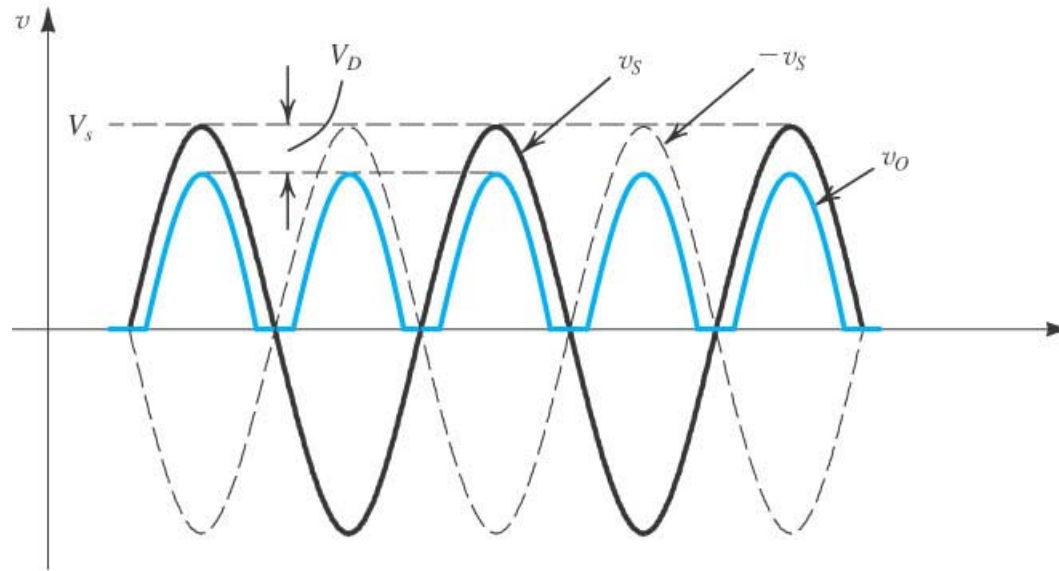


(c)

Bridge Rectifier

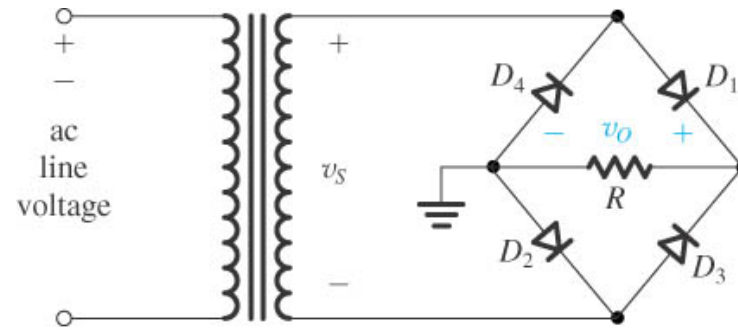


(a)

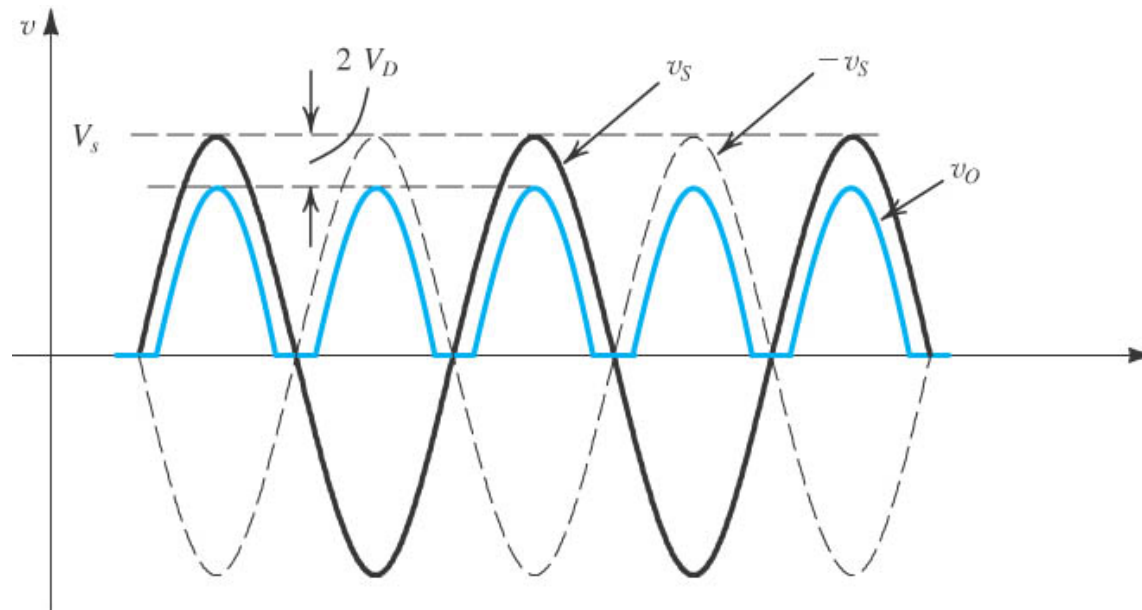

(b)

Bridge Rectifier

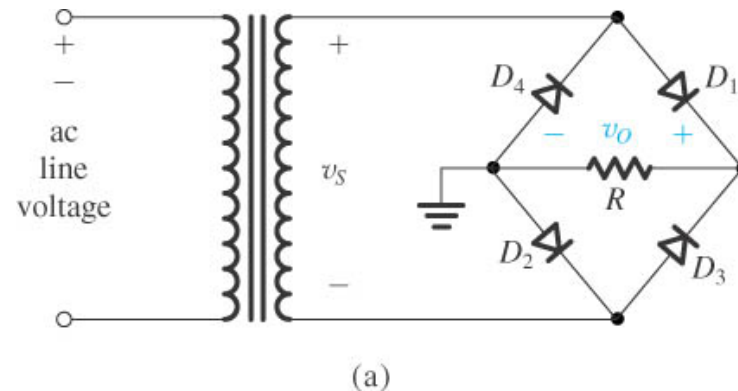

- **Properties**


- Uses four diodes.
- v_o is lower than v_s by two diode drops.
- Current flows through R in the same direction during both half cycles.

The peak inverse voltage (PIV) of each diode:


$$PIV = v_s - 2v_D + v_D = v_s - v_D$$

Peak Rectifier

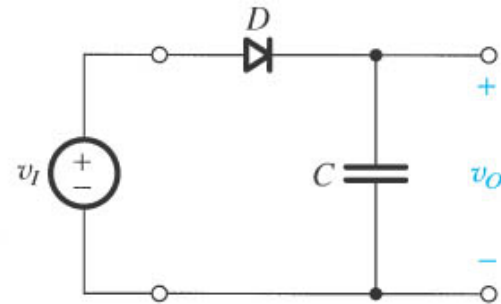Filter capacitor is used to reduce the variations in the rectifier output




(a)

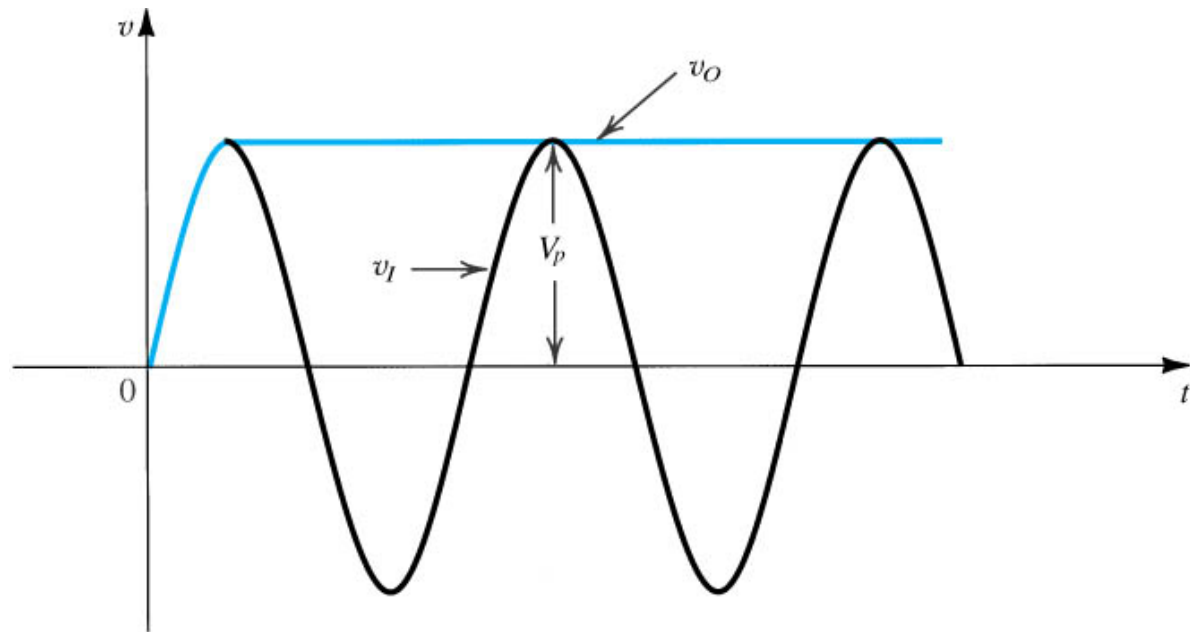

(b)


Rectifier with Filter Capacitor

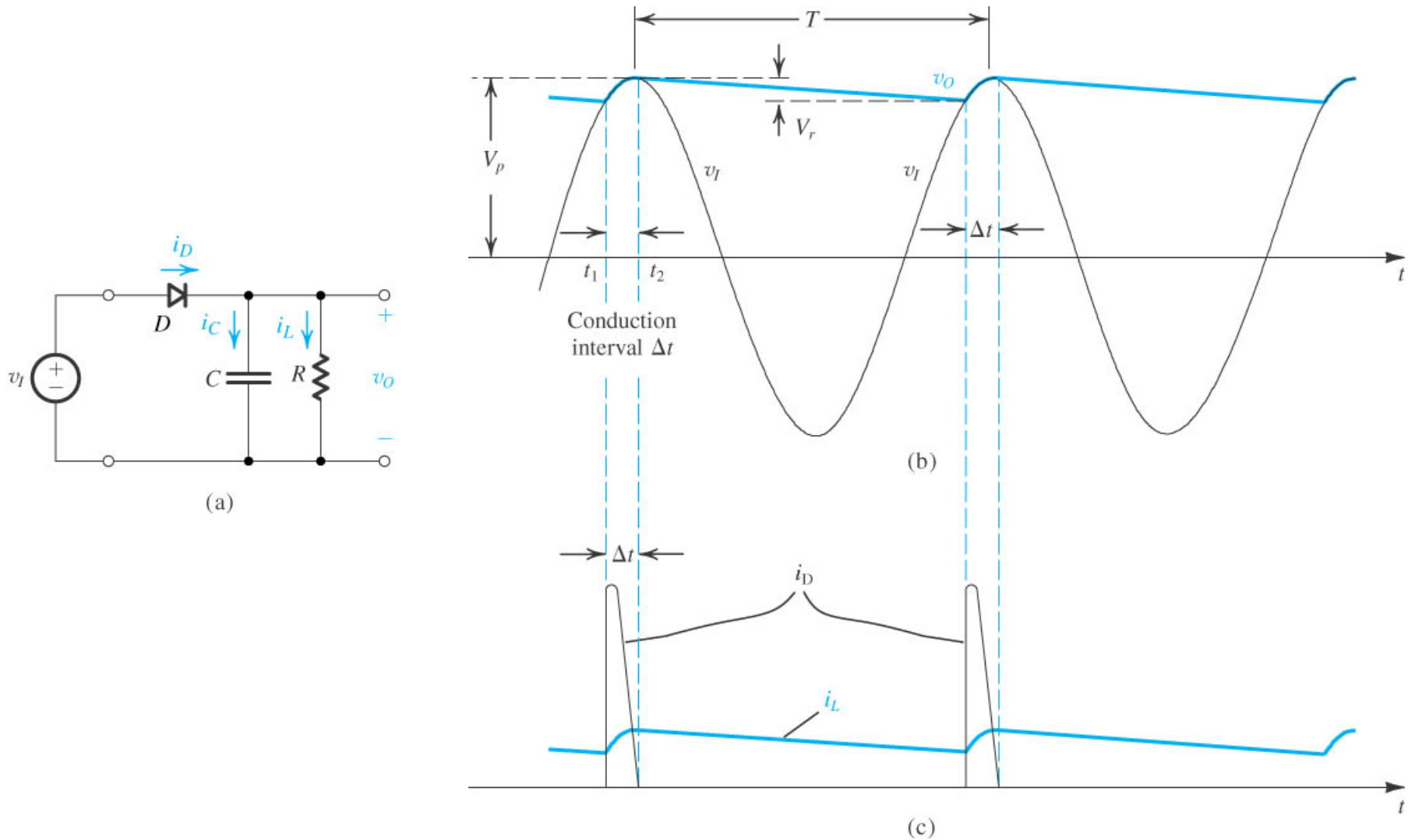

Rectifier with Filter Capacitor

- **Operation**

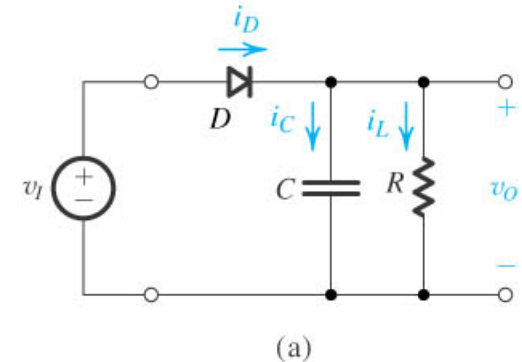- Diode conducts for brief interval Δt
- Conduction stops shortly after peak
- Capacitor discharges through R
- $CR \gg T$
- V_r is peak-to-peak ripple



$$i_L = v_o / R \quad I_L = V_p / R$$

$$i_D = i_C + i_L = C \frac{dv_I}{dt} + i_L$$





$$i_{D_{av}} = I_L \left(1 + \pi \sqrt{2V_p / V_r} \right)$$

$$v_o = V_p e^{-t/CR}$$



$$V_r \approx V_p \frac{T}{CR} = \frac{V_p}{fCR} = \frac{I_L}{fC}$$

$$i_{D_{max}} = I_L \left(1 + 2\pi \sqrt{2V_p / V_r} \right)$$

Diode Circuits - Rectification

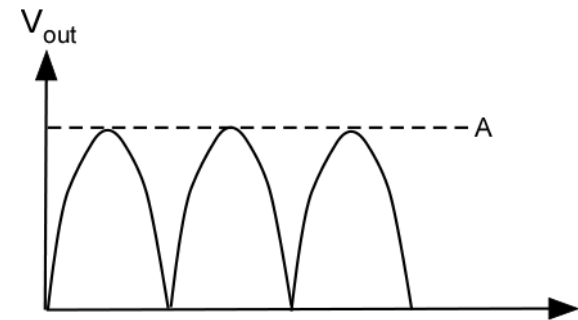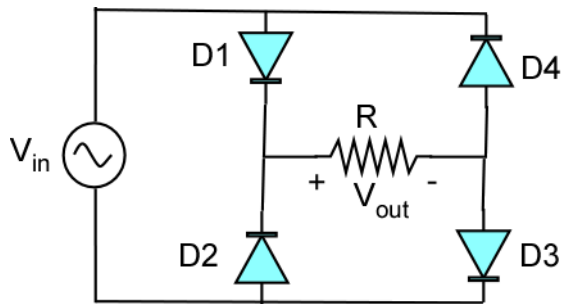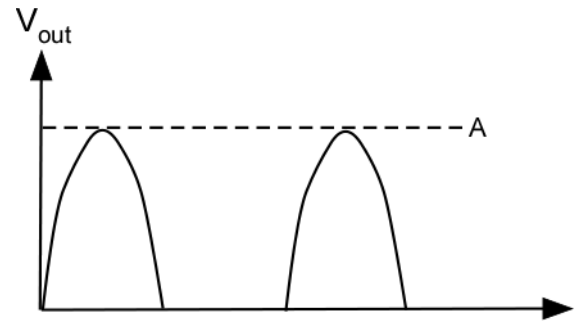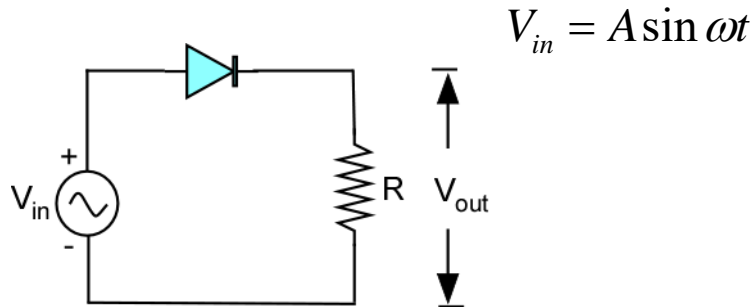

Rectification with ripple reduction.

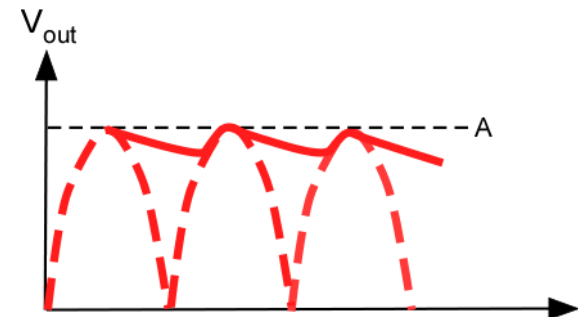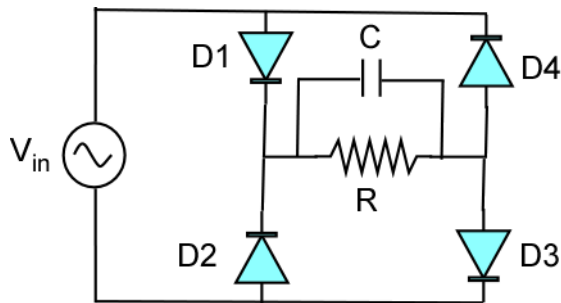

C must be large enough so that RC time constant is much larger than period