

ECE 342


Electronic Circuits

Lecture 7

DC Analysis of MOSFET


Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

MOS – Active Region

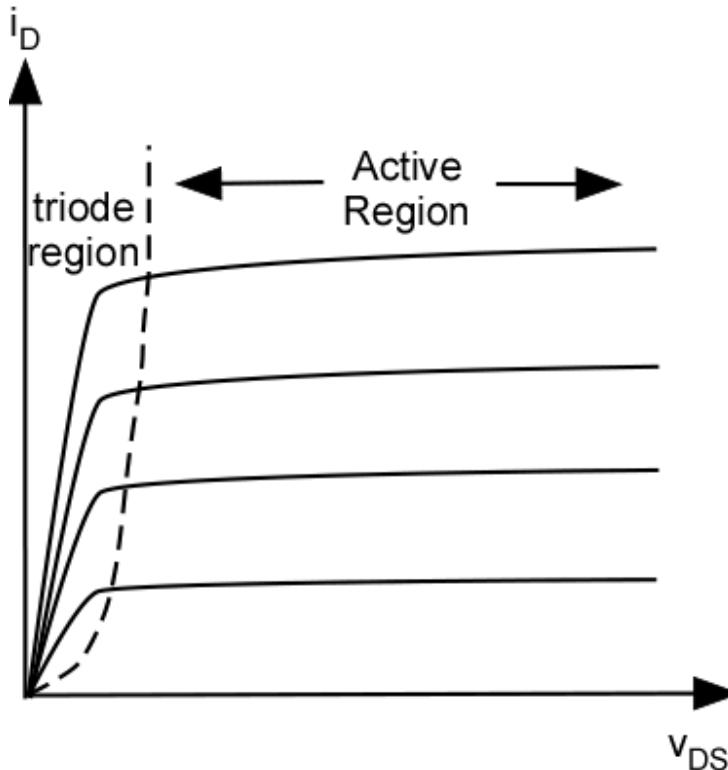

- **Saturation**
 - Channel is pinched off
 - Increase in V_{DS} has little effect on i_D
 - Square-law behavior wrt $(V_{GS} - V_T)$
 - Acts like a current source

Diode-Connected Transistor

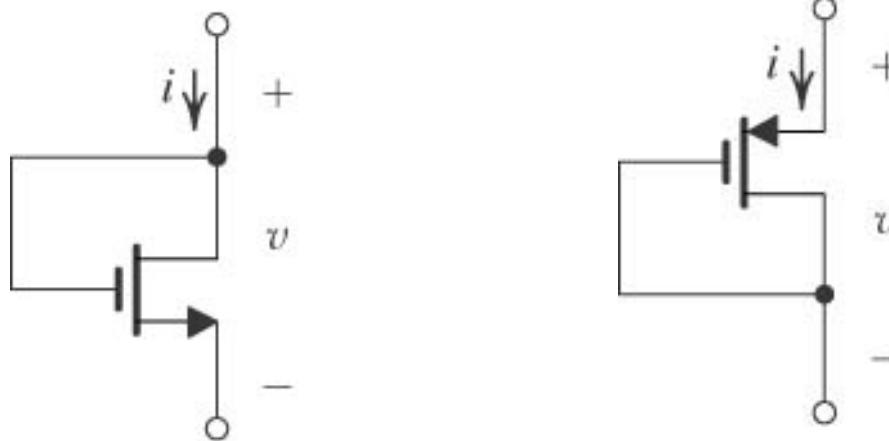

When the drain and gate of a MOSFET are connected together the result is a two-terminal device known as a diode-connected transistor

$$V_{GD} \leq V_T \quad \text{for saturation region. Since } V_{GD} \text{ is zero, then the device is always in the saturation region.}$$

Diode-Connected Transistor

$$i_D = i = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2$$

If we replace V_{GS} by V and use $k' = \frac{1}{2} k_n'$

$$i = k' \frac{W}{L} (V - |V_t|)^2$$

incremental resistance → $r = \left(\frac{\partial i}{\partial V} \right)^{-1} = \frac{1}{2k' \frac{W}{L} (V - |V_t|)} = \frac{1}{k_n' \frac{W}{L} V_{ov}}$

$$V = |V_t| + V_{ov}$$

Example

An MOS process technology has $L_{min} = 0.4 \mu\text{m}$, $t_{ox} = 8 \text{ nm}$, $\mu = 450 \text{ cm}^2/\text{V.s}$, $V_T = 0.7\text{V}$

(a) Find C_{ox} and $k_n' = \mu_n C_{ox}$

(b) $W/L = 8 \mu\text{m}/0.8\mu\text{m}$. Calculate V_{GS} , V_{DSmin} for operation in saturation with $I_D = 100 \mu\text{A}$

(c) Find V_{GS} for the device in (b) to operate as a $1 \text{ k}\Omega$ resistor for small v_{DS}

Example - Solution

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{8 \times 10^{-9}} = 4.32 \times 10^{-3} \text{ } F/m^2 = 4.32 \text{ } fF/\mu\text{m}^2$$

$$C_{ox} = 4.32 \text{ } fF/\mu\text{m}^2$$

$$k_n' = \mu_n C_{ox} = 450 \text{ } cm^2/V.s \times 4.32 \text{ } fF/\mu\text{m}^2 = 194 \text{ } \mu\text{A}/V^2$$

For operation in saturation region

$$i_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2$$

$$100 = \frac{1}{2} \times 194 \times \frac{8}{0.8} (V_{GS} - 0.7)^2 \Rightarrow V_{GS} - 0.7 = 0.32 \text{ } V \Rightarrow V_{GS} = 1.02 \text{ } V$$

$$V_{DS\min} = V_{GS} - V_T = 0.32 \text{ } V$$

$$V_{DS\min} = 0.32 \text{ } V$$

Example – (con't)

Triode region with v_{DS} very small

$$r_{DS} = \frac{v_{DS}}{i_D} \Big|_{small\ v_{DS}} = \frac{1}{k_n' \frac{W}{L} (V_{GS} - V_T)}$$

$$1000 = \frac{1}{[194 \times 10^{-6} \times 10 (V_{GS} - 0.7)]}$$

$$V_{GS} - 0.7 = 0.52\ V$$

$$V_{GS} = 1.22\ V$$

Body Effect

- **The body effect**

- V_T varies with bias between source and body
- Leads to modulation of V_T


Potential on substrate affects threshold voltage

$$V_T(V_{SB}) = V_{To} + \gamma \left[(2|\phi_F| + V_{SB})^{1/2} - (2|\phi_F|)^{1/2} \right]$$

$$|\phi_F| = \left(\frac{kT}{q} \right) \ln \left(\frac{N_a}{n_i} \right) \quad \text{Fermi potential of material}$$

$$\gamma = \frac{(2qN_a \epsilon_s)^{1/2}}{C_{ox}} \quad \text{Body bias coefficient}$$

Channel-Length Modulation

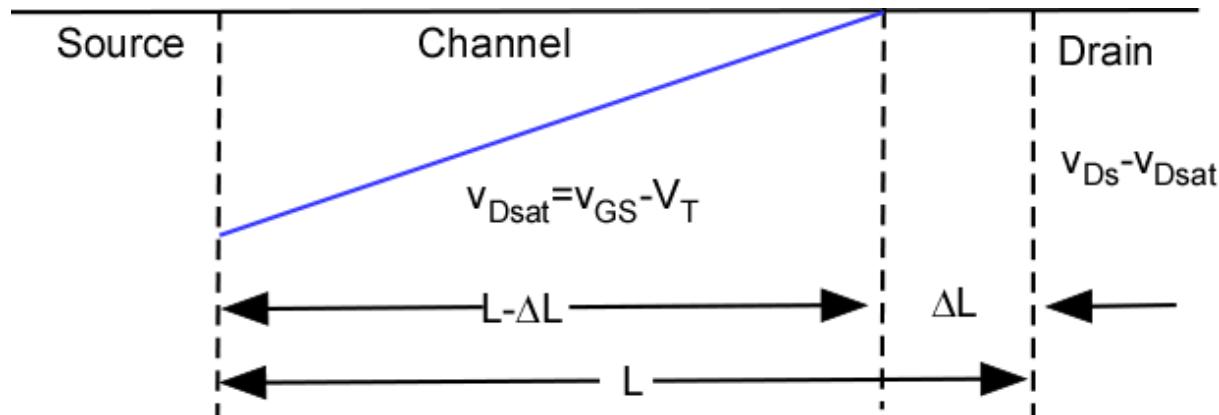


With depletion layer widening, the channel length is in effect reduced from L to $L - \Delta L \rightarrow$ Channel-length modulation

This leads to the following I-V relationship

$$i_D = \frac{1}{2} k_n \frac{W}{L} (v_{GS} - V_T)^2 (1 + \lambda v_{DS})$$

Where λ is a process technology parameter

Channel-Length Modulation

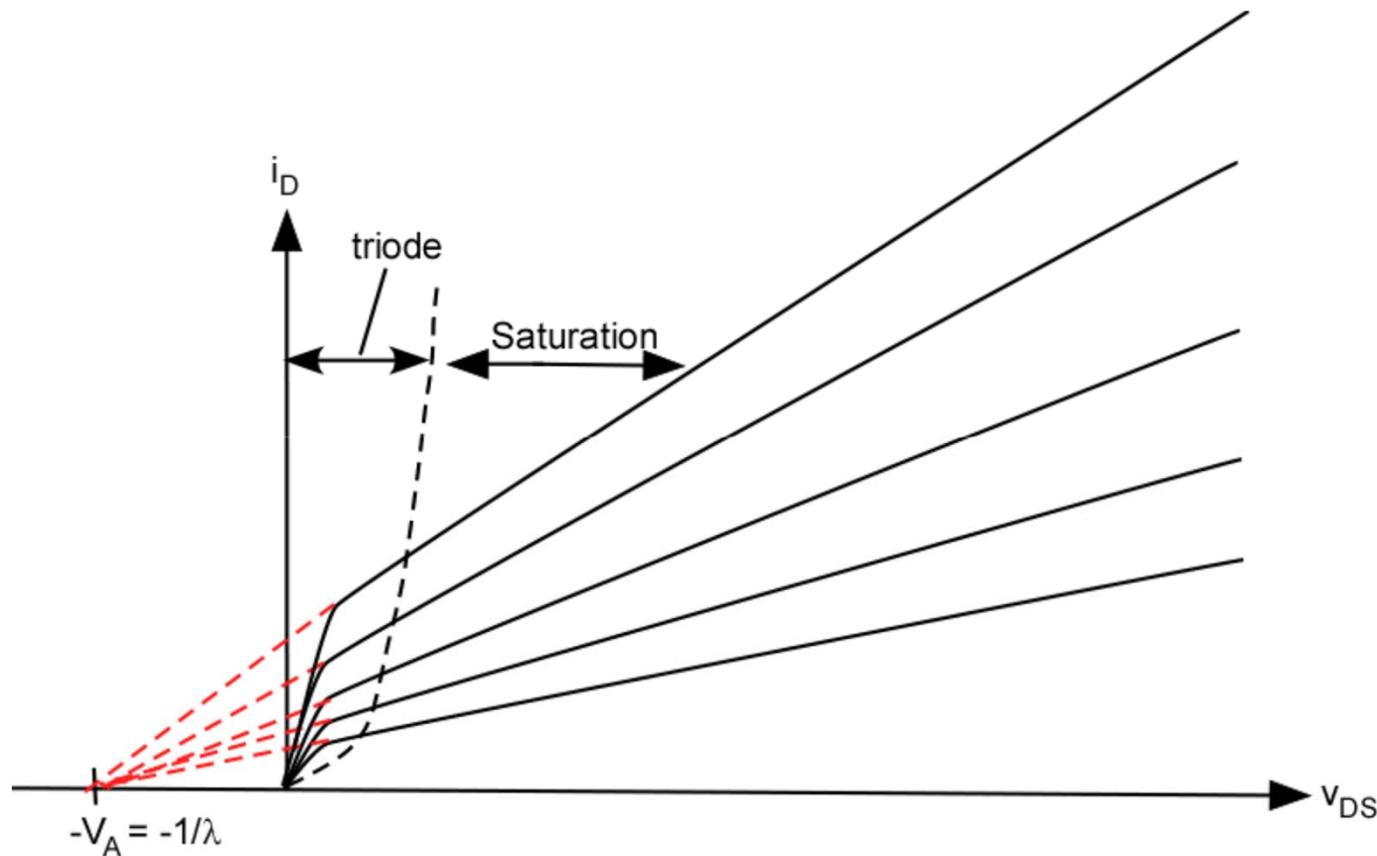

Channel-length modulation causes i_D to increase with v_{DS} in saturation region

Problem

A MOSFET has $V_T = 1$ V with measured data:

$V_{GS}(V)$	$V_{DS}(V)$	$I_D(\mu A)$
2	1	80
2	8	91

Find λ

(a) $V_{GS} > V_T \quad V_{DS} = V_{GS} - V_T \Rightarrow$ Pinchoff

(b) $V_{GS} > V_T \quad V_{DS} > V_{GS} - V_T = 1 V \Rightarrow$ Active region

Problem (cont')

Find i_D at pinchoff $V_{DSP} = V_{GS} - V_T = 1V$

$$I_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$I_{D1} = \frac{1}{2} k_n \frac{W}{L} (V_{GS1} - V_T)^2 (1 + \lambda V_{DS1})$$

$$I_{D2} = \frac{1}{2} k_n \frac{W}{L} (V_{GS2} - V_T)^2 (1 + \lambda V_{DS2})$$

Problem (cont')


$$R = \frac{1 + \lambda V_{DS1}}{1 + \lambda V_{DS2}} = \frac{91}{80} = 1.1375$$

$$1 + \lambda V_{DS2} = R + R\lambda V_{DS1}$$


$$\lambda(V_{DS2} - RV_{DS1}) = R - 1$$

$$\lambda = \frac{R - 1}{V_{DS2} - RV_{DS1}} = \frac{1.1375 - 1}{8 - 1.1375} = 0.02 V^{-1}$$

NMOS – IV Characteristics

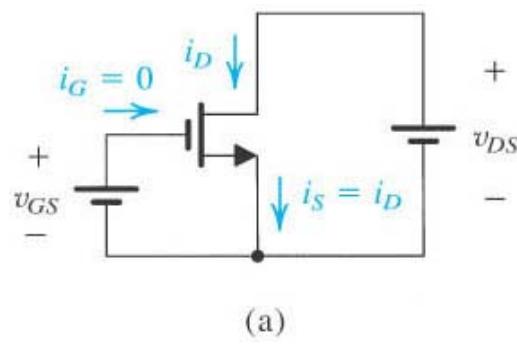


(a)

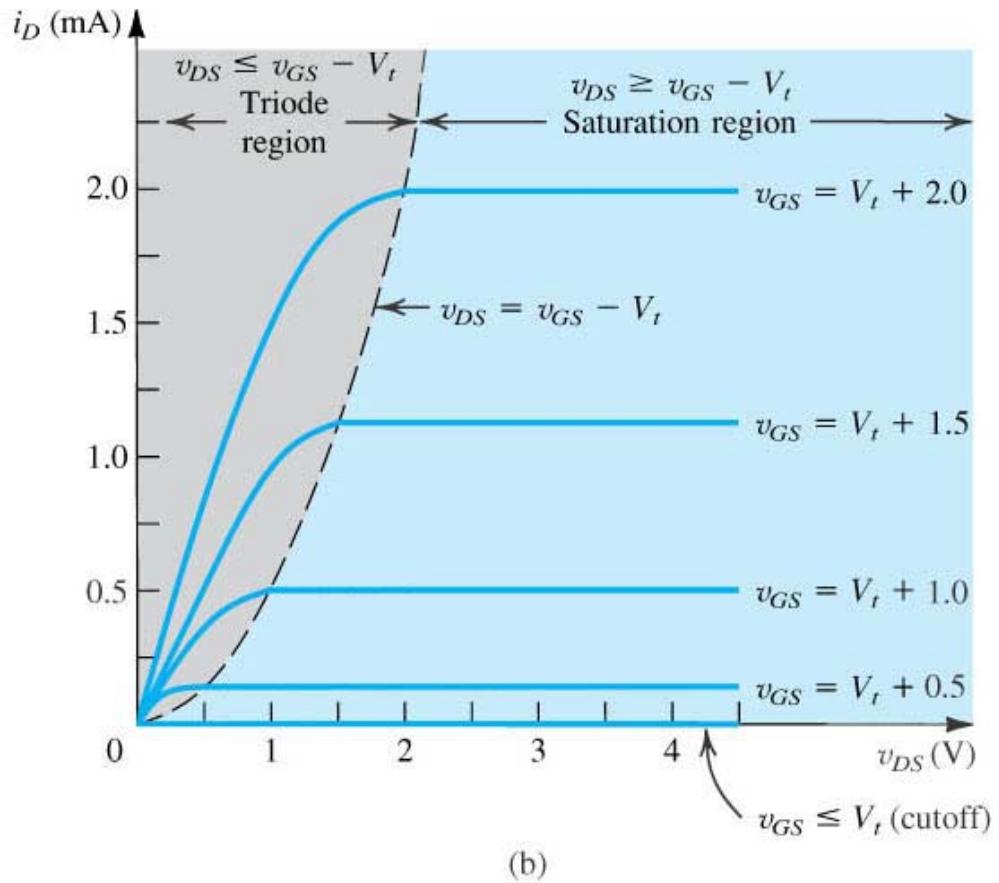

(b)

characteristics for a device with $k'_n(W/L) = 1.0 \text{ mA/V}^2$.

NMOS IV Curves

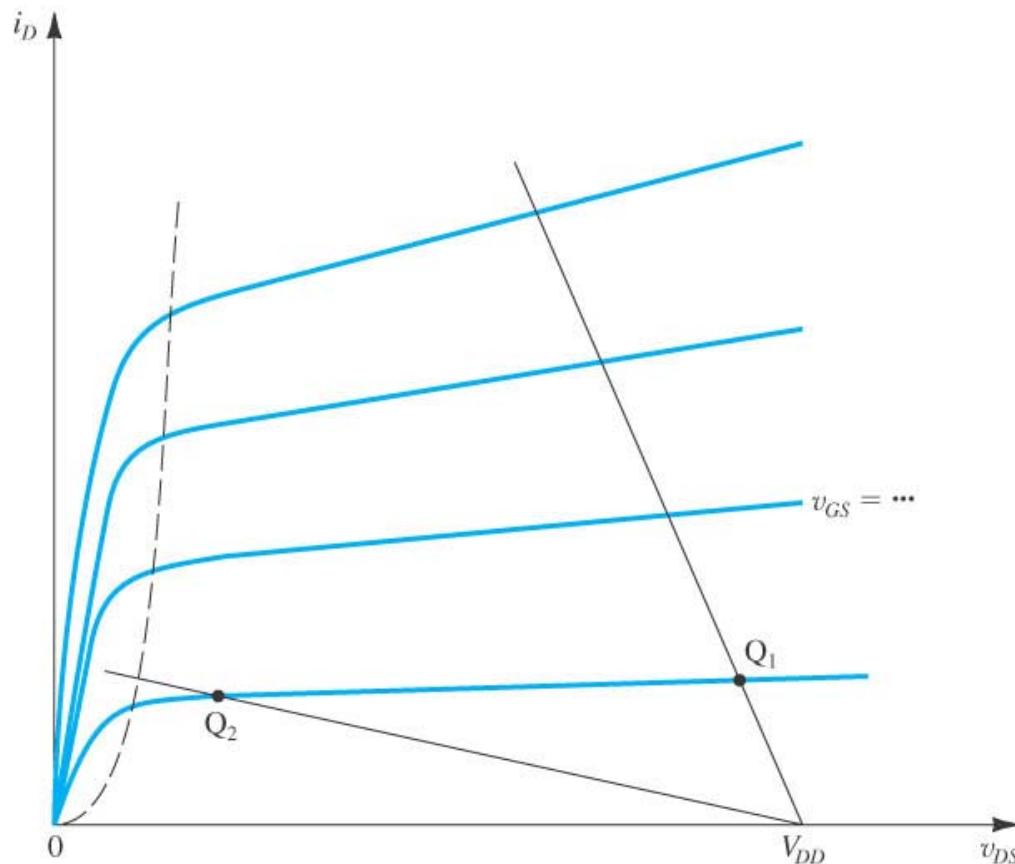


MOSFET Circuit at DC – Problem 1

The MOSFET in the circuit shown has $V_t = 1\text{V}$, $k_n' = 100\mu\text{A/V}^2$ and $\lambda = 0$. Find the required values of W/L and of R so that when $v_I = V_{DD} = +5\text{ V}$, $r_{DS} = 50 \Omega$ and $v_o = 50\text{ mV}$.

$$v_I = V_{GS} = 5\text{ V}, \quad v_o = V_{DS} = 0.05\text{ V}$$

$$r_{DS} = 50 \Omega = \frac{V_{DS}}{I_D} \Rightarrow I_D = \frac{0.05}{50} = 0.001\text{ A} = 1\text{ mA}$$
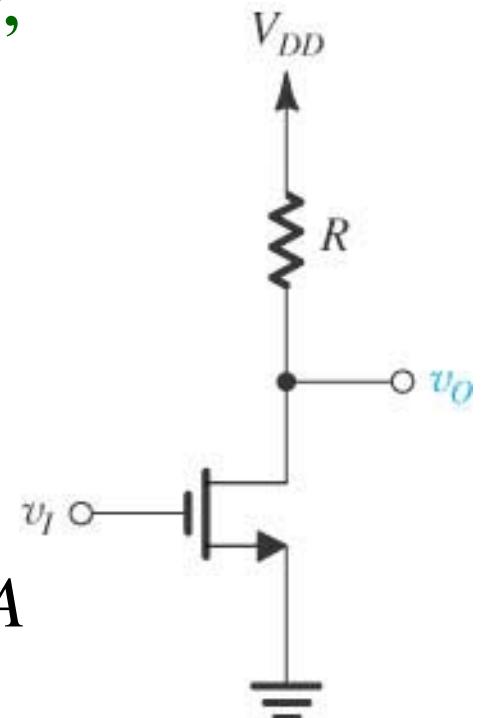
$$R = \frac{V_{DD} - v_o}{I_D} = \frac{5 - 0.05}{1} = 4.95\text{ k}\Omega$$




MOSFET Circuit at DC – Problem 1 (cont')

$V_{DS} < V_{GS} - V_t \Rightarrow$ triode region

$$I_D = k_n \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$1 = 100 \times 10^{-3} \frac{W}{L} \left[(5 - 1) \times 0.05 - \frac{0.05^2}{2} \right]$$

$$\frac{W}{L} = 50$$

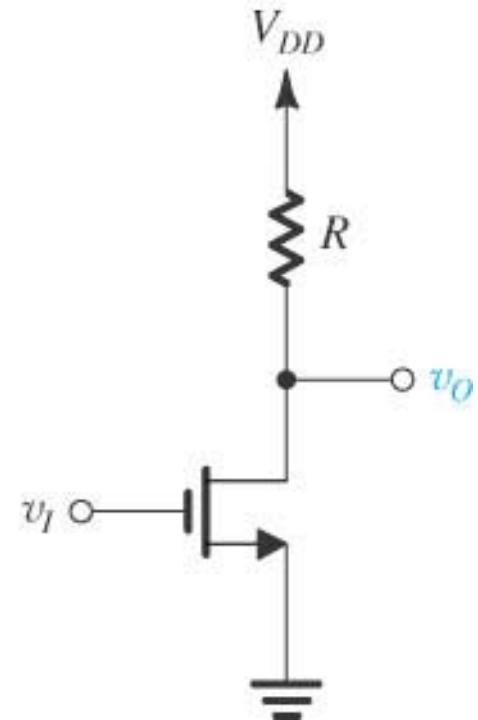


MOSFET Circuit at DC – Problem 2

The NMOS transistors in the circuit shown have $V_t = 1\text{V}$, $\mu_n C_{ox} = 120\mu\text{A/V}^2$, $\lambda = 0$ and $L_1=L_2=1\mu\text{m}$. Find the required values of gate width for each of Q_1 and Q_2 and the value of R , to obtain the voltage and current values indicated.

$$V_{GS1} = 1.5\text{V}$$

$$\text{Using } I_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_t)^2$$
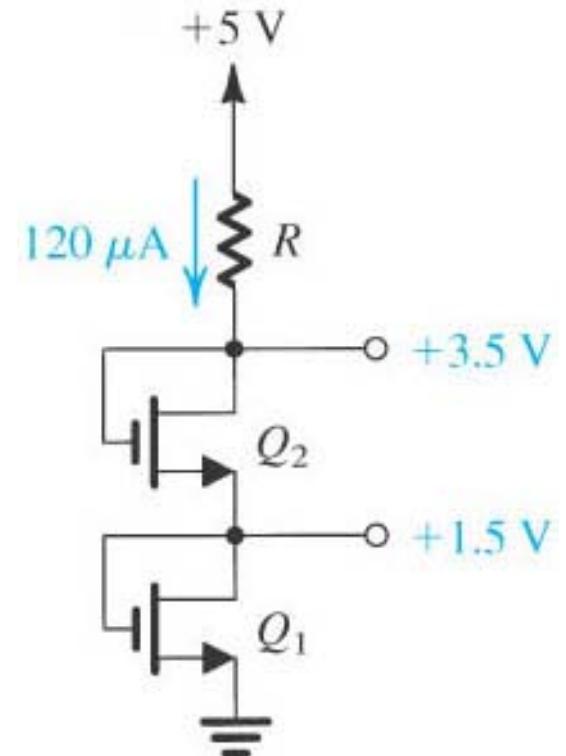
$$120 \mu\text{A} = \frac{1}{2} \times 120 \frac{W_1}{1} (1.5 - 1)^2 \Rightarrow W_1 = 8\mu\text{m}$$



MOSFET Circuit at DC – Problem 2

Using $I_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_t)^2$

$$V_{GS2} = 3.5 - 1.5 = 2V$$

$$120 \mu A = \frac{1}{2} \times 120 \frac{W_2^2}{1} (2 - 1)^2 \Rightarrow W_2 = 2 \mu m$$

$$R = \frac{5 - 3.5}{0.120} = 12.5 k\Omega$$

