

ECE 342


Electronic Circuits

Lecture 18

Common Emitter – Part 2

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@Illinois.edu

CE with External Resistors

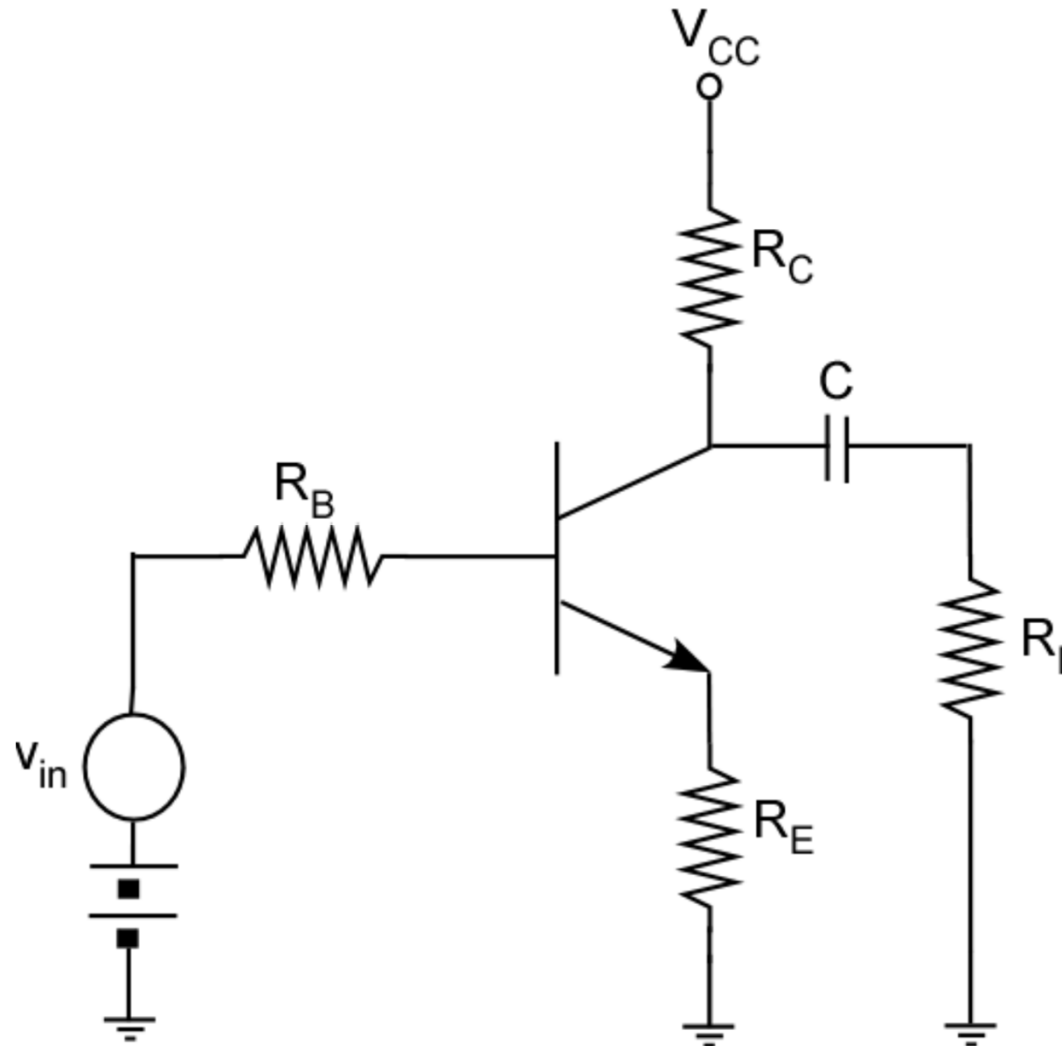


CE with External Resistors

$$v_{out} = -g_m v_\pi (R_L \parallel R_C)$$

$$\frac{v_x}{R_E} = g_m v_\pi + \frac{v_\pi}{r_\pi}$$
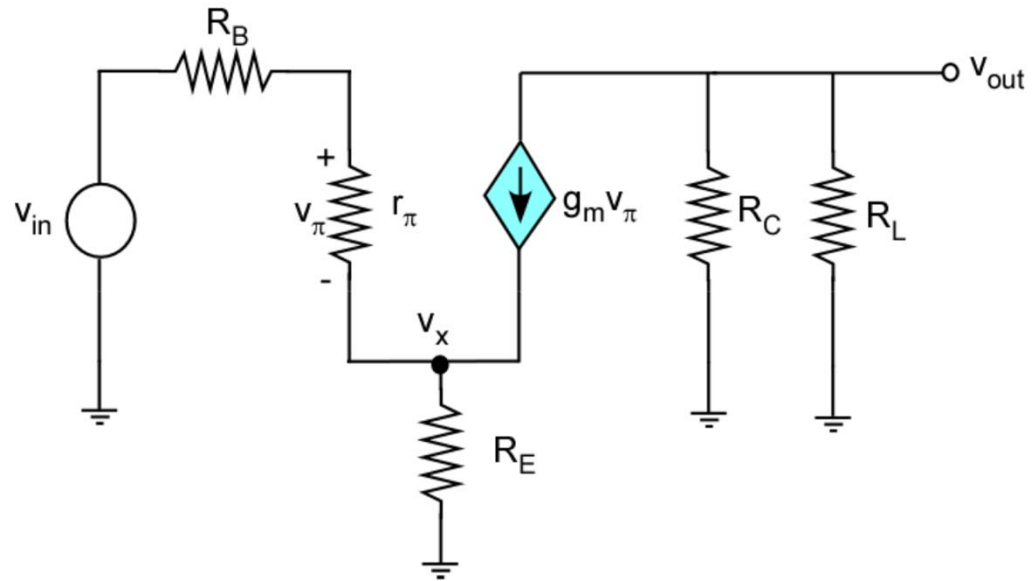
$$v_{in} = v_x + v_\pi + \frac{v_\pi}{r_\pi} R_B$$



$$v_{in} = \left(g_m R_E + \frac{R_E}{r_\pi} + 1 + \frac{R_B}{r_\pi} \right) v_\pi$$

$$v_{out} = - \frac{g_m (R_L \parallel R_C) v_{in}}{g_m R_E + \frac{R_E}{r_\pi} + 1 + \frac{R_B}{r_\pi}}$$

CE with External Resistors

$$\frac{v_{out}}{v_{in}} = -\frac{g_m r_\pi (R_L \parallel R_C)}{g_m r_\pi R_E + R_E + r_\pi + R_B} = -\frac{g_m r_\pi (R_L \parallel R_C)}{R_E (\beta + 1) + r_\pi + R_B}$$

$$A_{MB} = -g_m (R_L \parallel R_C) \frac{1}{\frac{R_E (\beta + 1)}{r_\pi} + \frac{R_B}{r_\pi} + 1}$$

$$A_{MB} = -\frac{\beta (R_L \parallel R_C)}{R_E (\beta + 1) + r_\pi + R_B}$$

R_E and R_B degrade the gain

CE with External Resistors

The gain can be written as:


$$A_{MB} = -\frac{\beta(R_L \parallel R_C)}{R_E(\beta+1) + r_\pi + R_B} = -\frac{\left(\frac{\beta}{\beta+1}\right)(R_L \parallel R_C)}{R_E + \frac{r_\pi}{(\beta+1)} + \frac{R_B}{(\beta+1)}}$$

and since $\frac{\beta}{(\beta+1)} = \alpha$ neglecting $\frac{R_B}{(\beta+1)}$

$$A_{MB} = -\frac{\alpha(R_L \parallel R_C)}{R_E + r_e}$$

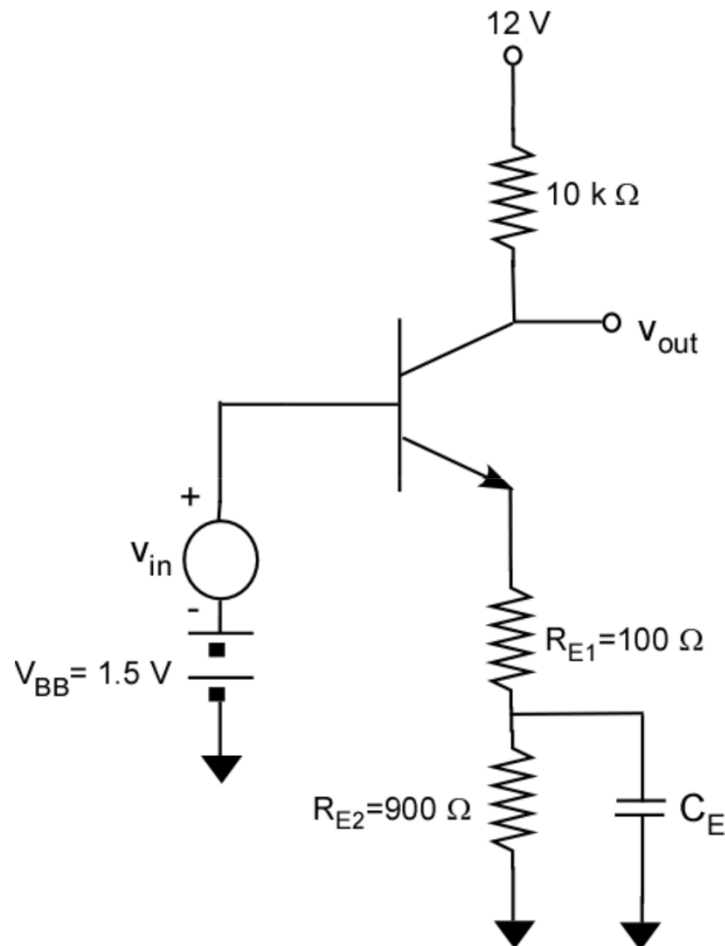Example

Given $V_{BEON}=0.6V$, find the gain for the circuit shown



$$V_{BQ} = 1.5 V$$

$$V_{EQ} = 1.5 V - 0.6 V = 0.9 V$$

$$I_E \approx \frac{0.9}{R_{E1} + R_{E2}} = \frac{0.9}{1 k\Omega} = 0.9 \text{ mA}$$

Example (Cont')

$$I_C \approx 0.9 \text{ mA} \Rightarrow V_{outQ} = 12 \text{ V} - 0.9 \times 10 = 3 \text{ V}$$

AC analysis: R_{E2} is shorted and $R_E = R_{E1} = 100 \Omega$. Since β is not known, use:

$$A_{MB} = -\frac{\alpha R_C}{R_E + r_e} \text{ with } \alpha \approx 1$$

$$r_e = \frac{V_T}{I_E} = \frac{26}{0.9} = 28.8 \Omega$$

$$A_{MB} = -\frac{10,000}{100 + 28.8} = -77.5$$

$$A_{MB} = -77.5$$