

ECE 342

Electronic Circuits


Lecture 19

CB and Emitter Follower


Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@Illinois.edu

Emitter Follower

circuit

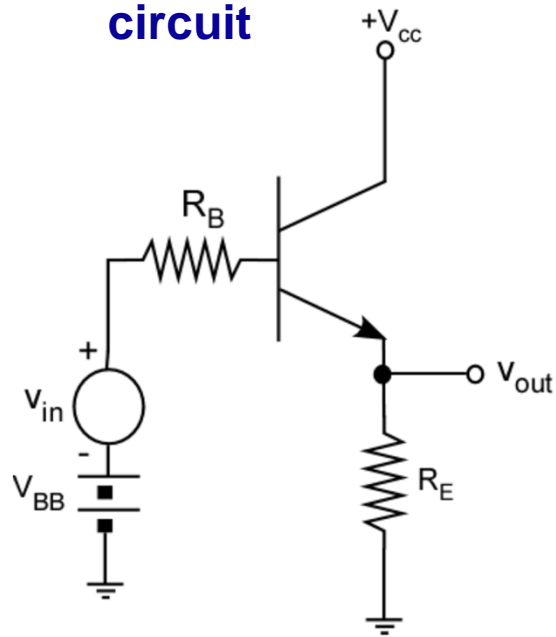

Incremental model

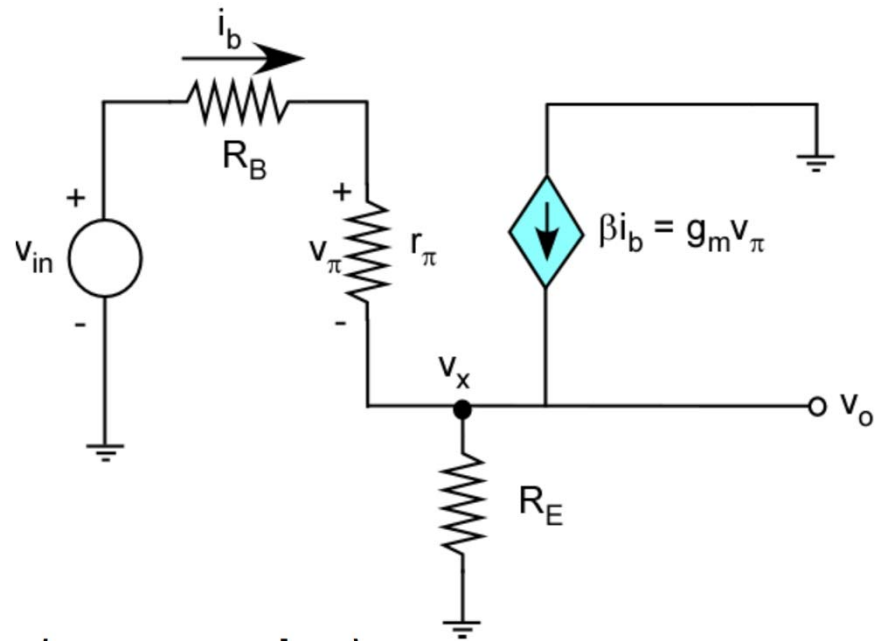

$$v_o = \left(g_m v_\pi + \frac{v_\pi}{r_\pi} \right) R_E = v_\pi \left(g_m + \frac{1}{r_\pi} \right) R_E$$

$$v_{in} = v_\pi + R_B i_b + v_o = v_\pi + v_\pi R_E \left(g_m + \frac{1}{r_\pi} \right) + \frac{v_\pi}{r_\pi} R_B$$

Emitter Follower

$$v_{in} = v_{\pi} \left[1 + \frac{R_B}{r_{\pi}} + R_E \left(g_m + \frac{1}{r_{\pi}} \right) \right]$$


$$\frac{v_o}{v_{in}} = \frac{\left(g_m + \frac{1}{r_{\pi}} \right) R_E}{\left(g_m + \frac{1}{r_{\pi}} \right) R_E + 1 + \frac{R_B}{r_{\pi}}} = \frac{(g_m r_{\pi} + 1) R_E}{(g_m r_{\pi} + 1) R_E + r_{\pi} + R_B}$$

Using $g_m r_{\pi} = \beta$

$$\frac{v_o}{v_{in}} = \frac{(\beta + 1) R_E}{(\beta + 1) R_E + r_{\pi} + R_B} \simeq 1$$

Emitter follower has unity voltage gain


Emitter Follower – Input Impedance

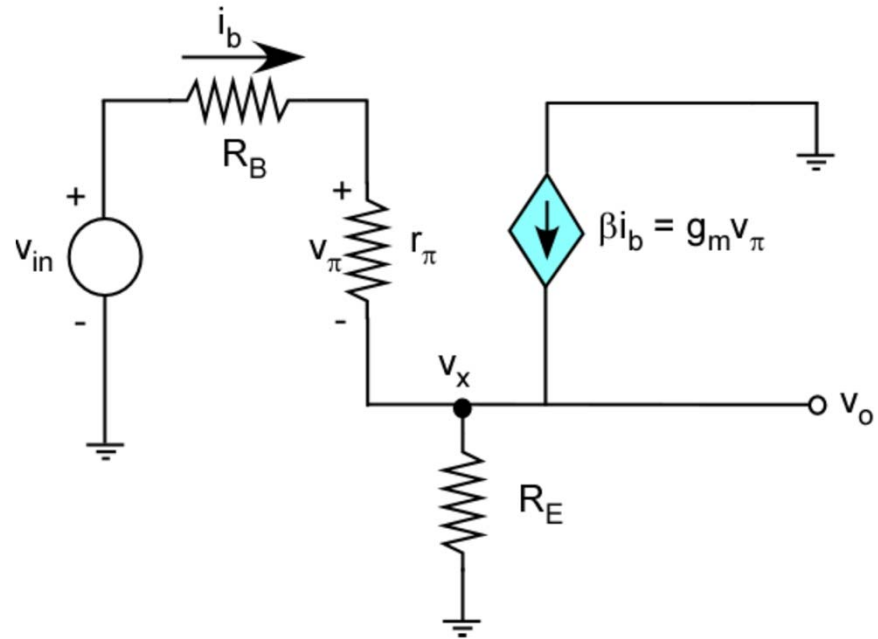

$$r_{in} = \frac{v_{in}}{i_b} = \frac{v_{\pi} \left[1 + R_B / r_{\pi} + R_E (g_m + 1 / r_{\pi}) \right]}{v_{\pi} / r_{\pi}}$$

$$r_{in} = r_{\pi} + R_B + R_E (\beta + 1)$$

Emitter Follower – Output Impedance

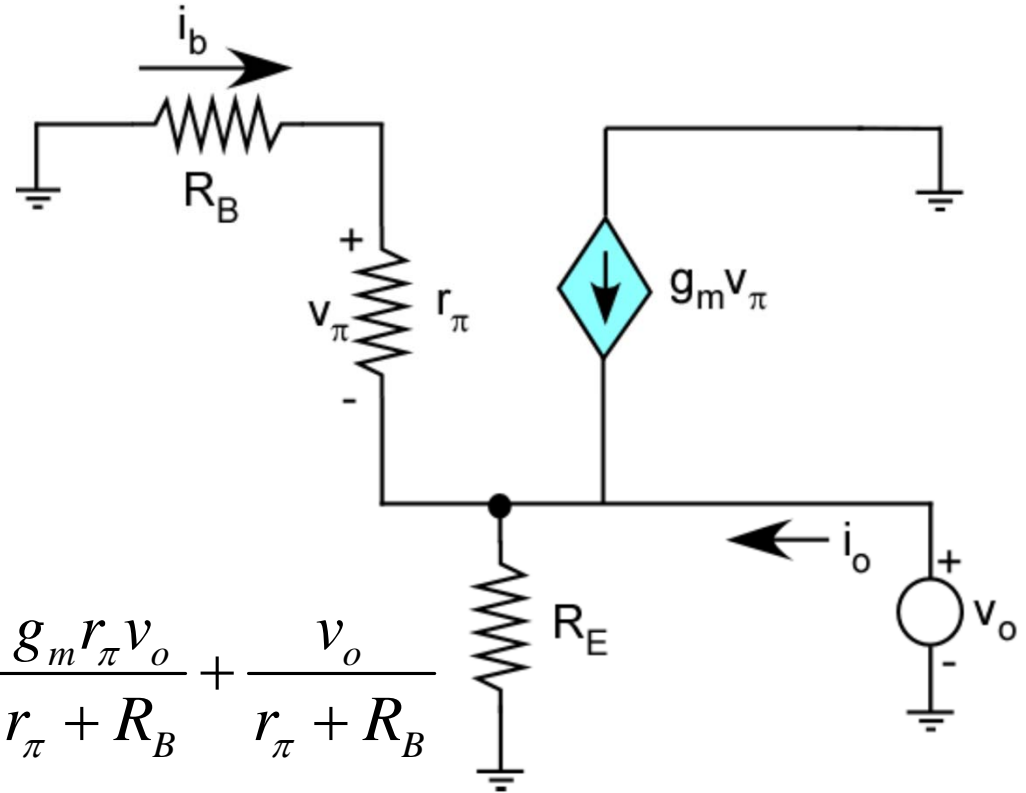

$$i_B = -\frac{v_o}{r_\pi + R_B}$$

$$i_o = \frac{v_o}{R_E} - g_m v_\pi + \frac{v_o}{r_\pi + R_B} = \frac{v_o}{R_E} + \frac{g_m r_\pi v_o}{r_\pi + R_B} + \frac{v_o}{r_\pi + R_B}$$

$$i_o = v_o \left[\frac{1}{R_E} + \frac{g_m}{r_\pi + R_B} + \frac{1}{r_\pi + R_B} \right] = v_o \left[r_\pi + R_B + R_E (\beta + 1) \right] \frac{1}{R_E (r_\pi + R_B)}$$

Output Impedance (cont')

Using $g_m r_\pi = \beta$


$$\frac{v_o}{i_o} = R_{out} = \frac{R_E (r_\pi + R_B)}{r_\pi + R_B + R_E (\beta + 1)} = \frac{R_E (r_\pi + R_B) / (\beta + 1)}{R_E + (r_\pi + R_B) / (\beta + 1)}$$

$$R_{out} = R_E \parallel (r_\pi + R_B) / (\beta + 1)$$

If we neglect R_B

$$A'_{MB} = \frac{(\beta + 1)R_E}{r_\pi + (\beta + 1)R_E} \quad \text{and} \quad R'_{out} = R_E \parallel \frac{r_\pi}{\beta + 1}$$

Common Base Configuration

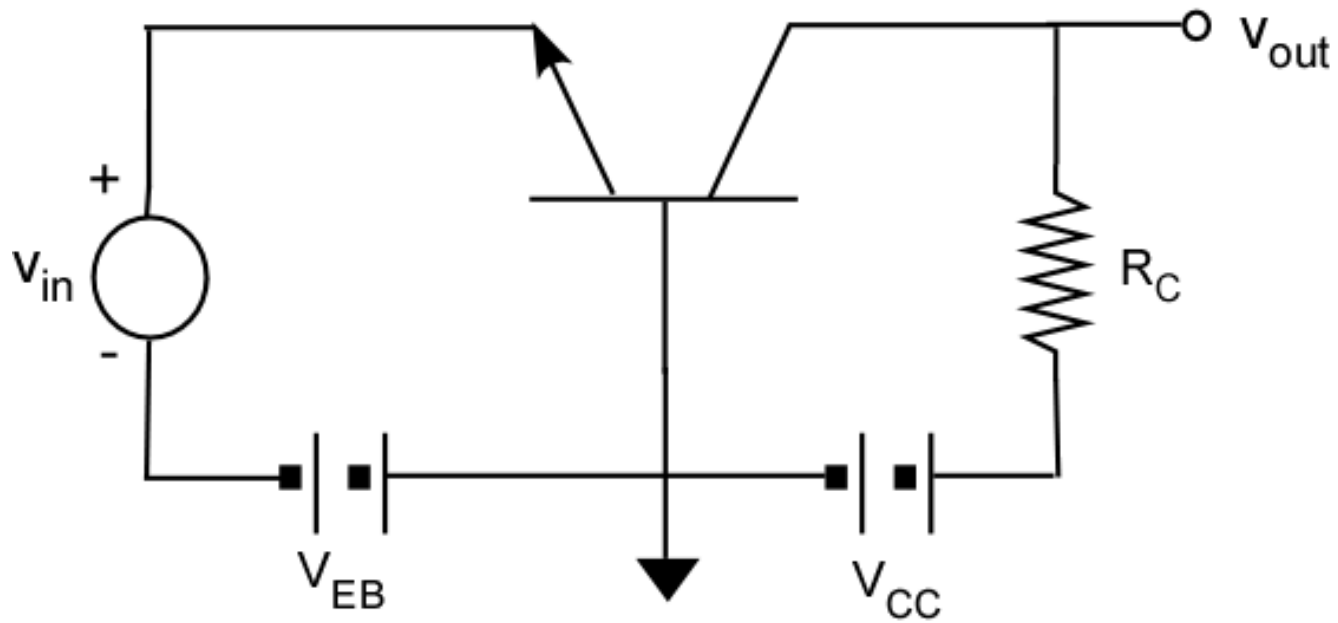


Common Base Configuration

$$v_i = -v_\pi, \quad v_o = -g_m v_\pi R_C = g_m v_i R_C$$

$$\text{Voltage gain} = \frac{v_o}{v_i} = g_m R_C = \frac{\alpha R_C}{r_e}$$

$$\text{Current gain} = \frac{i_o}{i_i} = \frac{g_m v_\pi}{i_i} = \frac{-g_m v_\pi}{\left(g_m + \frac{1}{r_\pi}\right)(-v_\pi)} = \frac{\beta}{\beta + 1} = \alpha$$
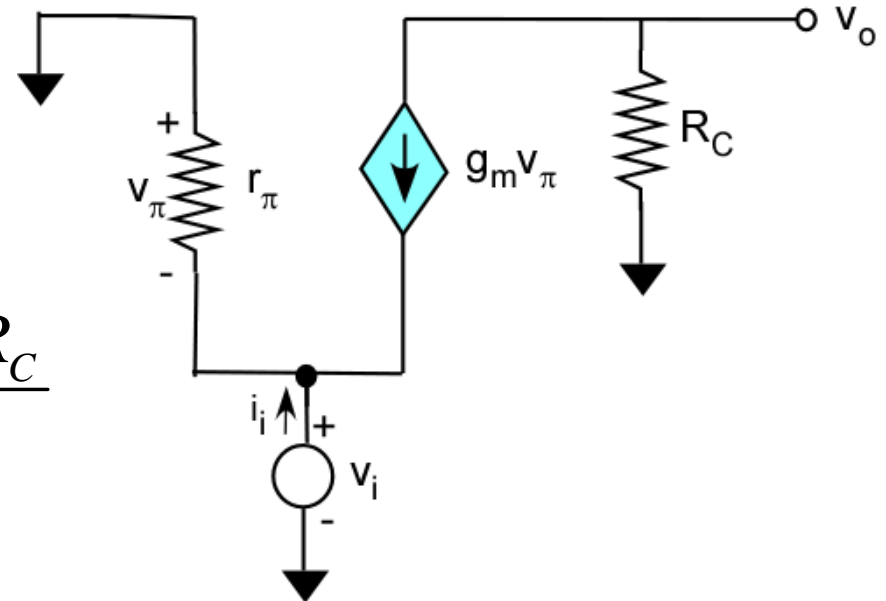
$$R_{out} = R_C \qquad r_{in} = \frac{r_\pi}{\beta + 1}$$



BJT Topologies - Summary

	CE	CB	EF
A_{vo}	$-g_m R_C$	$g_m R_C$	1
R_{in}	r_π	$\frac{r_\pi}{\beta + 1}$	$r_\pi + R_E (\beta + 1)$
R_{out}	R_C	R_C	$R_E \parallel r_\pi / (\beta + 1)$