

ECE 342

Electronic Circuits

Lecture 21

Transfer Functions - 2

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@Illinois.edu

Transfer Function Representation

In general, the transfer function of an amplifier can be expressed as

$$F_H(s) = a_m \frac{(s - Z_1)(s - Z_2) \dots (s - Z_m)}{(s - P_1)(s - P_2) \dots (s - P_m)}$$

Z_1, Z_2, \dots, Z_m are the **zeros** of the transfer function

P_1, P_2, \dots, P_m are the **poles** of the transfer function

s is a complex number $s = \sigma + j\omega$

3dB Frequency Determination

$$A(s) \equiv A_M F_H(s)$$

- Designer is interested in midband operation
- However needs to know upper 3-dB frequency
- In many cases some conditions are met:
 - Zeros are infinity or at very high frequencies
 - One of the poles (ω_{P1}) is at much lower frequency than other poles (→ dominant pole)
- If the conditions are met then $F_H(s)$ can be approximated by:

$$F_H(s) \equiv \frac{1}{1 + s / \omega_{P1}} \quad \text{and we have} \quad \omega_H \cong \omega_{P1}$$

3dB Frequency Determination

If the lowest frequency pole is at least 4 times away from the nearest pole or zero, it is a **dominant pole**

If there is no dominant pole, the 3-dB frequency ω_H can be approximated by:

$$\omega_H \cong 1 / \sqrt{\left(\frac{1}{\omega_{P1}^2} + \frac{1}{\omega_{P2}^2} + \dots \right) - 2 \left(\frac{1}{\omega_{Z1}^2} + \frac{1}{\omega_{Z2}^2} + \dots \right)}$$

Open-Circuit Time Constants

$$F_H(s) = \frac{1 + a_1s + a_2s^2 + \dots + a_ns^n}{1 + b_1s + b_2s^2 + \dots + b_ns^n}$$

The coefficients a and b are related to the frequencies of the zeros and poles respectively.

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \dots + \frac{1}{\omega_{pn}}$$

b_1 can be obtained by summing the individual time constants of the circuit using the *open-circuit time constant method*

Open-Circuit Time Constant Method

- The time constant of each capacitor in the circuit is evaluated. It is the product of the capacitance and the resistance seen across its terminals with:
 - All other internal capacitors open circuited
 - All independent voltage sources short circuited
 - All independent current sources opened
- The value of b_1 is computed by summing the individual time constants

$$b_1 = \sum_{i=1}^n C_i R_{i_o}$$

Open-Circuit Time Constant Method

- An approximation can be made by using the value of b_1 to determine the 3dB upper frequency point ω_H
- If the zeros are not dominant and if one of the poles P_1 is dominant, then

$$b_1 \approx \frac{1}{\omega_{P1}}$$


Assuming that the 3-dB frequency will be approximately equal to ω_{P1}

$$\omega_H \approx \frac{1}{b_1} = \frac{1}{\sum_i C_i R_{io}}$$

Bandwidth of Multistage Amplifier

- The poles of a multistage amplifier are difficult to obtain analytically
- An approximate value for the 3dB upper frequency point ω_{3dB} can be obtained by assigning an open circuit time constant τ_{i0} to each capacitor C_i

High-Frequency Behavior - Example

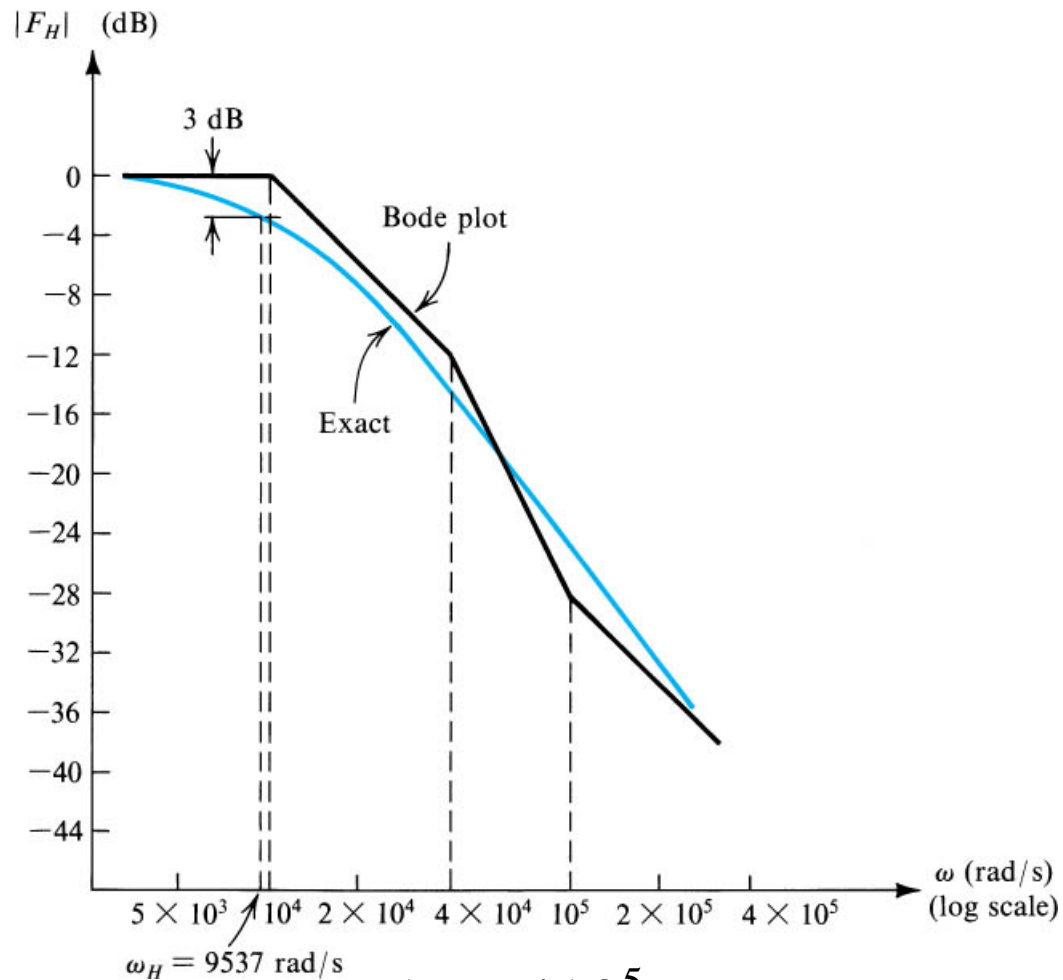

$$F_H(s) \equiv \frac{1 - s / 10^5}{(1 + s / 10^4)(1 + s / 4 \times 10^4)}$$