

# ECE 342

# Electronic Circuits

## Lecture 22



## Transistor Capacitances

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jesa@Illinois.edu
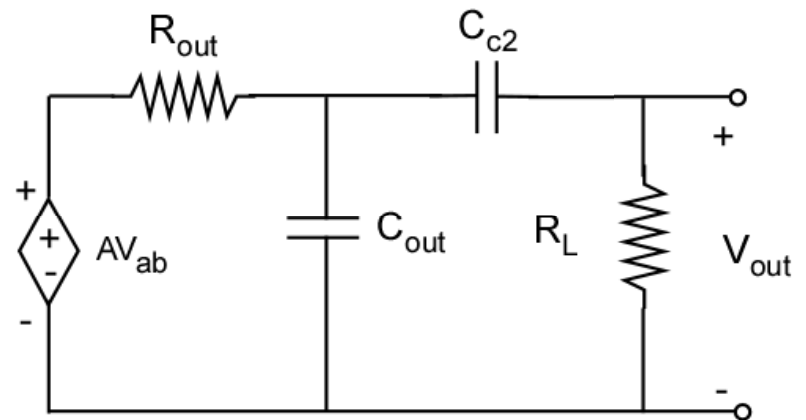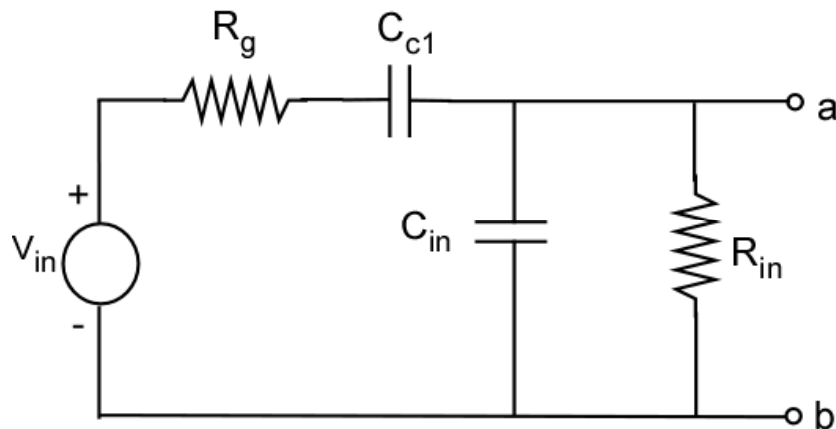
# Model for general Amplifying Element


$C_{c1}$  and  $C_{c2}$  are coupling capacitors (large)  $\rightarrow \mu\text{F}$

$C_{in}$  and  $C_{out}$  are parasitic capacitors (small)  $\rightarrow \text{pF}$


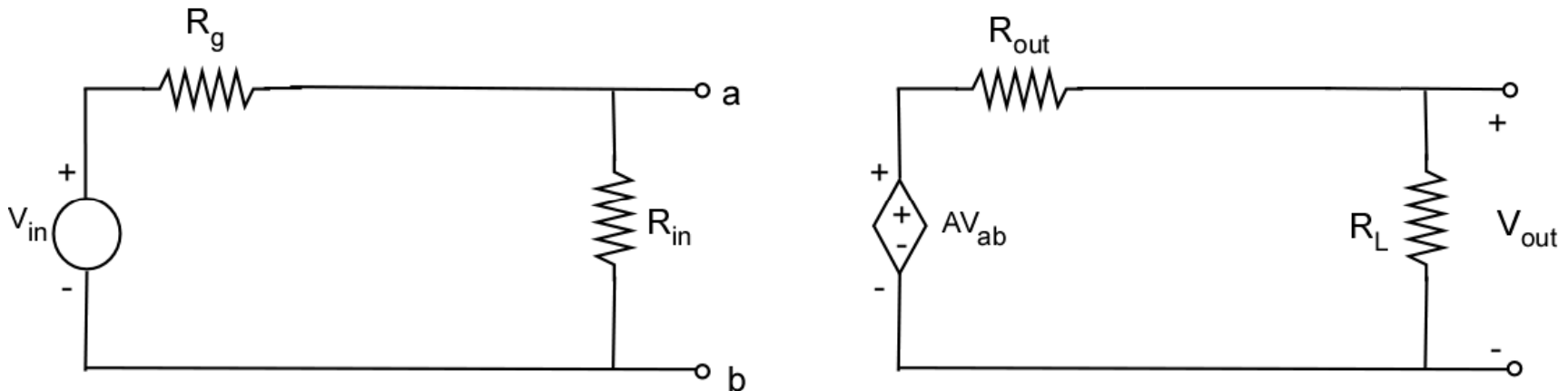
# Midband Frequencies



- Coupling capacitors are short circuits
- Parasitic capacitors are open circuits



$$A_{MB} = \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_g + R_{in}} A \frac{R_L}{R_{out} + R_L}$$
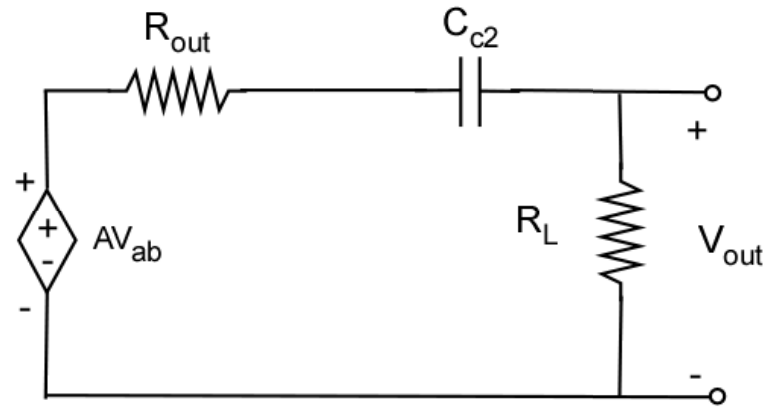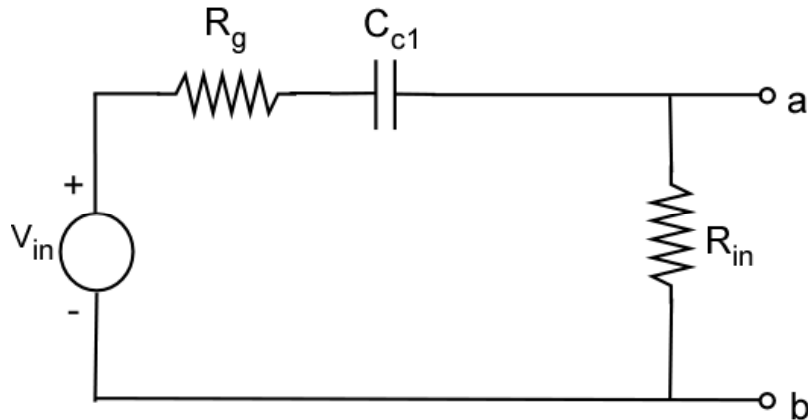
# Low Frequency Model

- Coupling capacitors are present
- Parasitic capacitors are open circuits



$$v_{ab} = \frac{v_{in} R_{in}}{R_g + R_{in} + \frac{1}{j\omega C_{c1}}} = \frac{v_{in} j\omega C_{c1} R_{in}}{1 + j\omega C_{c1} (R_g + R_{in})}$$

$$v_{ab} = v_{in} \frac{R_{in}}{R_g + R_{in}} \cdot \frac{j\omega C_{c1} (R_g + R_{in})}{\left[1 + j\omega C_{c1} (R_g + R_{in})\right]}$$

# Low Frequency Model

$$\text{define } f_{l1} = \frac{1}{2\pi(R_g + R_{in})C_{c1}} \text{ and } f_{l2} = \frac{1}{2\pi(R_L + R_{out})C_{c2}}$$

$$v_{ab} = v_{in} \frac{R_{in}}{R_g + R_{in}} \cdot \frac{jf / f_{l1}}{1 + jf / f_{l1}}$$

$$\text{Similarly, } v_{out} = Av_{ab} \frac{R_L}{R_L + R_{out}} \cdot \frac{jf / f_{l2}}{1 + jf / f_{l2}}$$

# Low Frequency Model

$$\text{Overall gain} = \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_g + R_{in}} \cdot A \cdot \frac{R_L}{R_L + R_{out}} \cdot \frac{jf / f_{l1}}{1 + jf / f_{l1}} \cdot \frac{jf / f_{l2}}{1 + jf / f_{l2}}$$

$$\frac{v_{out}}{v_{in}} = A_{MB} \cdot \frac{jf / f_{l1}}{1 + jf / f_{l1}} \cdot \frac{jf / f_{l2}}{1 + jf / f_{l2}}$$

# Example


$$R_{out} = 3 \text{ k}\Omega, R_g = 200 \text{ }\Omega, R_{in} = 12 \text{ k}\Omega, R_L = 10 \text{ k}\Omega$$
$$C_{c1} = 5 \text{ }\mu\text{F} \text{ and } C_{c2} = 1 \text{ }\mu\text{F}$$

$$f_{l1} = \frac{1}{2\pi(12,200 \times 5 \times 10^{-6})} = 2.61 \text{ Hz}$$


$$f_{l2} = \frac{1}{2\pi(13,000 \times 10^{-6})} = 12.2 \text{ Hz}$$
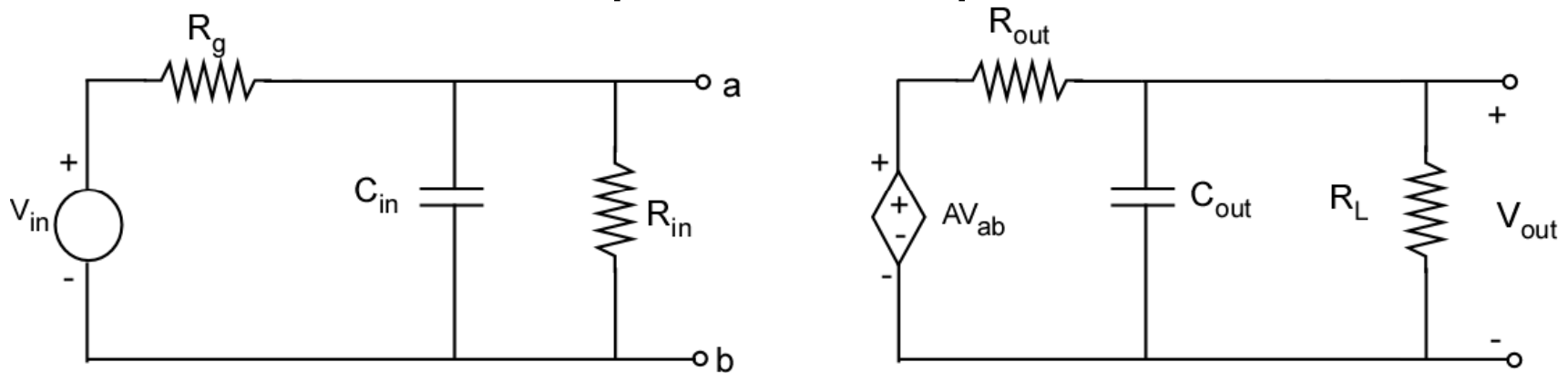
# High Frequency Model

- Assume coupling capacitors are short
- Account for parasitic capacitors



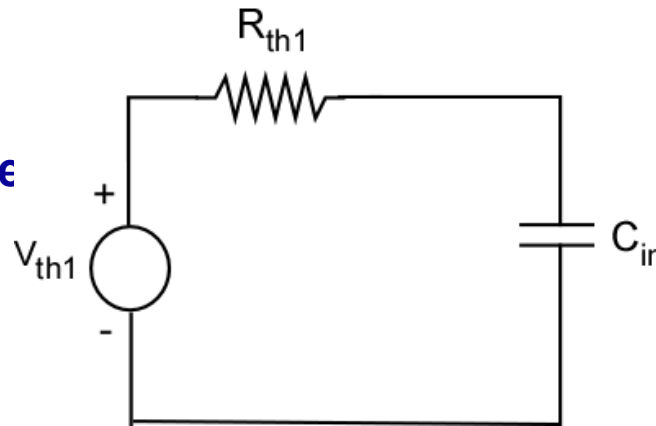Potential Thevenin  
equivalent for input as seen  
by  $C_{in}$



$$V_{th1} = \frac{v_{in} R_{in}}{R_g + R_{in}}$$

$$R_{th1} = R_g \parallel R_{in}$$



# High Frequency Model

$$v_{ab} = \frac{v_{in} R_{in}}{R_g + R_{in}} \cdot \frac{1}{1 + j\omega C_{in} R_{th1}}$$

$$v_{ab} = \frac{v_{in} R_{in}}{R_g + R_{in}} \cdot \frac{1}{1 + jf / f_{h1}} \quad \text{where} \quad f_{h1} = \frac{1}{2\pi R_{th1} C_{in}}$$

$$\text{Likewise } v_{out} = \frac{A v_{ab} R_L}{R_{out} + R_L} \cdot \frac{1}{1 + j\omega C_{out} R_{th2}}$$

$$\text{with } R_{th2} = R_{out} \parallel R_L$$

$$v_{out} = \frac{A v_{ab} R_L}{R_L + R_{out}} \cdot \frac{1}{1 + jf / f_{h2}} \quad \text{where} \quad f_{h2} = \frac{1}{2\pi R_{th2} C_{out}}$$

# High Frequency

Overall gain is:

$$\frac{v_o}{v_i} = A \cdot \frac{R_{in}}{R_{in} + R_g} \cdot \frac{R_L}{R_L + R_{out}} \cdot \frac{1}{1 + jf / f_{h1}} \cdot \frac{1}{1 + jf / f_{h2}}$$

or

$$\frac{v_o}{v_i} = A_{MB} \cdot \frac{1}{1 + jf / f_{h1}} \cdot \frac{1}{1 + jf / f_{h2}}$$

# Example

**Example:**  $R_{out} = 3 \text{ k}\Omega$ ,  $R_g = 200 \text{ }\Omega$ ,  $R_{in} = 12 \text{ k}\Omega$ ,  $R_L = 10 \text{ k}\Omega$   
 $C_{in} = 200 \text{ pF}$  and  $C_{out} = 40 \text{ pF}$

$$f_{h1} = \frac{1}{2\pi \times 2 \times 10^{-10} \times (12,200 \parallel 200)} = 4.05 \text{ MHz}$$

$$f_{h2} = \frac{1}{2\pi \times 40 \times 10^{-12} \times (10,000 \parallel 3,000)} = 1.72 \text{ MHz}$$

**Summary:** low-frequency < 12.2 Hz, High frequency > 1.72 MHz

$$\log\left(\frac{4.05 \times 10^6}{12.2}\right) = 5.52 \simeq 5 \text{ decades}$$

# MOSFET - Gate Capacitance Effect

Triode region:  $C_{gs} = C_{gd} = \frac{1}{2}WLC_{ox}$

Saturation region:  $C_{gs} = \frac{2}{3}WLC_{ox}$   $C_{gd} = 0$

Cutoff:  $C_{gd} = C_{gs} = 0$


$$C_{gb} = WLC_{ox}$$

# MOSFET – Junction Capacitances


Overlap capacitance (gate-to-source):  $C_{ov} = WL_{ov}C_{ox}$

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}}$$
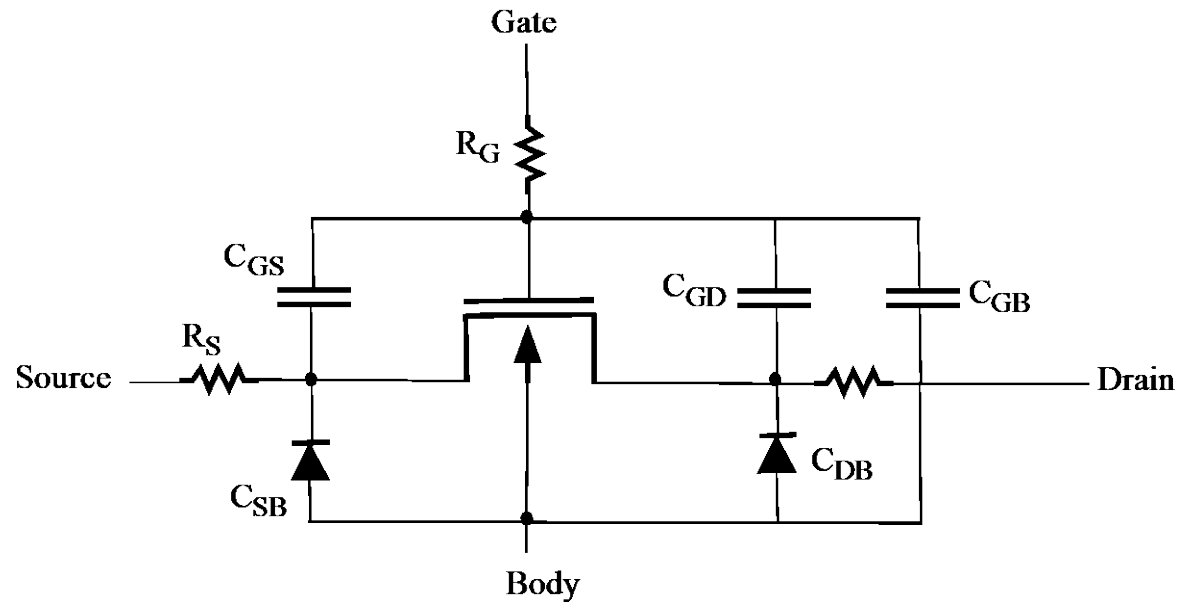
$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DB}}{V_o}}}$$



# MOSFET High-Frequency Model

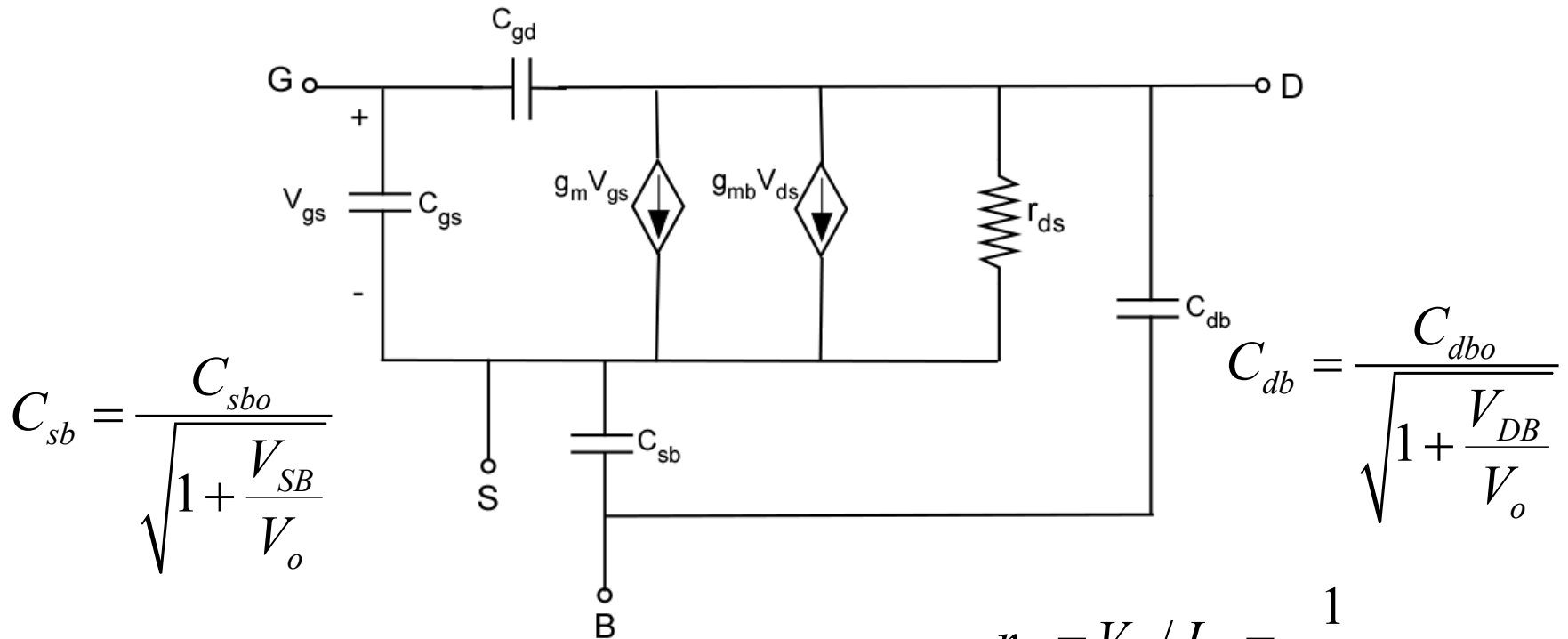

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}}$$

$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DB}}{V_o}}}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{eff} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \frac{2 I_D}{V_{eff}}$$

$$g_{mb} = \chi g_m = \frac{\gamma}{2 \sqrt{2 \phi_F + V_{sb}}} g_m$$

$$r_{ds} = V_A / I_D = \frac{1}{\lambda I_D}$$

$$C_{gs} = \frac{2}{3} W L C_{ox} + W L_{ov} C_{ox}$$

$$C_{gd} = W L_{ov} C_{ox}$$

# BJT Capacitances

Base: Diffusion Capacitance:  $C_{de}$  (small signal)

$$C_{de} \equiv \frac{dQ_n}{dv_{BE}}$$

where  $Q_n$  is the minority carrier charge in base

$$C_{de} = \tau_F \frac{di_C}{dv_{BE}} = \tau_F g_m = \frac{\tau_F I_C}{V_T}$$

where  $\tau_F$  is the forward transit time (time spent crossing base)

# BJT Capacitances

Base-emitter junction capacitance:

$$C_{je} = \frac{C_{je0}}{\left(1 - \frac{V_{BE}}{V_{oe}}\right)^m}$$

$C_{je0}$  is  $C_{je}$  at 0 V.  $V_{oe}$  is EBJ built in voltage  $\sim 0.9$  V  
 $m$  is the grading coefficient (typically, 0.2-0.5)



# BJT Capacitances

In hybrid pi model,  $C_{de} + C_{je} = C_{\pi}$

Collector-base junction capacitance

$$C_{\mu} = \frac{C_{\mu o}}{\left(1 + \frac{V_{CB}}{V_{oc}}\right)^m}$$


$C_{\mu o}$  is  $C_{\mu}$  at 0 V.  $V_{oc}$  is CBJ built in voltage  $\sim 0.9$  V

$C_{\pi}$  is around a few tens of pF

$C_{\mu}$  is around a few pF

$m$  is the grading coefficient (typically, 0.2-0.5)

# High-Frequency Hybrid- $\pi$ Model

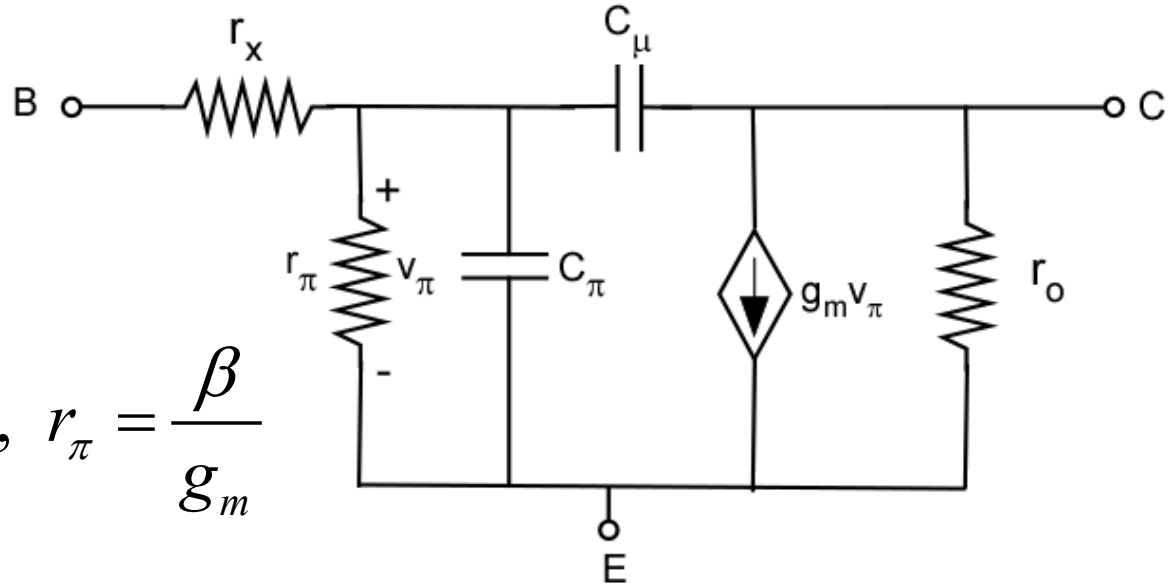


$$g_m = \frac{I_C}{V_T}, \quad r_o = \frac{|V_A|}{I_C}, \quad r_\pi = \frac{\beta}{g_m}$$



$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T}, \quad C_\pi = C_{de} + C_{je}, \quad C_{de} = \tau_F g_m$$

$$C_\mu = \frac{C_{jco}}{\left(1 + \frac{V_{CB}}{V_{oc}}\right)^m}, \quad m = 0.3 - 0.5 \quad f_T = \frac{g_m}{2\pi (C_\pi + C_\mu)}$$

# CS - Three Frequency Bands

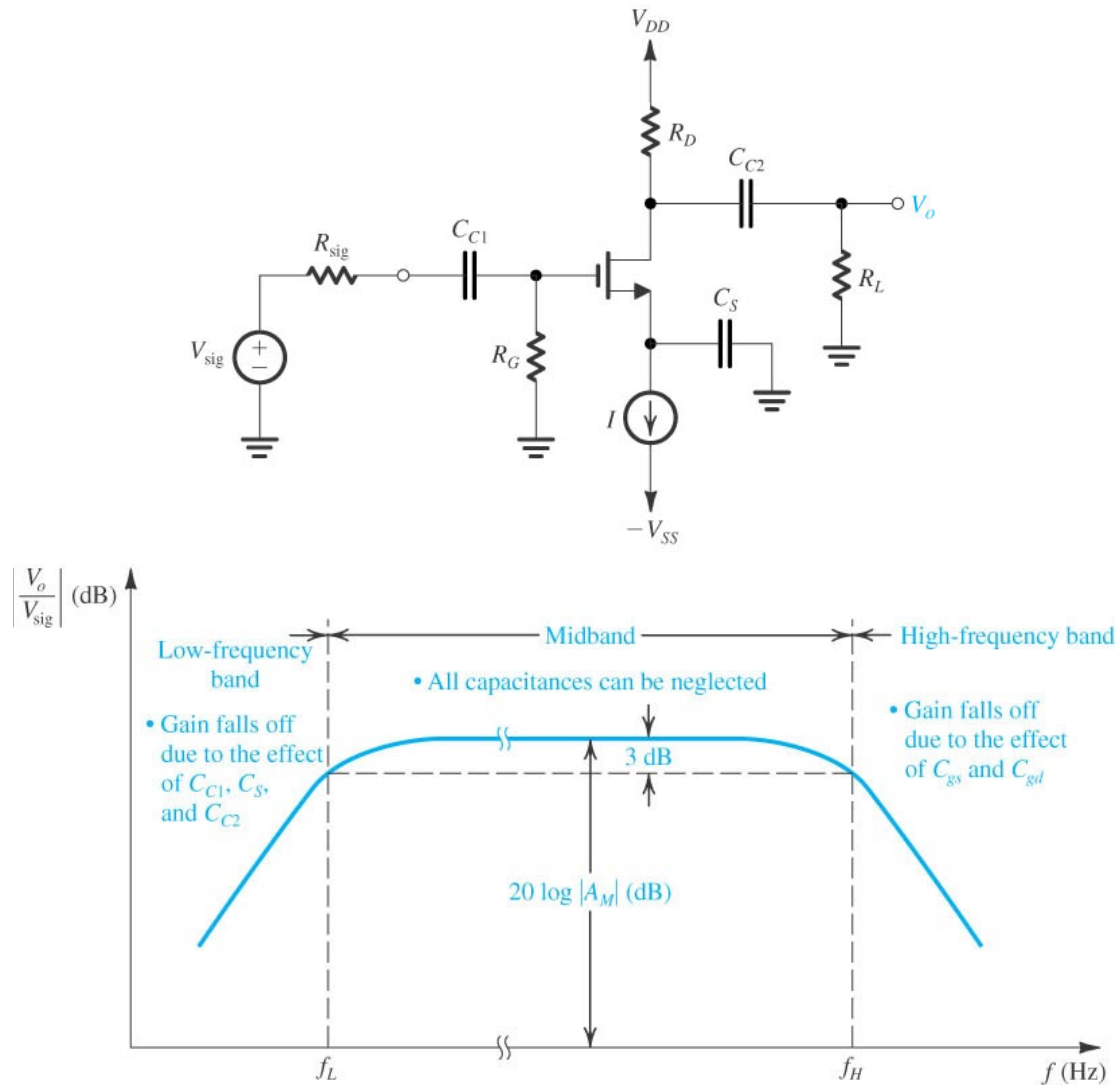


# CE - Three Frequency Bands

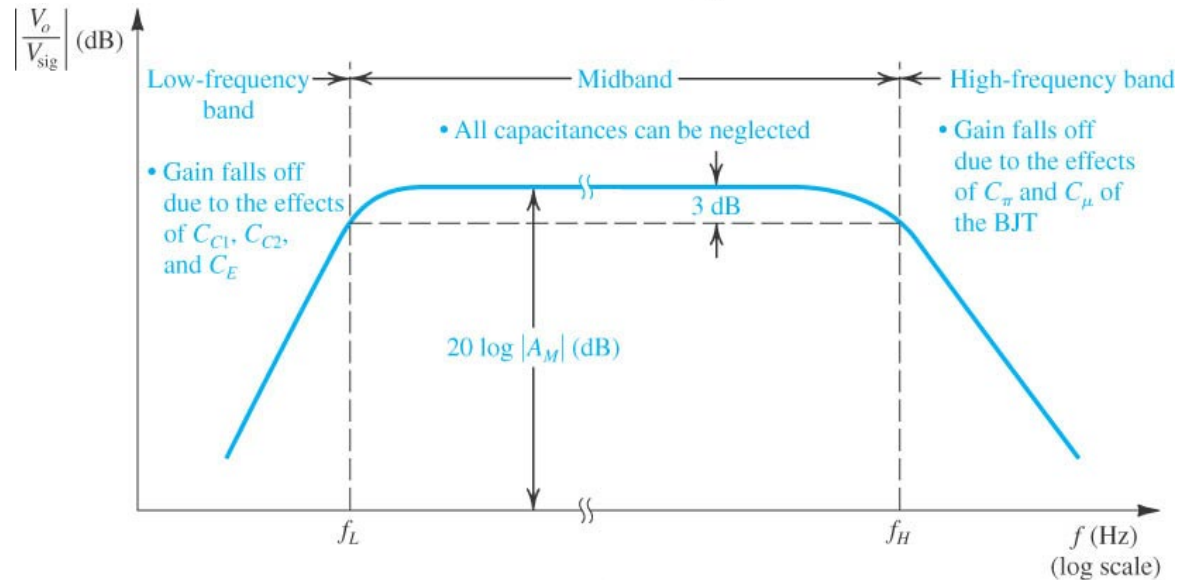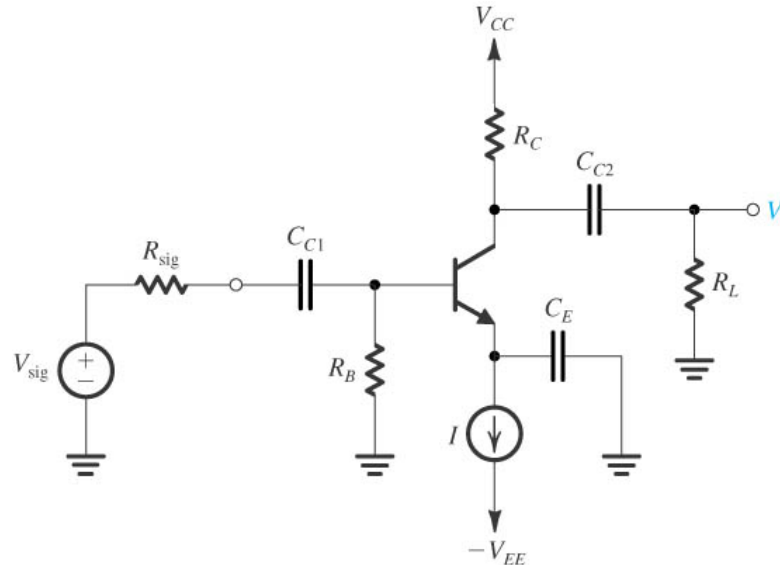
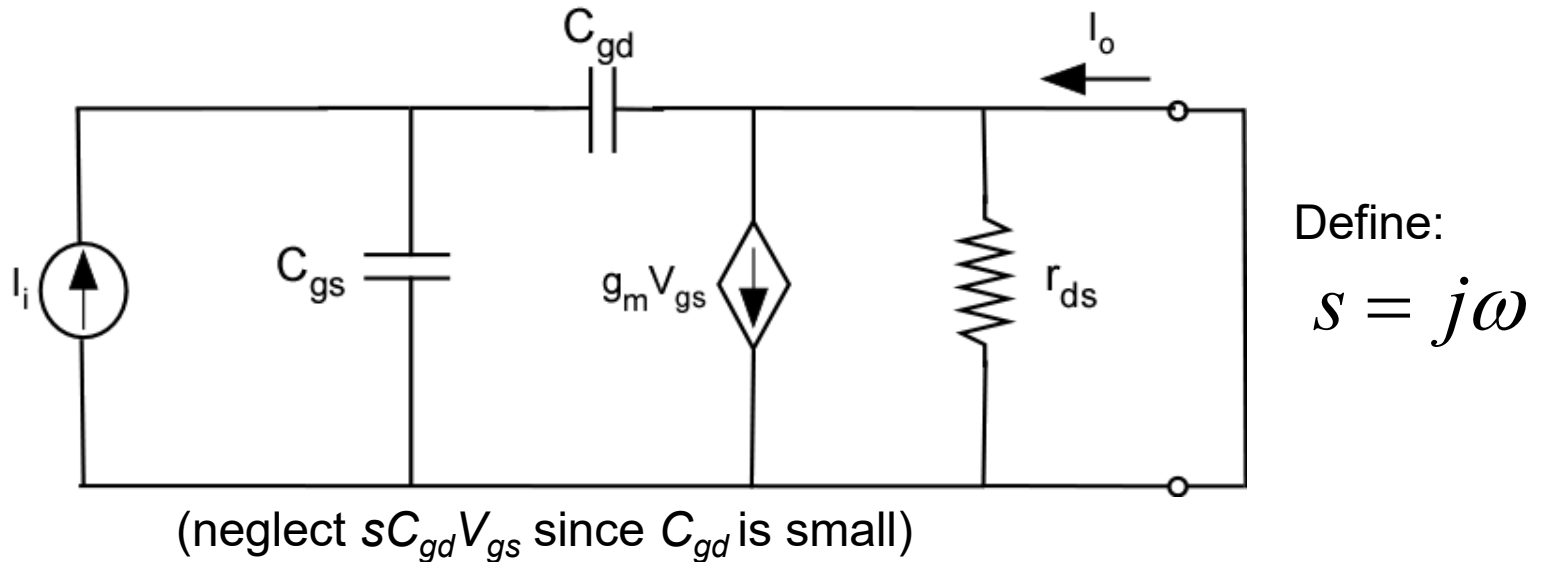
# Unity-Gain Frequency $f_T$

$f_T$  is defined as the frequency at which the short-circuit current gain of the common source configuration becomes unity



$$I_o = g_m V_{gs} - sC_{gd} V_{gs}$$

$$\frac{I_o}{I_i} = \frac{g_m}{s(C_{gs} + C_{gd})}$$

$$I_o \approx g_m V_{gs} \quad V_{gs} = \frac{I_i}{s(C_{gs} + C_{gd})}$$


# Calculating $f_T$

For  $s=j\omega$ , magnitude of current gain becomes unity at

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}} \Rightarrow f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$f_T \sim 100$  MHz for  $5\text{-}\mu\text{m}$  CMOS,  $f_T \sim$  several GHz for  $0.13\mu\text{m}$  CMOS

# BJT - Short-Circuit Current Gain

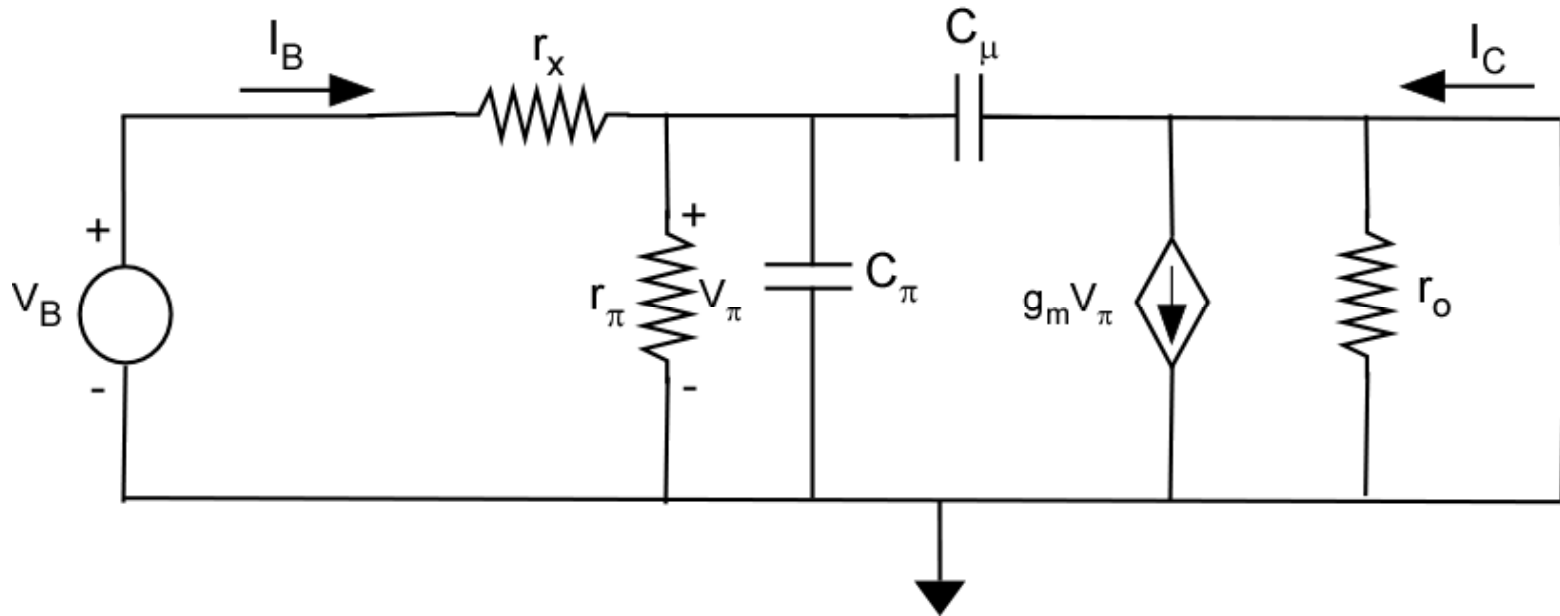

$$I_C = (g_m - sC_\mu) v_\pi$$

$$v_\pi = \frac{I_B}{\frac{1}{r_\pi} + sC_\mu + sC_\pi}$$

# BJT - Short-Circuit Current Gain

Define  $h_{fe}$  as short-circuit current gain

$$h_{fe} = \frac{I_C}{I_B} = \frac{g_m - sC_\mu}{\frac{1}{r_\pi} + s(C_\pi + C_\mu)}$$

$g_m \gg sC_\mu$  at freq. of interest

$$h_{fe} = \frac{I_C}{I_B} = \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi}$$



# BJT - Short-Circuit Current Gain

$$h_{fe} = \frac{\beta_o}{1 + s(C_\pi + C_\mu)r_\pi}$$

Define  $h_{fe}$  has a single pole (or STC) response.  
Unity gain bandwidth is for:

$$h_{fe} = \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi} = 1 \quad \text{or} \quad \frac{g_m}{2\pi f_T (C_\pi + C_\mu)} = 1$$

In some cases, if  $C_\mu$  is known, then

# BJT - Short-Circuit Current Gain

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

From which we get

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{g_m}{\omega_T}$$

$$\text{Thus, } C_\pi + C_\mu = \frac{g_m}{\omega_T} \Rightarrow C_\pi = \frac{g_m}{\omega_T} - C_\mu$$