

ECE 342

Electronic Circuits


Lecture 24

CS Frequency Response

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@Illinois.edu

MOSFET Amp Bandwidth

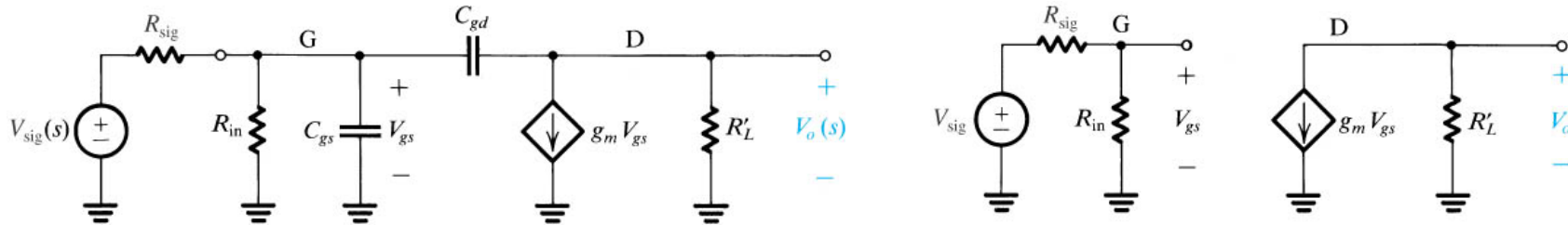
MOSFET amplifier has $R_{sig} = 100 \text{ k}\Omega$, $C_{gs} = C_{gd} = 1 \text{ pF}$, $g_m = 4 \text{ mA/V}$ and $R_L' = 3.33 \text{ k}\Omega$. Find midband voltage gain and 3-dB frequency.



$$A_M = \frac{V_o}{V_{sig}} = -\frac{R_{in}}{R_{in} + R_{sig}} (g_m R_L') = -\frac{420}{420 + 100} \times 4 \times 3.33 = -10.8$$

MOSFET Amp Analysis

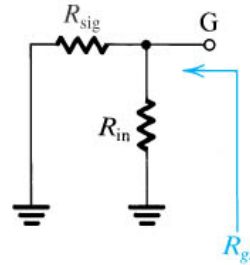To determine the 3-dB frequency, we first evaluate the time constant associated with C_{gs} . First, we determine the resistance R_{gs} seen by C_{gs} . The capacitance C_{gd} is removed and V_{sig} is short-circuited




$$R_{gs} = R_{in} \parallel R_{sig} = 420 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 80.8 \text{ k}\Omega$$

The time constant associated with C_{gs} is

$$\tau_{gs} = C_{gs} R_{gs} = 1 \times 10^{-12} \times 80.8 \times 10^3 = 80.8 \text{ ns}$$

MOSFET Amp Analysis

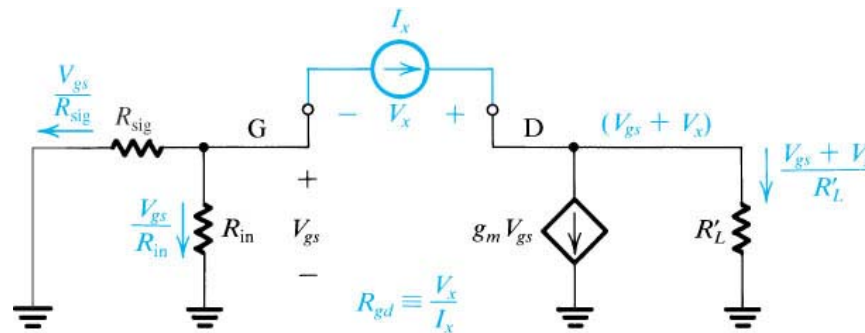The resistance R_{gd} seen by C_{gd} is found by setting $C_{gs} = 0$ and short-circuiting V_{sig}



$$I_x = -\frac{V_{gs}}{R_{in}} - \frac{V_{gs}}{R_{sig}}$$

$$V_{gs} = -I_x R'$$

$$R' = R_{in} \parallel R_{sig}$$

$$I_x = g_m V_{gs} + \frac{V_{gs} + V_x}{R'_L}$$

$$R_{gd} = \frac{V_x}{I_x} = R' + R'_L + g_m R'_L R'$$

MOSFET Amp Analysis

The open-circuit time constant of C_{gd} is

$$\tau_{gd} = C_{gd} R_{gd} = 1 \times 10^{-12} \times 1.16 \times 10^6 = 1160 \text{ ns}$$

The upper 3-dB frequency ω_H can now be determined from

$$\omega_H = \frac{1}{\tau_{gs} + \tau_{gd}} = \frac{1}{(80.8 + 1160) \times 10^{-9}} = 806 \text{ krad / s}$$

$$f_H = \frac{\omega_H}{2\pi} = 128.3 \text{ kHz}$$