

# ECE 342

## Electronic Circuits

### Lecture 33

# CMOS Characteristics

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jesa@illinois.edu

# Digital Circuits

$V_{IH}$ : Input voltage at high state  $\rightarrow V_{IHmin}$

$V_{IL}$ : Input voltage at low state  $\rightarrow V_{ILmax}$

$V_{OH}$ : Output voltage at high state  $\rightarrow V_{OHmin}$

$V_{OL}$ : Output voltage at low state  $\rightarrow V_{OLmin}$

Likewise for current we can define

Currents into input

$$\begin{array}{l} I_{IH} \leftrightarrow I_{IHmax} \\ I_{IL} \leftrightarrow I_{ILmax} \end{array}$$

Currents into output

$$\begin{array}{l} I_{OH} \leftrightarrow I_{OHmax} \\ I_{OL} \leftrightarrow I_{OLmax} \end{array}$$

# Voltage Transfer Characteristics (VTC)

The static operation of a logic circuit is determined by its VTC

- In low state: noise margin is  $NM_L$


$$NM_L = V_{IL} - V_{OL}$$

- In high state: noise margin is  $NM_H$

$$NM_H = V_{OH} - V_{IH}$$


- An ideal VTC will maximize noise margins

Optimum:  $NM_L = NM_H = V_{DD} / 2$

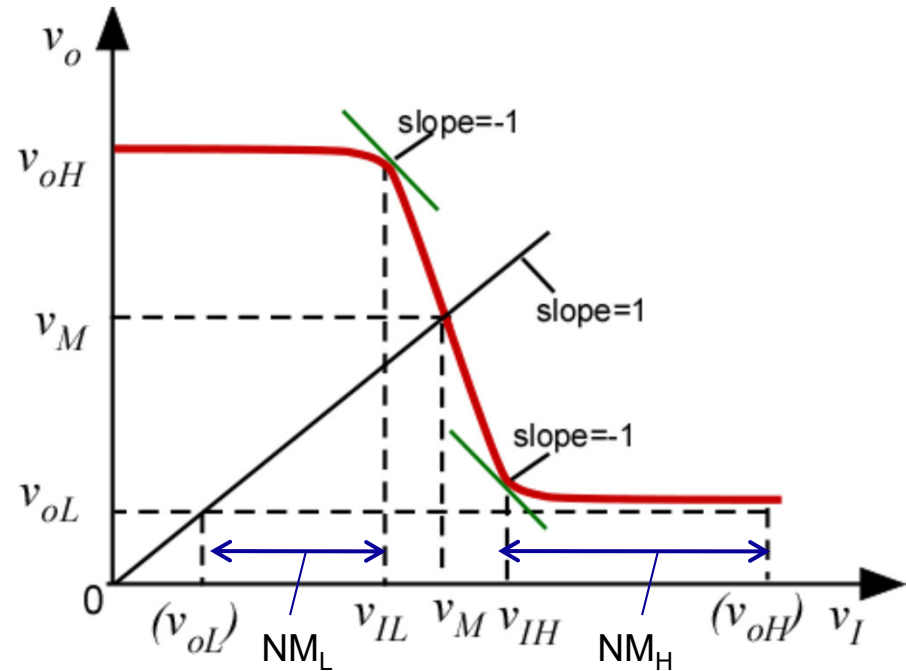

$V_{IL}$  and  $V_{IH}$  are the points where the slope of the VTC=-1

# Switching Time & Propagation Delay

 

# Switching Time & Propagation Delay

$t_r$ =rise time (from 10% to 90%)

$t_f$ =fall time (from 90% to 10%)

$t_{pLH}$ =low-to-high propagation delay

$t_{pHL}$ =high-to-low propagation delay

Inverter propagation delay:

$$t_p = \frac{1}{2} (t_{pLH} + t_{pHL})$$

# VTC and Noise Margins

For a logic-circuit family employing a 3-V supply, suggest an ideal set of values for  $V_{th}$ ,  $V_{IL}$ ,  $V_{IH}$ ,  $V_{OH}$ ,  $NM_L$ ,  $NM_H$ . Also, sketch the VTC. What value of voltage gain in the transition region does your ideal specification imply?

**Ideal 3V logic implies:**

$$V_{OH} = V_{DD} = 3.0V; \quad V_{OL} = 0.0V$$


$$V_{th} = V_{DD} / 2 = 3.0 / 2 = 1.5V;$$

$$V_{IL} = V_{DD} / 2 = 1.5V; \quad V_{IH} = V_{DD} / 2 = 1.5V$$
 
# VTC and Noise Margins

$$NM_H = V_{OH} - V_{IH} = 3.0 - 1.5 = 1.5V$$

$$NM_L = V_{IL} - V_{OL} = 1.5 - 0.0 = 1.5V$$



Inverting transfer characteristics

The gain in the transition region is:

$$\begin{aligned} (V_{OH} - V_{OL}) / (V_{IH} - V_{IL}) &= (3.0 - 0.0) / (1.5 - 1.5) \\ &= 3 / 0 = \infty V / V \end{aligned}$$

# CMOS Noise Margins

When inverter threshold is at  $V_{DD}/2$ , the noise margin  $NM_H$  and  $NM_L$  are equalized

$$NM_H = NM_L = \frac{3}{8} \left( V_{DD} + \frac{2}{3} V_{th} \right)$$

$NM_H$ : noise margin for high input


$NM_L$ : noise margin for low input

$V_{th}$ : threshold voltage

Noise margins are typically around  $0.4 V_{DD}$ ; close to half power-supply voltage →  
CMOS ideal from noise-immunity standpoint



# CMOS Inverter VTC

 

**$Q_P$  and  $Q_N$  are matched**

# CMOS Inverter VTC

## Derivation

- Assume that transistors are matched
- Vertical segment of VTC is when both  $Q_N$  and  $Q_P$  are saturated
- No channel length modulation effect  $\rightarrow \lambda = 0$
- Vertical segment occurs at  $v_i = V_{DD}/2$
- $V_{IL}$ : maximum permitted logic-0 level of input (slope=-1)
- $V_{IH}$ : minimum permitted logic-1 level of input (slope=-1)

To determine  $V_{IH}$ , assume  $Q_N$  in triode region and  $Q_P$  in saturation region

$$(v_I - V_t)v_o - \frac{1}{2}v_o^2 = \frac{1}{2}(V_{DD} - v_I - V_t)^2$$

Next, we differentiate both sides relative to  $v_i$

$$(v_I - V_t)\frac{dv_o}{dv_I} + v_o - v_o\frac{dv_o}{dv_I} = -(V_{DD} - v_I - V_t)$$

# CMOS Inverter VTC

Substitute  $v_i = V_{IH}$  and  $dv_o/dv_i = -1$

$$v_o = V_{IH} - \frac{V_{DD}}{2}$$

After substitutions, we get

$$V_{IH} = \frac{1}{8}(5V_{DD} - 2V_t)$$

Same analysis can be repeated for  $V_{IL}$  to get

$$V_{IL} = \frac{1}{8}(3V_{DD} + 2V_t)$$


# CMOS Inverter Noise Margins

$$V_{IH} = \frac{1}{8}(5V_{DD} - 2V_t)$$

$$V_{IL} = \frac{1}{8}(3V_{DD} + 2V_t)$$

$$NM_H = \frac{1}{8}(3V_{DD} + 2V_t)$$


$$NM_L = \frac{1}{8}(3V_{DD} + 2V_t)$$

 

**Symmetry in VTC → equal noise margins**
 
# Matched CMOS Inverter VTC

CMOS inverter can be made to switch at specific threshold voltage by appropriately sizing the transistors



$$\left(\frac{W}{L}\right)_p = \frac{\mu_n}{\mu_p} \left(\frac{W}{L}\right)_n$$

**Symmetrical transfer characteristics is obtained via matching  $\rightarrow$  equal current driving capabilities in both directions (pull-up and pull-down)**

# VTC and Noise Margins - Problem

An inverter is designed with equal-sized NMOS and PMOS transistors and fabricated in a 0.8-micron CMOS technology for which  $k_n' = 120 \mu\text{A}/\text{V}^2$ ,  $k_p' = 60 \mu\text{A}/\text{V}^2$ ,  $V_{tn} = |V_{tp}| = 0.7 \text{ V}$ ,  $V_{DD} = 3\text{V}$ ,  $L_n = L_p = 0.8 \mu\text{m}$ ,  $W_n = W_p = 1.2 \mu\text{m}$ , find  $V_{IL}$ ,  $V_{IH}$  and the noise margins.

**Equal sizes NMOS and PMOS, but  $k_n' = 2k_p'$**

$$V_t = 0.7\text{V}$$

**For  $V_{IH}$ :  $Q_N$  in triode and  $Q_P$  in saturation**

$$k_n' \left( \frac{W}{L} \right)_n \left[ (V_I - V_t) V_o - \frac{1}{2} V_o^2 \right] = \frac{1}{2} k_p' \left( \frac{W}{L} \right)_p (V_{DD} - V_I - V_t)^2$$

# VTC and Noise Margins – Problem (cont')

$$4(V_I - V_t)V_o - 2V_o^2 = (V_{DD} - V_I - V_t)^2 \quad (1)$$

**Differentiating both sides relative to  $V_I$  results in:**

$$\frac{\partial}{\partial V_I} : 4(V_I - V_t)\frac{\partial V_o}{\partial V_I} + 4V_o - 4V_o\frac{\partial V_o}{\partial V_I} = 2(V_{DD} - V_I - V_t)(-1)$$

**Substitute the values together with:**

$$V_I = V_{IH} \quad \text{and} \quad \frac{\partial V_o}{\partial V_I} = -1$$

## VTC and Noise Margins – Problem (cont')

$$4(V_{IH} - 0.7)(-1) + 4V_o + 4V_o = 2(V_{IH} - 3 + 0.7)$$

$$V_{IH} = \frac{8V_o + 7.4}{6} = 1.33V_o + 1.23 \quad (2)$$

From (1):  $4(V_{IH} - 0.7)V_o - 2V_o^2 = (3 - V_{IH} - 0.7)^2$

$$4(V_{IH} - 0.7)V_o - 2V_o^2 = (2.3 - V_{IH})^2 \quad (3)$$

solving (2) & (3):  $1.55V_o^2 + 4.97V_o - 1.14 = 0$

$$\Rightarrow V_o = 0.22 V \quad V_{IH} = 1.52 V$$



# VTC and Noise Margins – Problem (cont')

For  $V_{IL}$ :  $Q_N$  is in saturation and  $Q_P$  in triode

$$\frac{1}{2}k'_n \left(\frac{W}{L}\right)_n (V_I - V_t)^2 = k'_p \left(\frac{W}{L}\right)_p \left[ (V_{DD} - V_I - V_t)(V_{DD} - V_o) - \frac{1}{2}(V_{DD} - V_o)^2 \right]$$

$$(V_I - 0.7)^2 = (3 - V_I - 0.7)(3 - V_o) - \frac{1}{2}(3 - V_o)^2 \quad (1)$$

$$(V_I - 0.7)^2 = (2.3 - V_I)(3 - V_o) - \frac{1}{2}(3 - V_o)^2$$

$$\frac{\partial}{\partial V_I} \Rightarrow 2(V_I - 0.7) = (2.3 - V_I) \left( -\frac{\partial V_o}{\partial V_I} \right) - (3 - V_o) + (3 - V_o) \frac{\partial V_o}{\partial V_I}$$

## VTC and Noise Margins – Problem (cont')

$$V_I = V_{IL} \text{ and } \frac{\partial V_o}{\partial V_I} = -1$$

$$2V_{IL} - 1.4 = 2.3 - V_{IL} - 3 + V_o + 3 + V_o$$

$$V_{IL} = \frac{2}{3}V_o - 1.15$$

$$\text{From (1): } (V_{IL} - 0.7)^2 = (2.3 - V_{IL})(3 - V_o) - \frac{1}{2}(3 - V_o)^2$$

$$(0.66V_o - 1.85)^2 = (3.45 - 0.66V_o)(3 - V_o) - \frac{1}{2}(3 - V_o)^2$$

# VTC and Noise Margins – Problem (cont')


$$V_o = 2.96 V$$

$$V_{IL} = 0.81 V$$

## Noise Margins:

$$NM_H = 3 - 1.52 = 1.48 V$$

$$NM_L = 0.81 - 0 = 0.81 V$$

 

Since  $Q_N$  and  $Q_P$  are not matched, the VTC is not symmetric