

# ECE 342

# Electronic Circuits

## Lecture 35

## CMOS Logic

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jesa@Illinois.edu

# Digital Logic - Generalization

De Morgan's Law

$$\overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots$$

$$\overline{A \cdot B \cdot C \cdot \dots} = \bar{A} + \bar{B} + \bar{C} + \dots$$


Distributive Law

$$AB + AC + BC + BD = A(B + C) + B(C + D)$$

- **General Procedure**
  1. Design PDN to satisfy logic function
  2. Construct PUN to be complementary of PDN in every way
  3. Optimize using distributive rule
 
# CMOS Logic Gate Circuits

- **Two Networks**
  - Pull-down network (PDN) with NMOS
  - Pull-up network (PUN) with PMOS




**PUN conducts when inputs are low and consists of PMOS transistors**


**PDN consists of NMOS transistors and is active when inputs are high**

- **PDN and PUN utilize devices**
  - In parallel to form OR functions
  - In series to form AND functions

# Pull-Down Networks

 


$$\bar{Y} = A + B$$

 


$$\bar{Y} = AB$$

# Pull-Up Networks

 

$$Y = \bar{A} + \bar{B}$$

 

$$Y = \bar{A}\bar{B}$$

# Basic Logic Function




Basic  
Function

**INVERTER**

**NOR**

**NAND**

Symbol

   

# Devices  
PUN

**1**  
**PMOS**

**2**  
**PMOS-Series**

**2**  
**PMOS-Parallel**

# Devices  
PDN

**1**  
**NMOS**

**2**  
**NMOS-Parallel**

**2**  
**NMOS-Series**

Truth  
Table

	A	Y
	0	1
	1	0

	A	B	Y
	0	0	1
	0	1	0
	1	0	0
	1	1	0

	A	B	Y
	0	0	1
	0	1	1
	1	0	1
	1	1	0


# Pull-Down and Pull-Up Functions

**Pull-up network (PUN)**

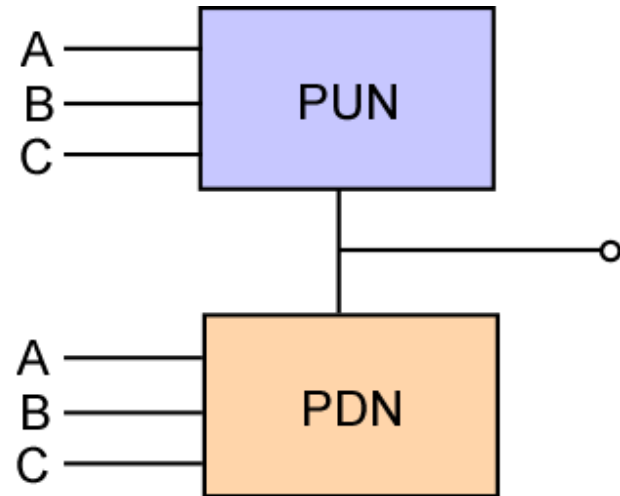**Pull-down network (PDN)**


- **Key features**

- When PDN switch is on, PUN switch is off and vice versa
- Conditions for being on and off are complementary




# Pull-Down and Pull-Up

**PDN-parallel NMOS**

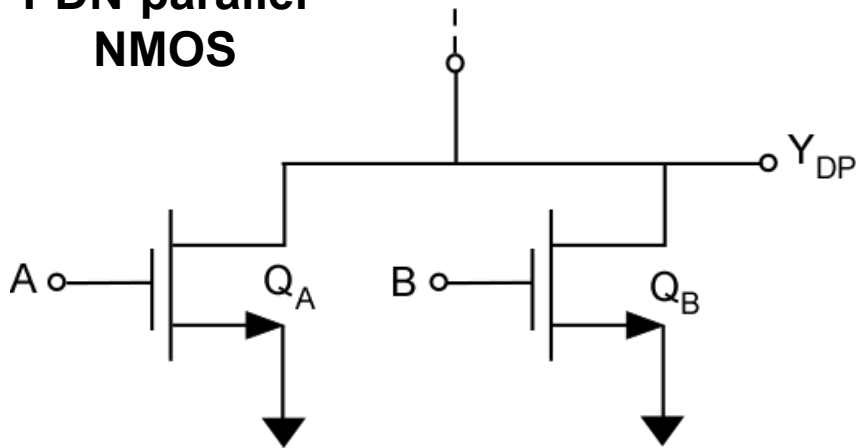

**PUN-series PMOS**

 

$$Y_{DP} = \overline{A + B}$$

Truth Tables

	A	B	$Y_{DP}$
	0	0	1
	0	1	0
	1	0	0
	1	1	0

$$Y_{US} = \overline{A} \overline{B}$$

	A	B	$Y_{US}$
	0	0	1
	0	1	0
	1	0	0
	1	1	0





# Pull-Down and Pull-Up

When  $Y_{DP}$  in PDN-parallel is low, this means that either A or B (or both) is high. When either A or B (or both) is high, either transistor (or both) in PUN-series are off  $\rightarrow Y_{US} = \text{low}$

When  $Y_{DP}$  in PDN-parallel is high, both A and B are low. Both transistors in PUN-Series are on creating a path to VDD.  $Y_{US} = \text{high} \rightarrow Y_{US} = Y_{DP}$ .

**PDN-Parallel and PUN-series are complementary**

# Pull-Down and Pull-Up

 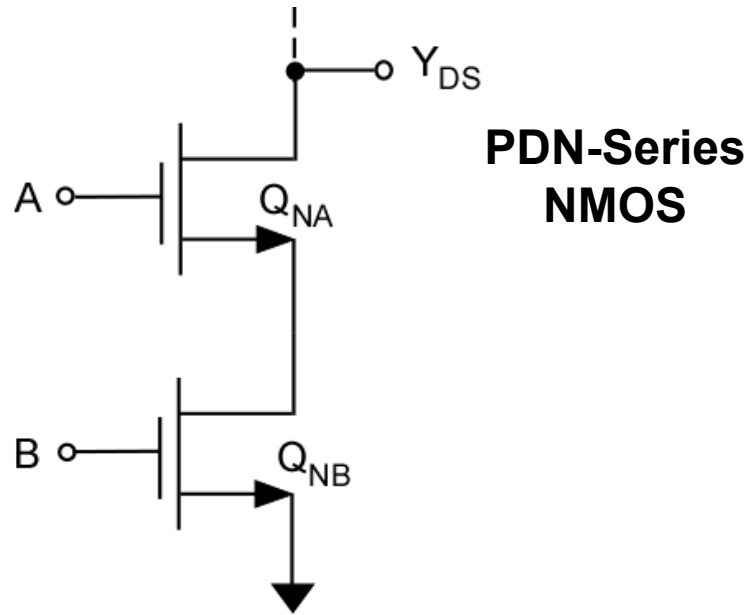

$$Y_{DS} = \overline{AB}$$

Truth Tables

	A	B	$Y_{DS}$
	0	0	1
	0	1	1
	1	0	1
	1	1	0

$$Y_{UP} = \overline{A} + \overline{B}$$

	A	B	$Y_{UP}$
	0	0	1
	0	1	1
	1	0	1
	1	1	0


# Pull-Down and Pull-Up

If  $Y_{DS}$  is low, both A and B must be high in which case both transistors in PUN-Parallel are off providing no path to  $V_{DD} \rightarrow Y_{UP} = \text{low} \rightarrow Y_{UP} = Y_{DS}$ .

If  $Y_{DS}$  is high, then either A or B (or both) are off (low) in which case either  $Q_{PA}$  or  $Q_{PB}$  in PUN-Parallel will be on and present a path to  $V_{DD}$ ; thus  $Y_{UP} = \text{high} \rightarrow Y_{UP} = Y_{DS}$


**PDN-Series and PUN-Parallel are complementary**

# Two-Input NOR Gate

 


$$Y = \overline{A + B} = \overline{A} \overline{B}$$

# Two-Input NOR Gate

 


**Actual**

 

**Ideal**

# Two-Input NAND Gate

 

$$Y = \overline{AB} = \overline{A} + \overline{B}$$


# Example

$$Y = \overline{\overline{AB} \cdot \overline{CD}}$$


Using De Morgan's Law

$$Y = \overline{\overline{AB} \cdot \overline{CD}} = AB + CD = (\overline{\overline{A} + \overline{B}}) \cdot (\overline{\overline{C} + \overline{D}})$$

Pull-down network

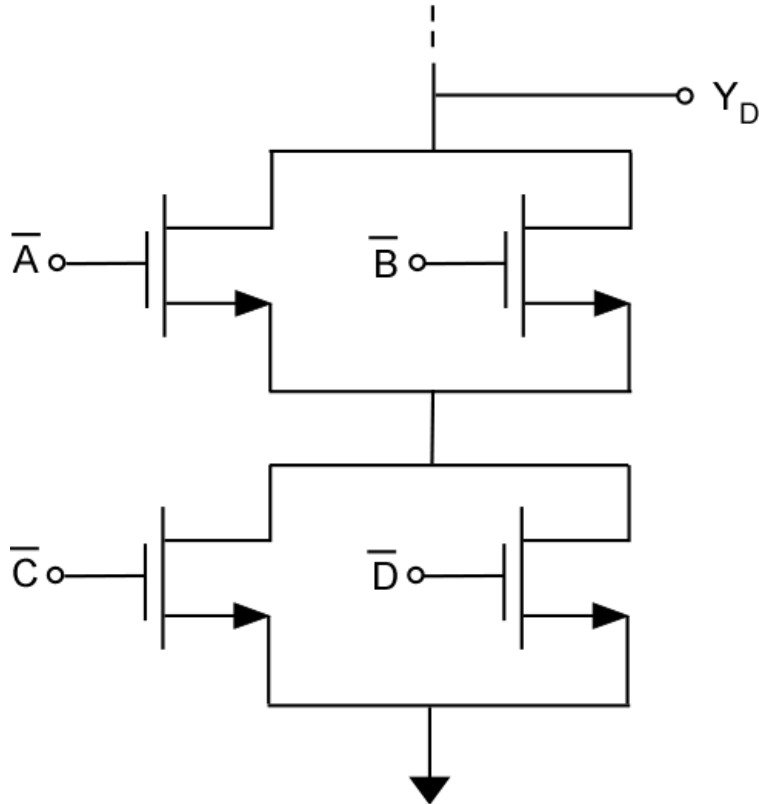


Pull-up network

 

# Example 1

Evaluate Logic Function

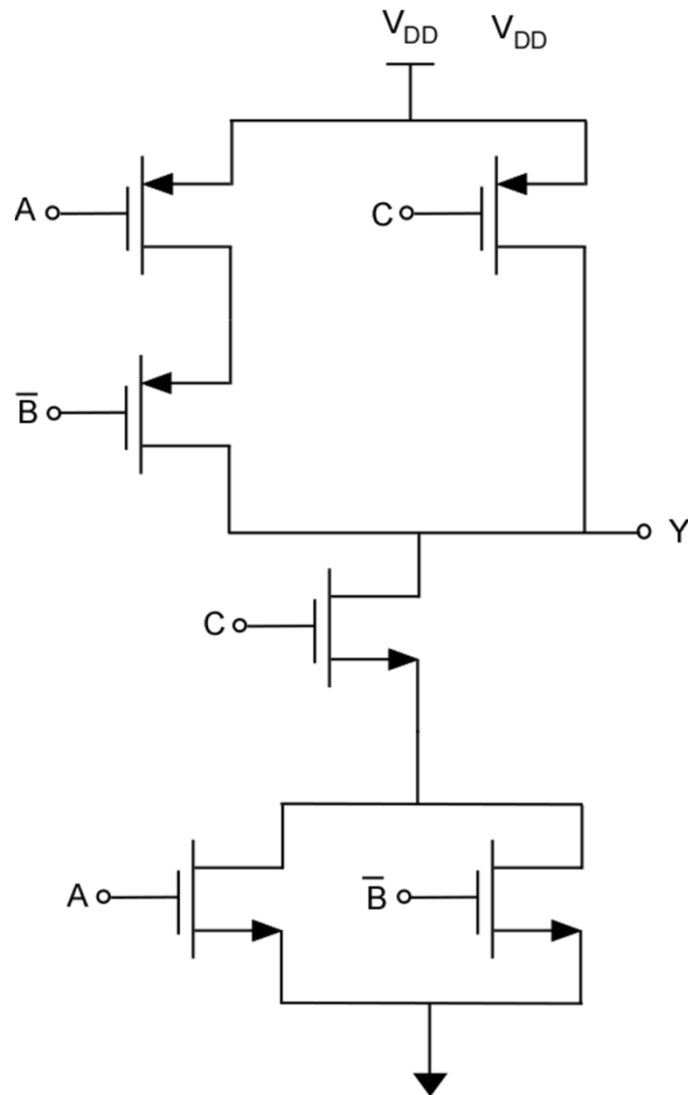

$$Y = \overline{(A + \bar{B})C} \text{ from pull down}$$

$$Y = \bar{A}B + \bar{C} \text{ from pull up}$$


$$\bar{A}B + \bar{C} = \overline{\overline{\bar{A}B} \cdot C} = \overline{(A + \bar{B})C}$$



# Example 2

Implement the function


$$\bar{Y} = A\bar{B} + C$$

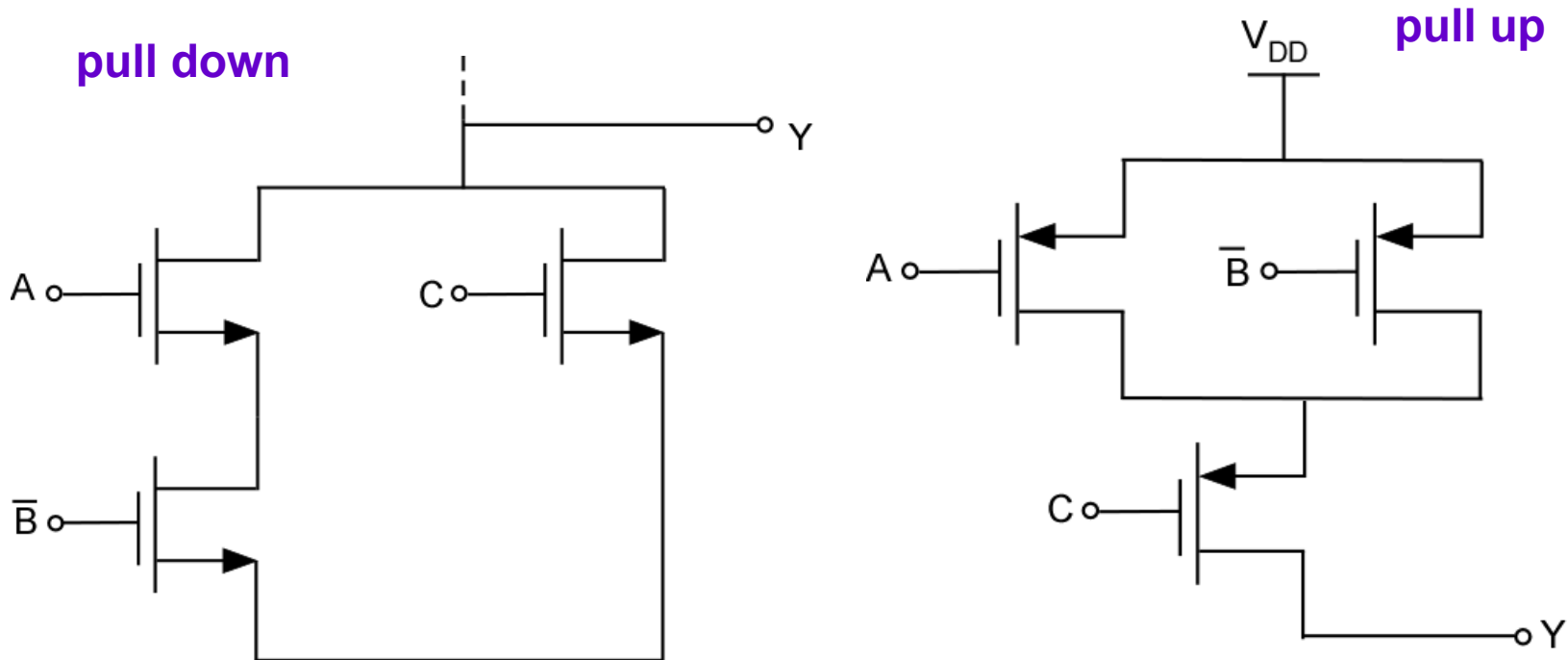


$$Y = \overline{A\bar{B} + C} = \overline{A\bar{B}} \cdot \bar{C} = (\bar{A} + B) \cdot \bar{C}$$
 
# Exclusive-OR (XOR) Function

$$Y = A\bar{B} + \bar{A}B \quad \bar{Y} = (\bar{A} + B)(A + \bar{B})$$



pull down

 

pull up

**XOR**

	A	B	Y
	0	0	0
	0	1	1
	1	0	1
	1	1	0

# Transistor Sizing

## Objectives


- PDN provides discharge current of at least that of an NMOS
- PUN provides charging current of at least that of a PMOS
- Worst case gate delay equal to that of basic inverter
- Find combination that results in lowest output current
- For transistors in parallel aspect ratios add
- For transistors in series, inverses of aspect ratios add

$$\text{Series} : \frac{1}{(W/L)_{eq}} = \frac{1}{(W/L)_1} + \frac{1}{(W/L)_2} + \dots + \frac{1}{(W/L)_M}$$


$$\text{Parallel} : (W/L)_{eq} = (W/L)_1 + (W/L)_2 + \dots + (W/L)_M$$

$$p = (W/L)_p \quad n = (W/L)_n$$

# Transistor Sizing

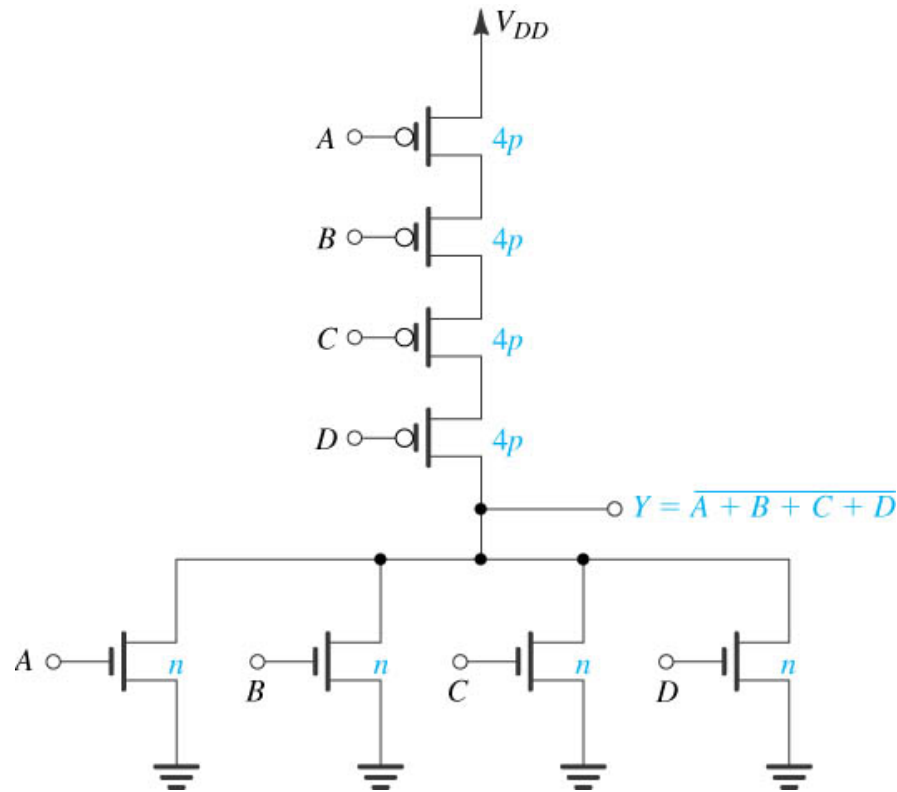



**NOR**

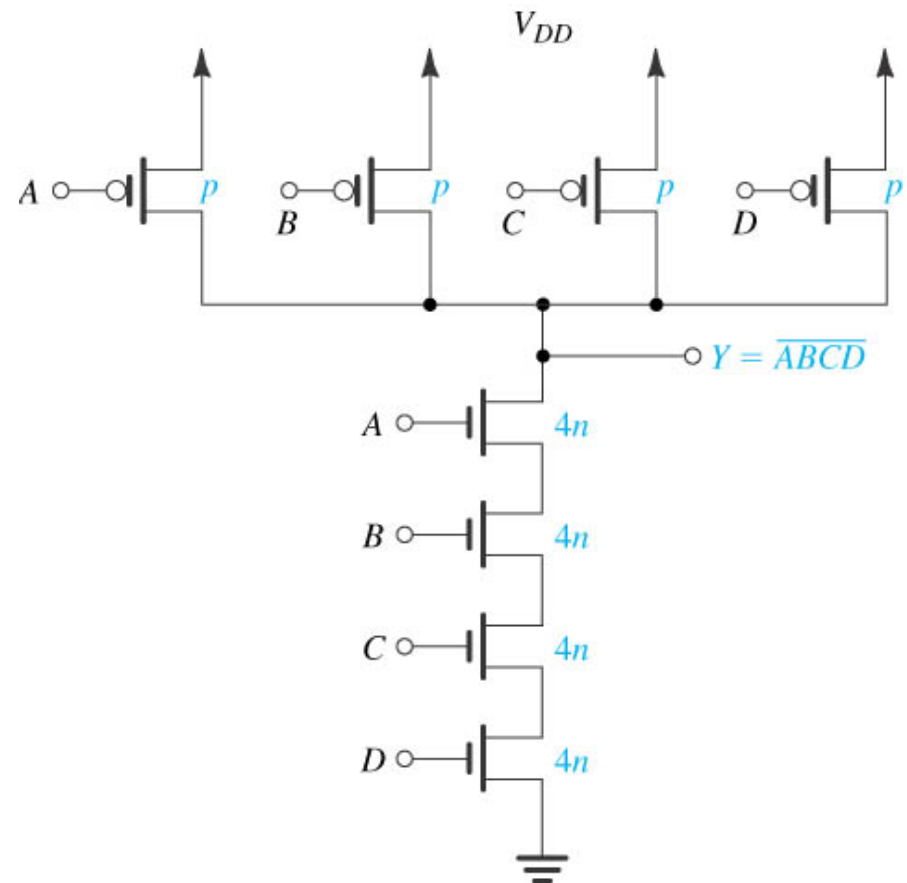

**NAND**
  
# Transistor Sizing – Example 1

Two approaches to realizing the OR function of six input variables. Assuming that the transistors in both circuits are properly sized to provide each gate with a current-driving capability equal to that of the basic matched inverter, find the number of transistors and the total area of each circuit. Assume the basic inverter to have a  $(W/L)_n$  ratio of  $1.2 \mu\text{m}/0.8 \mu\text{m}$  and a  $(W/L)_p$  ratio of  $3.6 \mu\text{m}/0.8 \mu\text{m}$ .



10.36

# Transistor Sizing – Example 1

For design (a), there are  $2(6)+2=14$  transistors:

All 7 NMOS use  $(W/L)_n = n$

1 PMOS uses  $(W/L)_p = p$

6 PMOS use  $(W/L)_p = 6p$

**Total Area =  $7(1.2)0.8 + 1(3.6)0.8 + 6(6)(3.6)0.8 = 113.3 \mu\text{m}^2$**

For design (b), there are  $2(3)2 + 1(2)2=16$  transistors:

6 NMOS use  $(W/L)_n = n$

6 PMOS use  $(W/L)_p = 3p$

2 PMOS use  $(W/L)_p = p$

2 NMOS use  $(W/L)_n = 2n$

**Total Area =  $70(1.2)0.8 = 67.2 \mu\text{m}^2$ , or 59% of (a)**