 



ECE 342

Review

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois



Thevenin Equivalent

 


- **Principle**

- Any linear two-terminal network consisting of current or voltage sources and impedances can be replaced by an equivalent circuit containing a single voltage source in series with a single impedance.

- **Application**

- To find the Thevenin equivalent voltage at a pair of terminals, the load is first removed leaving an open circuit. The open circuit voltage across this terminal pair is the Thevenin equivalent voltage.
- The equivalent resistance is found by replacing each independent voltage source with a short circuit (zeroing the voltage source), replacing each independent current source with an open circuit (zeroing the current source) and calculating the resistance between the terminals of interest. Dependent sources are not replaced and can have an effect on the value of the equivalent resistance.

Low-Pass Circuit

 

In frequency domain:

$$V_o = \frac{V_i}{R + \frac{1}{j\omega C}} \cdot \frac{1}{j\omega C}$$

$$V_o = \frac{V_i}{1 + j\omega RC} \Rightarrow A_v = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$


$$A_v = \frac{1}{1 + j\omega RC} = \frac{1}{1 + jf / f_2}$$

Low-Pass Circuit

$$f_o = \frac{1}{2\pi RC} = \frac{1}{2\pi\tau}$$

$\tau = RC = \text{time constant}$

At very high frequencies,
STC goes as

 

$$G = -20 \log \sqrt{1 + (\omega / \omega_o)^2}$$



$$G \simeq -20 \log(\omega / \omega_o) = -20X$$

where $X = \log(\omega / \omega_o)$

At high frequencies, slope of curve is -20 dB

if $X = 1 (\omega = 10\omega_o)$, decrease is $-20 \text{ dB} \Rightarrow -20 \text{ dB / decade}$


High-Pass Circuit

  

$$V_o = \frac{V_i R}{R + \frac{1}{j\omega C}} = \frac{V_i}{1 + \frac{1}{j\omega RC}}$$

$$A_v = \frac{V_o}{V_i} = \frac{1}{1 - j \frac{1}{2\pi f RC}} = \frac{1}{1 - j f_0 / f}$$


Octave & Decade

 

Overall gain $A(f)$ is

$$A(f) = A_o \cdot \frac{jf / f_{lo}}{1 + jf / f_{lo}} \cdot \frac{1}{1 + jf / f_{hi}}$$

PN Junction


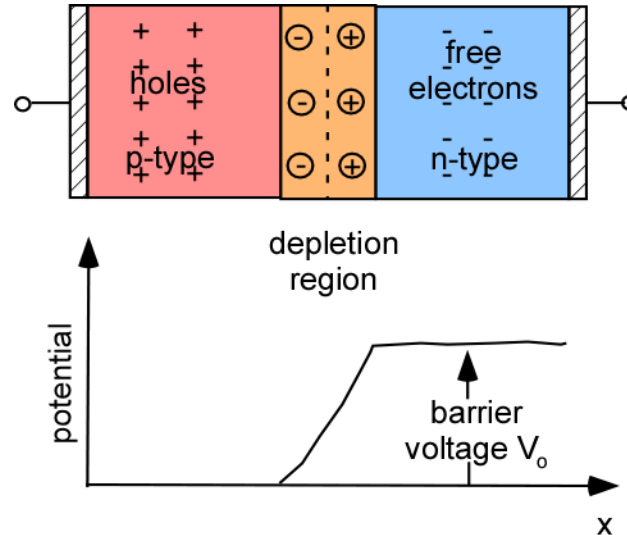


- **When a p material is connected to an n-type material, a junction is formed**
 - Holes from p-type diffuse to n-type region
 - Electrons from n-type diffuse to p-type region
 - Through these diffusion processes, recombination takes place
 - Some holes disappear from p-type
 - Some electrons disappear from n-type



A depletion region consisting of bound charges is thus formed
Charges on both sides cause electric field $\rightarrow$ potential = V_o

Diode Models



Exponential

  





Piecewise Linear

  





Constant-Voltage-Drop

  



Diode Models

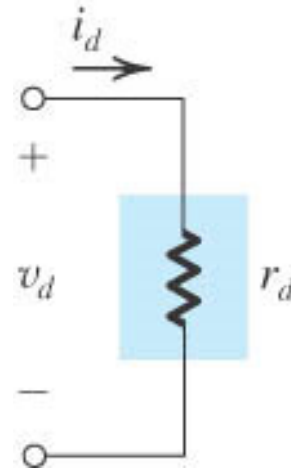   

Diode Circuits - Rectification

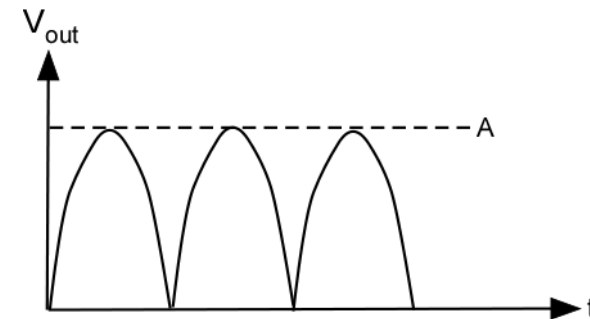   


Rectification with ripple reduction.

  


C must be large enough so that RC time constant is much larger than period

NMOS Transistor

 

- **NMOS Transistor**
 - N-Channel MOSFET
 - Built on p-type substrate
 - MOS devices are smaller than BJTs
 - MOS devices consume less power than BJTs

MOS Regions of Operation

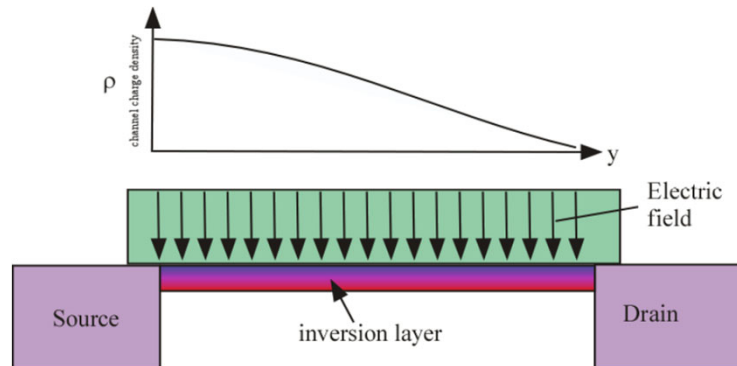


Triode

Resistive

$$V_{GS} > V_T$$


$$V_{DS} \text{ small}$$

 

Nonlinear

$$V_{GS} > V_T$$

$$V_{DS} < (V_{GS} - V_T)$$

 


Active

Saturation

$$V_{GS} > V_T$$

$$V_{DS} \geq V_{GS} - V_T$$

MOS – Triode Region - 1

 

$$I_D = \mu \frac{W}{L} C_{ox} [(V_{GS} - V_T) V_{DS}]$$

$$V_{DS} \ll (V_{GS} - V_T)$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9\epsilon_o}{t_{ox}}$$

C_{ox} : gate oxide capacitance


μ : electron mobility

L : channel length

W : channel width

V_T : threshold voltage


MOS – Triode Region

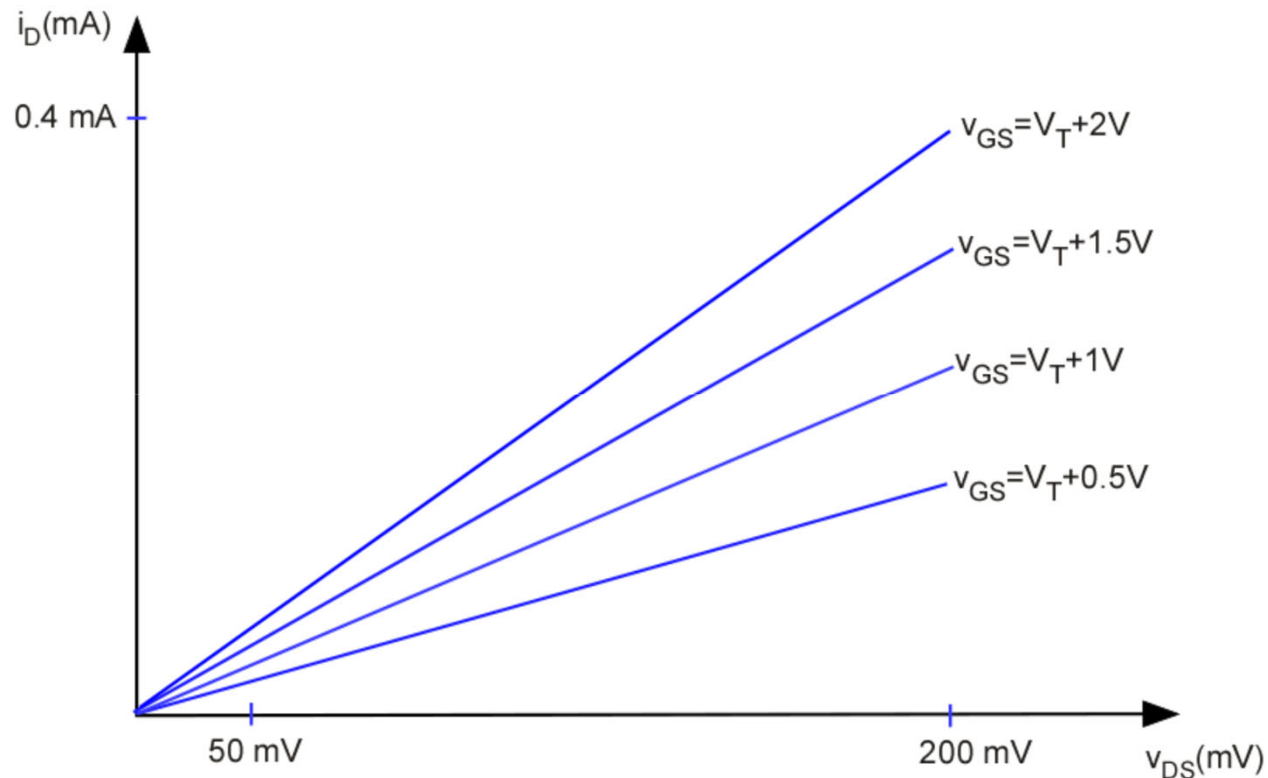

FET is like a linear resistor with

$$r_{ds} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)}$$

MOS – Triode Region - 2

 

$$V_{GS} > V_T$$

$$V_{DS} < (V_{GS} - V_T)$$


$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

- Charge distribution is nonuniform across channel
- Less charge induced in proximity of drain

MOS – Active (Saturation) Region

Saturation occurs at pinch off when

$$V_{DS} = (V_{GS} - V_T) = V_{DSP}$$

 

$$V_{GS} > V_T$$

$$V_{DS} > (V_{GS} - V_T) \\ \text{(saturation)}$$

$$I_D = \mu_n C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2$$

Body Effect

- **The body effect**

- V_T varies with bias between source and body
- Leads to modulation of V_T


Potential on substrate affects threshold voltage

$$V_T(V_{SB}) = V_{To} + \gamma \left[\left(2|\phi_F| + V_{SB} \right)^{1/2} - \left(2|\phi_F| \right)^{1/2} \right]$$

$$|\phi_F| = \left(\frac{kT}{q} \right) \ln \left(\frac{N_a}{n_i} \right) \quad \text{Fermi potential of material}$$

$$\gamma = \frac{(2qN_a\epsilon_s)^{1/2}}{C_{ox}} \quad \text{Body bias coefficient}$$

Channel-Length Modulation

 


With depletion layer widening, the channel length is in effect reduced from L to $L - \Delta L \rightarrow$ Channel-length modulation

This leads to the following I-V relationship

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_T)^2 (1 + \lambda v_{DS})$$



Where λ is a process technology parameter

Channel-Length Modulation

 

Channel-length modulation causes i_D to increase with v_{DS} in saturation region


PMOS Transistor

  

- All polarities are reversed from nMOS
- V_{GS} , V_{DS} and V_t are negative
- Current i_D enters source and leaves through drain
- Hole mobility is lower $\Rightarrow$ low transconductance
- nMOS favored over pMOS

Biasing of Amp

 Bias will provide quiescent points for input and output about which variations will take place. Bias maintain amplifier in active region.



$$V_I(t) = V_{QI} + v_I(t)$$


$$V_o(t) = V_{QO} + v_o(t)$$

$$v_o(t) = A_v v_I(t)$$

$$A_v = \left. \frac{dv_o}{dv_I} \right|_{at Q}$$

Amplifier characteristics are determined by bias point

Voltage Amplifier

 

$$\text{Voltage gain is: } \frac{v_o}{v_i} = A_v = \frac{A_{vo} R_L}{R_L + R_o}$$

$$\text{Input } v_i = v_s \frac{R_i}{R_i + R_s}$$

$$v_o = \frac{A_{vo} v_i R_L}{R_L + R_o}$$

Want R_i large (so $v_i \approx v_s$)
(actually want $R_i \gg R_s$) ideal
 $R_i = \infty$

Want R_o small (as small as possible) to achieve maximum gain $\rightarrow$ ideal $R_o = 0$

$$\text{Overall gain: } \frac{v_o}{v_s} = A_{vo} \frac{R_i}{R_i + R_s} \cdot \frac{R_L}{R_L + R_o}$$

Small-Signal Model

- **What is a small-signal incremental model?**
 - Equivalent circuit that only accounts for signal level fluctuations about the DC bias operating points
 - Fluctuations are assumed to be small enough so as not to drive the devices out of the proper range of operation
 - Assumed to be linear
 - Derives from superposition principle

Common Emitter Configuration

The emitter current I_E can be approximated as:

$$I_E \simeq I_S e^{V_{BE}/V_T}$$


An incremental conductance g_e can be defined as

$$g_e \equiv \frac{\partial I_E}{\partial V_{BE}} = \frac{I_S}{V_T} e^{V_{BE}/V_T} = \frac{I_E}{V_T}$$

From which we get:


$$r_e = \frac{1}{g_e} = \frac{V_T}{I_E}$$

Emitter resistance

 

$$\text{Usually, } V_T = 26 \text{ mV} \Rightarrow r_e = \frac{26 \text{ mV}}{I_E}$$

Hybrid- π Incremental Model for BJTs

 

r_π : input resistance looking into the base

r_x : parasitic series resistance looking into base – ohmic base resistance

g_m : BJT transconductance

$r_o = r_{ce}$: output collector resistance related to the Early effect

Hybrid- π Parameters

$$g_m = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{I_C = \text{constant}} = \frac{I_C}{V_T}$$

Can show that

r_π is defined as : $r_\pi = \frac{v_\pi}{i_b}$

Since $i_b = \frac{g_m v_\pi}{\beta}$ then $r_\pi = \frac{\beta}{g_m}$

$$r_\pi = (\beta + 1) r_e$$

$$g_m = \frac{\alpha}{r_e}$$


$$\beta = g_m r_\pi$$

$r_{ce} = r_o$ is associated with the Early effect

$$r_{ce} = r_o = \frac{|V_A|}{I_C} = \frac{|V_A|}{\beta I_B}$$

$$g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$$


Common Emitter (CE) Amplifier

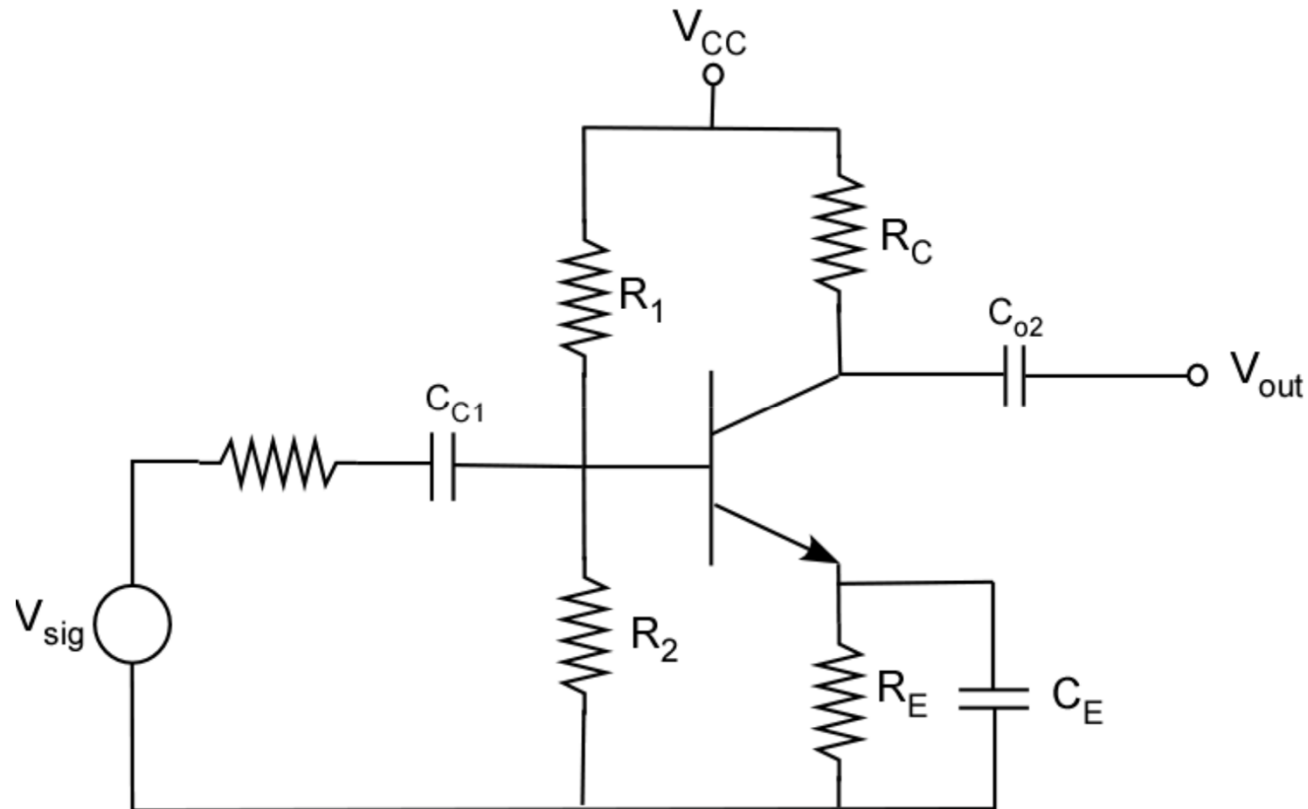

Bias: Choose R_1 & R_2 to set $V_B \rightarrow V_E$ is then set. Choose R_E to set $I_E \sim I_C$.
Quiescent point of V_{out} will be determined by R_C . Emitter is an AC short.

Incremental Model for CE Amplifier

Hybrid- π model (ignoring r_x)

 

$$R_B = R_1 \parallel R_2$$

$$R_{in} = \frac{v_i}{i_i} = R_B \parallel r_\pi$$

Sometimes $R_B \gg r_\pi$ and $R_{in} \simeq r_\pi$

CE Amplifier

Output Impedance

$$R_{out} = R_C \parallel r_o$$


$$\text{If } r_o \gg R_C, R_{out} \simeq R_C$$

$$\text{from which } A_v = A_{vo} \left(\frac{R_L}{R_L + R_o} \right)$$

It can be seen that if $R_{sig} \gg r_\pi$, the gain will be highly dependent on β . This is not good because of β variations

$$\text{If } R_{sig} \ll r_\pi, G_v \simeq -g_m (R_C \parallel R_L \parallel r_o)$$

CE with External Resistors

 

CE with External Resistors

$$\frac{v_{out}}{v_{in}} = -\frac{g_m r_\pi (R_L \parallel R_C)}{g_m r_\pi R_E + R_E + r_\pi + R_B} = -\frac{g_m r_\pi (R_L \parallel R_C)}{R_E (\beta + 1) + r_\pi + R_B}$$

$$A_{MB} = -g_m (R_L \parallel R_C) \frac{1}{\frac{R_E (\beta + 1)}{r_\pi} + \frac{R_B}{r_\pi} + 1}$$

$$A_{MB} = -\frac{\beta (R_L \parallel R_C)}{R_E (\beta + 1) + r_\pi + R_B}$$

R_E and R_B degrade the gain

CE with External Resistors

The gain can be written as:


$$A_{MB} = -\frac{\beta(R_L \parallel R_C)}{R_E(\beta+1) + r_\pi + R_B} = -\frac{\left(\frac{\beta}{\beta+1}\right)(R_L \parallel R_C)}{R_E + \frac{r_\pi}{(\beta+1)} + \frac{R_B}{(\beta+1)}}$$

and since $\frac{\beta}{(\beta+1)} = \alpha$ neglecting $\frac{R_B}{(\beta+1)}$

$$A_{MB} = -\frac{\alpha(R_L \parallel R_C)}{R_E + r_e}$$

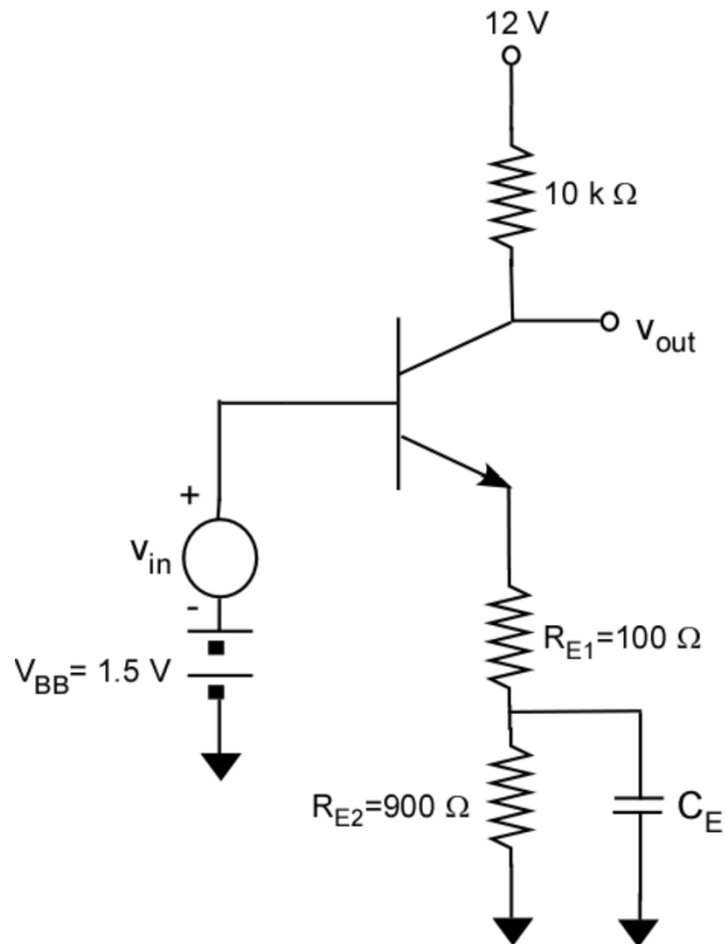Example

Given $V_{BEON}=0.6V$, find the gain for the circuit shown



$$V_{BQ} = 1.5 V$$

$$V_{EQ} = 1.5 V - 0.6 V = 0.9 V$$

$$I_E \simeq \frac{0.9}{R_{E1} + R_{E2}} = \frac{0.9}{1 k\Omega} = 0.9 mA$$

Example (Cont')

$$I_C \simeq 0.9 \text{ mA} \Rightarrow V_{outQ} = 12 \text{ V} - 0.9 \times 10 = 3 \text{ V}$$

AC analysis: R_{E2} is shorted and $R_E = R_{E1} = 100 \Omega$. Since β is not known, use:

$$A_{MB} = -\frac{\alpha R_C}{R_E + r_e} \text{ with } \alpha \simeq 1$$


$$r_e = \frac{V_T}{I_E} = \frac{26}{0.9} = 28.8 \Omega$$

$$A_{MB} = -\frac{10,000}{100 + 28.8} = -77.5$$


$$A_{MB} = -77.5$$

Emitter Follower

circuit

 

Incremental model

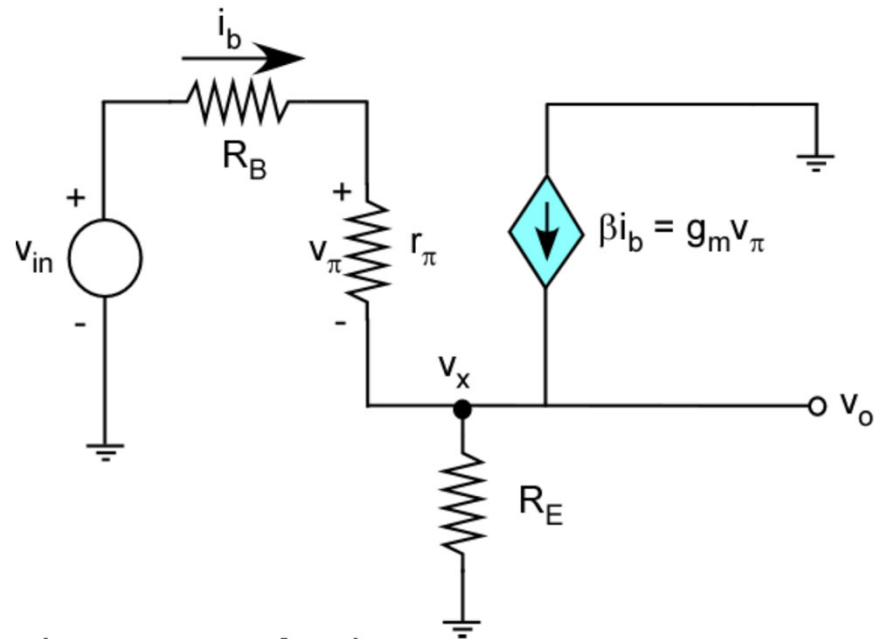

$$v_o = \left(g_m v_\pi + \frac{v_\pi}{r_\pi} \right) R_E = v_\pi \left(g_m + \frac{1}{r_\pi} \right) R_E$$

$$v_{in} = v_\pi + R_B i_b + v_o = v_\pi + v_\pi R_E \left(g_m + \frac{1}{r_\pi} \right) + \frac{v_\pi}{r_\pi} R_B$$

Emitter Follower

$$v_{in} = v_{\pi} \left[1 + \frac{R_B}{r_{\pi}} + R_E \left(g_m + \frac{1}{r_{\pi}} \right) \right]$$


$$\frac{v_o}{v_{in}} = \frac{\left(g_m + \frac{1}{r_{\pi}} \right) R_E}{\left(g_m + \frac{1}{r_{\pi}} \right) R_E + 1 + \frac{R_B}{r_{\pi}}} = \frac{(g_m r_{\pi} + 1) R_E}{(g_m r_{\pi} + 1) R_E + r_{\pi} + R_B}$$

Using $g_m r_{\pi} = \beta$

$$\frac{v_o}{v_{in}} = \frac{(\beta + 1) R_E}{(\beta + 1) R_E + r_{\pi} + R_B} \simeq 1$$

Emitter follower has unity voltage gain

Emitter Follower – Input Impedance

 

$$r_{in} = \frac{v_{in}}{i_b} = \frac{v_{\pi} \left[1 + R_B / r_{\pi} + R_E (g_m + 1 / r_{\pi}) \right]}{v_{\pi} / r_{\pi}}$$


$$r_{in} = r_{\pi} + R_B + R_E (\beta + 1)$$

Emitter Follower – Output Impedance

$$i_B = -\frac{v_o}{r_\pi + R_B}$$

$$i_o = \frac{v_o}{R_E} - g_m v_\pi + \frac{v_o}{r_\pi + R_B} = \frac{v_o}{R_E} + \frac{g_m r_\pi v_o}{r_\pi + R_B} + \frac{v_o}{r_\pi + R_B}$$
 
$$i_o = v_o \left[\frac{1}{R_E} + \frac{g_m}{r_\pi + R_B} + \frac{1}{r_\pi + R_B} \right] = v_o \left[r_\pi + R_B + R_E (\beta + 1) \right] \frac{1}{R_E (r_\pi + R_B)}$$



Output Impedance (cont')

Using $g_m r_\pi = \beta$


$$\frac{v_o}{i_o} = R_{out} = \frac{R_E (r_\pi + R_B)}{r_\pi + R_B + R_E (\beta + 1)} = \frac{R_E (r_\pi + R_B) / (\beta + 1)}{R_E + (r_\pi + R_B) / (\beta + 1)}$$

$$R_{out} = R_E \parallel (r_\pi + R_B) / (\beta + 1)$$

If we neglect R_B

$$A'_{MB} = \frac{(\beta + 1)R_E}{r_\pi + (\beta + 1)R_E} \quad \text{and} \quad R'_{out} = R_E \parallel \frac{r_\pi}{\beta + 1}$$

Common Base Configuration

 

Common Base Configuration


$$v_i = -v_\pi, \quad v_o = -g_m v_\pi R_C = g_m v_i R_C$$

$$\text{Voltage gain} = \frac{v_o}{v_i} = g_m R_C = \frac{\alpha R_C}{r_e}$$

$$\text{Current gain} = \frac{i_o}{i_i} = \frac{g_m v_\pi}{i_i} = \frac{-g_m v_\pi}{\left(g_m + \frac{1}{r_\pi}\right)(-v_\pi)} = \frac{\beta}{\beta + 1} = \alpha$$

$$R_{out} = R_C$$


$$r_{in} = \frac{r_\pi}{\beta + 1}$$

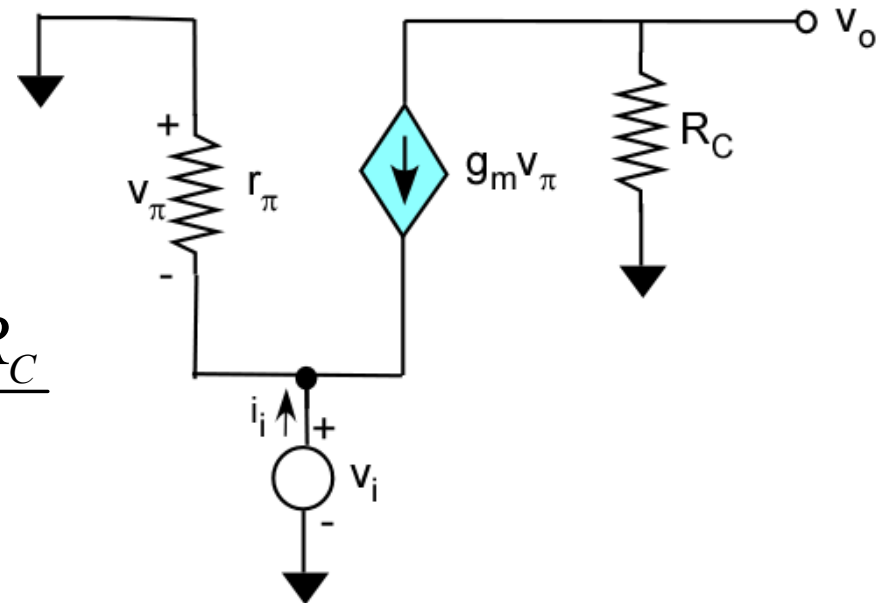

BJT Topologies - Summary

	CE	CB	EF
A_{vo}	$-g_m R_C$	$g_m R_C$	1
R_{in}	r_π	$\frac{r_\pi}{\beta + 1}$	$r_\pi + R_E (\beta + 1)$
R_{out}	R_C	R_C	$R_E \parallel r_\pi / (\beta + 1)$


Common Source MOSFET Amplifier

 

Bias is to keep MOS in saturation region

Common Source MOSFET Amplifier

 Small-Signal Equivalent Circuit for MOS (device only)



$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_T)^2$$

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{GS}=V_{GSQ}} = \frac{2I_D}{V_{eff}}$$

where $V_{GS} - V_T = V_{eff}$

Which leads to

$$g_m = \sqrt{2k'_n} \sqrt{W/L} \sqrt{I_D}$$

g_m is proportional to $= \sqrt{W/L}$

MOSFET Output Impedance

To calculate r_{ds} , account for λ

$$r_{ds} = \left. \frac{\partial V_{DS}}{\partial I_D} \right|_{V_{GS}=V_{GSQ}} = \frac{1}{\lambda \mu \frac{W}{2L} C_{ox} [V_{GS} - V_T]^2} = \frac{1}{\lambda I_{DP}}$$

$$I_{DP} = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_T)^2$$

r_{ds} , accounts for channel width modulation resistance.

MOSFET Output Impedance

To calculate r_{ds} , account for λ


$$r_{ds} = \left. \frac{\partial V_{DS}}{\partial I_D} \right|_{V_{GS}=V_{GSQ}} = \frac{1}{\lambda \mu \frac{W}{2L} C_{ox} [V_{GS} - V_T]^2} = \frac{1}{\lambda I_{DP}}$$

$$I_{DP} = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_T)^2$$

r_{ds} , accounts for channel width modulation resistance.

Midband Frequency Gain

Incremental model for complete amplifier

 

$$A_{MB} = \frac{v_{out}}{v_{in}} = -\frac{R_B}{R_B + R_g} g_m \frac{r_{ds} R_D}{r_{ds} + R_D}$$

Body Effect

Potential on substrate affects threshold voltage

$$V_T(V_{SB}) = V_{To} + \gamma \left[\left(2|\phi_F| + V_{SB} \right)^{1/2} - \left(2|\phi_F| \right)^{1/2} \right]$$

$$|\phi_F| = \left(\frac{kT}{q} \right) \ln \left(\frac{N_a}{n_i} \right) \quad \text{Fermi potential of material}$$

$$\gamma = \frac{\left(2qN_a\epsilon_s \right)^{1/2}}{C_{ox}} \quad \text{Body bias coefficient}$$

Body Effect – (Con't)

Define g_{mb} as the body transconductance


$$g_{mb} = \left. \frac{\partial I_D}{\partial V_{BS}} \right|_{\substack{V_{GS} = \text{constant} \\ V_{DS} = \text{constant}}}$$

Can show that


$$g_{mb} = \chi g_m$$

$$\text{where } \chi = \frac{\partial V_T}{\partial V_{SB}} = \frac{\gamma}{2\sqrt{\phi_F + V_{SB}}}$$

Source Follower Configuration

 

 Since source is not tied to the substrate, we need to model the body effect. Note: substrate is always tied to ground.



$$G_L = \frac{1}{R_L}$$

Define $g_{ds} = \frac{1}{r_{ds}}$ and $G = g_{ds} + g_{mb} + G_L$

Source Follower

$$v_{out} = \frac{g_m v_{gs}}{G} = \frac{g_m (v_{in} - v_{out})}{G}$$

$$v_{out} g_{ds} + v_{out} G_L + g_{mb} v_{out} = g_m v_{gs}$$

$$v_{out} G = g_m v_{gs} \Rightarrow v_{out} = \frac{g_m v_{gs}}{G} = \frac{g_m (v_{in} - v_{out})}{G}$$

$$v_{out} G = g_m v_{in} - g_m v_{out}$$

Source Follower

$$v_{out} G = g_m v_{gs} \Rightarrow v_{out} (G + g_m) = g_m v_{in}$$

$$A_{GS} = \frac{g_m}{g_m + G} = \frac{g_m}{g_m + g_{mb} + g_{ds} + G_L}$$

$$A_{GS} = \frac{g_m}{g_m + G} = \frac{g_m}{g_m + g_{mb} + g_{ds} + G_L}$$

Source Follower

Neglecting G_L and g_{ds} (since they are small)

$$A_{GS} = \frac{g_m}{g_m + g_{mb}} \approx 1 \quad \text{This value is close to 1}$$

Output impedance of source follower


$$R_{out} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel r_{ds} \parallel R_L$$

Internal output impedance


$$r_{out} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel r_{ds} \leftarrow \text{This value is low}$$

Common Gate Amplifier

Circuit

 

Small-Signal Model

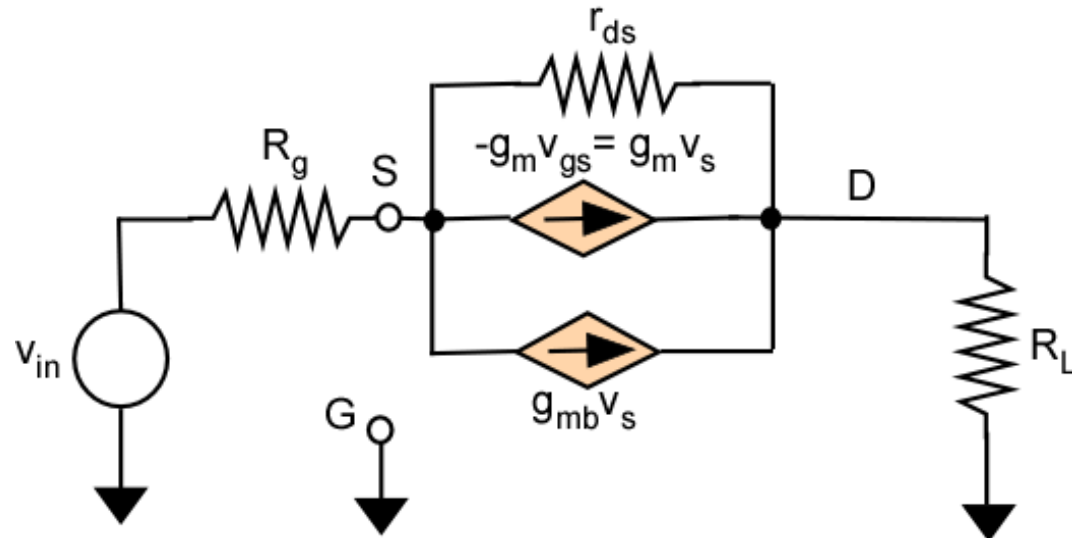

Common Gate Amplifier

$$A_{MB} = \frac{g_m + g_{mb} + g_{ds}}{G_L + g_{ds} + (g_m + g_{mb} + g_{ds})G_L / G_g}$$

$g_{ds} \ll (g_m + g_{mb})$ to get


$$A_{MB} = \frac{(g_m + g_{mb})R_L}{1 + (g_m + g_{mb})R_g}$$

- **Common Gate (CG)**
 - CG amplifier is non-inverting
 - CG amplifier has low input impedance
 - CG is unity current-gain amplifier

MOS Topologies - Ideal

	CS	CG	SF
A_{vo}	$-g_m R_D$	$g_m R_D$	1
R_{in}	∞	$\frac{1}{g_m}$	∞
R_{out}	R_D	R_D	$\frac{1}{g_m}$

Low-Pass Circuit

 


In frequency domain:
$$V_o = \frac{V_i}{R + \frac{1}{j\omega C}} \cdot \frac{1}{j\omega C}$$

$$V_o = \frac{V_i}{1 + j\omega RC} \Rightarrow A_v = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$

$$A_v = \frac{1}{1 + j\omega RC} = \frac{1}{1 + jf / f_2}$$



Low-Pass Circuit
 
$$f_2 = \frac{1}{2\pi RC} = \frac{1}{2\pi\tau}$$



$$\tau = 2\pi RC = \text{time constant}$$

High-Pass Circuit

 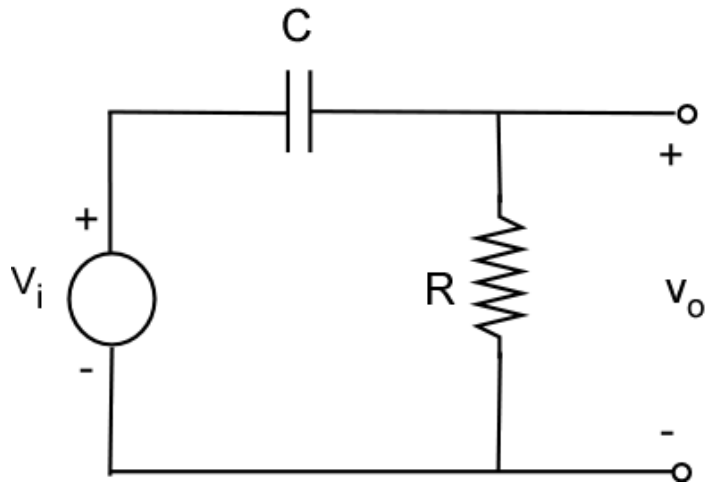


$$V_o = \frac{V_i R}{R + \frac{1}{j\omega C}} = \frac{V_i}{1 + \frac{1}{j\omega RC}}$$


$$A_v = \frac{V_o}{V_i} = \frac{1}{1 - j \frac{1}{2\pi f RC}} = \frac{1}{1 - j f_2 / f}$$

$$f_2 = \frac{1}{2\pi RC}$$

Three Frequency Bands

 

MOSFET High-Frequency Model

 

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}}$$

$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DB}}{V_o}}}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{eff} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{eff}}$$



$$g_{mb} = \chi g_m = \frac{\gamma}{2\sqrt{2\phi_F + V_{sb}}} g_m$$

$$r_{ds} = V_A / I_D = \frac{1}{\lambda I_D}$$

$$C_{gs} = \frac{2}{3} W L C_{ox} + W L_{ov} C_{ox}$$


$$C_{gd} = W L_{ov} C_{ox}$$

CS - Three Frequency Bands

  

Unity-Gain Frequency f_T

 f_T is defined as the frequency at which the short-circuit current gain of the common source configuration becomes unity



Define:

$$s = j\omega$$

(neglect $sC_{gd}V_{gs}$ since C_{gd} is small)

$$I_o = g_m V_{gs} - sC_{gd}V_{gs}$$

$$\frac{I_o}{I_i} = \frac{g_m}{s(C_{gs} + C_{gd})}$$

$$I_o \approx g_m V_{gs} \quad V_{gs} = \frac{I_i}{s(C_{gs} + C_{gd})}$$


Calculating f_T

For $s=j\omega$, magnitude of current gain becomes unity at


$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}} \Rightarrow f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$f_T \sim 100$ MHz for 5- μm CMOS, $f_T \sim$ several GHz for 0.13 μm CMOS

CS - High-Frequency Response

 

CS - High-Frequency Response

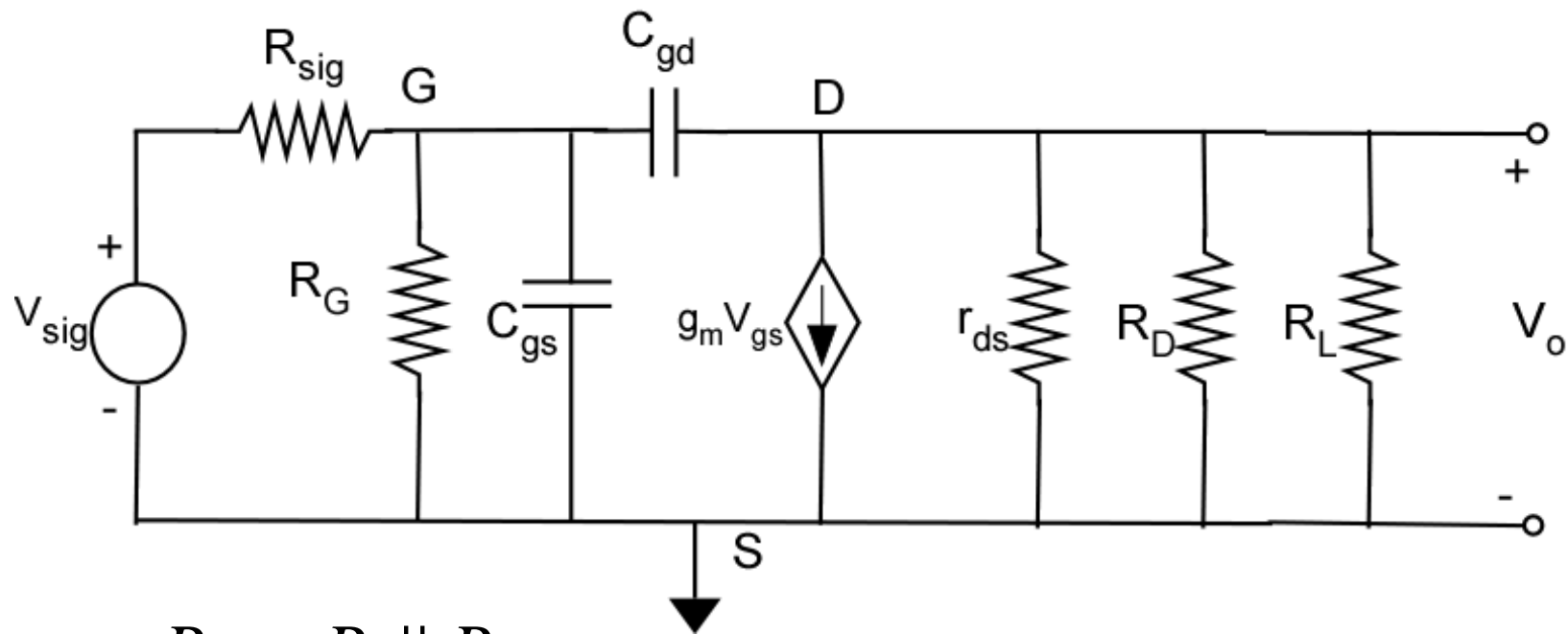


$$R_G = R_1 \parallel R_2$$

CS - High-Frequency Response

$$R'_{sig} = R_{sig} \parallel R_G$$
 
$$R'_L = r_{ds} \parallel R_D \parallel R_L$$



$$I_{gd} = sC_{gd} (V_{gs} - V_o) = sC_{gd} \left[V_{gs} - (-g_m R'_L V_{gs}) \right]$$

$$I_{gd} = sC_{gd} (1 + g_m R'_L) V_{gs}$$

CS – Miller Effect


Define C_{eq} such that

$$sC_{eq}V_{gs} = sC_{gd} \left(1 + g_m R'_L\right) V_{gs}$$

$$V_o = -g_m R'_L V_{gs}$$

$$C_{eq} = C_{gd} \left(1 + g_m R'_L\right) = \text{Miller Capacitance}$$
 
$$v_{in} = \frac{R_g V_{sig}}{R_g + R_{sig}}$$



CS – Miller Effect

$$V_{gs} = \left(\frac{R_G V_{sig}}{R_G + R_{sig}} \right) \frac{1}{1 + jf / f_o}$$

f_o is the corner frequency of the STC circuit

$$f_o = \frac{1}{2\pi C_{in} R'_{sig}}$$

$$C_{in} = C_{gs} + C_{eq} = C_{gs} + \overbrace{C_{gd} (1 + g_m R'_L)}^{Miller}$$


CS – Miller Effect

$$\frac{V_o}{V_{sig}} = - \left(\frac{R_G}{R_G + R_{sig}} \right) g_m R'_L \frac{1}{1 + jf / f_o}$$

$$\frac{V_o}{V_{sig}} = \frac{A_M}{1 + jf / f_H}$$

$$f_H = f_o = \frac{1}{2\pi C_{in} R'_{sig}}$$



High-Frequency Hybrid- π Model

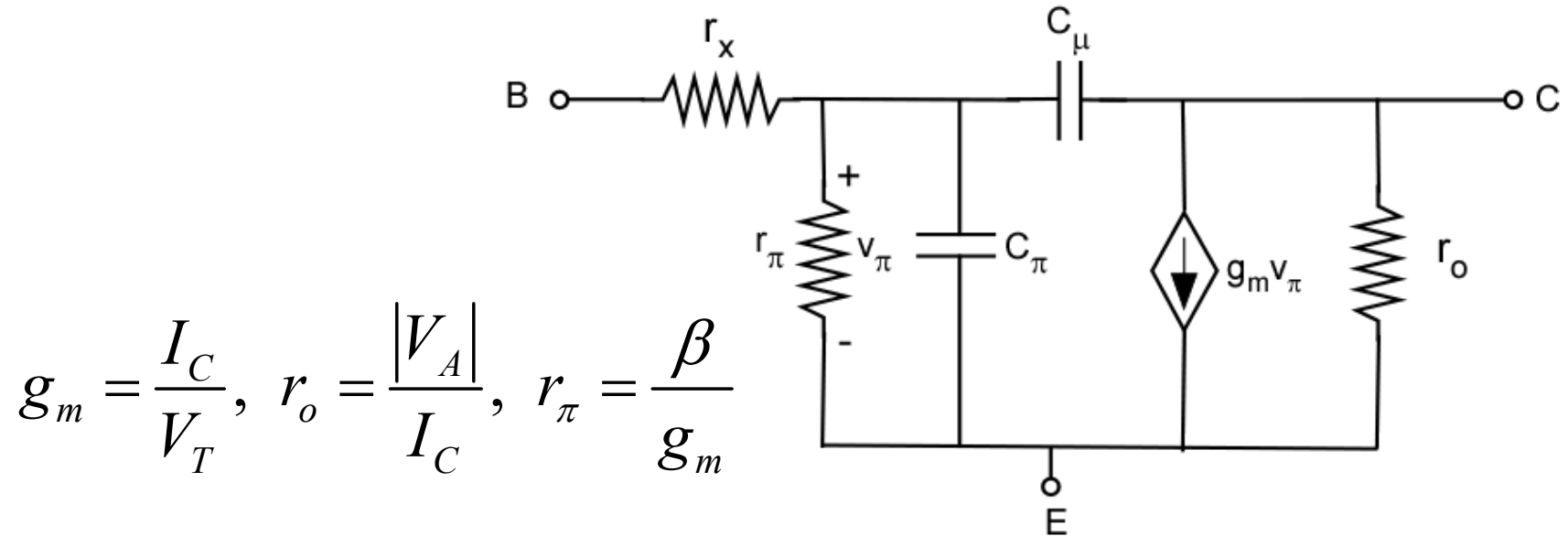


$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T}, \quad C_\pi = C_{de} + C_{je}, \quad C_{de} = \tau_F g_m$$

$$C_\mu = \frac{C_{jco}}{\left(1 + \frac{V_{CB}}{V_{oe}}\right)^m}, \quad m = 0.3 - 0.5 \quad f_T = \frac{g_m}{2\pi (C_\pi + C_\mu)}$$


CE - Three Frequency Bands

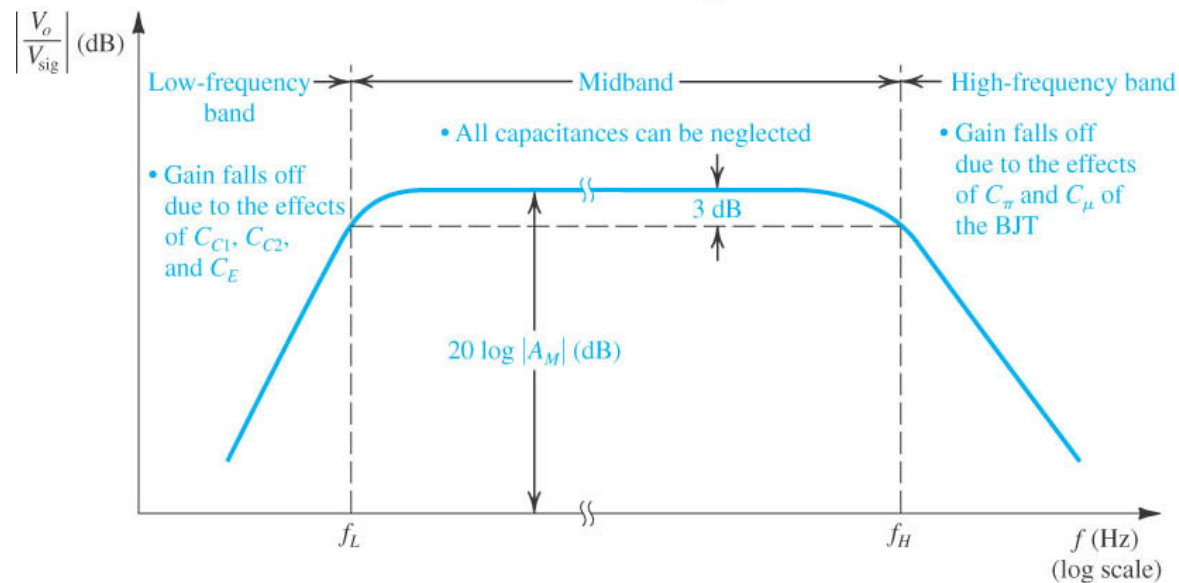 


CE High-Frequency Model

 

CE High-Frequency Model

 

CE High-Frequency Model

 

$$V'_{sig} = V_{sig} \cdot \frac{R_B}{R_B + R_{sig}} \cdot \frac{r_\pi}{r_\pi + r_x + (R_{sig} \parallel R_B)}$$


CE High-Frequency Model

$$R'_{sig} = r_{\pi} \parallel \left[r_x + \left(R_{sig} \parallel R_B \right) \right]$$

$$R'_L = r_o \parallel R_C \parallel R_L$$

$$V_o \simeq -g_m v_{\pi} R'_L$$

Bipolar Miller Effect

 

The left hand side of the circuit at XX' knows the existence of C_μ only through the current $I_\mu \rightarrow$ replace C_μ with C_{eq} from base to ground

Bipolar Miller Effect


$$I_{\mu} = sC_{\mu} (v_{\pi} - v_o) = sC_{\mu} \left[v_{\pi} - (-g_m R'_L v_{\pi}) \right]$$

$$I_{\mu} = sC_{\mu} (1 + g_m R'_L) v_{\pi}$$

$$sC_{eq} v_{\pi} = I_{\mu} = sC_{\mu} (1 + g_m R'_L) v_{\pi}$$

$$C_{eq} = C_{\mu} (1 + g_m R'_L), \text{ Miller capacitance for BJT}$$

Bipolar Miller Effect

 

$$v_\pi = v'_{sig} \frac{1}{1 + jf / f_o}$$

$$f_o = \frac{1}{2\pi C_{in} R'_{sig}}$$

Bipolar Miller Effect (cont')


$$\text{where } C_{in} = C_{\pi} + C_{eq} = C_{\pi} + C_{\mu} (1 + g_m R'_L)$$

$$\frac{V_o}{V_{sig}} = \left[\frac{R_B}{R_B + R_{sig}} \cdot \frac{r_{\pi} g_m R'_L}{r_{\pi} + r_x + (R_{sig} \parallel R_B)} \right] \left[\frac{1}{1 + jf / f_o} \right]$$

$$\frac{V_o}{V_{sig}} = A_M \frac{1}{1 + jf / f_o}$$

$$f_H = f_o = \frac{1}{2\pi C_{in} R'_{sig}}$$

Short-Circuit Current Gain

 

$$I_C = (g_m - sC_\mu) v_\pi$$

$$v_\pi = \frac{I_B}{\frac{1}{r_\pi} + sC_\mu + sC_\pi}$$

Short-Circuit Current Gain (Cont')

Define h_{fe} as short-circuit current gain

$$h_{fe} = \frac{I_C}{I_B} = \frac{g_m - sC_\mu}{\frac{1}{r_\pi} + s(C_\pi + C_\mu)}$$

$g_m \gg sC_\mu$ at freq. of interest

$$h_{fe} = \frac{I_C}{I_B} = \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi}$$

Short-Circuit Current Gain (con't)

$$h_{fe} = \frac{\beta_o}{1 + s(C_\pi + C_\mu)r_\pi}$$

Define h_{fe} has a single pole (or STC) response.
Unity gain bandwidth is for:

$$h_{fe} = \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi} = 1 \quad \text{or} \quad \frac{g_m}{2\pi f_T (C_\pi + C_\mu)} = 1$$

In some cases, if C_μ is known, then

Short-Circuit Current Gain (con't)


$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

From which we get


$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{g_m}{\omega_T}$$

$$\text{Thus, } C_\pi + C_\mu = \frac{g_m}{\omega_T} \Rightarrow C_\pi = \frac{g_m}{\omega_T} - C_\mu$$

CS – Miller Effect – Exact Analysis

 

CS – Miller Effect – Exact Analysis

 

$$G_i = \frac{1}{R_i} \quad G_D = \frac{1}{R_D} \quad G_g = \frac{1}{R_g} \quad g_{ds} = \frac{1}{r_{ds}} \quad R'_D = R_D \parallel r_{ds} = \frac{1}{G_D + g_{ds}}$$

$$\frac{v_o}{v_i} = - \frac{G_i R'_D (g_m - s C_{gd})}{G_i + G_g + s [C_{gs} + C_{gd}] + s C_{gd} R'_D [G_i + G_g] + s C_{gd} g_m R'_D + s^2 C_{gd} C_{gs} R'_D}$$

CS – Miller Effect – Exact Analysis

We neglect the terms in s^2 since

$$\left| s^2 C_{gd} C_{gs} R'_D \right| \ll \left| s C_{gd} g_m R'_D \right| \quad \text{or} \quad \left| s C_{gs} \right| \ll \left| g_m \right|$$

$$\frac{v_o}{v_i} = - \frac{G_i R'_D (g_m - s C_{gd})}{G_i + G_g + s \left[C_{gs} + C_{gd} (1 + g_m R'_D) + C_{gd} R'_D (G_i + G_g) \right]}$$

If we multiply through by $R_i = \frac{1}{G_i}$

CS – Miller Effect – Exact Analysis

$$\frac{v_o}{v_i} = - \frac{R'_D (g_m - sC_{gd})}{1 + R_i G_g + s \left\{ R_i \left[C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D (1 + R_s G_g) \right\}}$$

From which we extract the 3-dB frequency point

$$f_H = \frac{1 + R_i G_g}{2\pi \left\{ R_i \left[C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D (1 + R_i G_g) \right\}}$$

CS – Miller Effect – Exact Analysis


If G_g is negligible

$$f_H \simeq \frac{1}{2\pi \left\{ R_i \left[C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D \right\}}$$

If $R_i = 0$

$$f_H \simeq \frac{1}{2\pi C_{gd} R'_D}$$

BJT-CE – Miller Effect – Exact Analysis

 

$$G_i = \frac{1}{R_i}$$


$$G_C = \frac{1}{R_C}$$

$$g_\pi = \frac{1}{r_\pi}$$

$$g_o = \frac{1}{r_o}$$

$$R'_C = R_C \parallel r_o = \frac{1}{G_C + g_o}$$

BJT-CE – Miller Effect – Exact Analysis

 

$$\frac{v_o}{v_i} = - \frac{G_s R'_C (g_m - s C_\mu)}{G_i + g_\pi + s [C_\pi + C_\mu] + s C_\mu R'_C [G_i + g_\pi] + s C_\mu g_m R'_C + s^2 C_\mu C_\pi R'_C}$$

BJT-CE – Miller Effect – Exact Analysis

We neglect the terms in s^2 since

$$\left| s^2 C_\mu C_\pi R'_C \right| \ll \left| s C_\mu g_m R'_C \right| \quad \text{or} \quad \left| s C_\pi \right| \ll \left| g_m \right|$$

$$\frac{v_o}{v_i} = - \frac{G_i R'_C (g_m - s C_\mu)}{G_i + g_\pi + s \left[C_\pi + C_\mu (1 + g_m R'_C) + C_\mu R'_C (G_i + g_\pi) \right]}$$

If we multiply through by $R_i = \frac{1}{G_i}$

$$\frac{v_o}{v_i} = - \frac{R'_C (g_m - s C_\mu)}{1 + R_i g_\pi + s \left\{ R_i \left[C_\pi + C_\mu (1 + g_m R'_C) \right] + C_\mu R'_C (1 + R_i g_\pi) \right\}}$$

BJT-CE – Miller Effect – Exact Analysis


$$f_H = \frac{1 + R_i g_\pi}{2\pi \left\{ R_i \left[C_\pi + C_\mu (1 + g_m R'_C) \right] + C_\mu R'_C (1 + R_i g_\pi) \right\}}$$

If $R_i = 0$

$$f_H \simeq \frac{1}{2\pi C_\mu R'_C}$$

 Example


For the discrete common-source MOSFET amplifier shown, the transistor has $V_T = 1\text{V}$, $mC_{ox}(W/L) = 0.25\text{ mA/V}^2$, $I = 0$, $C_{gs} = 3\text{ pF}$, $C_{gd} = 2.7\text{ pF}$ and $V_A = 20\text{ V}$. Assume that the coupling capacitors are short circuits at midband and high frequencies.



(a) Find the 3dB bandwidth if $R_i = 0$

(b) Find the 3dB bandwidth if $R_i = 100\ \Omega$

Example – Part (a)

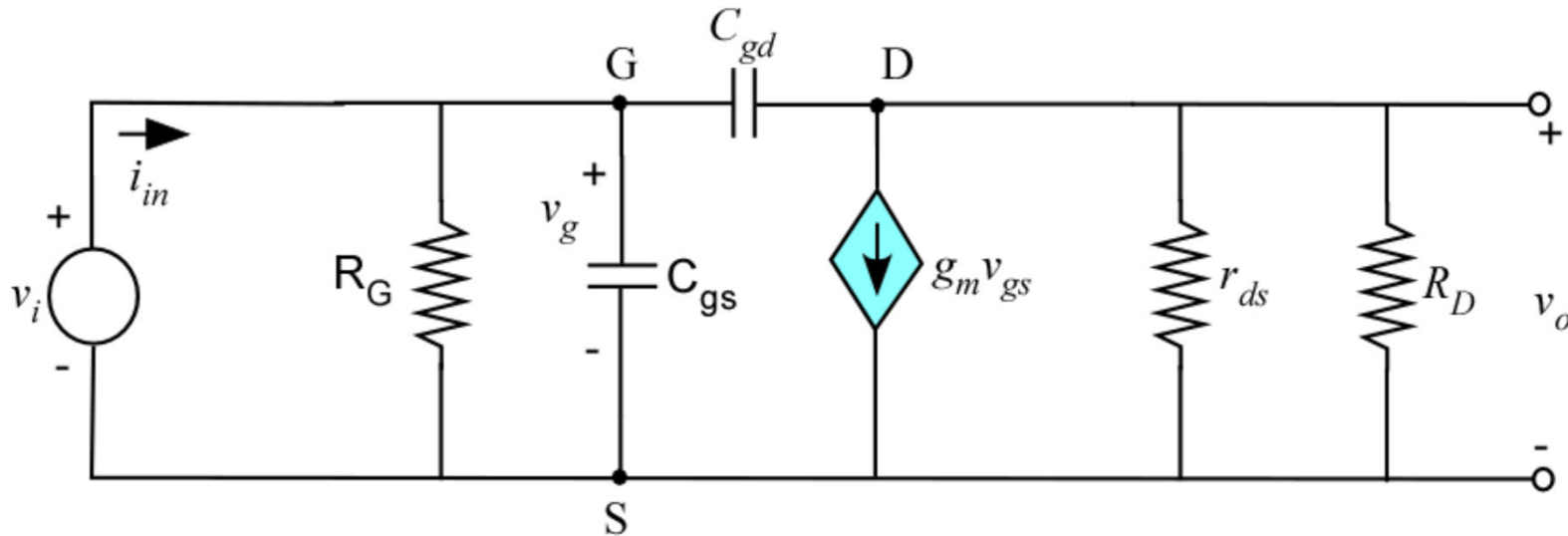


If $R_i = 0$,

$$f_{3dB} = \frac{1}{2\pi C_{gd} R'_D} \quad r_{ds} = \frac{|V_A|}{I_D} = \frac{20}{1.516} = 13 \text{ k}\Omega$$

$$R'_D = R_D \parallel r_{ds} = 13 \parallel 2 = 1.736 \text{ k}\Omega$$

$$f_{3dB} = \frac{1}{2\pi 2.7 \times 10^{-12} \times 1.736 \times 10^3} = 33.95 \text{ MHz}$$

Example Part (b)

 


If $R_i = 100 \, \Omega$,

$$g_m R'_D = 0.870 \times 1.736 = 1.51$$

$$f_H \approx \frac{1}{2\pi \left\{ R_i \left[C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D \right\}}$$


$$f_H \approx \frac{1}{2\pi \left\{ 0.1 \left[3 + 2.7 (1 + 1.51) \right] + 2.7 \times 1.736 \right\}} = 28 \text{ MHz}$$

Common Base (CB) Amplifier

 

High-Frequency Analysis of CB Amplifier

 Exact analysis is too tedious → approximate




From current gain analysis

$$\omega_{in-3dB} = \frac{1}{C_{\pi} \left[R_S \parallel R_E + \frac{r_x}{1 + \beta} \right] \parallel \left[\frac{r_{\pi}}{1 + \beta} \right]}$$

$$\omega_{out-3dB} = \frac{1}{C_{\mu} R_L}$$


The amplifier's upper cutoff frequency will be the lower of these two poles.

Emitter Follower

 

Emitter Follower High-Frequency

 Exact analysis is too tedious → approximate



$$A'_v(s) = \frac{g_m R_L}{1 + g_m R_L} \frac{1 + \frac{sC_\pi}{g_m}}{1 + \frac{sC_\pi R_E}{(1 + g_m R_E)}}$$

$$\omega_{3dB} = \frac{1 + g_m R_E}{R_E C_\pi} \simeq \frac{g_m}{C_\pi + C_\mu} = \omega_T$$

Bandwidth of Multistage Amplifier

- The time constant τ_{io} is the product of the capacitance and the resistance seen across its terminals with:
 - All other internal capacitors open circuited
 - All independent voltage sources short circuited
 - All independent current sources opened
- The upper 3dB frequency point ω_{3dB} is then found by using :

$$\omega_{3dB} = \frac{1}{\sum \tau_{io}}$$

Open-Circuit Time Constant Method

- The time constant of each capacitor in the circuit is evaluated. It is the product of the capacitance and the resistance seen across its terminals with:
 - All other internal capacitors open circuited
 - All independent voltage sources short circuited
 - All independent current sources opened
- The value of b_1 is computed by summing the individual time constants

$$b_1 = \sum_{i=1}^n C_i R_{io}$$

Open-Circuit Time Constant Method


- An approximation can be made by using the value of b_1 to determine the 3dB upper frequency point ω_H
- If the zeros are not dominant and if one of the poles P_1 is dominant, then

$$b_1 \simeq \frac{1}{\omega_{P1}}$$

Assuming that the 3-dB frequency will be approximately equal to ω_{P1}


$$\omega_H \approx \frac{1}{b_1} = \frac{1}{\sum_i C_i R_{io}}$$

Series-Shunt Feedback

 


Voltage mixing-voltage sampling feedback

Shunt- Series Feedback

 


Current mixing-current sampling feedback

Series-Series Feedback

 


Voltage mixing-current sampling feedback

Shunt-Shunt Feedback

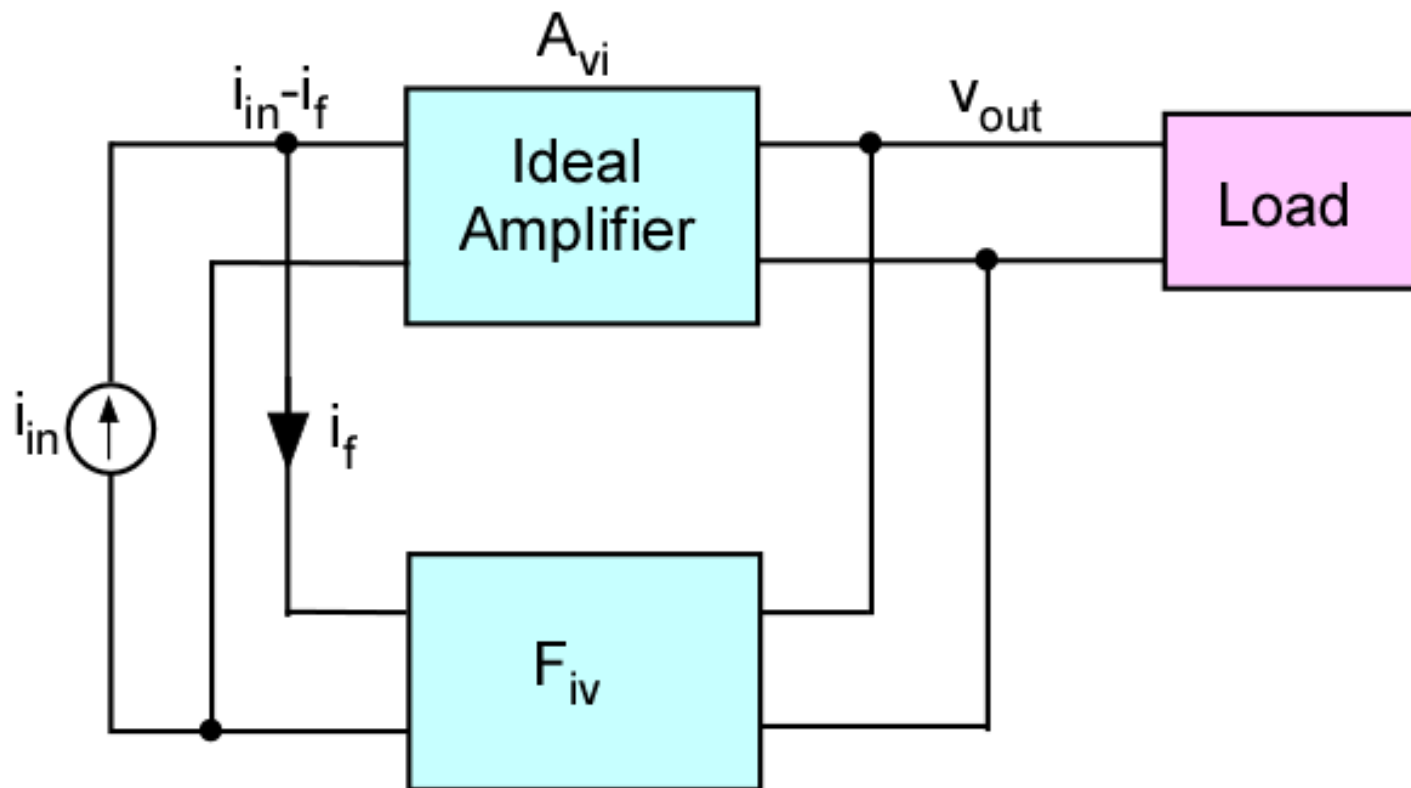

Current mixing-voltage sampling feedback


Series-Shunt Feedback : h-Parameters

 

$$|h_{12}|_{\text{basic amplifier}} \ll |h_{12}|_{\text{feedback network}}$$

$$|h_{21}|_{\text{feedback network}} \ll |h_{21}|_{\text{basic amplifier}}$$

Inverting Configuration

 


We introduce R_F (or R_2) to reduce gain (from inf)

- When R_F is connected to terminal 1, we talk about negative feedback. If R_F is tied to terminal 2, we have positive feedback

Inverting Configuration


Closed-Loop gain
 
$$\frac{v_o}{v_I} = -\frac{R_F}{R_1} = G$$



Observe that the closed-loop gain is the ratio of external components → we can make the closed-loop as accurate as we want. Gain is smaller but more accurate.

Non-Inverting Configuration

 

$$\text{Assume gain is } \infty \Rightarrow v_{ID} = \frac{v_o}{A} \rightarrow 0$$

Non-Inverting Configuration

Virtual short $\Rightarrow v_2 = v_I = v_1$

$$v_I \frac{(R_a + R_F)}{R_a} = v_o$$

$$G = \frac{v_o}{v_I} = 1 + \frac{R_F}{R_a}$$

$$G = 1 + \frac{R_F}{R_a}$$

Frequency Response – Non-Inverting

$$A_{ni}(f) = \frac{A_{MBni}}{1 + jf / f_{2ni}}$$

$$GBW_{ni} = A_{MBni} f_{2ni} = \frac{A_{MBoa}}{1 + A_{MBoa} F} \cdot f_{2oa} (1 + A_{MBoa} F)$$

$$GBW_{ni} = A_{MBni} f_{2ni} = A_{MBoa} f_{2oa} = GBW_{oa}$$

Gain-Bandwidth product is constant


Frequency Response – Non-Inverting

Midband voltage gain is reduced from A_{MBoa} to A_{MBni}

The upper 3-dB frequency will be greater than that of the op amp by the same factor of gain reduction.

If the low-frequency gain of the op amp is $A_{MBoa} = 200,000$ and with resistors $A_{MBni} = 40$, the gain is reduced by a factor of 5,000. If the basic 3-dB frequency is 5 Hz, the noninverting 3dB frequency will be 25 kHz.

Complementary MOS

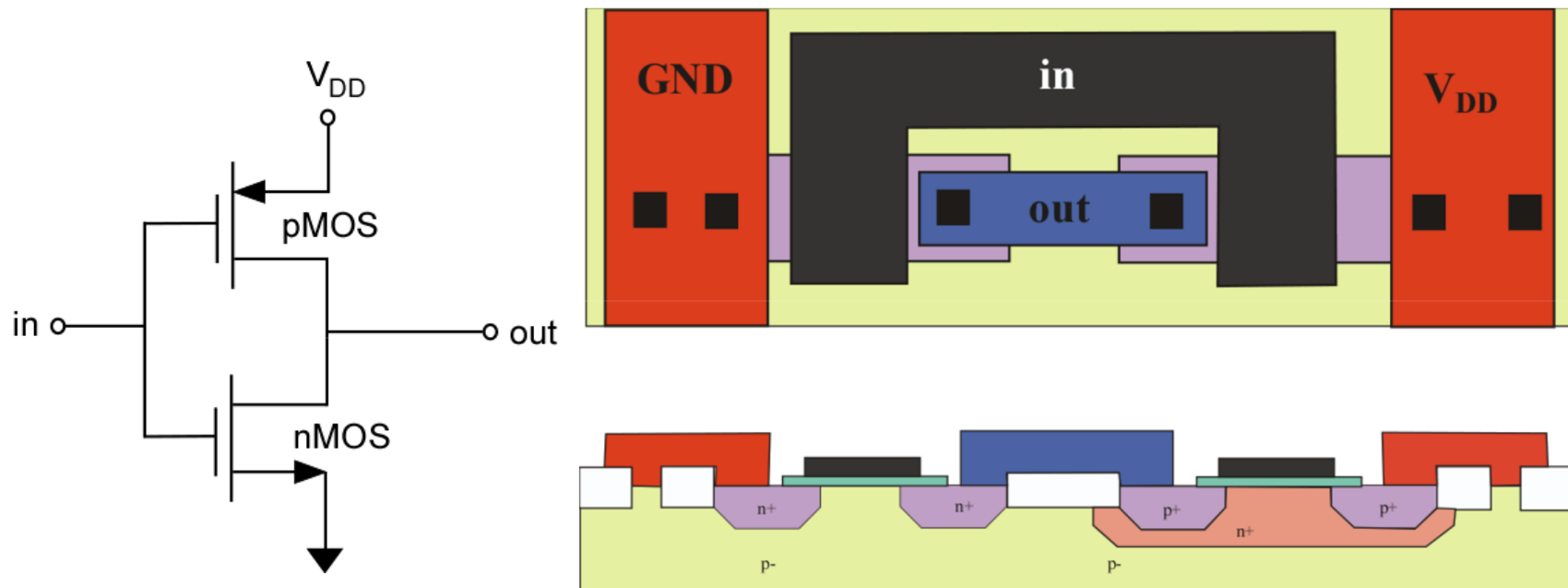

- **CMOS Characteristics**
 - Combine nMOS and pMOS transistors
 - pMOS size is larger for electrical symmetry

Voltage Transfer Characteristics (VTC)

The static operation of a logic circuit is determined by its VTC

- In low state: noise margin is NM_L


$$NM_L = V_{IL} - V_{OL}$$

- In high state: noise margin is NM_H

$$NM_H = V_{OH} - V_{IH}$$


- An ideal VTC will maximize noise margins

Optimum: $NM_L = NM_H = V_{DD} / 2$

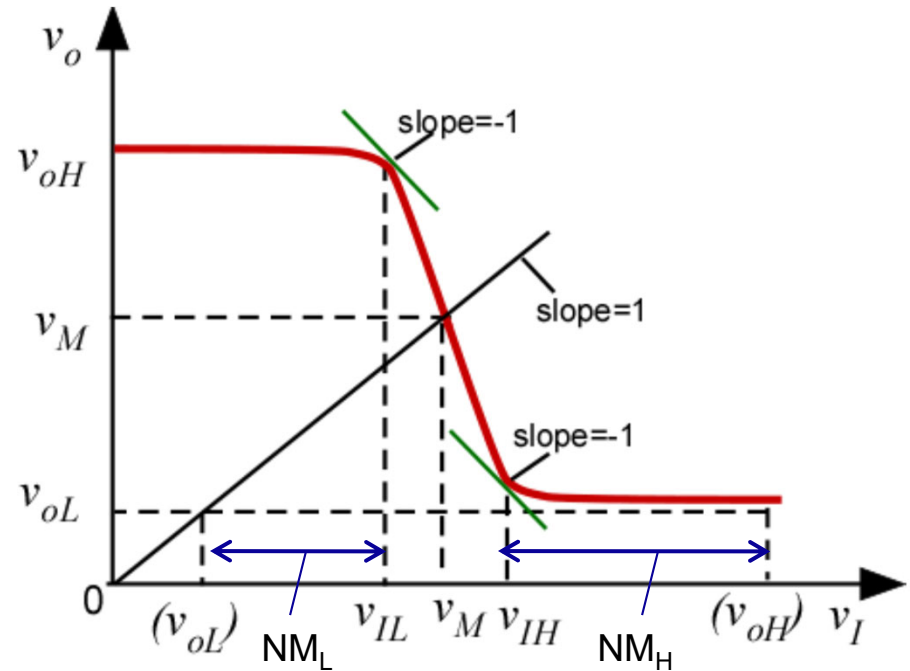

V_{IL} and V_{IH} are the points where the slope of the VTC=-1

Switching Time & Propagation Delay

 

Switching Time & Propagation Delay

t_r =rise time (from 10% to 90%)

t_f =fall time (from 90% to 10%)

t_{pLH} =low-to-high propagation delay

t_{pHL} =high-to-low propagation delay

Inverter propagation delay:
$$t_p = \frac{1}{2} (t_{pLH} + t_{pHL})$$

CMOS Noise Margins

When inverter threshold is at $V_{DD}/2$, the noise margin NM_H and NM_L are equalized

$$NM_H = NM_L = \frac{3}{8} \left(V_{DD} + \frac{2}{3} V_{th} \right)$$


NM_H : noise margin for high input

NM_L : noise margin for low input

V_{th} : threshold voltage

Noise margins are typically around $0.4 V_{DD}$; close to half power-supply voltage → CMOS ideal from noise-immunity standpoint

CMOS Switch

 

CMOS switch is called an inverter

CMOS Switch – Input Low

NMOS


$$V_{GSN} < V_{TN} \Rightarrow \text{OFF}$$

r_{dsn} high


PMOS

$$r_{dsp} = \frac{1}{k'_p \left(\frac{W}{L} \right)_p (V_{DD} - |V_{TP}|)}$$

r_{dsp} is low

 

CMOS Switch – On State

 


- **ON State (V_{in} : high)**
 - pMOS transistor is off
 - Path from V_{out} to ground is through nMOS $\rightarrow V_{out}$: low

CMOS Switch – Input High

NMOS

$$r_{dsn} = \frac{1}{k'_n \left(\frac{W}{L} \right)_n (V_{DD} - V_{TN})}$$

r_{dsn} is low

 


PMOS

$$V_{GSP} > V_{TP} \Rightarrow OFF$$

r_{dsp} high

Matched CMOS Inverter VTC

 CMOS inverter can be made to switch at specific threshold voltage by appropriately sizing the transistors



$$\left(\frac{W}{L}\right)_p = \frac{\mu_n}{\mu_p} \left(\frac{W}{L}\right)_n$$

Symmetrical transfer characteristics is obtained via matching $\rightarrow$ equal current driving capabilities in both directions (pull-up and pull-down)

Digital Logic - Generalization

De Morgan's Law

$$\overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots$$

$$\overline{A \cdot B \cdot C \cdot \dots} = \bar{A} + \bar{B} + \bar{C} + \dots$$

Distributive Law

$$AB + AC + BC + BD = A(B + C) + B(C + D)$$

- **General Procedure**
 1. Design PDN to satisfy logic function
 2. Construct PUN to be complementary of PDN in every way
 3. Optimize using distributive rule

Basic Logic Function




Basic
Function

INVERTER

NOR

NAND

Symbol

   

Devices
PUN

1
PMOS

2
PMOS-Series

2
PMOS-Parallel

Devices
PDN

1
NMOS

2
NMOS-Parallel

2
NMOS-Series

Truth
Table

	A	Y
	0	1
	1	0


	A	B	Y
	0	0	1
	0	1	0
	1	0	0
	1	1	0

	A	B	Y
	0	0	1
	0	1	1
	1	0	1
	1	1	0

Pull-Down and Pull-Up Functions

Pull-up network (PUN)

Pull-down network (PDN)

 


- **Key features**

- When PDN switch is on, PUN switch is off and vice versa
- Conditions for being on and off are complementary

Pull-Down and Pull-Up

PDN-parallel NMOS

 


$$Y_{DP} = \overline{A + B}$$

	A	B	Y_{DP}
	0	0	1
	0	1	0
	1	0	0
	1	1	0

Truth Tables


PUN-series PMOS

 

$$Y_{US} = \overline{A} \overline{B}$$


	A	B	Y_{US}
	0	0	1
	0	1	0
	1	0	0
	1	1	0

Two-Input NOR Gate

 

$$Y = \overline{A + B} = \overline{A}\overline{B}$$


Pull-Down and Pull-Up

 

$$Y_{DS} = \overline{A} \overline{B}$$

	A	B	Y_{DS}
	0	0	1
	0	1	1
	1	0	1
	1	1	0

PUN-Parallel PMOS

 


$$Y_{UP} = \overline{A} + \overline{B}$$

	A	B	Y_{UP}
	0	0	1
	0	1	1
	1	0	1
	1	1	0

Truth Tables


Two-Input NAND Gate

 

$$Y = \overline{AB} = \overline{A} + \overline{B}$$

Exclusive-OR (XOR) Function

 
$$Y = A\bar{B} + \bar{A}B \quad \bar{Y} = (\bar{A} + B)(A + \bar{B})$$



pull down

XOR

	A	B	Y
	0	0	0
	0	1	1
	1	0	1
	1	1	0

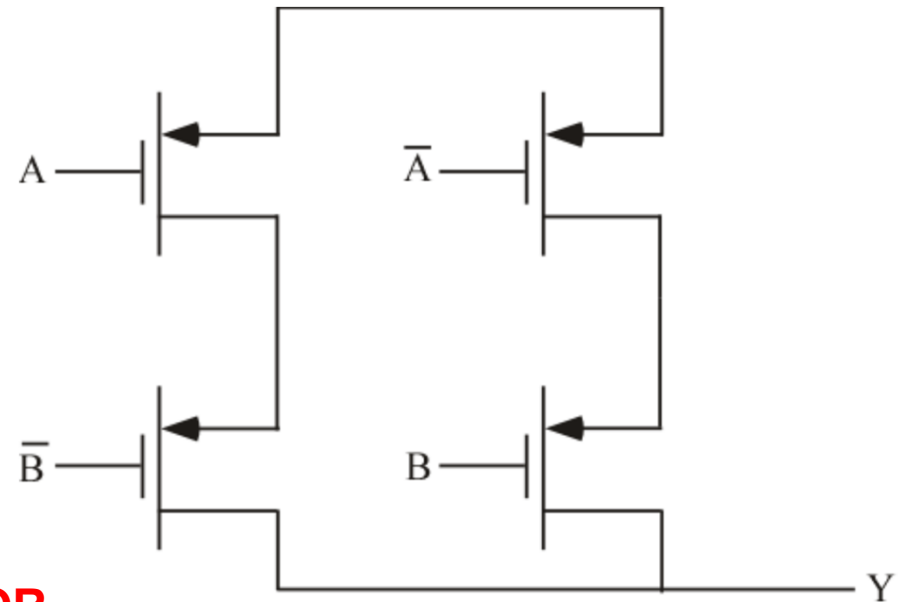

pull up