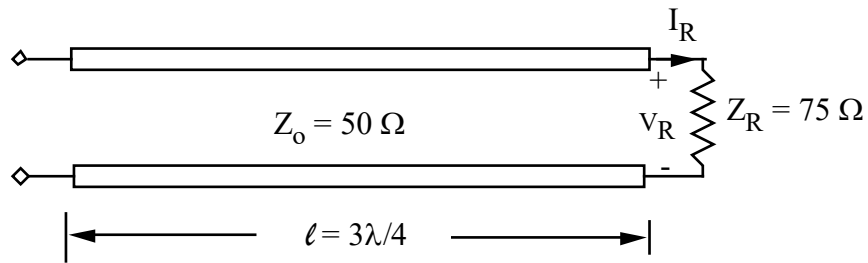


1. Consider the transmission line system shown in the figure above.

- Find the input impedance Z_{in} .
- Find the current drawn from the generator
- Find the time-average power delivered to the load

2. A lossless transmission line of characteristic impedance $75 \, \Omega$ is terminated by some complex load, Z_L . If the distance from the load to the location of the first impedance minimum is measured to be $.304\lambda$ and the impedance at that point is $22.5 \, \Omega$, using the Smith Chart find:

- a) The SWR.
- b) The load impedance, Z_L .
- c) The reflection coefficient, $\bar{\Gamma}_L$.
- d) Distance to the first voltage maximum.
- e) Value of the line impedance at this point.
- f) The distance to the closest point to the load where the real part of the line impedance is $75 \, \Omega$.
- g) Is the impedance at the point located in part f inductive or capacitive?




3. Given the lossless transmission line shown above,

- Find the reflection coefficient Γ_R and the standing wave ratio (SWR) for this loaded transmission line.
- Sketch the standing wave patterns for the magnitude of the voltage along this transmission line in terms of V_R .
- Determine the impedance at the input of this loaded transmission line.
- If a sinusoidal generator $10 \angle 0^\circ \text{ V}$, which has a source impedance of $100 \, \Omega$ is connected to this loaded transmission line, what is the time average power delivered to the $75\text{-}\Omega$ load.

4. Answer the following questions using a Smith chart. Clearly identify significant features on the chart. A transmission line with characteristic impedance $50\ \Omega$ is terminated by a load of impedance $Z_L = 40 + j50\ \Omega$.

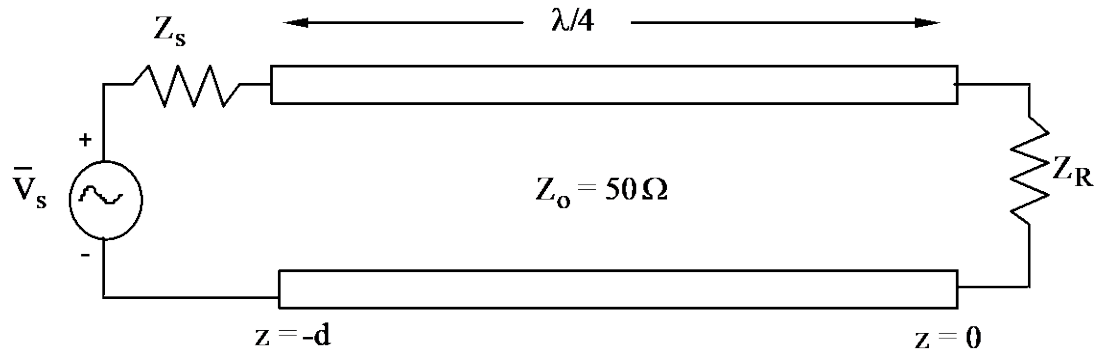- (a) What is the SWR?
- (b) What is the phase of Γ_L ?
- (c) What is the normalized admittance at the load?
- (d) What is the normalized admittance at $d = 12.2\lambda$ toward the generator from the load?
- (e) What is the phase of Γ at $d = 12.2\lambda$ toward the generator from the load?
- (f) What is the shortest distance from the load at which a short-circuited stub could be attached to achieve an impedance match?
- (g) What would the normalized input admittance of the stub be?



5. For the above figure, let $\bar{V}_s = 1$ volt, $Z_s = 30 \Omega$, and $Z_R = 40 \Omega$.

- What is the impedance at the input of the line ($z = -d$)?
- What is the phasor current through Z_s ?
- What is the phasor current through Z_R ?
- What is the time-average power delivered to the load?