### **ECE 451 Automated Microwave Measurements**

# Homework #4 Due Wednesday, March 26, 2025

# MODELING MICROSTRIP LINE USING ADS

#### Introduction

While direct measurement of a device is the most accurate way to determine its behavior, it is often also the most expensive and time-consuming. With the advent of the digital computing age, we now have access to powerful simulation tools that allow for computer-aided engineering (CAE). These tools allow an engineer to simulate a design with extremely high-fidelity so that he or she can optimize a design before fabrication.

In this homework assignment, you will be using Keysight Advanced Design System (ADS) to model a pre-existing microstrip line whose S parameters you measured in Experiment 5. You will use the existing microstrip line models in ADS along with some lumped elements to generate S parameters which will be compared against measurement.

#### Background

You will be modeling a microstrip line that looks like this (which you measured in Experiment 5):



It is on an FR4 substrate, which is an extremely common substrate due to its affordability. FR4 is a composite material composed of woven fiberglass cloth with a flame-resistant epoxy material that binds it together. A thin layer of copper foil is laminated to both sides of it. This foil is either milled or etched away to form the desired microstrip pattern and then connectors are soldered on.

The connectors for this device are SMA connectors. They are coaxial RF connectors that offer excellent electrical performance from DC to 17 GHz. Typically these connectors are tightened to 8 lb in with a torque wrench to ensure a good impedance match and minimize reflections.

#### Procedure

- 1) Open ADS and create a new workspace. In the main workspace window, click to create a new schematic and name it "microstrip." Close the Schematic Wizard Window that pops up.
- 2) First, you are going to create the microstrip substrate. This item defines the parameters of the substrate that the microstrip line is on (permittivity, loss tangent, thickness, etc.). It can be

found in the "TLines-Microstrip" library as shown in Figure 2 and it is which can be clicked and placed on the schematic. Set the following parameters:

- a. H = 1.56 mm
- b. Er = 4.8
- c. T = 0.02 mm

File	Edit	Select	View	Insert	Options	Tools	Layout	Simulate	Wind	low	Dyn	amicLin	c De	signGu	uide	Help					
	Ē	<b>-</b>		<u>}   +</u>	-   )	< 9	91	2]   +‡+	0	<b>P</b> e	<b>9</b> e	<b>e</b>	. 🎍			( <b>)</b>	ŧĨ	*	X	<u>.</u>	
TLin	es-Micro	strip		-			• 🖓 •			<b>∼</b> ₹= 17	$\mathbf{i}$		2 4		ų۳		w j	<b>•</b>			
Palette		<b>8</b> '	• •		• •							• •	• •	• •	• •		•	• •	• •		
[ <b>*</b>	<mark>  -</mark> 3		• •			• • •						• •	• •	• •	• •		·	• •		· ·	
MSUB	MSUB	ST .	• •		•	• • •		• • •				• •	• •	• •	• •		·	• • •		· ·	
		, i	• •		· ·		• •	• • •				• •	• •	• •	• •		·			• •	
Maclin	Macli	F :															÷				
-		<b>.</b>																			
MSARN						. 🤨	MSub			. /											
						+ .∟			•				•								
MBstut	Mefi	, 1						· · ·		•		•		•				• •			
			• •	• • •	• •	· · · •	1=1.56 mr	ni i i	• •	•	• •		•		• •	• •	·	• •	• •	• •	
Melin	Heor		• •		• •	· · · •	Er=4.8		• •	ų.	·	• •	• •	// ·	• •	·			• •	• •	
			• •		• •		/lur=1 Cond-1 OF			• •		$\sim$ $\cdot$	• •	· ·	• •	•	•			• •	
- <del>C</del>			• •		• •	· · · · ·	lu=3.9e+0	034 mil		• •	• •	• •	· .	• •	• •			· · · ·			
Mcroso							[=0.02 mn	n									. /				
1 2	-00	H .				p	lanD=0 Rough=0 r	nil · ·							. ~						
Mourve	Mua					E	Bbase=										$\checkmark$				
		L .				[	Opeaks=														
MICAP			• •					· · ·				• •	• •	• •	• •					· ·	
	Ψ		• •		• •			· · ·						• •	• •		·		• •	• •	-
MICAPS		*4 🔻	•					0.1						2.00					•		
Select: Enter the starting point								0 items			ads_d	evice:dr	awing	-2.00	0, 0.625	<b>)</b>	-4.8	15, 2.25	in		

Figure 2: Creating the microstrip substrate. Library selection is boxed in red.

-

3) Next, find the microstrip line in the same library: MLIN. Place five of them down on the schematic as shown in Figure 3. Give them the same widths and lengths as shown in the figure. Each one of these represents a segment of the microstrip line that we are modeling. We measured the width and length of these microstrip lines with a caliper for your convenience.

File	Edit	Select	View	Insert	Options	Tools	Layout	Simulate	Window	DynamicLink	DesignGuid	le Help				
	Ē	<b>-</b>		<u>}</u>   <b>≬→ </b>	-   🗡	9	95	2] +∳+ [	<u>i</u> 🌮	🥺 🤣 🤙	🛃 🔔	<u>a</u> 🖨	1 î	* 🕅	<u> </u>	•
TLin	es-Micro	ostrip		•			- ()-	L 0110 - VAR	<u>∎</u> R=17	NAME 🐰	🕈 🥨 🌵	1	m 🛵			
Palette	•	8								·						. *
MICAP		PZ 🔺			. **			*		4		<b>.</b>	≁	•		
					MLI TL1	N <sub>.</sub>		MLIN TL2		MLIN TL3	MLIN TL4		MLIN TL5		• •	
			• •	• • •	Sút	ost="MSi	ib1"	Subst=	'MSub1"	Subst="MSub	1" Subst=	"MSub1"	Subs	t="MSub	1" –	
الد. Miang	Mlan	g6	· · · ·		/V= L=5	2.7 mm 3.25 mn	 a	W =1.54	imm : : 3 mm - : :	W=2.7 mm L=55.70 mm	W =7.62 L=20.20	2 mm 8 mm	W=2. L=53	7 mm 42 mm	· ·	
Mlang(		#• :F	· ·			• •	 Moute	· · · ·				••••	· ·		 	
	· · · ·	] )C ≡	· · ·			+ ·	MŞUŖ				· · · · · ·		· · ·	· · ·	• •	
	ہ ا Mrir	H	· ·	 			MSub H≂1 /6 Fr=4 S	mr /					· ·		· ·	·
rindela	i indr	ibr	· ·	· · ·	· · ·	· ·	Mur=1 Cond=1	.0E+50.					· ·		· ·	
ŀĐ	•œ	₽	•••			· ·	Hu=3.96 T=0.021	e+034 mil mm		<pre></pre>			7 :		· ·	:
rindwb	r rinde	elm					IanD=0	0 mil								
rindsb		) UB					- Bbase= Dpeaks	=								
		- -	• •			• •	, Divodito						• •		• •	- <del>-</del>
Select	: Enter	the start	ing poin	t				0 items		ads_device:dra	wing -2.125,	-0.875	-6.000,	-1.250	in	E Lat

Figure 3: Placing the microstrip line segments.

4) Now, switch to the "Simulation-S\_Param" library. Click on and place two of them

then click on spin and place one of them as shown in Figure 4. The terminations are like the measurement ports on a network analyzer and the "SP" block is the simulation controller.

File	Edit	Select	View	Insert	Options	Tools	Layout	Simulate	Window	DynamicLink	DesignGuide	Help			
	6	<b>  </b>		3   +	-   🗡	19	61	2∐ +∯+ [	<u>i</u> 🗘 🧕	<b>e</b> e e	1 🗟 🕹	2 🖨 (	ñ 😹		
Sim	ulation-S	_Param		▼ a	ds_simulatior	n:Term	- 🖓	0110 VAR	L R-17		← 🤹 🜵	<b>1</b> M	v 🛵		
Palette	:	8	· · ·			· · ·									
SP	SP L	ab													
Sweep Plan		yp	· · · · · ·		Term *	-	<mark></mark>		<del></del> -					 m	· ·
			· · · · · ·	1 ( <b>\$</b>	Nun ( Z=50 Ohm	TL1 Subst="	MSub1"	TL2 Subst="N	ISub1" Su	3 TL bst="MSub1" Su	4 ////////////////////////////////////	MLIN TL5 Subst="MSub	1" \$ <sup>™</sup>	rm∠ im=2 =50 Ohm	· ·
Option	s Tern		· · · · · ·	1.		W=21 L=1	nm mm	W=1.54 r L=20.13 r	nm W= nm L=	=2.7 mm W 55.70 mm L=	=7.62 mm 20.28 mm	N=2.7 mm L=53.42 mm	°.₩°.		
RefNe	t RefN	D S N et	: : :	<u> </u>			 								
-		ลิไ			• • • •		· · MSu			SPARAMETERS	<b>.</b>				
OscTes	t Net					• •	MS /B M' ub1		3_Para						
NdSet	NdSe Nam	e l					- 1.50 Er~5.8	3 m	Start= Stor	GHz 0 GHz					
			· · · · · ·	· · · · · ·	· · · ·	· · ·	Mur=1	1.0E+50	Ster	0 Gn.					· ·
Outpu	Tem	ย่	· · · · · ·	· · ·		· · ·	Hu=3.9 T=0.02	99+034 mil 1 mm		· · · · · /	· · · · · ·				
Meas		וו	· · ·				Rough	=0 mil : :			· · · ·				
	MaxG	ain					Dpeak	s=				. 7			
PwrGai	n VoltG	ain 🔻	• • •												
Selec	: Enter	the start	ing poi	nt				0 items		ads_device:drav	wing -3.125, -2.	750	-0.625, -5.7	50	in at

Figure 4: Adding S-parameter Terminations and Simulation Controller.

5) Double click on the "S-Parameters" Block and set the parameters as shown in Figure 5.

Then use and to complete the circuit as shown in Figure 6 to complete the circuit. Then press to simulate the circuit. Doing this generates the S parameters for this circuit. **Print this schematic out and include it with your homework.** 

_Param I P1	Instance N	lame		_							
Freque	ency	Para	meters	No	ise	Outp	ut 🕛 🕨				
	Frequence	y		<b>.</b>			ן ר				
	Swee	р Тур	2	Linear		•					
	Start/Stop Center/Span										
	Start		300		kHz	•					
	Stop		6		GHz	-					
	Step-siz	e	3.7498	31	MHz	-					
	Num. of	fpts.	1601		]						
	Use	sweep	o plan			Ŧ					

Figure 5: Setting the S-parameter simulation block parameters.

File	Edit	Selec	t	Viev	v I	Inse	rt	Op	otio	ns	Тос	ols	Lay	out	Si	mul	late	W	ind	ow	Dy	/nar	nicL	ink	D	esig	nGui	ide	н	elp								
	ŕ		è		8	1	≁ļ	<b> </b> +	0	X		9	6		<u>2</u>	+	÷	0	4	)	Q	Ę	ŧ	ġ	-		È	1	2	2		ĩÞ		K	X	Ş		
Simu	lation-9	_Paran	n			•	ad	ls_rf	lib:G	ROL	JND		-	0-	4	0	110	<u>ii</u>	ΝĒ	17	1		۲	#2 25	+	٢	4	Ų₽	1		Ŵ	A  ;						
2 Delette		-	•							•															•			•			· ·						•	
Palette					· ·			• •	·	•		•	• •	• •		• •		•			• •		· ·	·	• •		• •			• •			• •	•	• •	•	•	
(2)	0	5 <u>^</u>	·	·	• •	·	•	• •	•	•	• •	•	• •	• •	·	• •	• •	•	• •	·	• •	·	• •	•	• •	·	• •	•	·	• •	·	·	• •	•	• •	•	• •	
SP	SP L	.ab		:		÷	:		÷	:					÷			:		÷	: :	÷		÷		÷	: :	:	÷	: :	÷	÷		÷	: :			
Sween	1 20											_								_				_					-									
Plan		2 WD				· 🛉	÷	.Terr	n.	0	<u>-</u>	ب		• •		L	_	•		┖				╸							•	÷ i	ę.	Ten	m		•	
			·	·	• •	-	٤I	Nur	n1 n=1		TL1	γ.	• •	• •	·	TL2	N	•	• •	TL.	ли 3	·	• •	TL.	JN . 4	·	• •	·	MLIN TL5		•	· -	۶	Nu	m2 m=2	•	•	
			:				۱I	Z=5	0 01	m.	Súb	st="N	MSub	14		Sub	st="1	/ISub	1"	Su	bst="	MSu	b1"	Su	ibst=	MSu	b1"		Súbs	t="K	//Súb	14	٦.	Z=!	50 Oh	m		
Uption:		<u> </u>					Τ		4.		5	2.7 m 3.25	nm mm		÷	W=	1.54 0.1	mm mr		E=	≈2.71 55.70	nn mm		L=	=7.6 20.2	2 mm 3 mm			W=2 L=53	. / m 1.42 i	mm. mm	1	Ŧ					
		]§					-		•			•																					-					
RefNe	Refl	let	·	·	• •	·	·	• •	·	•	• •			_			• / •	1		<u></u>	$\sim$		• •		<u>.</u>	·	• •	•	·	• •	·	·	• •	·	• •	•	•	
( AG	Line	an	•	•	• •	·	•	• •	•	•	• •		· [ ·	MS	1.1	•	•		2	1	ΡĂ	RA)		RS	1	•	• •	•	•	• •	•	•	• •	•	• •	•	• •	
OscTes	t Ne											+		MSUE	5				SI			-																
		_												MSub H=1	1 18 m/r			× .	SP						•		• •											
NdSet	NdS Nan	et ne	•	·	• •	·	·	• •	÷	•		•	· • i	Er=4)	B ·	•		·	Sto	3	JO kH GH	•	• •	•	•	•	• •	•	•		·	·	• •		• •	•	•	
		=	· ·	•	• •	•	•	• •	•	•	• •	•	• • •	Mur=: Cond:	1 . =1.0F	+50	• •	•	Ste	p≐			• •	•	1	•	• •	•		• •		ř	• •	•	• •	•	•	
SP	Dis	P.												Hu=3	90+0	134 n	nil																					
loadbad		E												T=0.0 Ten Da	2 mn ⊧∩ `	٩											1.				1.							
Meas	1	۳.	•	·	· ·	·	•	• •	·	•		•	• • •	Rougi	h=0 n	nil -		•		•	• •	·		·	• •		• ~		•	• •	•	•		·	• •	•	•	
Eqn	Max6	iain	•	·	• •	·	•	• •	·	•	• •	•		Bbas( Doeal	9= . (s=	• •	• •	•		·	• •	·	• •	·	• •	·	• •			-	•	·	• •	•	• •	•	• •	
נייייניו						÷	:		÷													÷		÷				:				:						
PurGai		iain –																																				-
Calact	- Enter	the sta	1												0						a da						750	2 5	00			0.27	75 7		-			
Select	: enter	une sta	ntiñ		unt				E:			1	Т	1	•	iten	ns			1	ads	ae	vice:		VINC	• -1	.750	. 5.3	00			9.51	D. 4	.5/:	,		in	1.1

Figure 6: The circuit ready for simulation.

- 6) When the data display window pops up, use the datafile tool to import the "Touchstone" S-paramter you measured in Part 2, Experiment 5. Plot S<sub>11</sub>, S<sub>21</sub>, S<sub>12</sub>, and S<sub>22</sub> in dB for both datasets as shown in Figure 7.
- 7) Notice that we have excellent match for  $S_{11}$  and  $S_{22}$ , but a poor match for  $S_{21}$  and  $S_{12}$ .



Figure 7: Data display comparing simulated data with measured data. The S<sub>11</sub> and S<sub>22</sub> match reasonably well, but the S<sub>21</sub> and S<sub>12</sub> do not match.

#### **Improving the Model**

8) We now attempt to improve the model by providing a simple lumped element model for the SMA connector. Our simple model for an SMA connector is a series resistor and inductor and a shunt capacitor, as shown in Figure 8. Lumped elements can be found in the "Lumped-Components" library. The inductor lumped element model also contains a series resistance parameter that can be used instead of having an actual series resistor, as the figure denotes. An SMA Connector Model should be made for both the input and the output, as shown in Figure 9. Good values for the inductor, resistor, and capacitor are 6.4 ohms, 2 nH, and 0.5 pF, respectively. Use the tuning feature in ADS to tune your R, L, C values in order to

optimize your lumped model. The link below is to a video that describes how to tune your parameters to optimize the match of your model to your measurements in ADS.



#### Tuning instructional video: https://www.youtube.com/watch?v=OcHV9qFGy1U





Figure 9: The completed microstrip line model included the SMA connector models at both the input and the output.

# Discussion

9) These values should improve your match, particularly for lower frequencies, but they will not be perfect since there are higher-order effects at work that cannot be accurately described with such a simplistic model. There is always a tradeoff between the sophistication of a model and how accurate it is. The benefit of generating an accurate model is that it can have some useful predictive power that might save design time in the future. Be cautious in your use of tuning and optimization algorithms. It is very easy to depend on the simulation power of your software while disregarding the fundamentals that you have learned, leading to much wasted time. It can also be tempting to over-optimize your model, wasting time perfecting something that only needs to work roughly. Gaining work experience and seeking the advice of those who have this experience will give you insight on how to find the best balance for these concerns.

For further study, here is a link to a paper describing a very sophisticated model of the SMA connector. Feel free to explore it if you are interested: <u>https://www.aetjapan.com/software/pdf/434.pdf</u> http://www.piers.org/piers2k4Pisa/session\_05/05\_01.pdf

# **Conclusion Questions:**

- 1. How does an electromagnetic wave propagate through a microstrip line?
- 2. Briefly explain how a microstrip line differs from a coplanar waveguide?
- 3. How did adding the lumped element model of the SMA connectors affect our match to the measured data? After tuning, what R, L, C values gave you the optimized match of your model to measurements?
- 4. What might account for the differences between simulation and measurement? What aspects of the real device were not modelled?
- 5. Over which frequency range is our model accurate? Why do you think this is true?