

NAME Solutions

NETID _____

MIDTERM EXAM

ECE 451

March 10, 2021

Instructions: Write your name and NetID where indicated. This examination consists of 4 problems. This is an open-book and open-notes exam. Use 50Ω as the reference impedance for all measurement systems.

Problem 1 (25 pts)	Problem 2 (25 pts)	Problem 3 (25 pts)	Problem 4 (25 pts)	Total (100 pts)


Mason's non-touching loop rule:

$$T = \frac{P_1 \left[1 - \sum L(1)^{(1)} + \sum L(2)^{(1)} - \dots \right] + P_2 \left[1 - \sum L(1)^{(2)} + \sum L(2)^{(2)} - \dots \right] + \dots}{1 - \sum L(1) + \sum L(2) - \sum L(3) + \dots}$$

1. The matrices below are measured scattering parameters. In each case, indicate the characteristics that apply by checking in the appropriate boxes.

	$\begin{bmatrix} 0.8 & 0.6 \\ 0.6 & j0.8 \end{bmatrix}$	$\begin{bmatrix} 0 & 0.1 \\ 10 & 0 \end{bmatrix}$	$\begin{bmatrix} 0 & e^{-(\alpha+j\beta)d} \\ e^{-(\alpha+j\beta)d} & 0 \end{bmatrix}, \alpha, \beta > 0$
active	No	Yes	No
reciprocal	Yes	No	Yes
lossy	No	No	Yes

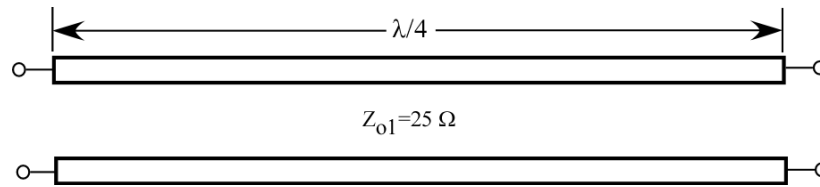2. For the transmission line shown below, write the scattering parameter matrix as measured on a 50- Ω network analyzer.



Solutions

$$S_{11} = \frac{(1 - X^2)\Gamma}{1 - X^2\Gamma^2} \quad \text{and} \quad S_{21} = \frac{(1 - \Gamma^2)X}{1 - X^2\Gamma^2}$$

$$\text{with } \Gamma = \frac{Z_{o1} - Z_o}{Z_{o1} + Z_o} \quad \text{and} \quad X = e^{-j\frac{2\pi}{\lambda}l}$$

$$X = e^{-j\frac{2\pi}{\lambda} \frac{\lambda}{4}} = e^{-j\pi/2} = -j$$

$$\Gamma = \frac{25 - 50}{25 + 50} = \frac{-25}{100} = -\frac{1}{4}$$

$$S_{11} = \frac{(1 - (-j)^2)(-1/4)}{1 - (-j)^2(1/16)} = \frac{-2(1/4)}{1 + 1/16} = -0.6$$

$$S_{21} = \frac{(1 - 1/16)(-j)}{1 - (-j)^2(1/16)} = \frac{-8j/16}{1 + 1/16} = -j0.8$$

$$S = \begin{bmatrix} -0.6 & -j0.8 \\ -j0.8 & -0.6 \end{bmatrix}$$

3. A transmission line of characteristic impedance Z_o , length d , propagation velocity v , and propagation constant β is terminated with an open.

- Find the input impedance Z_{in} . Express your answers in terms of Z_o , β , and d
- Draw a rough sketch of Z_{in}/Z_o for βd ranging from 0 to π and label the frequency bands where the transmission line looks capacitive and where it looks inductive.
- At what frequencies does this open transmission line look like a short circuit?


Solutions

(a) For a transmission line of length d , we have:

$$Z_{in} = Z_o \left\{ \frac{Z_L + jZ_o \tan \beta d}{Z_o + jZ_L \tan \beta d} \right\}$$

If $Z_L \rightarrow \infty$, then $Z_{in} = -jZ_o \cotan \beta d$

(b)

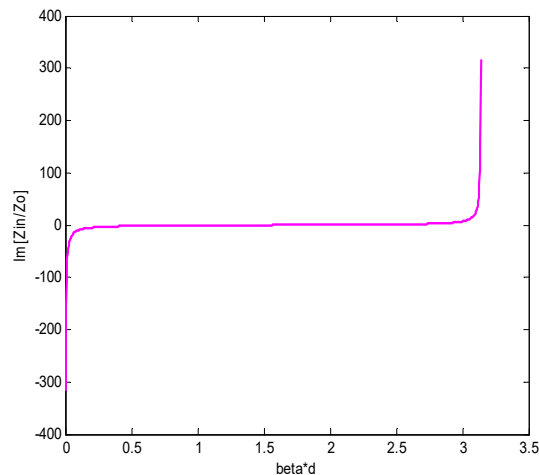

(c) The TL looks like a short for $\beta d = \frac{(2n+1)\pi}{2}$, $n = 0, 1, 2, \dots$ or

$$\frac{2\pi f d}{v} = \frac{(2n+1)\pi}{2}, n = 0, 1, 2, \dots$$

where v is the propagation velocity in the TL. This leads to: $f = \frac{(2n+1)v}{4d}$, $n = 0, 1, 2, \dots$

If $n = 0$, $f = v/4d$

4. A lossless transmission line has the following per unit length parameters: $L = 80 \text{ nH}\cdot\text{m}^{-1}$, $C = 200 \text{ pF}\cdot\text{m}^{-1}$. Consider a traveling wave on the transmission line with a frequency of 1 GHz.

- (a) What is the attenuation constant?
- (b) What is the phase constant?
- (c) What is the phase velocity?
- (d) What is the characteristic impedance of the line?
- (e) When the dielectric in the transmission line is replaced with air ($\epsilon_r = 1$), the capacitance per unit length of the line is found to be $C(\text{air}) = 50 \text{ pF}\cdot\text{m}^{-1}$. What was the effective relative permittivity of the dielectric?

(a) $\alpha = 0$

(b) $\beta = \omega\sqrt{LC} = 25.13 \text{ radians / m}$

(c) $v_p = \omega / \beta = \frac{1}{\sqrt{LC}} = 2.5 \times 10^8 \text{ m / s}$

(d) $Z_o = \sqrt{L/C} = 20 \Omega$

(e) $\epsilon_r = \frac{200}{50} = 4$