

# ECE 451


# Advanced Microwave Measurements

## Lossy Transmission Lines


Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jschutt@emlab.uiuc.edu

# Loss in Transmission Lines

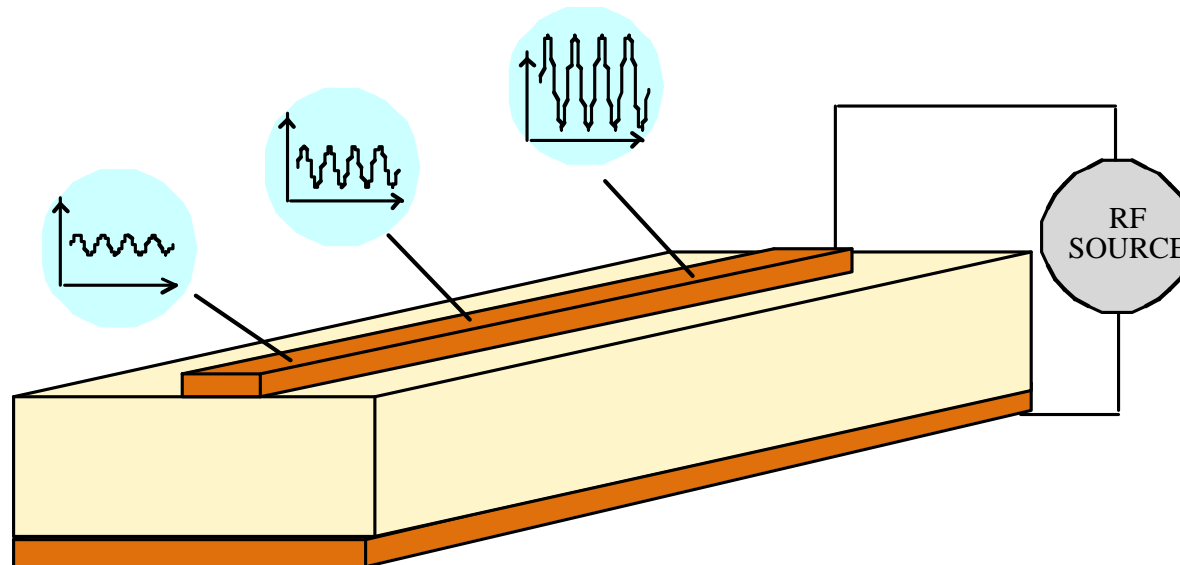

Signal amplitude decreases with distance from the source.




# Skin Effect in Lines

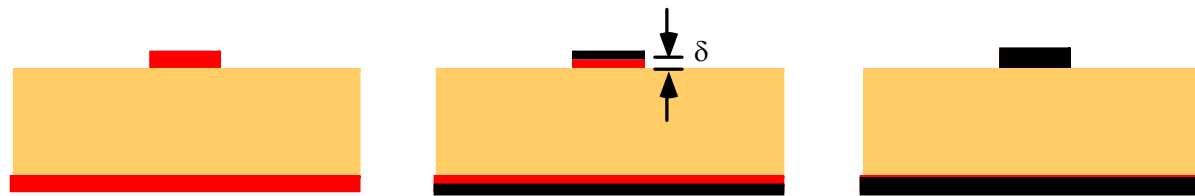


Low Frequency

High Frequency

Very High Frequency

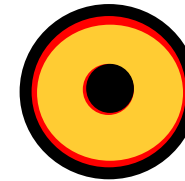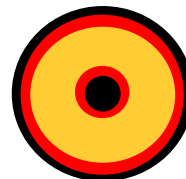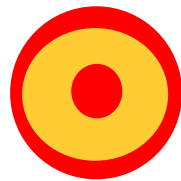

# Skin Effect in Microstrip

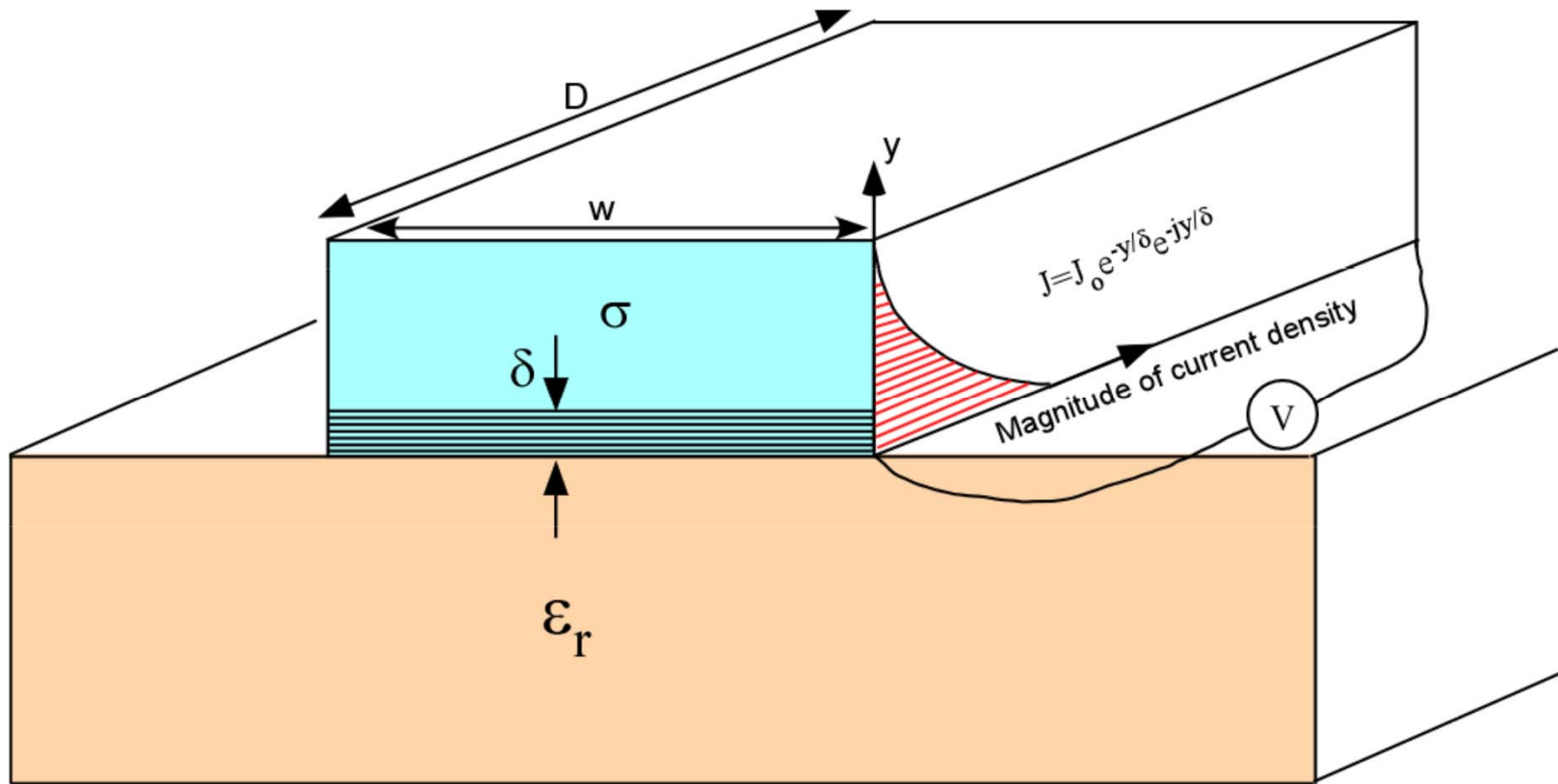

H. A. Wheeler, "Formulas for the skin effect," Proc. IRE, vol. 30, pp. 412-424, 1942

# Skin Effect in Microstrip

Current density varies as

$$J = J_o e^{-y/\delta} e^{-jy/\delta}$$

Note that the phase of the current density varies as a function of  $y$

$$I = \int_0^{\infty} J_o w e^{-y/\delta} e^{-jy/\delta} dy = \frac{J_o w \delta}{1 + j}$$

$$\sigma E_o = J_o \Rightarrow E_o = \frac{J_o}{\sigma}$$

The voltage measured over a section of conductor of length  $D$  is:

$$V = E_o D = \frac{J_o D}{\sigma}$$

# Skin Effect in Microstrip

The skin effect impedance is

$$Z_{skin} = \frac{V}{I} = \frac{J_o D (1+j)}{\sigma J_o w \delta} = \frac{D}{w} (1+j) \sqrt{\pi f \mu \rho}$$

where  $\rho = \frac{1}{\sigma}$  is the bulk resistivity of the conductor


$$Z_{skin} = R_{skin} + jX_{skin}$$

with

$$R_{skin} = X_{skin} = \frac{D}{w} \sqrt{\pi f \mu \sigma}$$

**→ Skin effect has reactive (inductive) component**

# Lossy Transmission Line

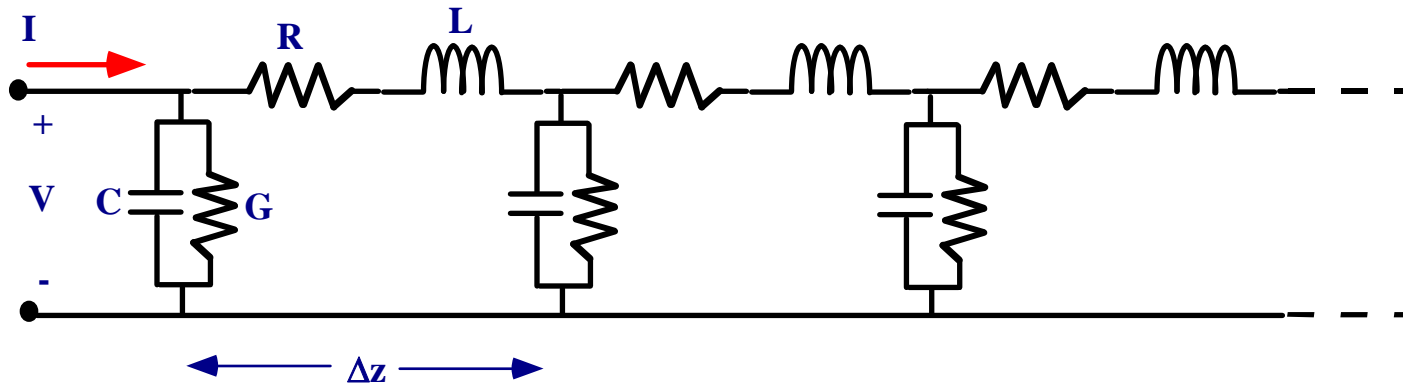


## Telegraphers Equation: Time Domain

$$-\frac{\partial V}{\partial z} = RI + L \frac{\partial I}{\partial t}$$

$$-\frac{\partial I}{\partial z} = GV + C \frac{\partial V}{\partial t}$$

# Lossy Transmission Line

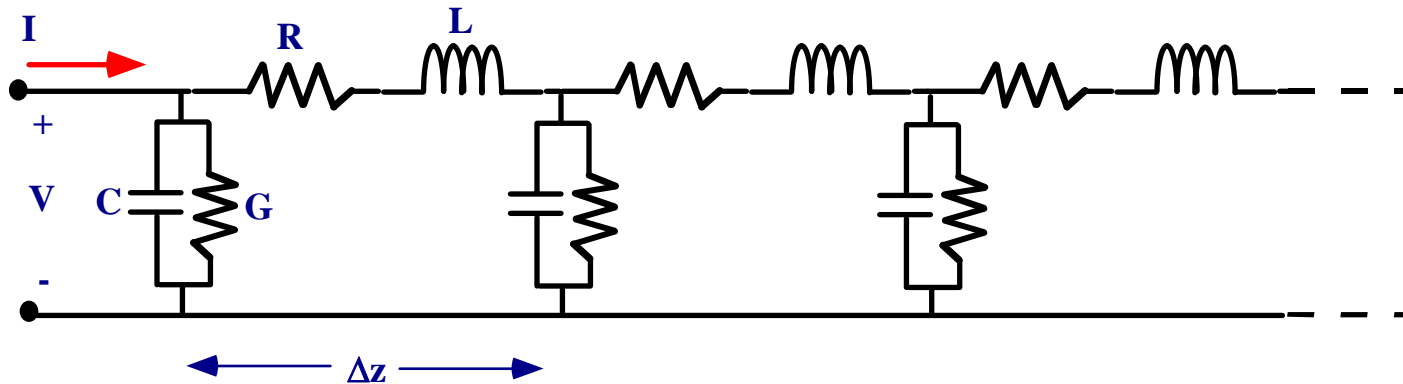


## Telegraphers Equation: Frequency Domain

$$-\frac{\partial V}{\partial z} = (R + j\omega L)I = ZI$$

$$-\frac{\partial I}{\partial z} = (G + j\omega C)V = YV$$



# Lossy Transmission Line

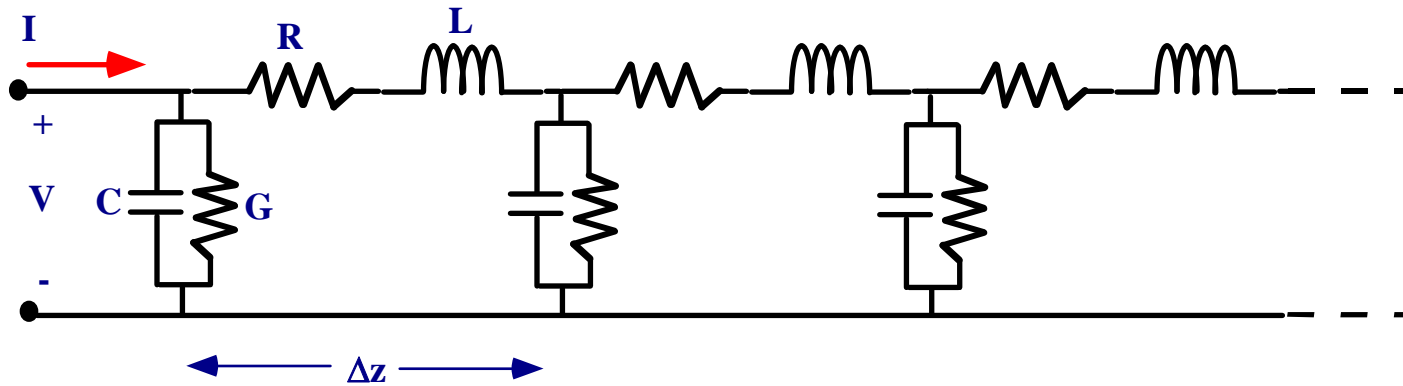


## Telegraphers Equation: Frequency Domain

$$-\frac{\partial^2 V}{\partial z^2} = (R + j\omega L)(G + j\omega C)V = ZYV = \gamma^2 V$$

$$-\frac{\partial^2 I}{\partial z^2} = (G + j\omega C)(R + j\omega L)I = YZI = \gamma^2 I$$

# Lossy Transmission Line

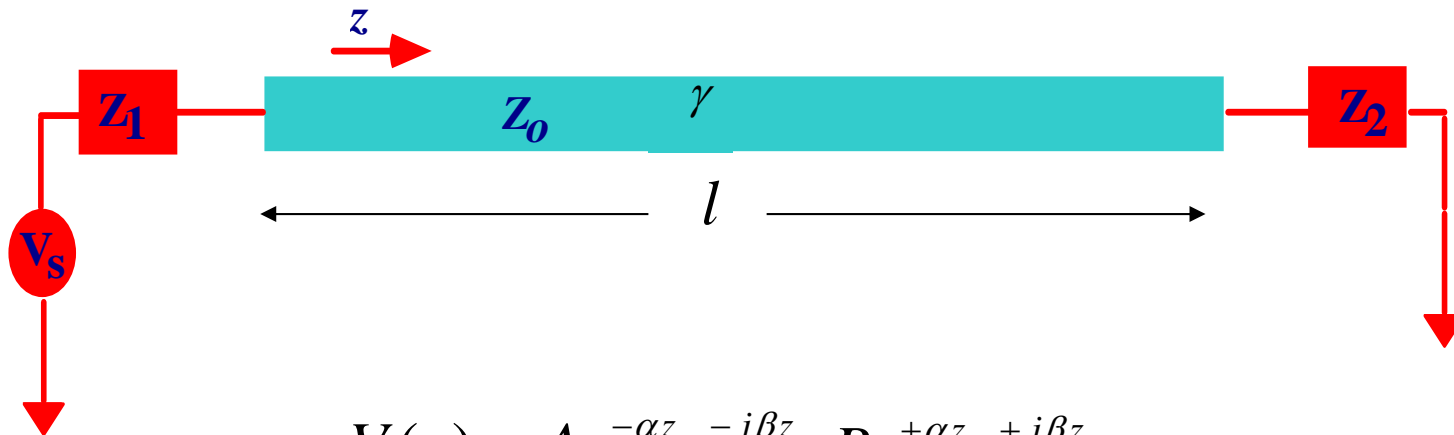

$$V(z) = Ae^{-\alpha z} e^{-j\beta z} + Be^{+\alpha z} e^{+j\beta z}$$

$$I(z) = \frac{1}{Z_0} \left[ Ae^{-\alpha z} e^{-j\beta z} - Be^{+\alpha z} e^{+j\beta z} \right]$$


$$Z_0 = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$


# Lossy Transmission Line



**forward wave**

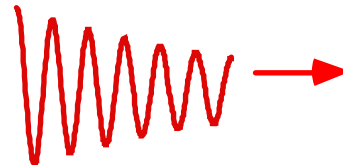


**backward wave**

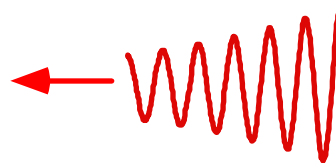


# Effects of Losses

- Signal attenuation

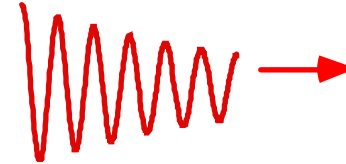


- Dispersion  $\gamma = \alpha(\omega) + j\beta(\omega) = \sqrt{(R + j\omega L)(G + j\omega C)}$

- Rise time degradation

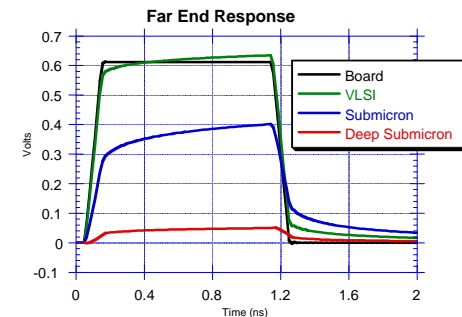

# Special Case – Low Loss

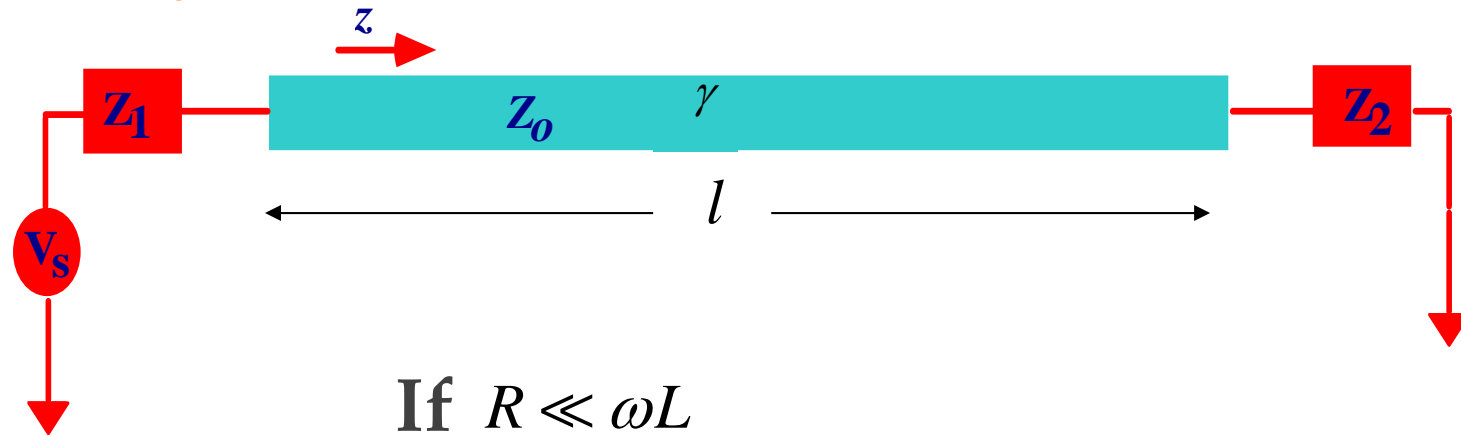

If  $R \ll \omega L$

and  $G \ll \omega C$

$$Z_o = \sqrt{\frac{j\omega L \left(1 + \frac{R}{j\omega L}\right)}{j\omega C \left(1 + \frac{G}{j\omega C}\right)}} \approx \sqrt{\frac{L}{C}}$$

$$\gamma = \alpha + j\beta$$

$$\alpha \approx \frac{1}{2} \left( R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right)$$

$$\beta \approx \omega \sqrt{LC} \quad v_p = \frac{\omega}{\beta} \approx \frac{1}{\sqrt{LC}}$$