

# ECE 451


# Advanced Microwave Measurements

## S Parameters


Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jschutt@emlab.uiuc.edu

# Transfer Function Representation

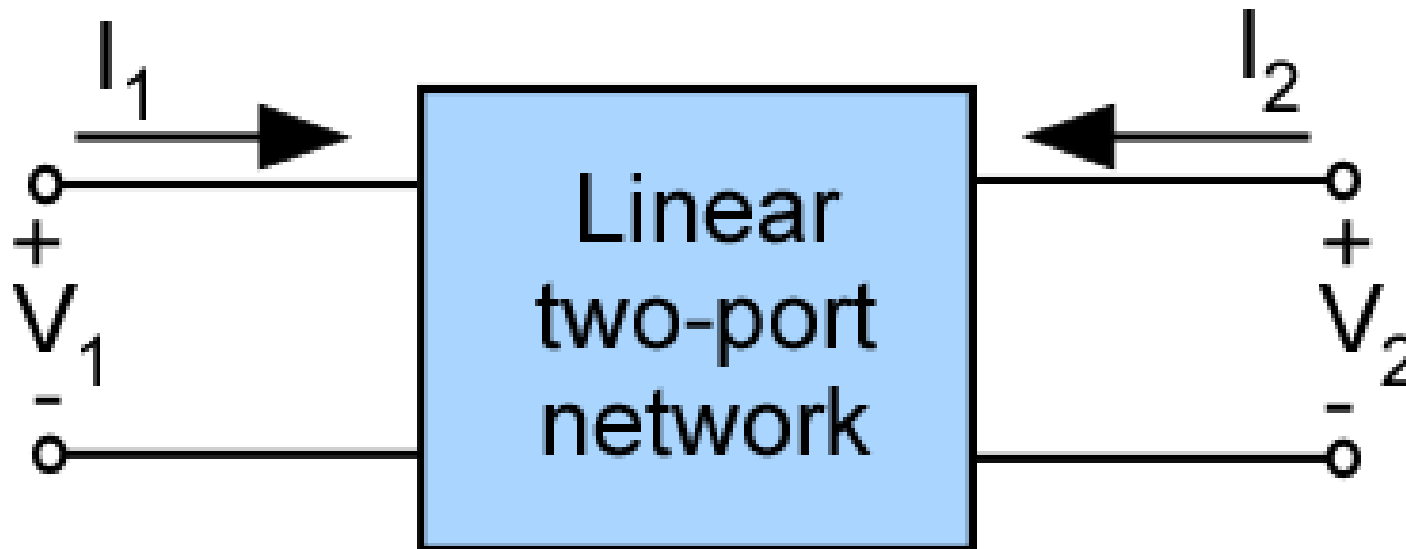

Use a two-terminal representation of system for input and output


# Y-parameter Representation

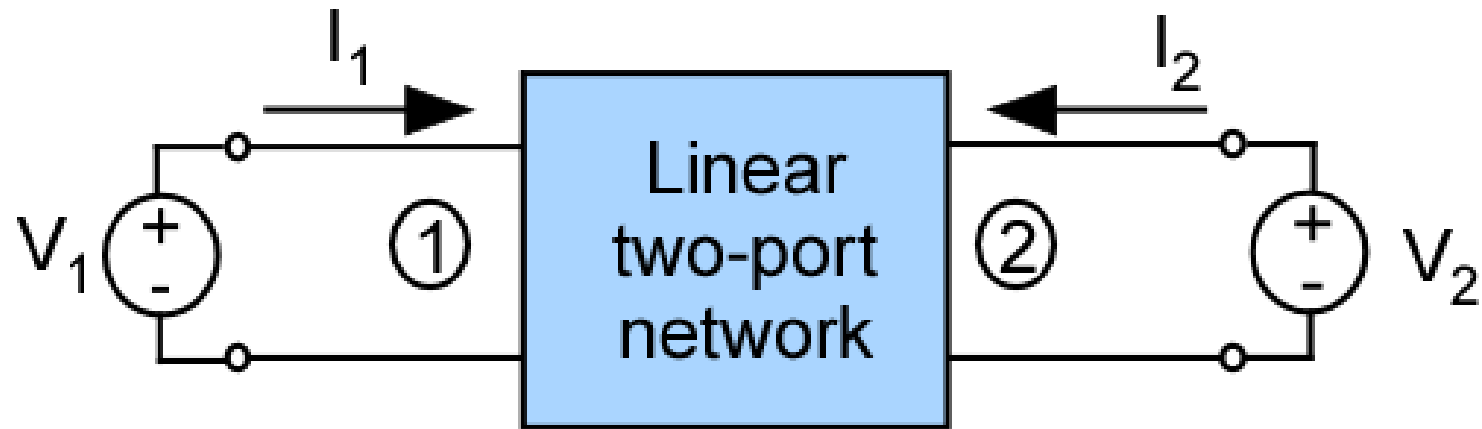

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$


# Y Parameter Calculations

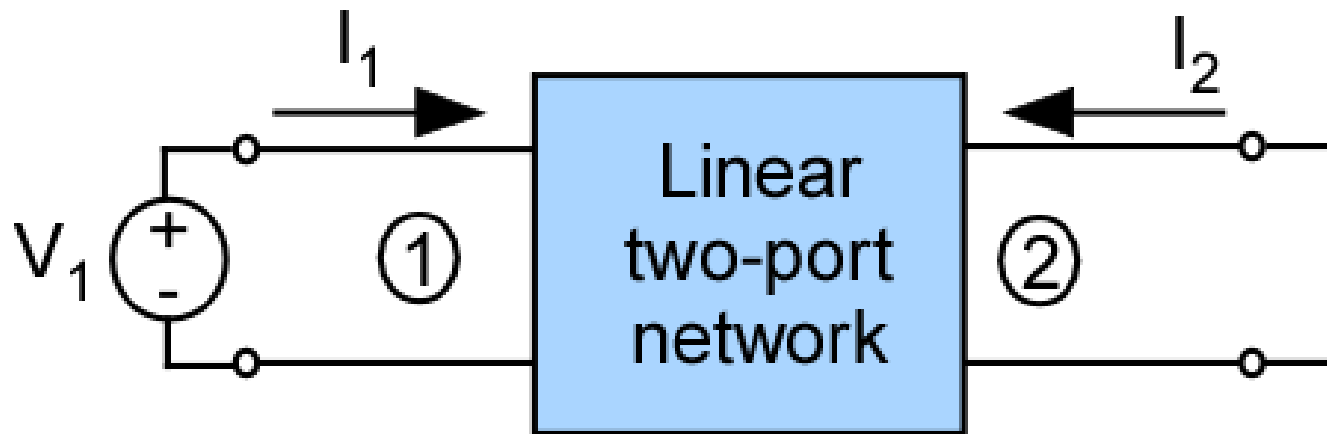

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

To make  $V_2=0$ , place a short at port 2


# Z Parameters

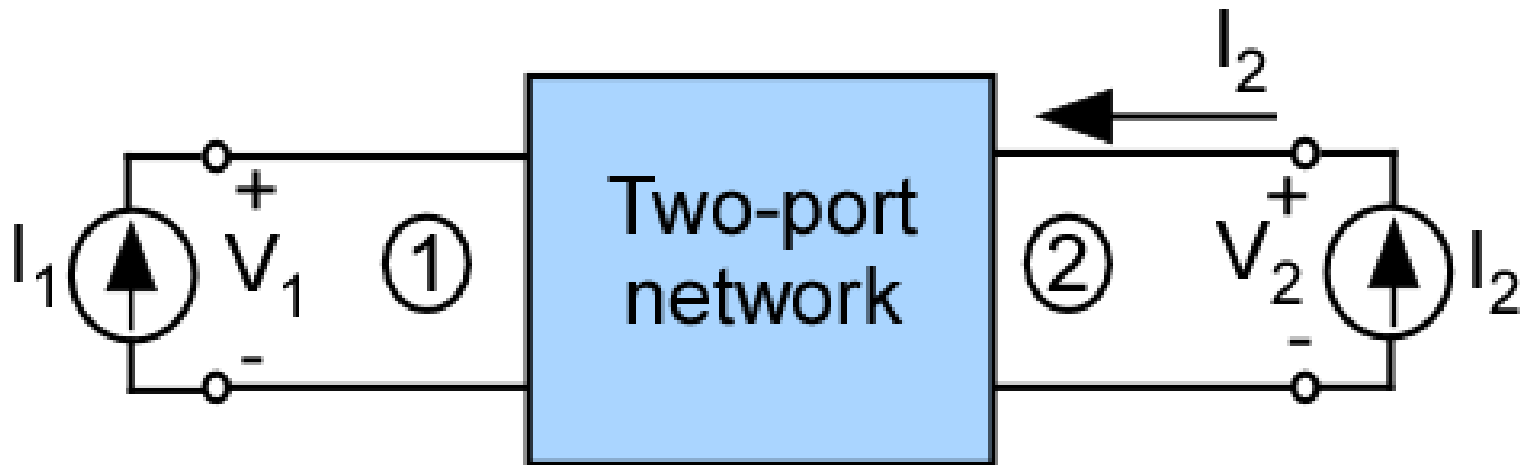

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$


# Z-parameter Calculations

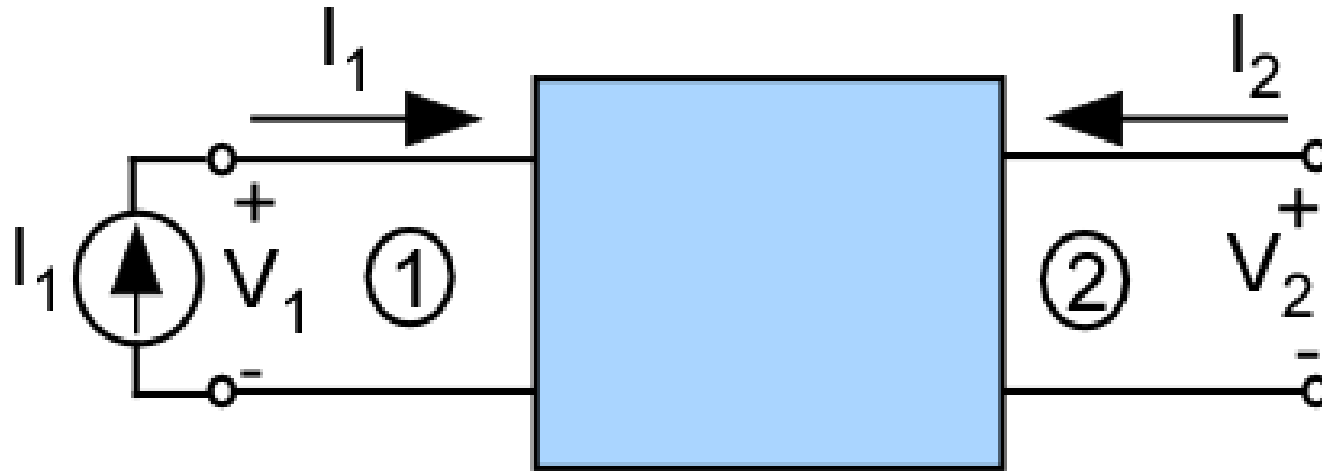

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

To make  $I_2=0$ , place an open at port 2


# H Parameters

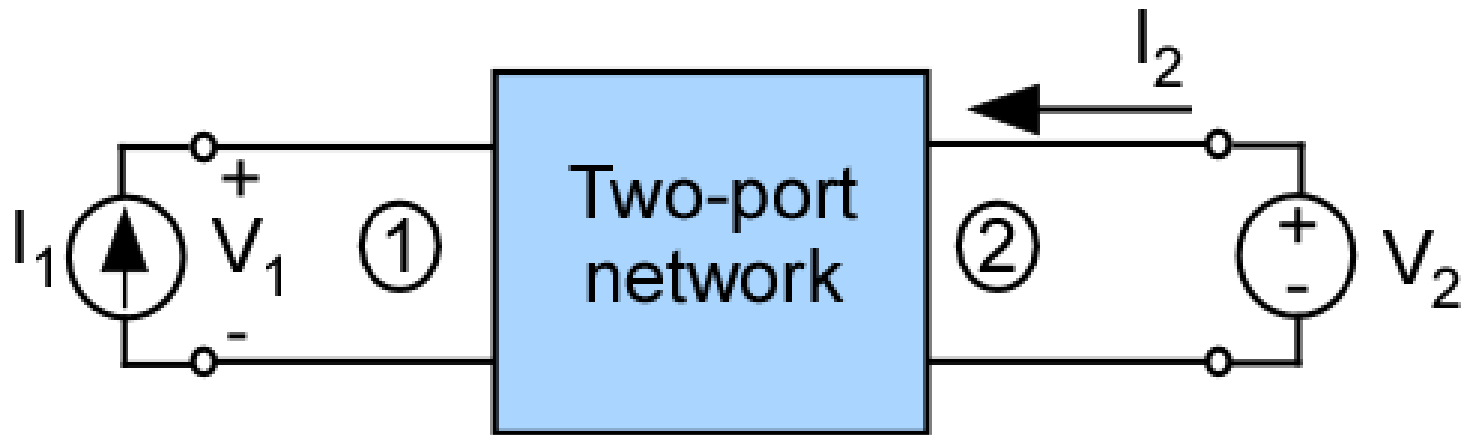

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

# H Parameter Calculations

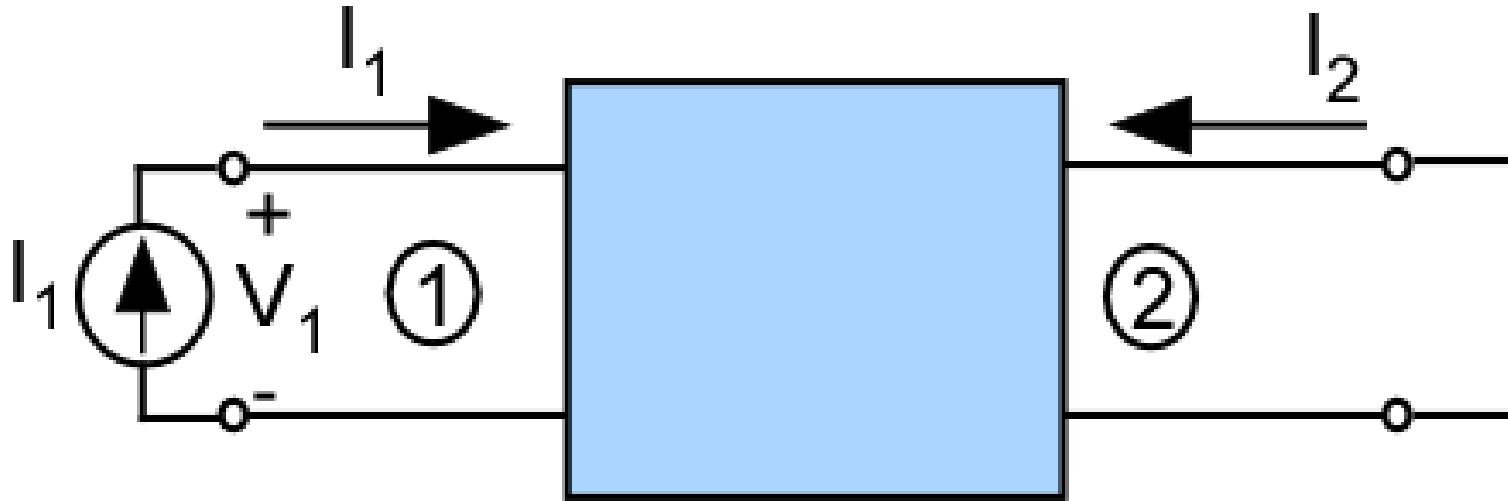


$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

To make  $V_2=0$ , place a short at port 2




# G Parameters

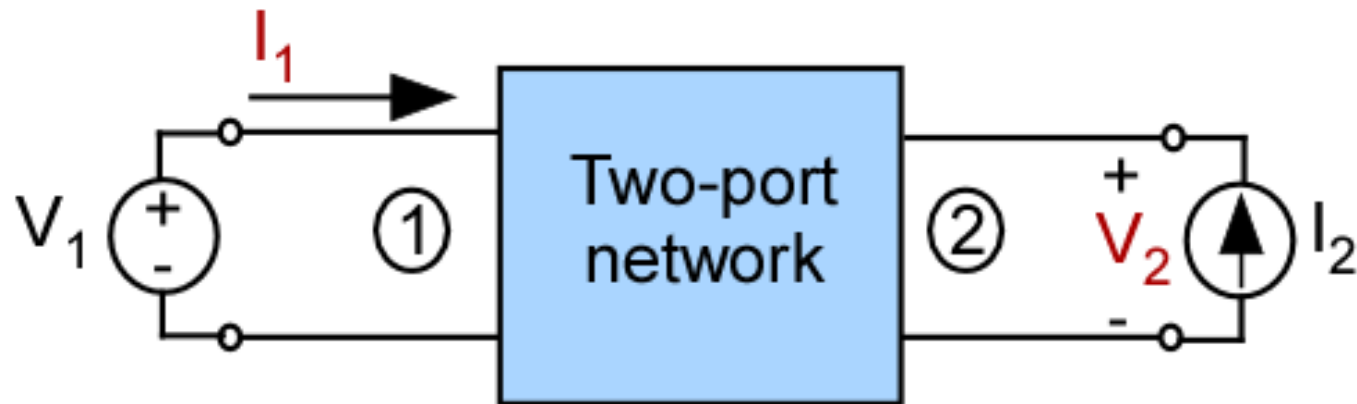

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$


# G-Parameter Calculations

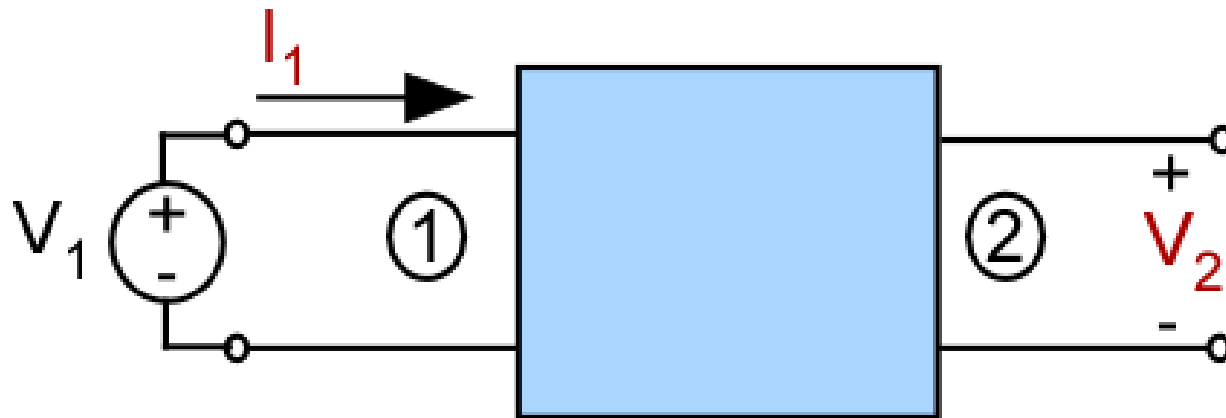

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} \qquad g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

To make  $I_2=0$ , place an open at port 2

# Y-Parameters of TL

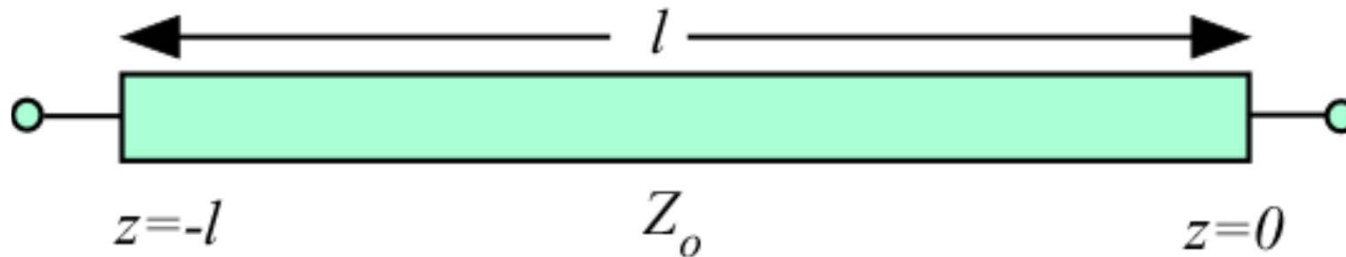


Find the Y-parameters of a lossless transmission line with propagation constant  $\beta$  and characteristic impedance  $Z_o$  (admittance  $Y_o$ )

$$V(z) = V_+ e^{-j\beta z} + V_- e^{+j\beta z}$$

$$I(z) = Y_o (V_+ e^{-j\beta z} - V_- e^{+j\beta z})$$

Let port 1 be at  $z=-l$  and port 2 at  $z=0$

# Y-Parameters of TL

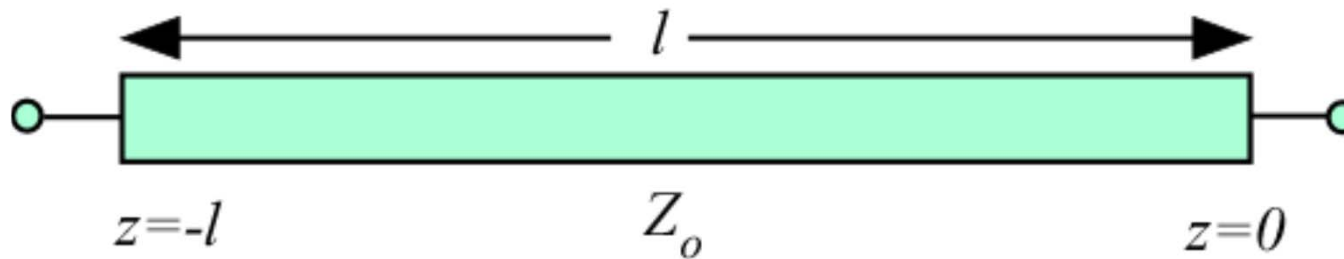

at port 1

$$V_1 = V_+ e^{+j\beta l} + V_- e^{-j\beta l}$$

$$I_1 = Y_o (V_+ e^{+j\beta l} - V_- e^{-j\beta l})$$


at port 2 ( $z = 0$ )

$$V_2 = V_+ + V_-$$

$$I_2 = -Y_o (V_+ - V_-)$$

$$V_+ = \frac{V_2 - Z_o I_2}{2} \quad \text{and} \quad V_- = \frac{V_2 + Z_o I_2}{2}$$

# Y-Parameters of TL

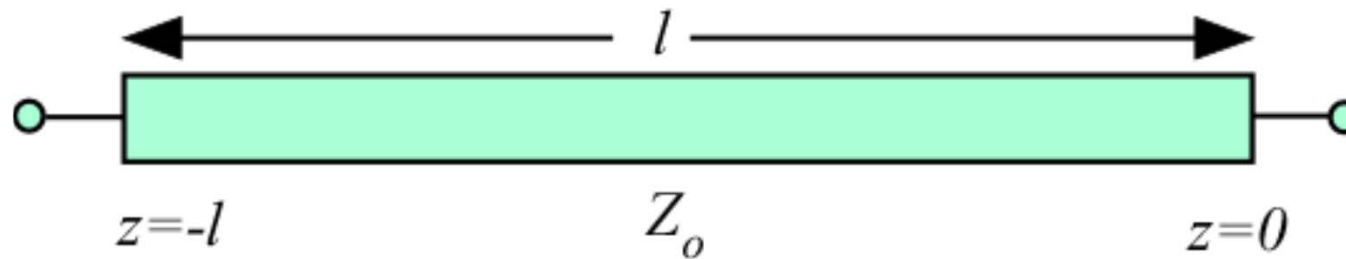

So that

$$V_1 = \left( \frac{V_2 - Z_o I_2}{2} \right) e^{+j\beta l} + \left( \frac{V_2 + Z_o I_2}{2} \right) e^{-j\beta l}$$


$$I_1 = Y_o \left( \frac{V_2 - Z_o I_2}{2} \right) e^{+j\beta l} - Y_o \left( \frac{V_2 + Z_o I_2}{2} \right) e^{-j\beta l}$$

and

$$V_1 = V_2 \cos \beta l - Z_o I_2 j \sin \beta l$$

$$I_1 = +Y_o V_2 j \sin \beta l - I_2 \cos \beta l$$

# Y-Parameters of TL

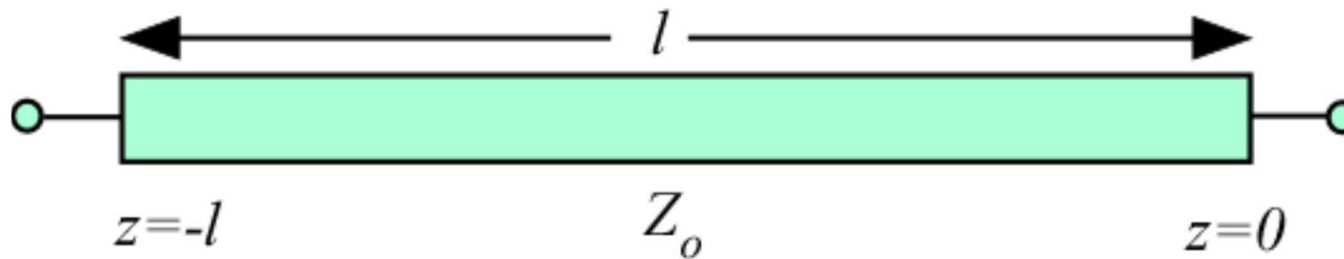

Using definitions for  $Y_{11}$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{-I_2 \cos \beta l}{-jZ_o I_2 \sin \beta l} = \frac{-jY_o \cos \beta l}{\sin \beta l}$$

and

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-I_2}{-jZ_o I_2 \sin \beta l} = \frac{+jY_o}{\sin \beta l}$$

$$Y_{22} = Y_{11} \text{ by symmetry}$$

$$Y_{12} = Y_{21} \text{ by reciprocity}$$

# TWO-PORT NETWORK REPRESENTATION



## Z Parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$


## Y Parameters

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

- **At microwave frequencies, it is more difficult to measure total voltages and currents.**
- **Short and open circuits are difficult to achieve at high frequencies.**
- **Most active devices are not short- or open-circuit stable.**

# Wave Approach

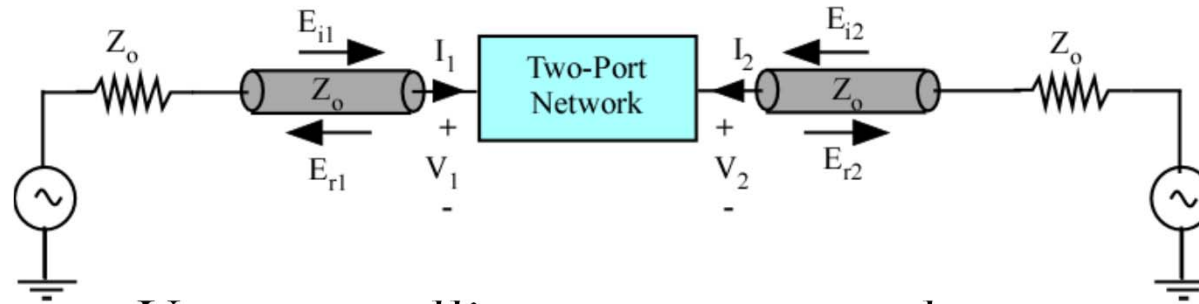

*Use a travelling wave approach*


$$V_1 = E_{i1} + E_{r1} \quad V_2 = E_{i2} + E_{r2}$$

$$I_1 = \frac{E_{i1} - E_{r1}}{Z_o} \quad I_2 = \frac{E_{i2} - E_{r2}}{Z_o}$$

- **Total voltage and current are made up of sums of forward and backward traveling waves.**
- **Traveling waves can be determined from standing-wave ratio.**



# Wave Approach

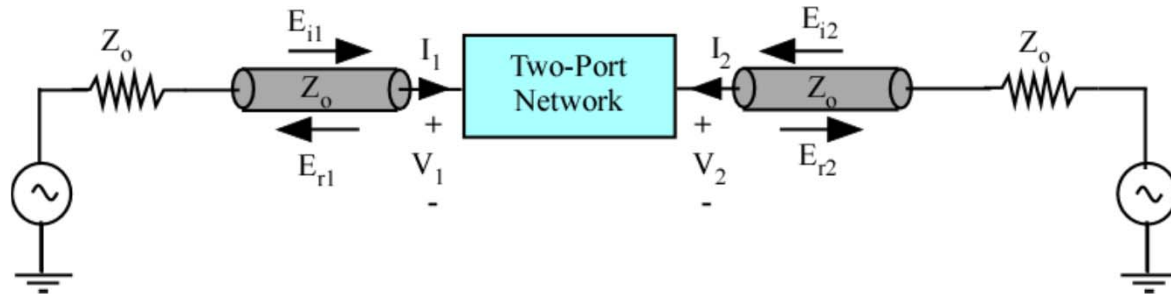

$$a_1 = \frac{E_{i1}}{\sqrt{Z_o}}$$

$$a_2 = \frac{E_{i2}}{\sqrt{Z_o}}$$

$$b_1 = \frac{E_{r1}}{\sqrt{Z_o}}$$


$$b_2 = \frac{E_{r2}}{\sqrt{Z_o}}$$

**$Z_o$  is the reference impedance of the system**

$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

# Wave Approach

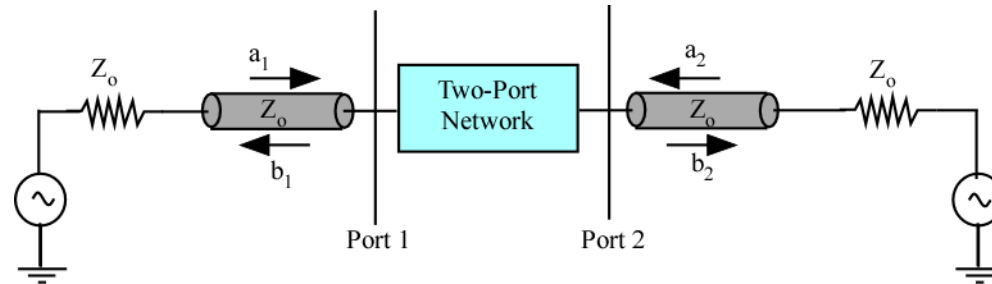

$$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0}$$

$$S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1=0}$$


$$S_{22} = \frac{b_2}{a_2} \Big|_{a_1=0}$$

**To make  $a_i = 0$**

- 1) Provide no excitation at port  $i$
- 2) Match port  $i$  to the characteristic impedance of the reference lines.

**CAUTION :  $a_i$  and  $b_i$  are the traveling waves in the reference lines.**


# S-Parameters of Resistor

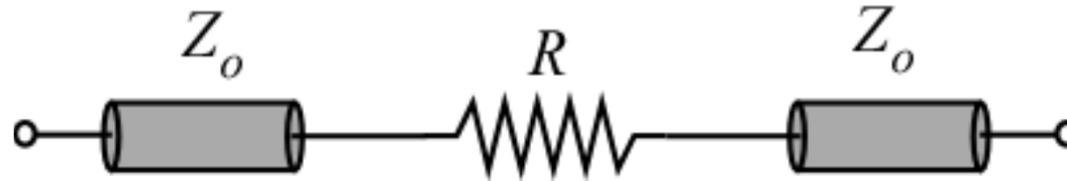

## Determine S-Parameter of 2-port resistance

- Insert  $R$  between two reference TL
- Provide excitation at port 1 for  $S_{11}$  and  $S_{21}$
- Provide excitation at port 2 for  $S_{12}$  and  $S_{22}$
- Can use symmetry and reciprocity


# S-Parameters of Resistor

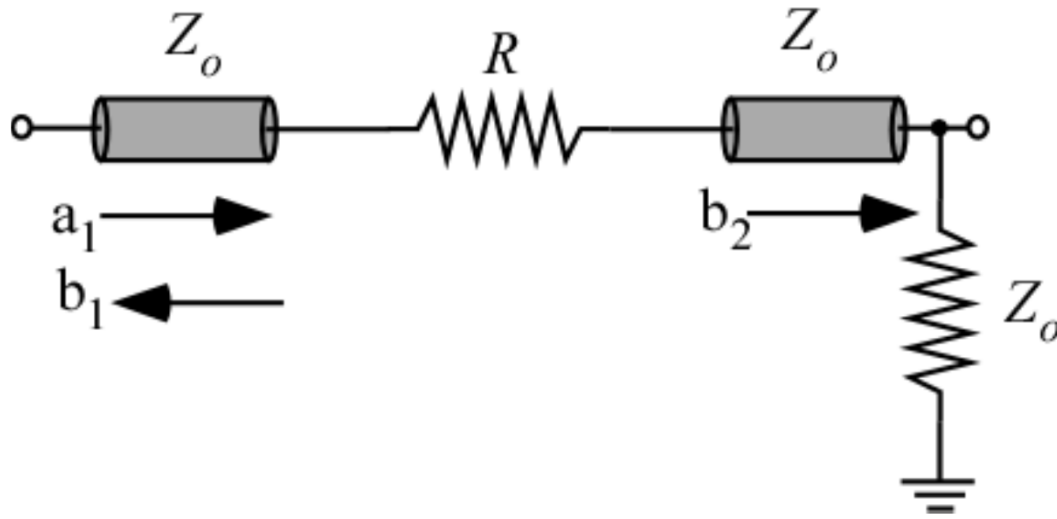

$$S_{11} = \frac{b_1}{a_1} = \Gamma = \frac{(R + Z_o) - Z_o}{(R + Z_o) + Z_o} = \frac{R}{R + 2Z_o}$$

$$S_{11} = \frac{R}{R + 2Z_o} \quad \text{and by symmetry,} \quad S_{22} = \frac{R}{R + 2Z_o}$$

# Calculating $S_{21}$ of Resistor

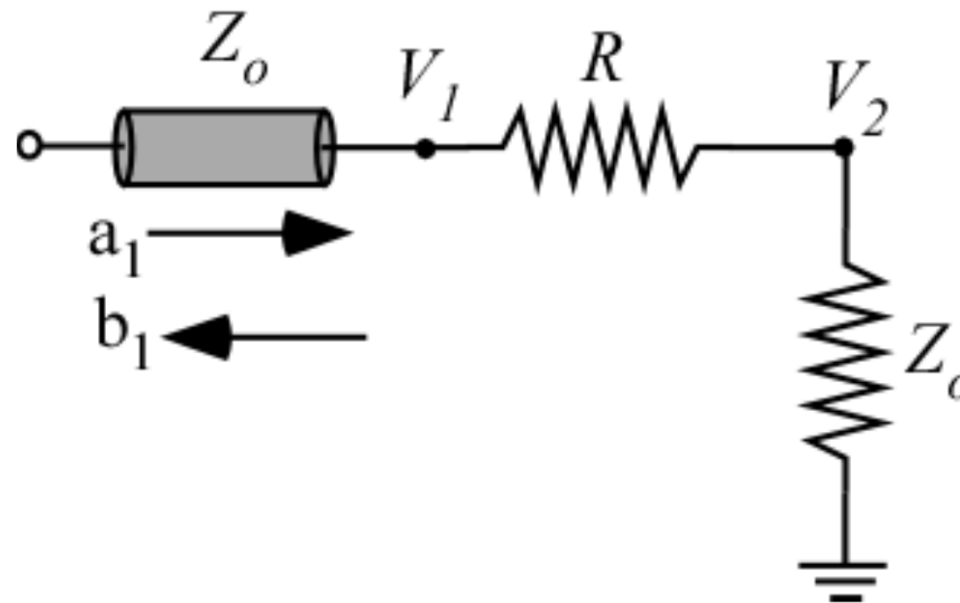

Since  $a_2=0$ , the total voltage in port 2 is:  $V_2 = b_2\sqrt{Z_o}$


$$V_2 = \frac{V_1 Z_o}{R_1 + Z_o} = \frac{\sqrt{Z_o} (a_1 + b_1) Z_o}{R_1 + Z_o} = \frac{\sqrt{Z_o} (a_1 + S_{11} a_1) Z_o}{R_1 + Z_o}$$

# S-Parameters of Resistor

$$V_2 = \frac{Z_o \sqrt{Z_o} (1 + S_{11}) a_1}{R_1 + Z_o} = \frac{2Z_o a_1 \sqrt{Z_o}}{R_1 + 2Z_o}$$

$$S_{21} = \frac{b_2}{a_1} = \frac{V_2}{\sqrt{Z_o}} \frac{1}{a_1} = \frac{2Z_o}{R + 2Z_o}$$
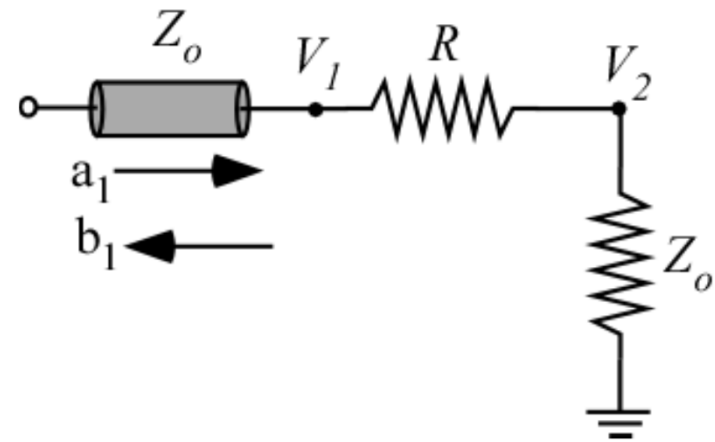
$$S_{21} = \frac{2Z_o}{R + 2Z_o} \quad \text{and by reciprocity,} \quad S_{12} = \frac{2Z_o}{R + 2Z_o}$$



S parameters of  
resistor R

$$S = \begin{bmatrix} \frac{R}{R + 2Z_o} & \frac{2Z_o}{R + 2Z_o} \\ \frac{2Z_o}{R + 2Z_o} & \frac{R}{R + 2Z_o} \end{bmatrix}$$

# N-Port S Parameters

$$\begin{bmatrix} b_1 \\ b_2 \\ \cdot \\ b_n \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdot & \cdot \\ S_{21} & S_{22} & \cdot & \cdot \\ \cdot & \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot & S_{nn} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ \cdot \\ a_n \end{bmatrix}$$

$$\mathbf{b} = \mathbf{S}\mathbf{a}$$

If  $b_i = 0$ , then no reflected wave on port  $i \rightarrow$  port is matched

$$a_i = \frac{V_i^+}{\sqrt{Z_{oi}}}$$

$V_i^+$  : incident voltage wave in port  $i$

$V_i^-$  : reflected voltage wave in port  $i$

$$b_i = \frac{V_i^-}{\sqrt{Z_{oi}}}$$

$Z_{oi}$  : impedance in port  $i$

# N-Port S Parameters

$$\mathbf{v} = \sqrt{Z_o}(\mathbf{a} + \mathbf{b}) \quad (1) \quad \mathbf{i} = \frac{1}{\sqrt{Z_o}}(\mathbf{a} - \mathbf{b}) \quad (2) \quad \mathbf{v} = \mathbf{Z}\mathbf{i} \quad (3)$$

Substitute (1) and (2) into (3)

$$\sqrt{Z_o}(\mathbf{a} + \mathbf{b}) = \mathbf{Z} \frac{1}{\sqrt{Z_o}}(\mathbf{a} - \mathbf{b})$$

Defining  $\mathbf{S}$  such that  $\mathbf{b} = \mathbf{S}\mathbf{a}$  and substituting for  $\mathbf{b}$

$$Z_o(\mathbf{U} + \mathbf{S})\mathbf{a} = Z_o(\mathbf{U} - \mathbf{S})\mathbf{a}$$

$\mathbf{U}$  : unit matrix

$\mathbf{S} \rightarrow \mathbf{Z}$

$$\mathbf{Z} = Z_o(\mathbf{U} + \mathbf{S})(\mathbf{U} - \mathbf{S})^{-1}$$

$\mathbf{Z} \rightarrow \mathbf{S}$

$$\mathbf{S} = (\mathbf{Z} + Z_o\mathbf{U})^{-1}(\mathbf{Z} - Z_o\mathbf{U})$$



# N-Port S Parameters

If the port reference impedances are different, we define  $\mathbf{k}$  as

$$\mathbf{k} = \begin{bmatrix} \sqrt{Z_{o1}} & & & \\ & \sqrt{Z_{o2}} & & \\ & & \ddots & \\ & & & \sqrt{Z_{on}} \end{bmatrix}$$

$$\mathbf{v} = \mathbf{k}(\mathbf{a} + \mathbf{b}) \quad \text{and} \quad \mathbf{i} = \mathbf{k}^{-1}(\mathbf{a} - \mathbf{b}) \quad \text{and} \quad \mathbf{k}(\mathbf{a} + \mathbf{b}) = \mathbf{Z}\mathbf{k}^{-1}(\mathbf{a} - \mathbf{b})$$

$\mathbf{Z} \rightarrow \mathbf{S}$

$$\mathbf{S} = (\mathbf{Z}\mathbf{k}^{-1} + \mathbf{k})(\mathbf{Z}\mathbf{k}^{-1} - \mathbf{k})$$

$\mathbf{S} \rightarrow \mathbf{Z}$

$$\mathbf{Z} = \mathbf{k}(\mathbf{U} + \mathbf{S})(\mathbf{U} - \mathbf{S})^{-1}\mathbf{k}$$

# Normalization

Assume original S parameters as  $S_1$  with system  $k_1$ . Then the representation  $S_2$  on system  $k_2$  is given by

## Transformation Equation

$$S_2 = \left[ \mathbf{k}_1(\mathbf{U} + S_1)(\mathbf{U} - S_1)^{-1} \mathbf{k}_1 \mathbf{k}_2 + \mathbf{k}_2 \right]^{-1} \left[ \mathbf{k}_1(\mathbf{U} + S_1)(\mathbf{U} - S_1)^{-1} \mathbf{k}_1 \mathbf{k}_2 - \mathbf{k}_2 \right]$$

If  $Z$  is symmetric,  $S$  is also symmetric

# Dissipated Power

$$P_d = \frac{1}{2} \mathbf{a}^T (\mathbf{U} - \mathbf{S}^T \mathbf{S}^*) \mathbf{a}^*$$

The dissipation matrix  $\mathbf{D}$  is given by:

$$\mathbf{D} = \mathbf{U} - \mathbf{S}^T \mathbf{S}^*$$

Passivity insures that the system will always be stable provided that it is connected to another passive network

For passivity

- (1) the determinant of  $\mathbf{D}$  must be  $\geq 0$
- (2) the determinant of the principal minors must be  $\geq 0$

# Dissipated Power

When the dissipation matrix is 0, we have a lossless network →

$$\mathbf{S}^T \mathbf{S}^* = \mathbf{U}$$

The  $\mathbf{S}$  matrix is unitary.

For a lossless two-port:

$$|S_{11}|^2 + |S_{21}|^2 = 1$$

$$|S_{22}|^2 + |S_{12}|^2 = 1$$

If in addition the network is reciprocal, then

$$S_{12} = S_{21} \quad \text{and} \quad |S_{11}| = |S_{22}| = \sqrt{1 - |S_{12}|^2}$$