


ECE 451

Advanced Microwave Measurements

Transmission Lines - TDR

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jschutt@emlab.uiuc.edu

Determining V_+

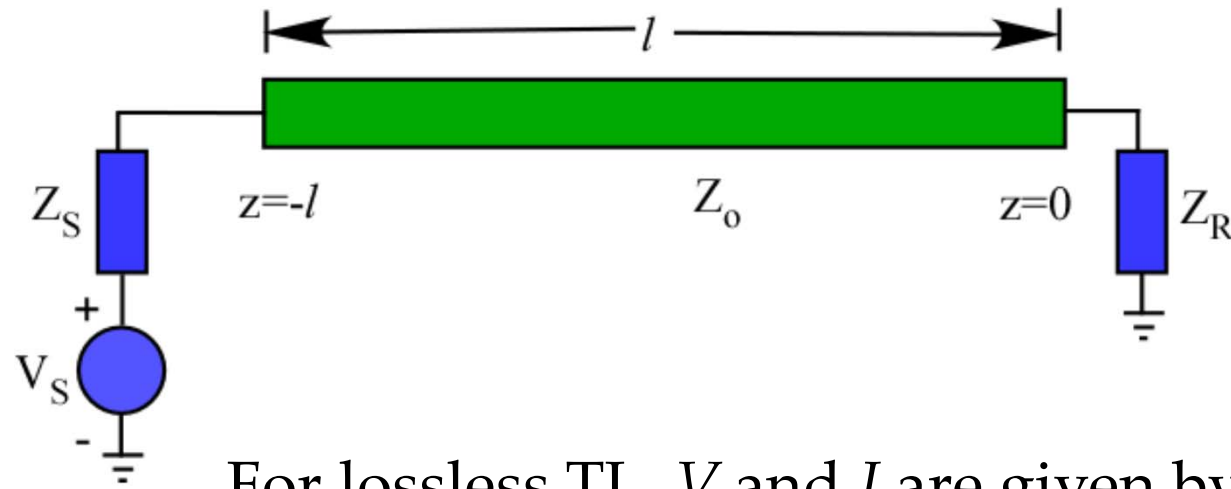

For lossless TL, V and I are given by

$$V(z) = V_+ e^{-j\beta z} \left[1 + \Gamma_R e^{+2j\beta z} \right]$$


reflection coefficient
at the load

$$\Gamma_R = \frac{Z_R - Z_0}{Z_R + Z_0}$$

$$I(z) = \frac{V_+ e^{-j\beta z}}{Z_0} \left[1 - \Gamma_R e^{+2j\beta z} \right]$$

$$\text{At } z = -l, \quad V_S = Z_S I(-l) + V(-l)$$

Determining V_+

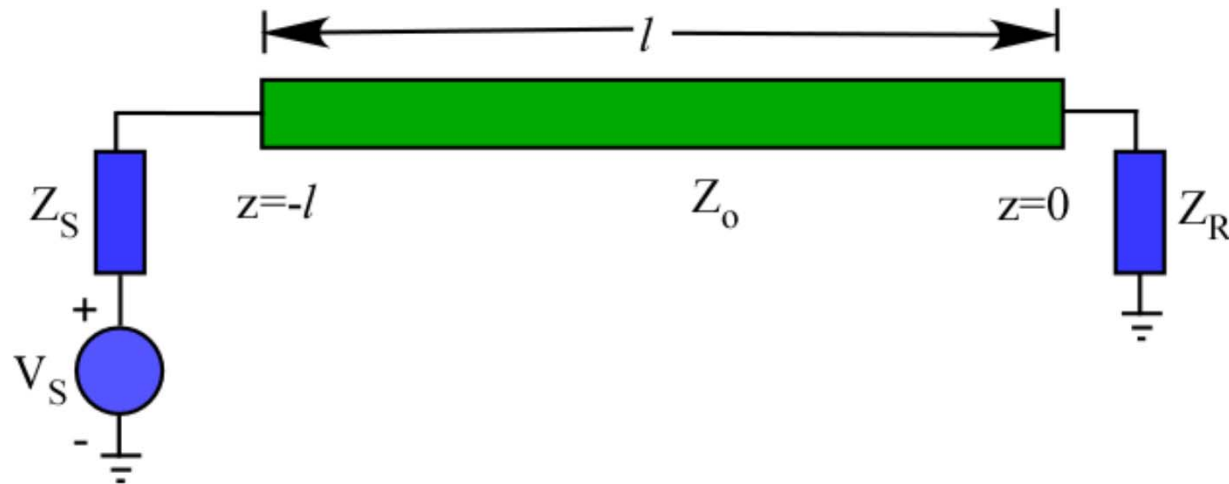

this leads to

$$V_S = V_+ e^{+j\beta l} (1 + \Gamma_R e^{-2j\beta l}) + \frac{Z_S}{Z_o} V_+ e^{+j\beta l} (1 - \Gamma_R e^{-2j\beta l})$$

or


$$V_S = V_+ \left(e^{+j\beta l} + \Gamma_R e^{-j\beta l} + \frac{Z_S}{Z_o} e^{+j\beta l} - \Gamma_R \frac{Z_S}{Z_o} e^{-j\beta l} \right)$$

$$V_S = V_+ \left(e^{+j\beta l} \left(1 + \frac{Z_S}{Z_o} \right) + \Gamma_R e^{-j\beta l} \left(1 - \frac{Z_S}{Z_o} \right) \right)$$

Determining V_+

Divide through by $\left(1 + \frac{Z_S}{Z_o}\right) = \frac{1}{T_S}$

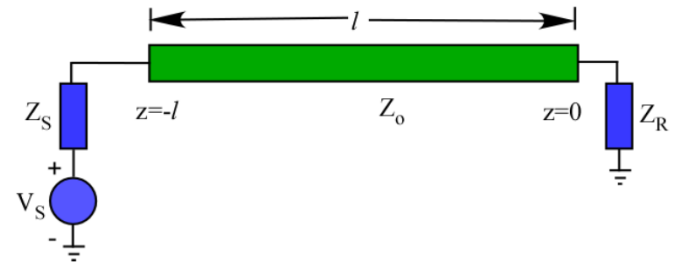
$$V_+ \left(e^{+j\beta l} - \Gamma_S \Gamma_R e^{-j\beta l} \right) = T_S V_S$$



with $T_S = \left(1 + \frac{Z_S}{Z_o}\right)^{-1} = \frac{Z_o}{Z_S + Z_o}$ and $\Gamma_S = \frac{Z_S - Z_o}{Z_S + Z_o}$

From which
$$V_+ = \frac{T_S V_S e^{-j\beta l}}{1 - \Gamma_S \Gamma_R e^{-2j\beta l}}$$


TL Example

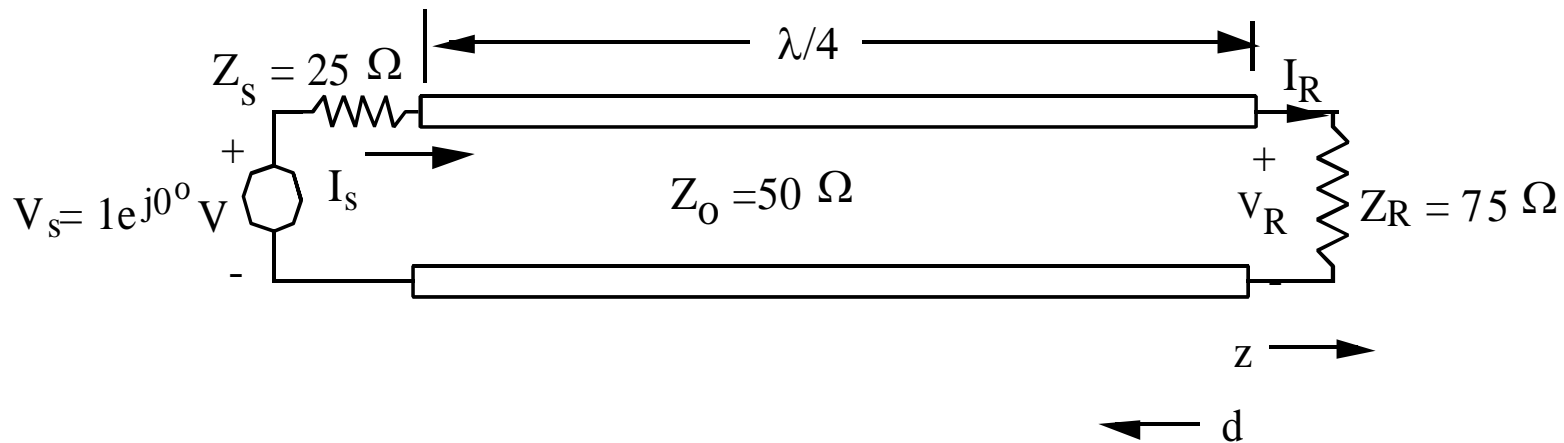

A signal generator having an internal resistance $Z_s = 25 \Omega$ and an open circuit phasor voltage $V_s = 1e^{j0}$ volt is connected to a 50- Ω lossless transmission line as shown in the above picture. The load impedance is $Z_R = 75 \Omega$ and the line length is $\lambda/4$.

Find the magnitude and phase of the load current I_R .

TL Example – Cont'

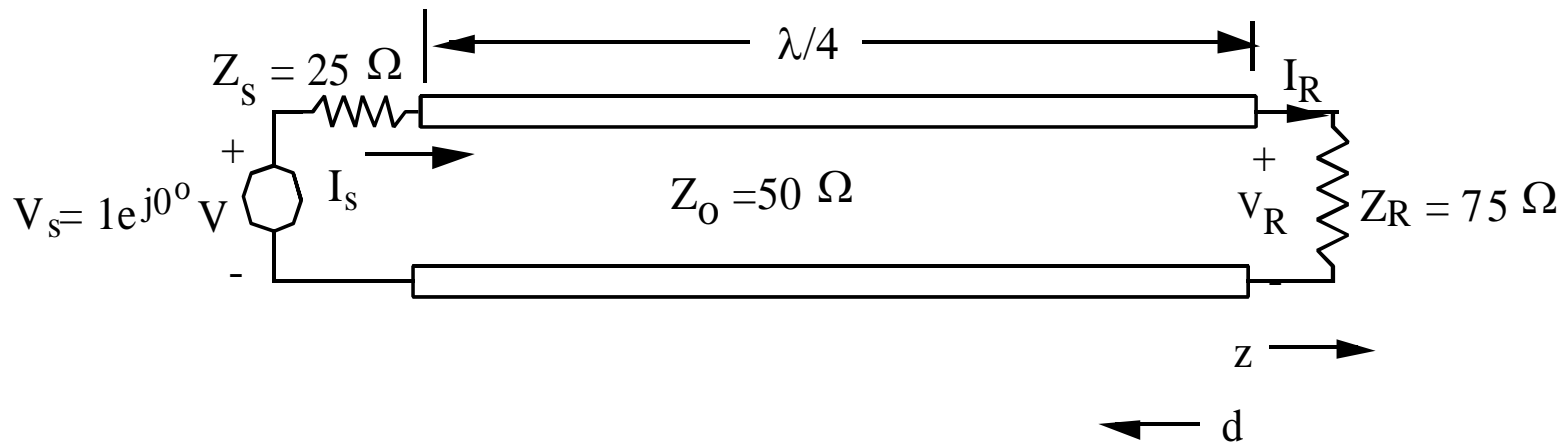

$$V_+ = \frac{T_s V_s e^{-j\beta l}}{1 - \Gamma_R \Gamma_s e^{-2j\beta l}}$$

$$T_s = \frac{Z_o}{Z_s + Z_o} = \frac{50}{50 + 25} = 2/3$$

$$\Gamma_s = \frac{Z_s - Z_o}{Z_s + Z_o} = \frac{25 - 50}{25 + 50} = -1/3$$

$$\Gamma_R = \frac{Z_R - Z_o}{Z_R + Z_o} = \frac{75 - 50}{75 + 50} = 1/5$$

TL Example – Cont'

$$\beta l = \frac{2\pi}{\lambda} \frac{\lambda}{4} = \frac{\pi}{2} \Rightarrow e^{-j\beta l} = -j$$

$$V_+ = \frac{(2/3)(1)(-j)}{1 - (-1/3)(1/5)(-1)} = \frac{-j2/3}{1 - 1/15} = -j5/7$$

$$V_+ = -j0.714285 \text{ V}$$

$$I_R = \frac{V_+}{Z_o} [1 - \Gamma_R] = -j \frac{0.714285}{50} [1 - 0.2] = -j \frac{0.714285 \times 0.8}{50}$$

$$I_R = -j0.0114285 \text{ A}$$

Geometric Series Expansion

Since $|\Gamma_S \Gamma_R e^{-2j\beta l}| \leq 1$

V_+ can be expanded in a geometric series form

$$V_+ = \frac{T_S V_S e^{-j\beta l}}{1 - \Gamma_S \Gamma_R e^{-2j\beta l}}$$

$$V_+ = T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^k e^{-2j\beta k l} e^{-j\beta l}$$

$$V(z) = T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^k e^{-j\beta l(2k+1)} e^{-j\beta z} + T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^{k+1} e^{-j\beta l(2k+1)} e^{+j\beta z}$$

$$\beta = \frac{\omega}{v}$$

$$V(z) = T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^k e^{-j\frac{\omega}{v}[z+(2k+1)l]} + T_S \sum_{k=0}^{\infty} V_S \Gamma_S^k \Gamma_R^{k+1} e^{-j\frac{\omega}{v}[z+(2k+1)l]}$$

TL Time-Domain Solution

$$v(z, t) = T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^k v_s \left(t - \frac{(2k+1)l + z}{v_o} \right) \\ + T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^{k+1} v_s \left(t - \frac{(2k+1)l - z}{v_o} \right)$$

at $z=0$

$$v(0, t) = T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^k v_s \left(t - \frac{(2k+1)l}{v_o} \right) \\ + T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^{k+1} v_s \left(t - \frac{(2k+1)l}{v_o} \right)$$

TL Time-Domain Solution

At $z=-l$

$$v(-l, t) = T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^k v_s \left(t - \frac{(2k+1)l + l}{v_o} \right)$$

$$+ T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^{k+1} v_s \left(t - \frac{(2k+1)l + l}{v_o} \right)$$

$$v(-l, t) = T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^k v_s \left(t - \frac{2kl}{v_o} \right)$$

$$+ T_S \sum_{k=0}^{\infty} \Gamma_S^k \Gamma_R^{k+1} v_s \left(t - \frac{2(k+1)l}{v_o} \right)$$

TL - Time-Domain Reflectometer

For TDR, $Z_S = Z_o \rightarrow \Gamma_S = 0$, and retain only $k=1$

$$v(-l, t) = T_S v_s(t) + T_S \Gamma_R v_s\left(t - \frac{2l}{v_o}\right)$$

