

# ECE 451

# Advanced Microwave Measurements

## TL Characterization

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
[jesa@illinois.edu](mailto:jesa@illinois.edu)

# Maxwell's Equations

$$\nabla \times E = -\frac{\partial B}{\partial t}$$

**Faraday's Law of Induction**

$$\nabla \times H = J + \frac{\partial D}{\partial t}$$

**Ampère's Law**

$$\nabla \cdot D = \rho$$

**Gauss' Law for electric field**

$$\nabla \cdot B = 0$$


**Gauss' Law for magnetic field**

**Constitutive Relations**

$$B = \mu H$$

$$D = \epsilon E$$

# Wave Propagation

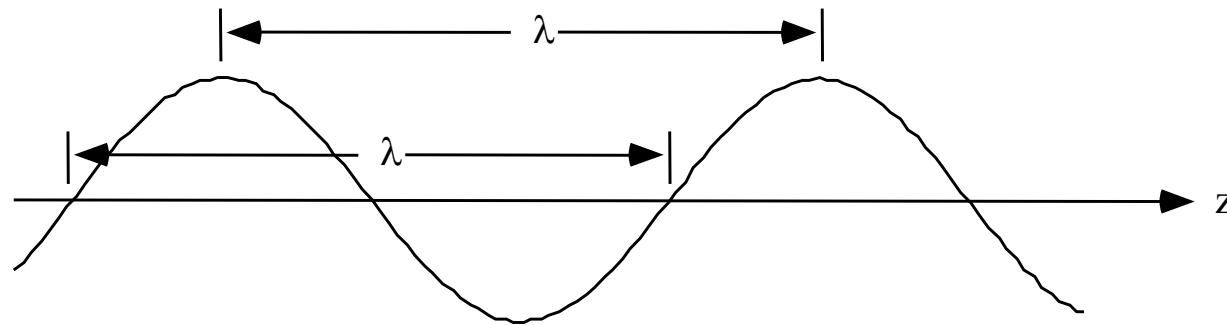

Wavelength :  $\lambda$

$$\lambda = \frac{\text{propagation velocity}}{\text{frequency}}$$

# Why Transmission Lines ?

**In Free Space**


**At 10 KHz :  $\lambda = 30 \text{ km}$**

**At 10 GHz :  $\lambda = 3 \text{ cm}$**

**Transmission line behavior is prevalent when the structural dimensions of the circuits are comparable to the wavelength.**

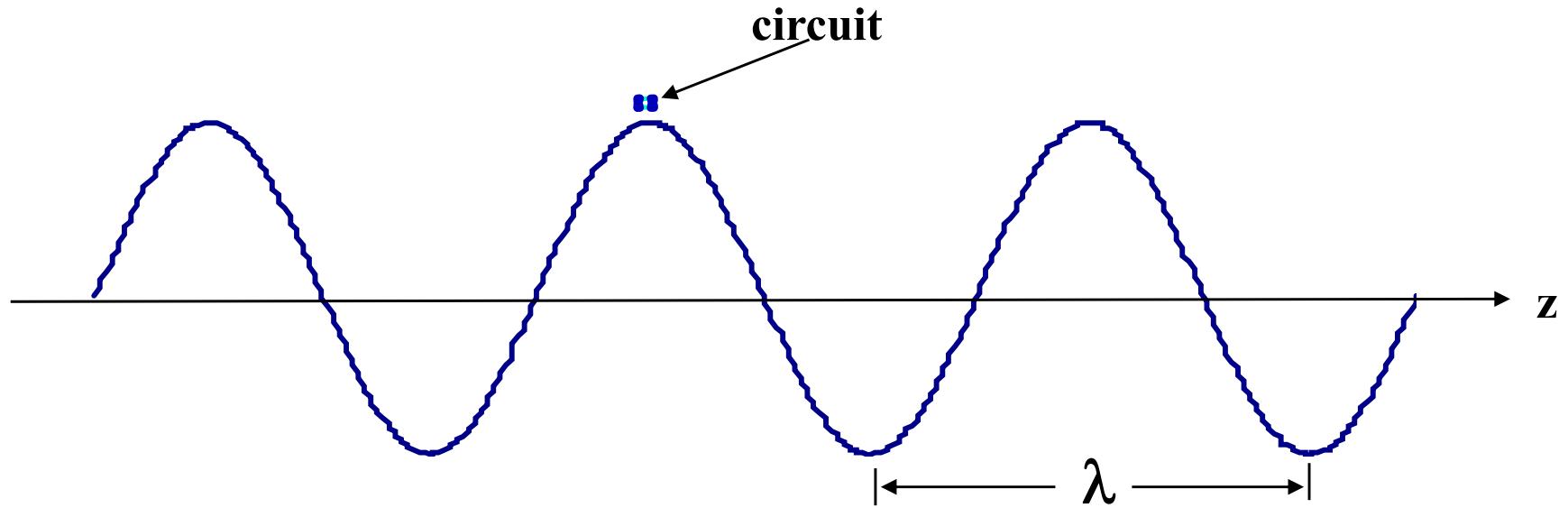
# Transmission Line Model

Let  $d$  be the largest dimension of a circuit



If  $d \ll \lambda$ , a lumped model for the circuit can be used

# Transmission Line Model

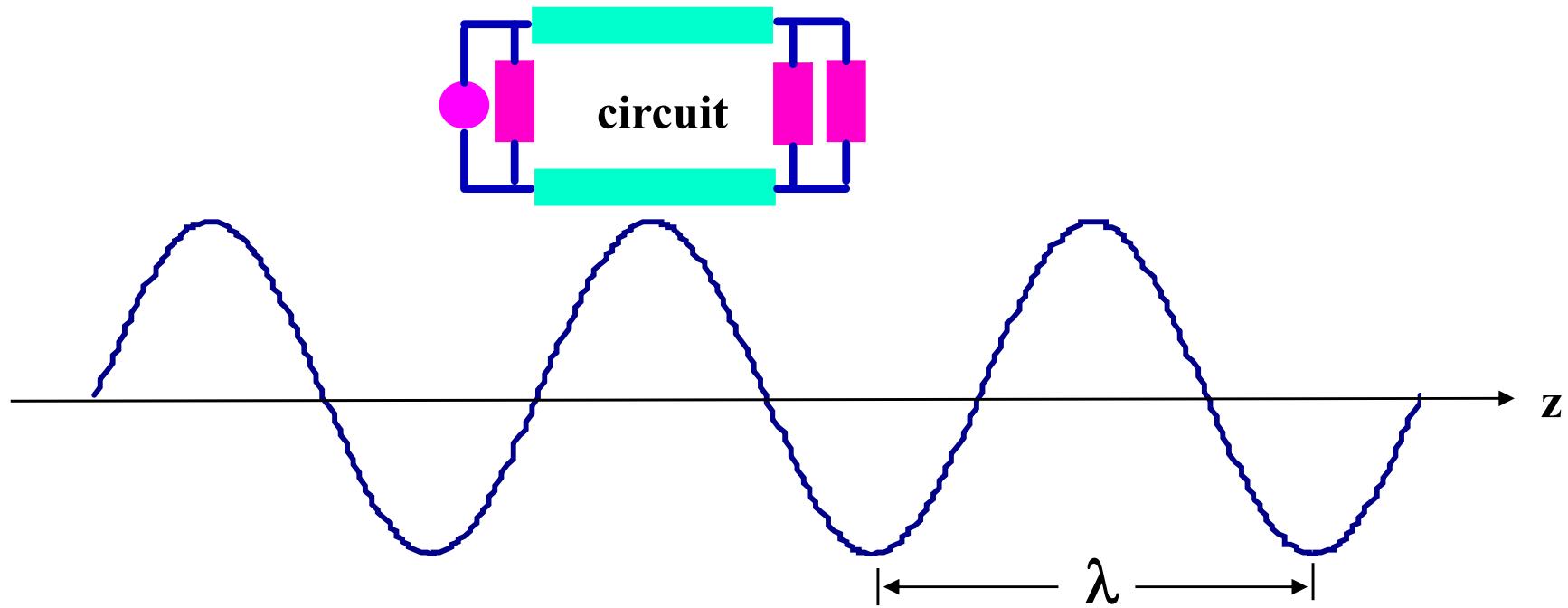


If  $d \approx \lambda$ , or  $d > \lambda$  then use transmission line model

# Modeling Interconnections

Low Frequency


Mid-range  
Frequency

High Frequency

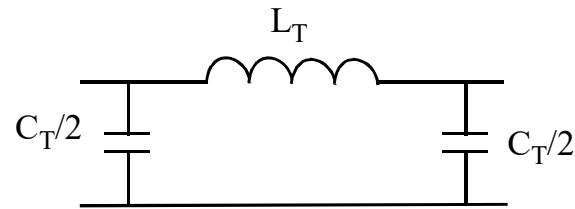

Short


or

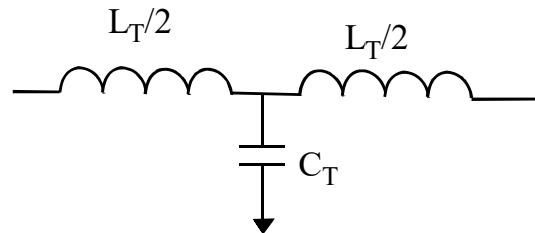

Lumped  
Reactive CKT


Transmission  
Line

# Dispersion & Velocities

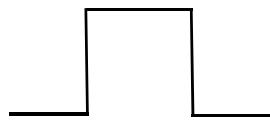


$$\beta = 2\pi f \sqrt{LC}$$

Ideal channel

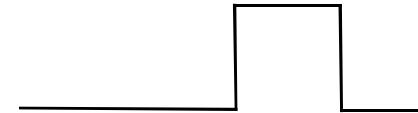

$$velocity = \frac{1}{\sqrt{LC}}$$

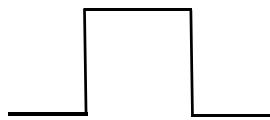

$$\beta = 2\pi fh(f)$$

Dispersive channel



$$velocity = g(f)$$

$$Phase\ velocity = \omega / \beta$$

$$Group\ velocity = \left( \frac{d\beta}{d\omega} \right)^{-1}$$

# Parallel-Plate Waveguide

$$\nabla^2 \mathbf{E} + \omega^2 \mu \epsilon \mathbf{E} = 0$$

**TE<sub>mn</sub> modes:**  $E_z = 0, H_z \neq 0, H_x \neq 0$


$$E_y = E_o \sin(\beta_x x) e^{-jkz} \quad \beta_x = \frac{m\pi}{a} \quad k = \beta_z = \sqrt{\omega^2 \mu \epsilon - \left(\frac{m\pi}{a}\right)^2}$$

Wave will propagate if  $f > f_c = \frac{m}{2a\sqrt{\mu \epsilon}}$

**TM<sub>mn</sub> modes:**  $H_z = 0, E_z \neq 0, E_x \neq 0$

$$H_y = H_o \cos(\beta_x x) e^{-jkz}$$

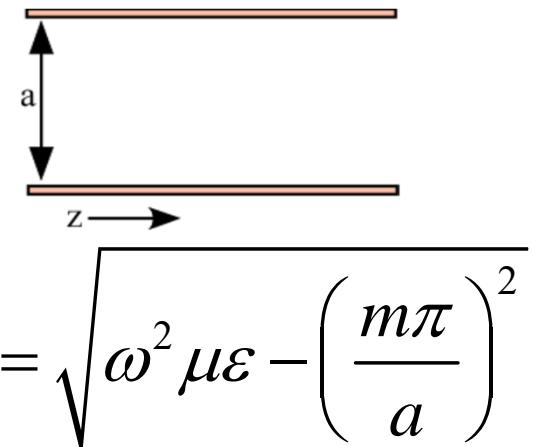Same dispersion relation as TE<sub>mn</sub> modes



# TEM Mode

Special case  $m=0 \rightarrow \text{TM}_0$  or TEM mode



$$E_z = 0, H_z = 0, E_x \neq 0, H_y \neq 0$$

$$k = \beta_z = \omega\sqrt{\mu\epsilon}$$


$$E_x = E_o e^{-jkz} = \sqrt{\frac{\mu}{\epsilon}} H_o e^{-jkz}$$

$$Z_o = \sqrt{\frac{\mu}{\epsilon}}$$

$$H_y = H_o e^{-jkz}$$

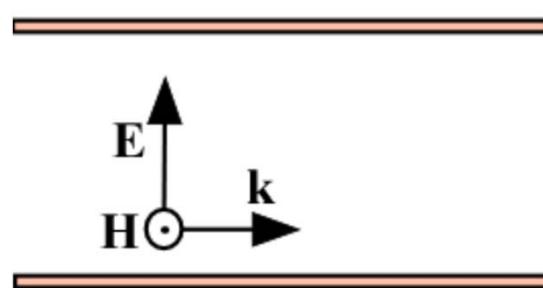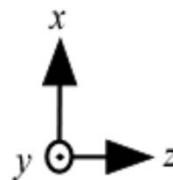

# Parallel-Plate in TEM

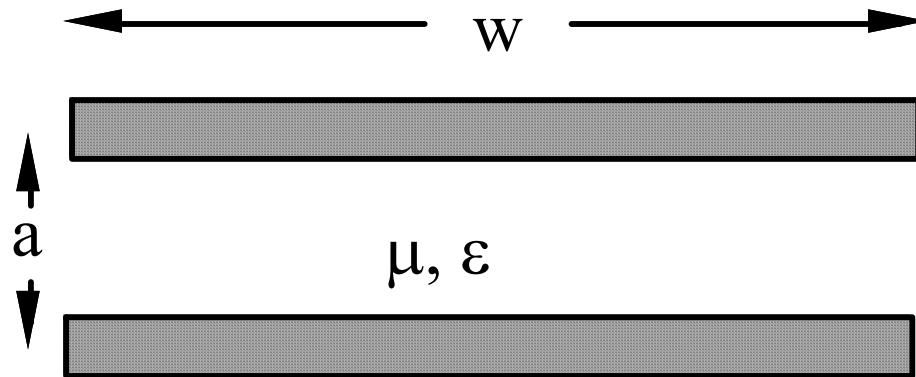

$$L = \frac{\mu a}{w}$$

$$C = \frac{\epsilon w}{a}$$

# Coaxial Cables

## Laplace's Equation for potential $\psi$

$$\nabla^2 \psi = 0 \Rightarrow \frac{1}{\rho} \frac{\partial}{\partial \rho} \left( \rho \frac{\partial \psi}{\partial \rho} \right) + \frac{1}{\rho^2} \frac{\partial^2 \psi}{\partial \phi^2} = 0$$


$$\text{Solution : } \psi(\rho, \phi) = \frac{V_o \ln(b/\rho)}{\ln(b/a)}$$

For a TEM mode of propagation

$$L = \frac{\mu}{2\pi} \ln(b/a)$$

$$C = \frac{2\pi\epsilon}{\ln(b/a)}$$
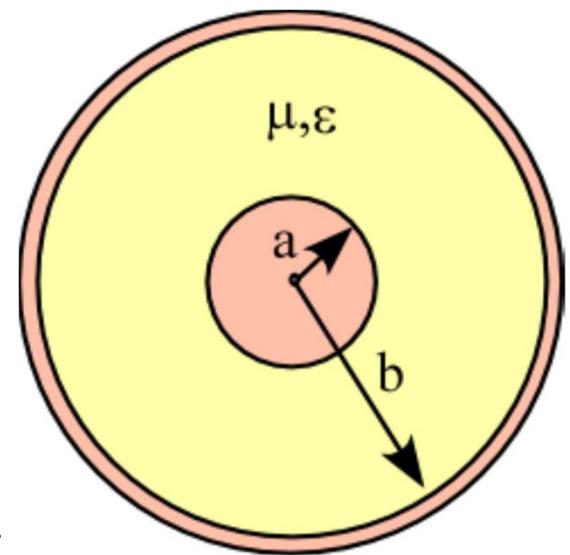
$$\beta = \omega \sqrt{LC} = \omega \sqrt{\mu\epsilon} \quad Z_o = \sqrt{L/C} = \frac{\sqrt{\mu/\epsilon}}{2\pi} \ln(b/a)$$



# Coaxial Cables

Higher order modes: TE modes:  $H_z = h_z(\rho, \phi) e^{-j\beta z}$

$$\left( \frac{\partial^2}{\partial \rho^2} \frac{1}{\rho} \frac{\partial^2}{\partial \phi^2} + k^2 - \beta^2 = 0 \right) h_z = 0$$


The first higher order mode is the  $\text{TE}_{11}$  mode

Approximate solution for  $k_c$  is:  $k_c = \frac{2}{a+b}$


From  $k_c$ , find cutoff frequency  $f_c$

$$f_c = \frac{ck_c}{2\pi\sqrt{\epsilon_r}} = \frac{vk_c}{2\pi}$$
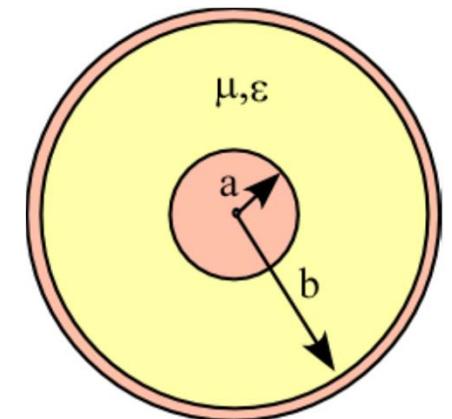
$$f_c = \frac{2c}{(a+b)2\pi\sqrt{\epsilon_r}} = \frac{c}{\sqrt{\epsilon_r}\pi(a+b)}$$



# Coaxial Line with Losses

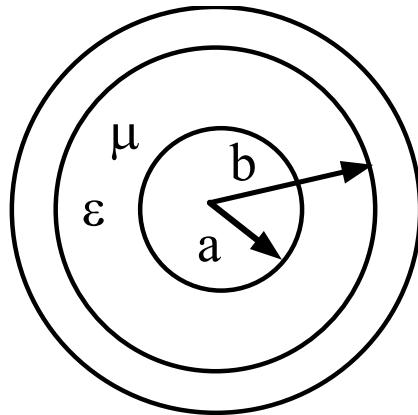


Infinite Conductivity

$$Z_o = \frac{\sqrt{\mu/\epsilon}}{2\pi} \ln(b/a)$$

Finite Conductivity

$$Z_o = \frac{\sqrt{\mu/\epsilon}}{2\pi} \ln(b/a) \left[ 1 + \frac{(1/a + 1/b)}{4\sqrt{\pi f \mu \sigma} \ln(b/a)} (1 - j) \right]$$


# Types of Transmission Lines

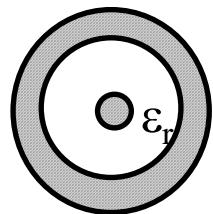


Coaxial line




Waveguide

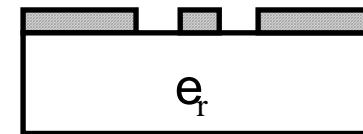


Coplanar line

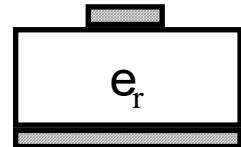

Microstrip

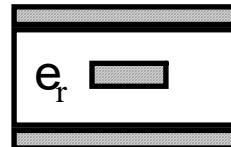


Stripline

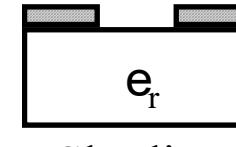

Slot line


# Parallel-plate Transmission Line

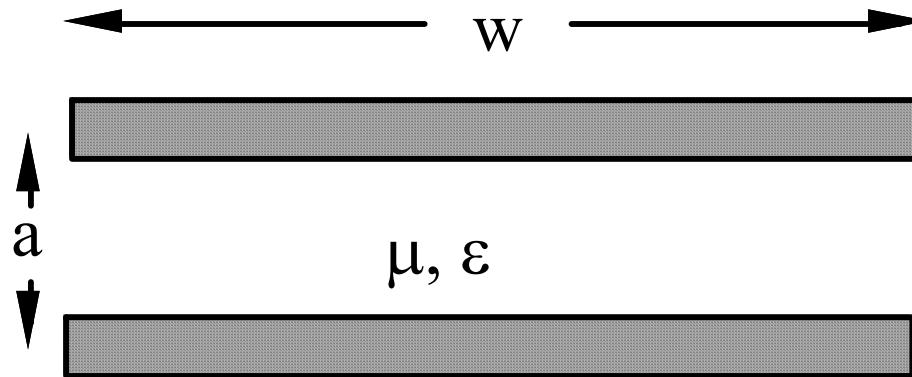


$$L = \frac{\mu a}{w}$$

$$C = \frac{\epsilon w}{a}$$

# Microstrip and stripline

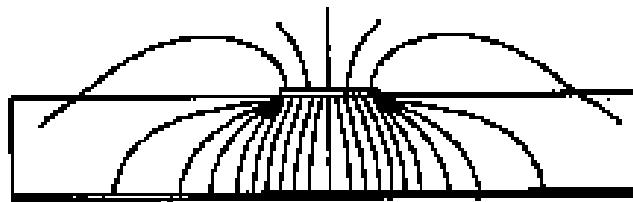


Microstrip

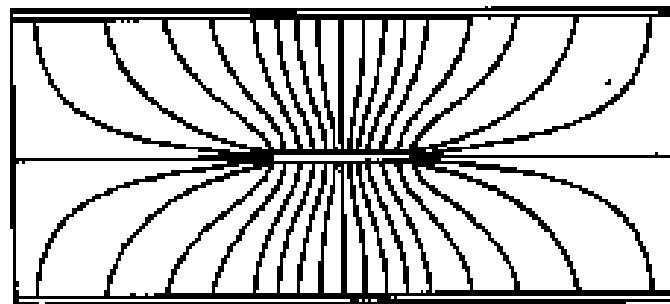

Stripline

Wave propagation in stripline is closer to the TEM mode of propagation and the propagation of velocity is approximately  $c/\sqrt{\epsilon_r}$ .


# Microstrip – Analysis Equations

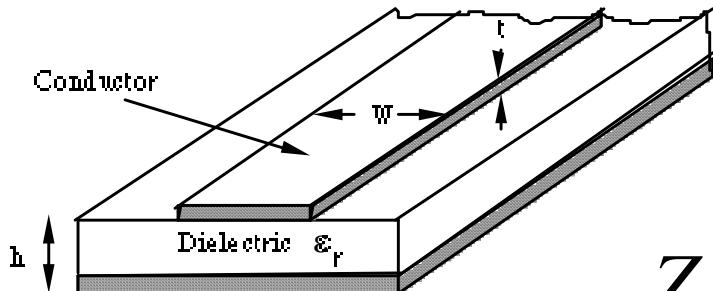

(a)

$$w/h < 3.3$$
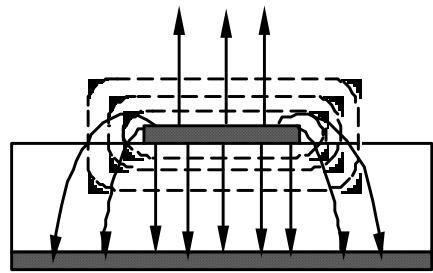
$$Z_o = \frac{119.9}{\sqrt{2(\epsilon_r + 1)}} \ln \left[ 4 \frac{h}{w} + \sqrt{16 \left( \frac{h}{w} \right)^2 + 2} \right]$$



Electric field lines

Magnetic field lines

(b)

$$w/h > 3.3$$

$$Z_o = \frac{119.9\pi}{2\sqrt{\epsilon_r}} \left\{ \frac{w}{2h} + \frac{\ln(4)}{\pi} + \frac{\ln(e\pi^2/16)}{2\pi} \left( \frac{\epsilon_r - 1}{\epsilon_r^2} \right) \right. \\ \left. + \frac{\epsilon_r + 1}{2\pi\epsilon_r} \left[ \ln \frac{\pi e}{2} + \ln \left( \frac{w}{2h} + 0.94 \right) \right] \right\}$$

# Microstrip Analysis & Synthesis Equations

$$\varepsilon_e = \frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12d/W}}$$


$$Z_o = \begin{cases} \frac{60}{\sqrt{\varepsilon_e}} \ln \left( \frac{8d}{W} + \frac{W}{4d} \right) & \text{for } W/d \leq 1 \\ \frac{120\pi}{\sqrt{\varepsilon_e} [W/d + 1.393 + 0.667 \ln(W/d + 1.444)]} & \text{for } W/d \geq 1 \end{cases}$$

$$\frac{W}{d} = \begin{cases} \frac{8e^A}{e^{2A} - 2} & \text{for } W/d < 2 \\ \frac{2}{\pi} \left[ B - 1 - \ln(2B - 1) + \frac{\varepsilon_r - 1}{2\varepsilon_r} \left\{ \ln(B - 1) + 0.39 - \frac{0.61}{\varepsilon_r} \right\} \right] & \text{for } W/d > 2 \end{cases}$$

$$A = \frac{Z_o}{60} \sqrt{\frac{\varepsilon_r + 1}{2}} + \frac{\varepsilon_r - 1}{\varepsilon_r + 1} \left( 0.23 + \frac{0.11}{\varepsilon_r} \right)$$

$$B = \frac{377\pi}{2Z_o \sqrt{\varepsilon_r}}$$

# Microstrip

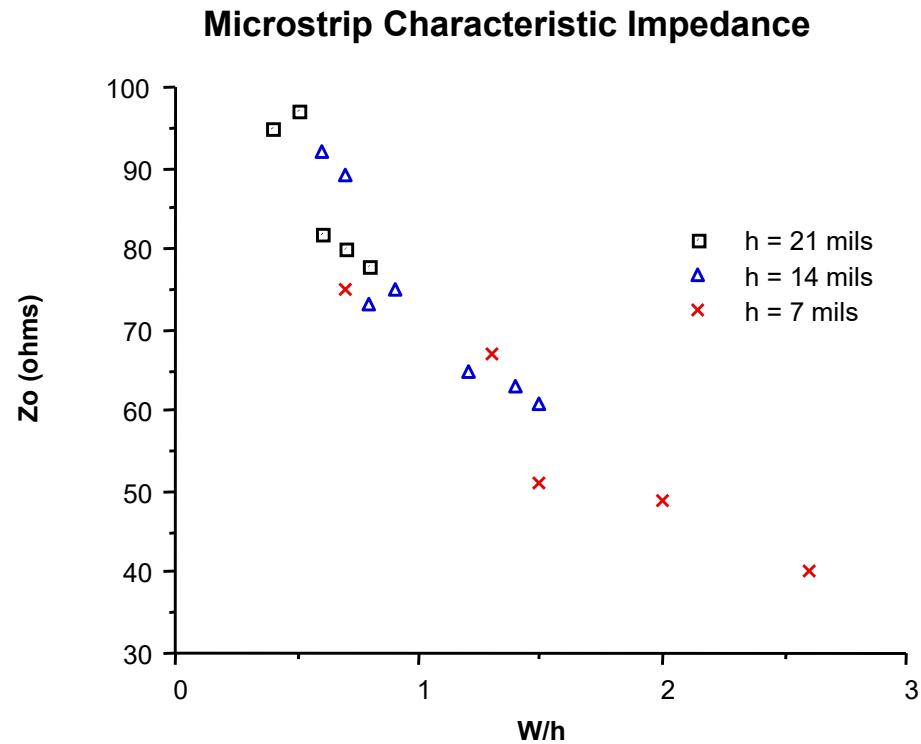

**dielectric constant : 4.3.**


# Surface Waves – TM Modes

Assume the form:

$$E_z(x, y, z) = e_z(x, y) e^{-j\beta z}$$

$$\left( \frac{\partial^2}{\partial x^2} + \epsilon_r k_o^2 - \beta^2 \right) e_z(x, y) = 0 \quad \text{Inside dielectric}$$
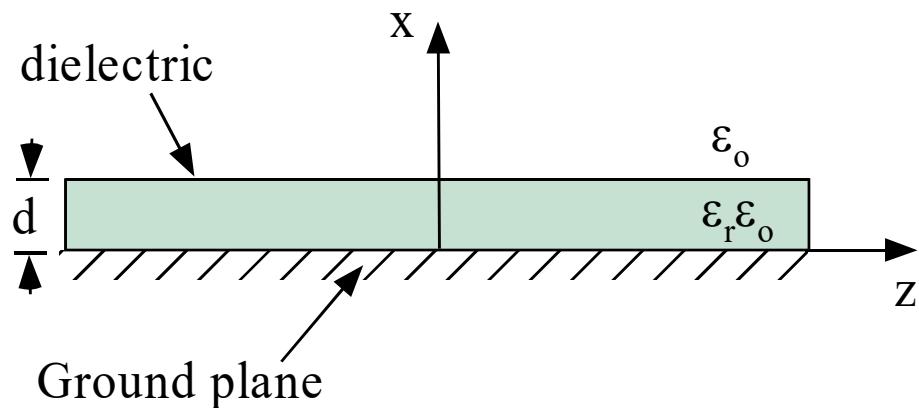
$$\left( \frac{\partial^2}{\partial x^2} + k_o^2 - \beta^2 \right) e_z(x, y) = 0 \quad \text{Outside dielectric}$$



Dispersion relations

$$k_c^2 = \epsilon_r k_o^2 - \beta^2$$

$$h^2 = \beta^2 - k_o^2$$

# Surface Waves – TM Modes: Solutions

Solutions are:

$$e_z(x, y) = A \sin k_c x + B \cos k_c x$$

$$e_z(x, y) = C e^{hx} + D e^{-hx}$$

$$E_z(x, y, z) = 0 \text{ at } x=0$$

$$E_z(x, y, z) < \infty, \text{ for } x \rightarrow \infty$$

$$E_z(x, y, z) \text{ continuous at boundary}$$


$$H_y(x, y, z) \text{ continuous at boundary}$$

$$A \sin k_c d = D e^{-hd}$$

$$\frac{\epsilon_r A}{k_c} \cos k_c d = \frac{D}{h} e^{-hd}$$

Inside dielectric

Outside dielectric

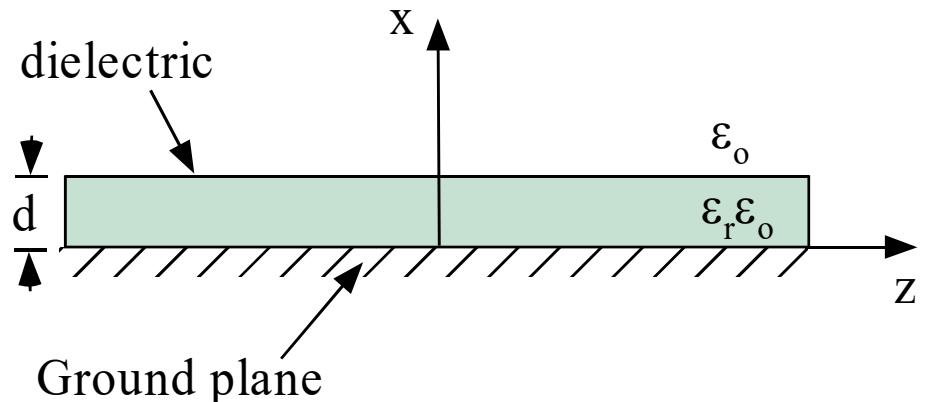

$$k_c \tan k_c d = \epsilon_r h$$


$$k_c^2 + h^2 = (\epsilon_r - 1) k_o^2$$

# Surface Waves – TM Modes: Solutions

$$(k_c d)^2 + (hd)^2 = (\epsilon_r - 1)(k_o d)^2$$

$$k_c d \tan k_c d = \epsilon_r h d$$

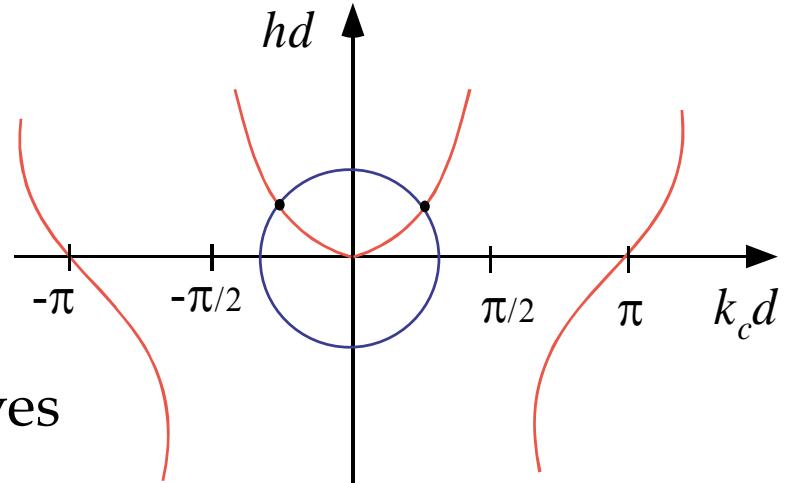Solution is found at intersection of curves



First TM mode is TM<sub>0</sub> mode

Cutoff frequencies for TM modes are given by:

$$f_c = \frac{nc}{2d\sqrt{\epsilon_r - 1}}, \quad n = 0, 1, 2, \dots$$


# Surface Waves – TE Modes

Assume the form:

$$H_z(x, y, z) = h_z(x, y)e^{-j\beta z}$$

$$\left( \frac{\partial^2}{\partial x^2} + \epsilon_r k_o^2 - \beta^2 \right) h_z(x, y) = 0 \quad \text{Inside dielectric}$$
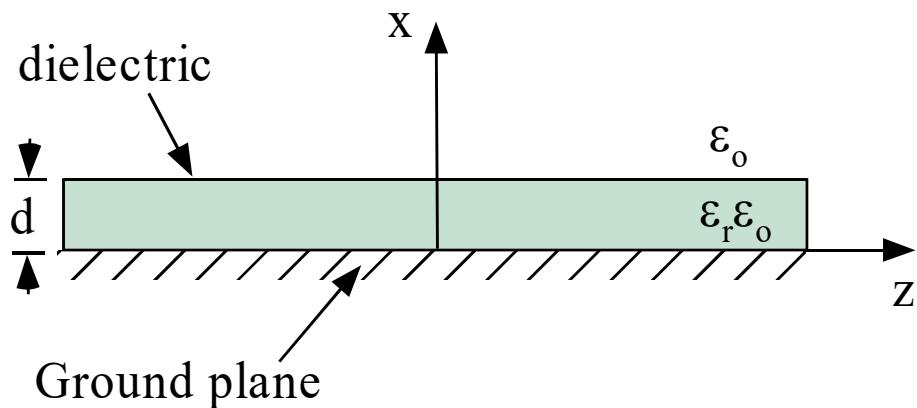
$$\left( \frac{\partial^2}{\partial x^2} + k_o^2 - \beta^2 \right) h_z(x, y) = 0 \quad \text{Outside dielectric}$$



Dispersion relations

$$k_c^2 = \epsilon_r k_o^2 - \beta^2$$

$$h^2 = \beta^2 - k_o^2$$

# Surface Waves – TE Modes: Solutions

Solutions are:

$$h_z(x, y) = A \sin k_c x + B \cos k_c x$$


Inside dielectric

$$h_z(x, y) = C e^{hx} + D e^{-hx}$$

Outside dielectric

After matching the boundary conditions
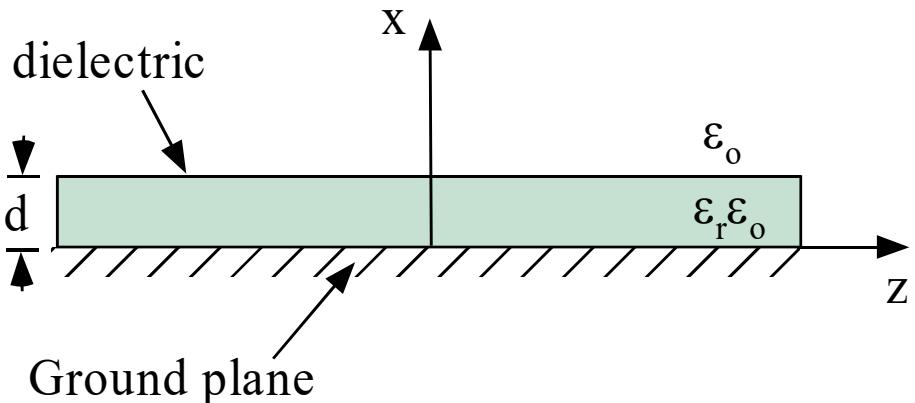
$$\frac{-B}{k_c} \sin k_c d = \frac{D}{h} e^{-hd}$$



$$B \cos k_c d = D e^{-hd}$$

$$-k_c \cot k_c d = h$$

$$k_c^2 + h^2 = (\epsilon_r - 1) k_o^2$$

# Surface Waves – TE Modes: Solutions

$$(k_c d)^2 + (hd)^2 = (\epsilon_r - 1)(k_o d)^2$$


$$-k_c d \cot k_c d = hd$$

Solution is found at intersection of curves

Negative values of  $h$  must be excluded

Cutoff frequencies for TE modes are given by:

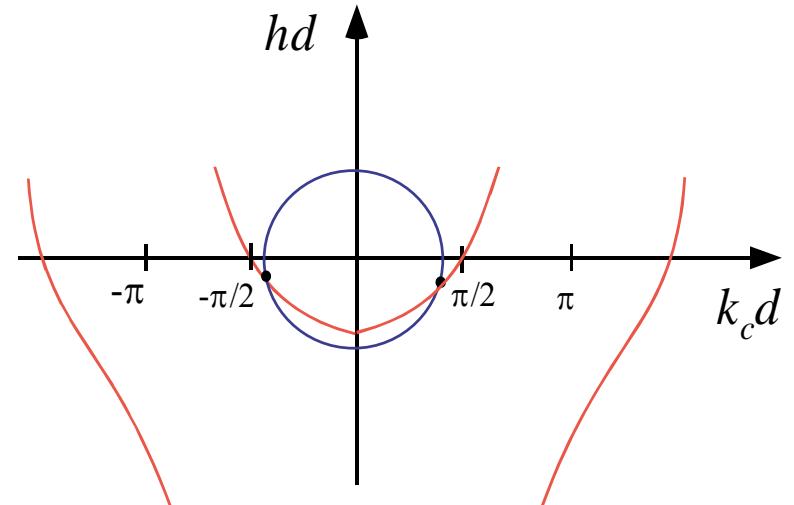
$$f_c = \frac{(2n-1)c}{4d\sqrt{\epsilon_r - 1}}, \quad n = 1, 2, 3, \dots$$



Modes will occur in the following order:

TM<sub>0</sub>, TE<sub>1</sub>, TM<sub>1</sub>, TE<sub>2</sub>, TM<sub>2</sub>

# Coplanar Waveguide

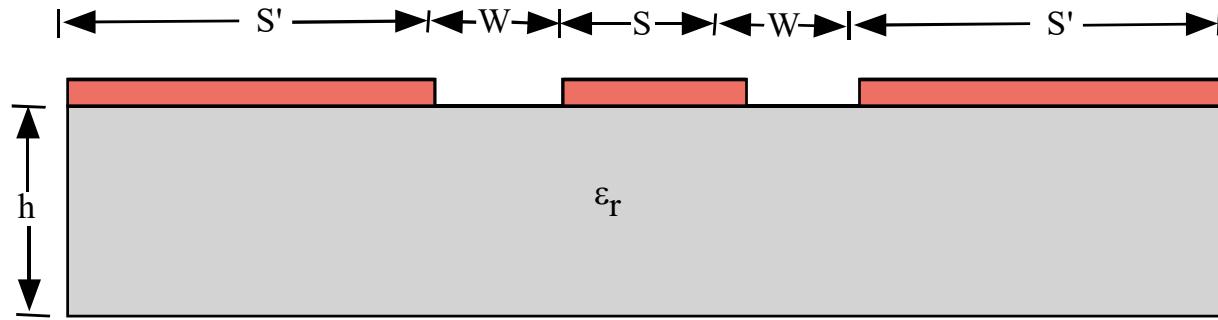

$K(k)$ : Complete Elliptic Integral of the first kind

$$k = \frac{S}{S + 2W}$$


$$Z_{ocp} = \frac{30\pi}{\sqrt{\epsilon_r + 1}} \frac{K'(k)}{K(k)} \text{ (ohm)}$$

$$K'(k) = K(k')$$

$$k' = (1 - k^2)^{1/2}$$

$$v_{cp} = \left( \frac{2}{\epsilon_r + 1} \right)^{1/2} c$$

# Coplanar Strips

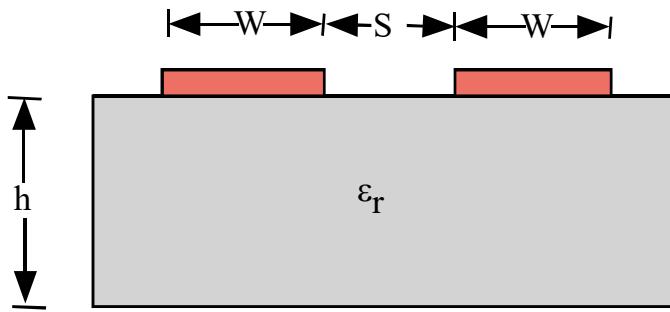


$$Z_{ocs} = \frac{120\pi}{\sqrt{\epsilon_r + 1}} \frac{K'(k)}{K(k)} \text{ (ohm)}$$

# Qualitative Comparison


Characteristic	Microstrip	Coplanar Wguide	Coplanar strips
$\epsilon_{\text{eff}}^*$	~6.5	~5	~5
Power handling	High	Medium	Medium
Radiation loss	Low	Medium	Medium
Unloaded Q	High	Medium	Low or High
Dispersion	Small	Medium	Medium
Mounting (shunt)	Hard	Easy	Easy
Mounting (series)	Easy	Easy	Easy

\* Assuming  $\epsilon_r=10$  and  $h=0.025$  inch

# TEM PROPAGATION

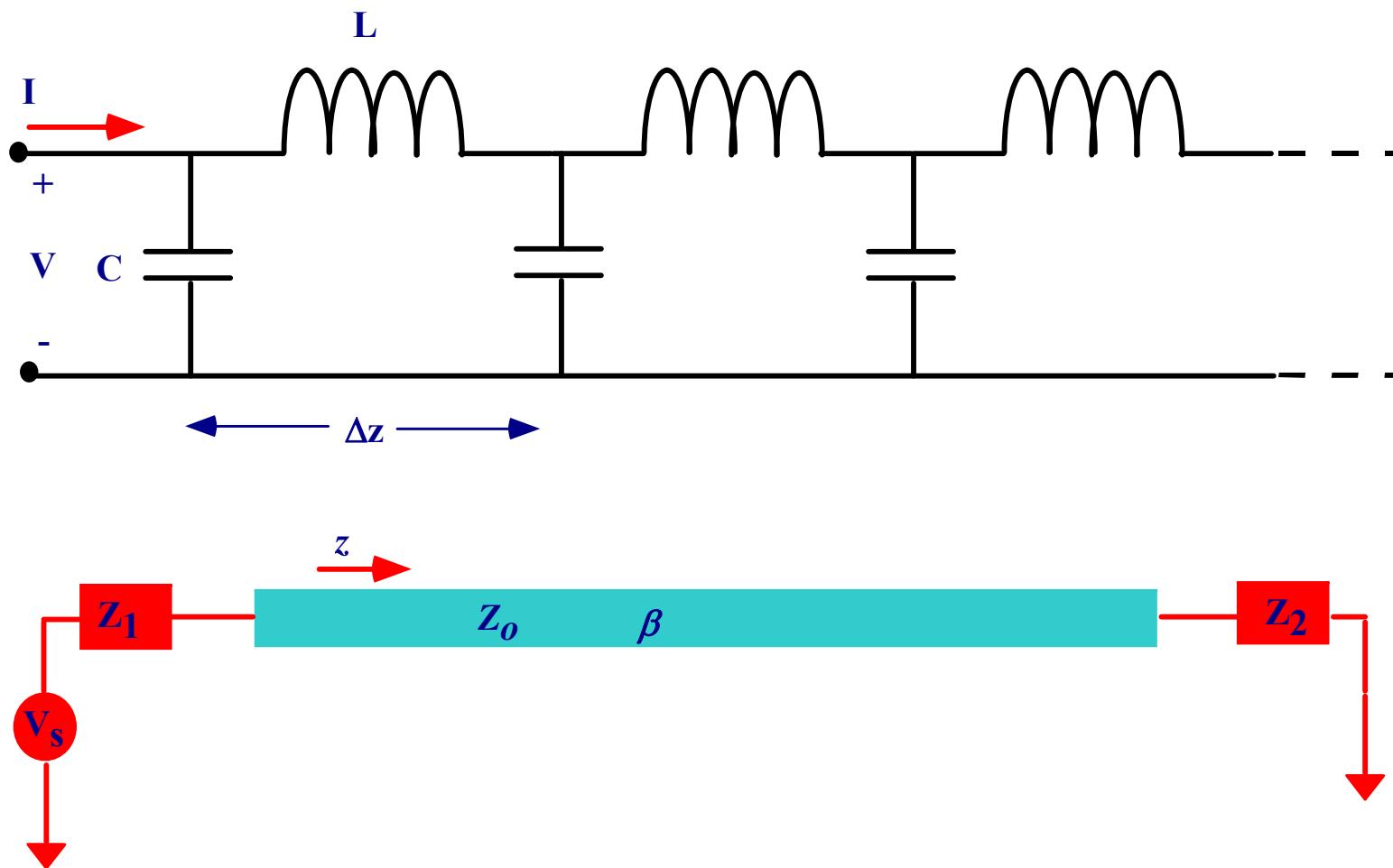

# Telegrapher's Equations

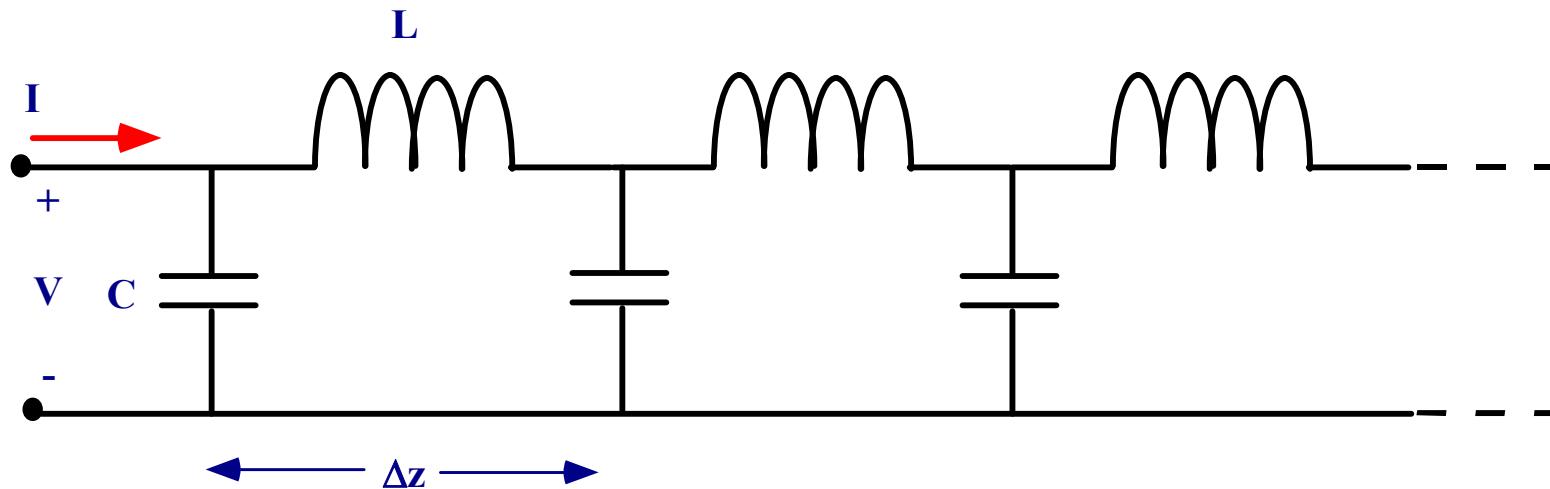

$$-\frac{\partial V}{\partial z} = L \frac{\partial I}{\partial t}$$


$$-\frac{\partial I}{\partial z} = C \frac{\partial V}{\partial t}$$

**L:** Inductance per unit length.

**C:** Capacitance per unit length.

# Transmission Line Solutions

(Frequency Domain)

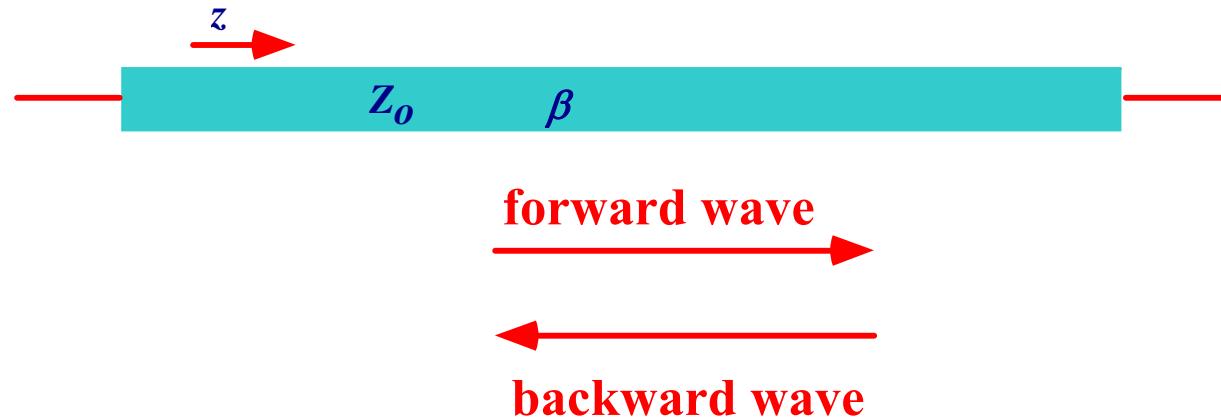


$$\beta = \omega\sqrt{LC}$$

$$V(z) = Ae^{-j\beta z} + Be^{+j\beta z}$$

$$Z_o = \sqrt{\frac{L}{C}}$$

$$I(z) = \frac{1}{Z_o} [Ae^{-j\beta z} - Be^{+j\beta z}]$$


# Coaxial-Microstrip Transition

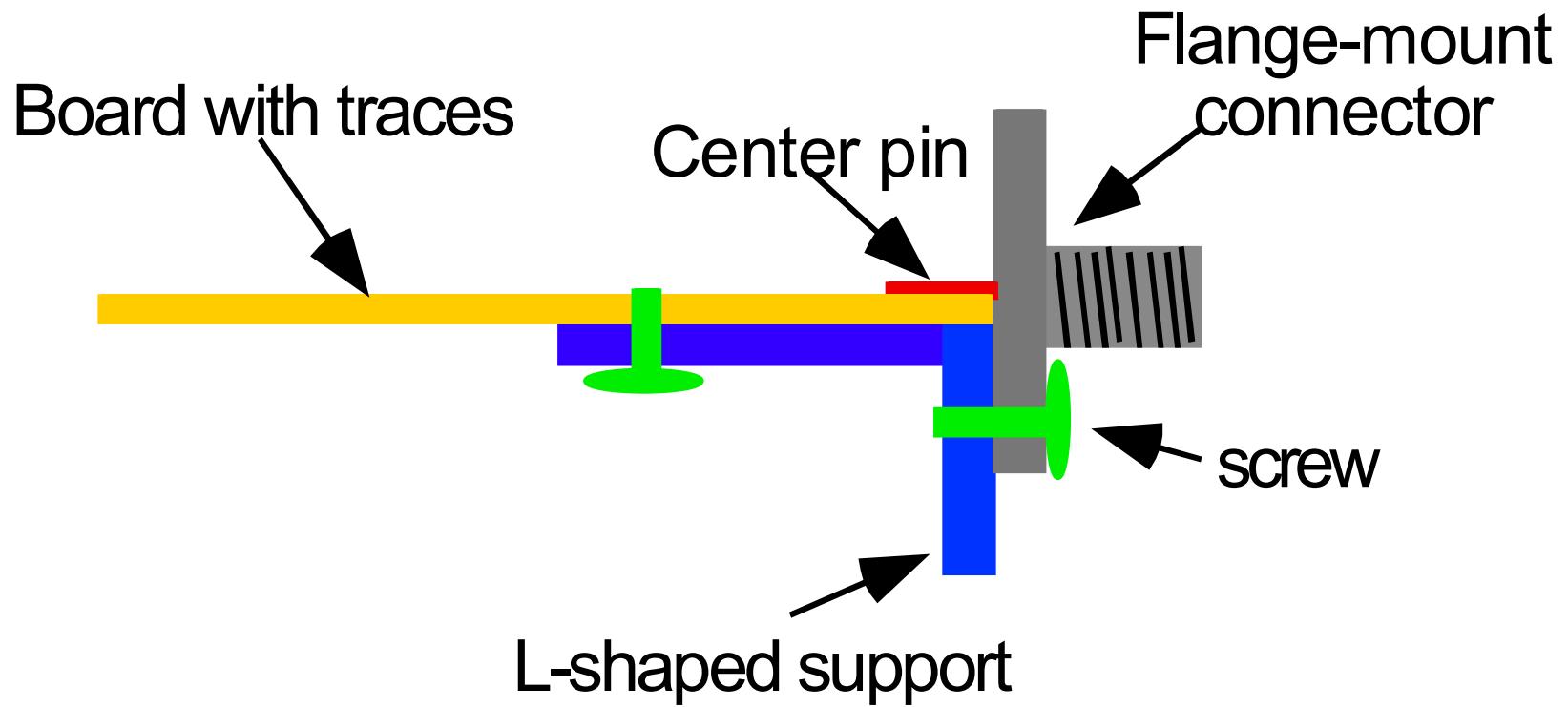


**Remove effects of discontinuities before processing data!**

# Coaxial-Microstrip Transition


With parasitics

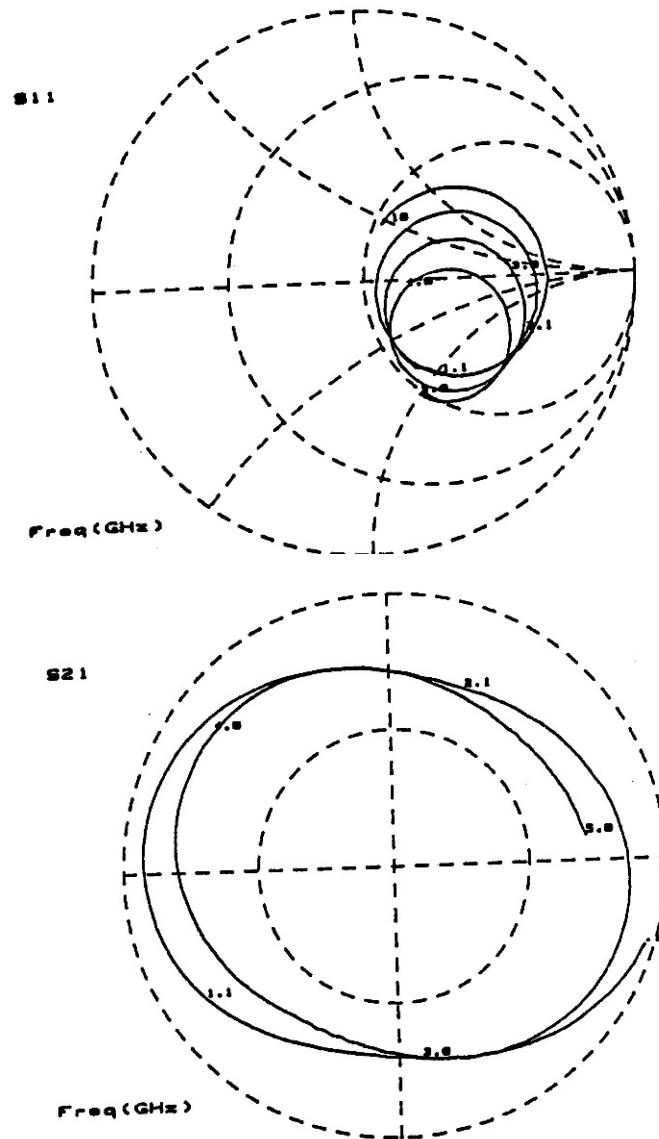


No parasitics

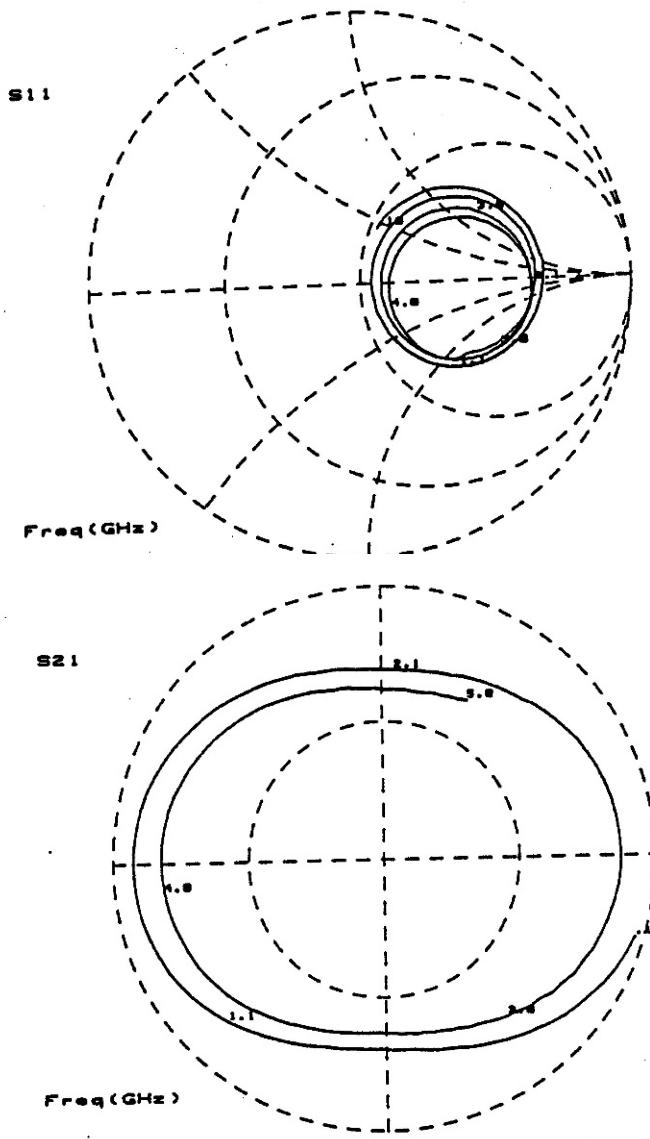

# Coaxial-Microstrip Transition

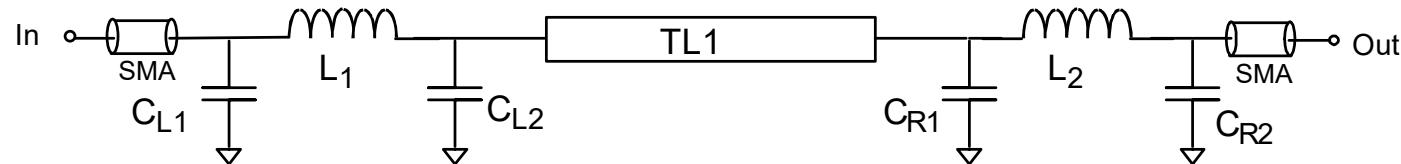


Equivalent Circuit

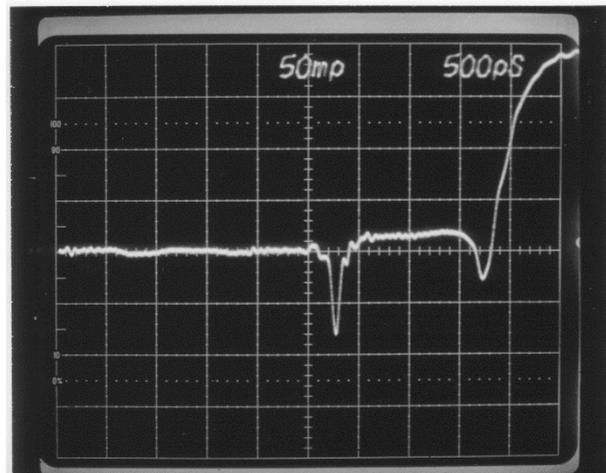

TDR Plot

# Low-Frequency TL Approximation

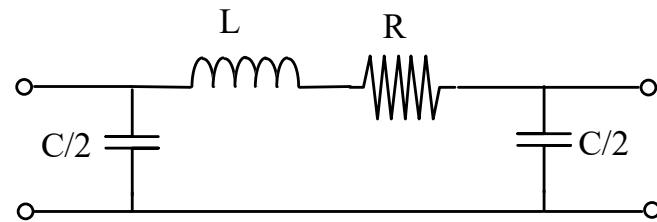

$$P = (R + j\omega L)(1 + j\omega CZ_o/2)$$

$$Y = j\omega CZ_o/2$$



$$S_{11} = \frac{P - 2YZ_o - YP}{2Z_o + P + 2YZ_o + YP} \quad S_{21} = \frac{2Z_o}{2Z_o + P + 2YZ_o + YP}$$

$$A = 2Z_o(1 - S_{21})$$


$$Y = \frac{A - 2S_{11}S_{21}Z_o - S_{11}A}{4S_{21}Z_o + 2S_{11}S_{21}Z_o + S_{11}A + A} \quad P = A - 2YS_{21}Z_oS_{21}(1 + Y)$$
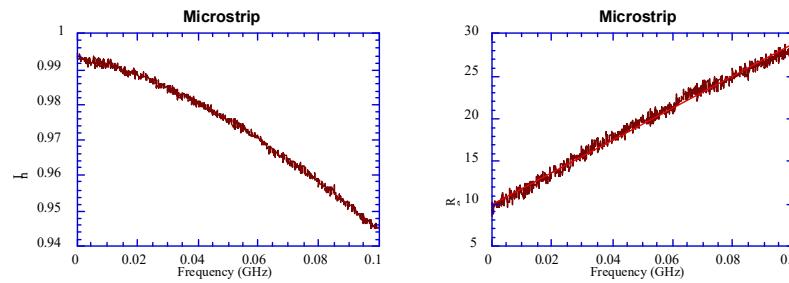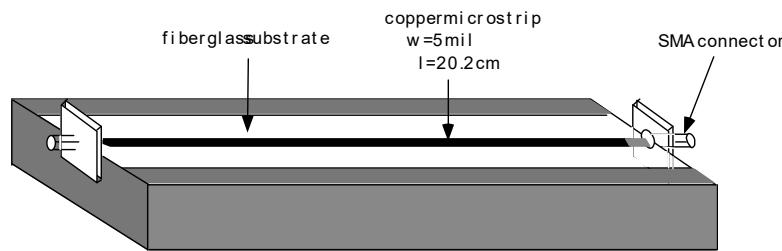
# Low-Frequency Model for Microstrip

- Lumped Model
- Use extraction algorithm



# High-Frequency Characterization

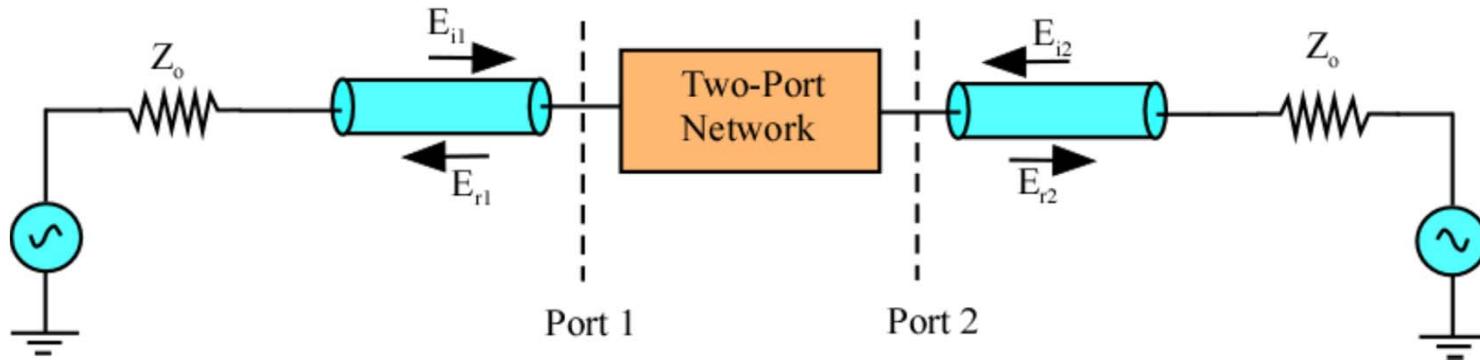

## Transmission-Line Scattering Parameters

$$S_{21} = \frac{(1 - \Gamma^2)X}{1 - \Gamma^2 X^2} \quad S_{11} = \frac{(1 - X^2)\Gamma}{1 - \Gamma^2 X^2}$$

$$X = e^{-\gamma d}$$

$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\Gamma = \frac{Z_c - Z_o}{Z_c + Z_o}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

# TL Extraction Formulas

$$X = e^{-\gamma d} = e^{-j\beta d} e^{-\alpha d} \quad X = e^{-\gamma d} = \frac{(S_{11} + S_{21}) - \Gamma}{1 - (S_{11} + S_{21})\Gamma}$$

$$\Gamma = Q \pm \sqrt{Q^2 - 1}$$

$$Q = \frac{\{S_{11}^2 - S_{21}^2\} + 1}{2S_{11}}$$

$$R = \text{Re}\{\gamma Z_c\}$$

$$G = \text{Re}\left\{\frac{\gamma}{Z_c}\right\}$$

$$L = \frac{1}{\omega} \text{Im}\{Z_c \gamma\}$$

$$C = \frac{1}{\omega} \text{Im}\left\{\frac{\gamma}{Z_c}\right\}$$

# Low-Loss Approximation

If we assume  $R \ll \omega L$

and  $G \ll \omega C$

$$Z_c \cong \sqrt{\frac{L}{C}}$$

$$\gamma \cong \frac{R}{2} \sqrt{\frac{C}{L}} + j\omega\sqrt{LC} = \frac{R}{2Z_c} + j\frac{\omega}{v_p}$$

$$\alpha \cong \frac{R}{2Z_c} \quad \beta \cong \frac{\omega}{v_p}$$

# TL Extraction Formulas



$$\alpha = -\frac{\ln(|X|)}{d}$$

$$R = -\frac{2Z_c \ln(|X|)}{d}$$





$$\frac{\Delta\phi}{\Delta\omega} = -\frac{d}{v_p}$$

$$v_p = -\frac{d}{\frac{\Delta\phi}{\Delta\omega}}$$



# Example: Category-5 Cable (long)

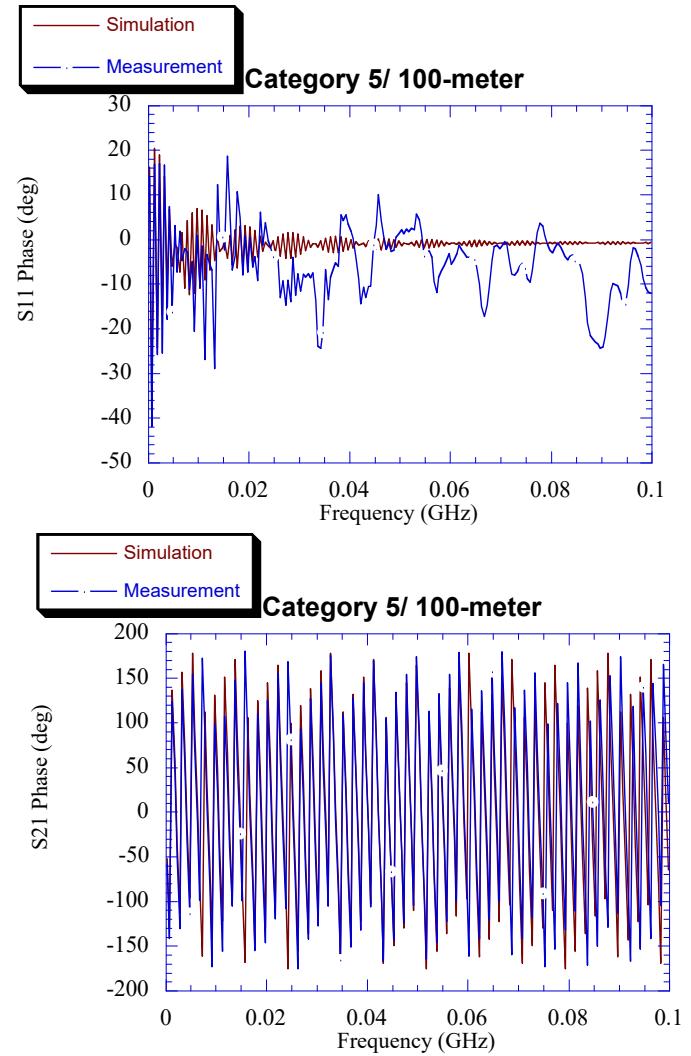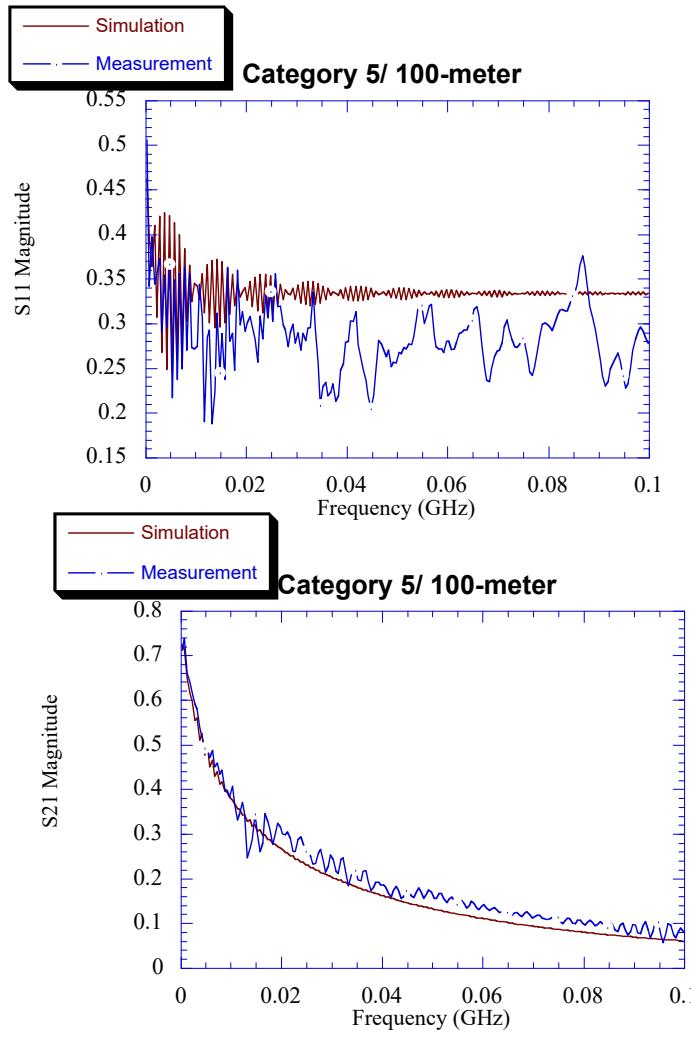

# Example: Category-5 Cable (short)

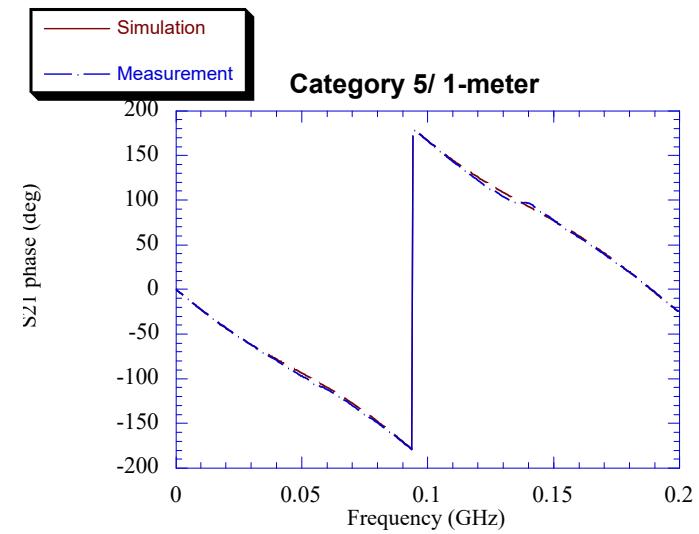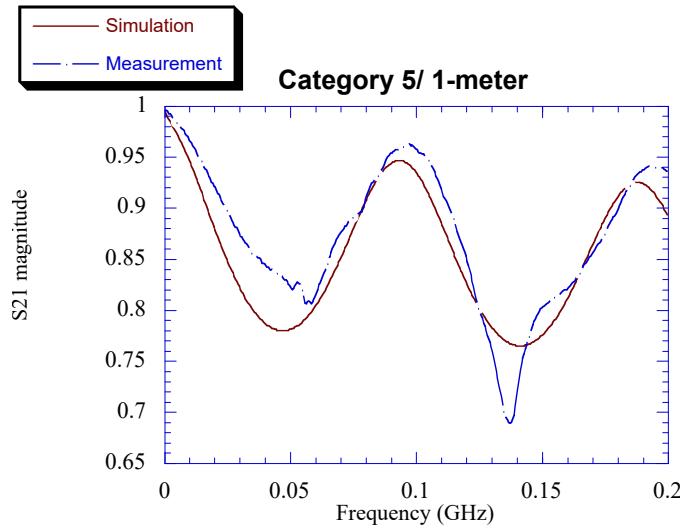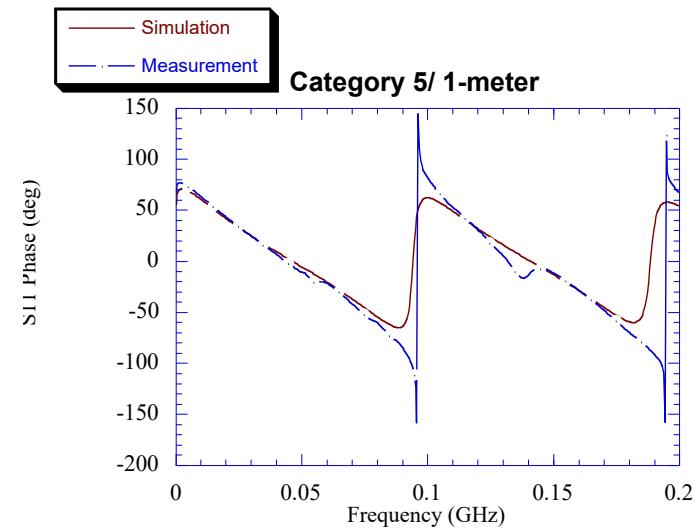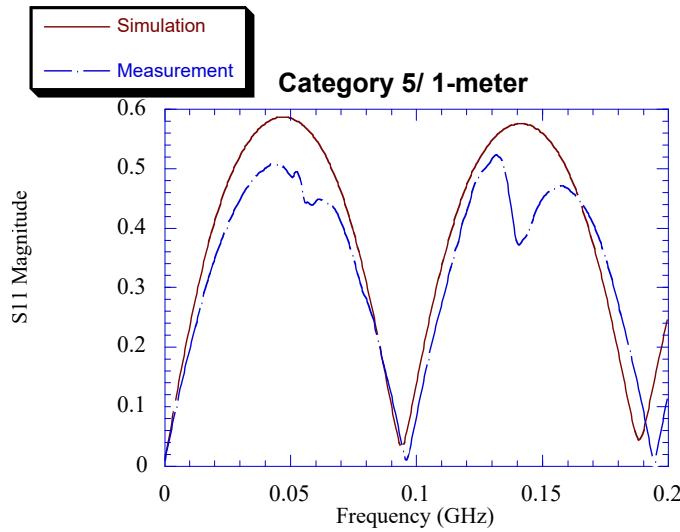
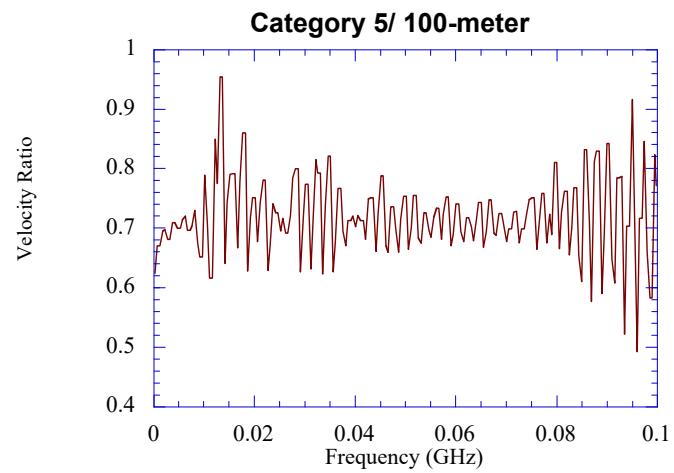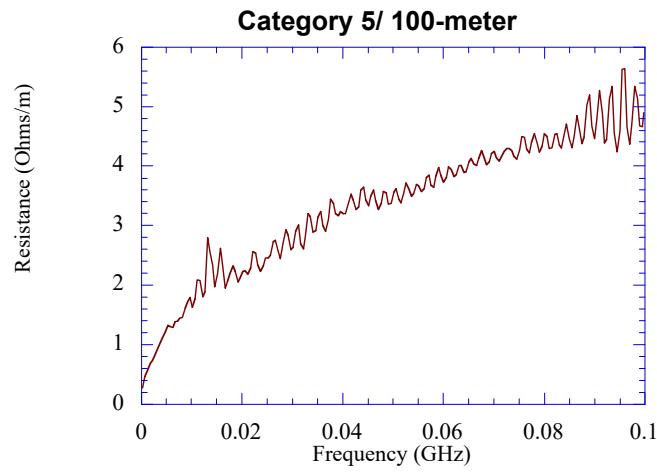
# Category-5 Cable – Loss Characteristics



# Cable Loss Model


$$R(f) = R_s * f^p$$

$$\nu_r = \nu_{ro} + \nu_{rs} * f$$


$$Z = R(f) + j\omega L = R_{skin} + j(R_{skin} + \omega L)$$

	$\frac{Z_0}{(\Omega)}$	$\frac{V_{ro}}{(m/ns)}$	$\frac{V_{rs}}{(m/ns-GHz)}$	$\frac{R_s}{(\Omega/m-GHz^p)}$	$p$	$\frac{f_{max}}{(GHz)}$
<b>Category 5</b>	100	0.724	-0.165	15.38	0.482	0.2
<b>24-Ga</b>	100	0.678	1.157	29.03	0.593	0.1
<b>Category 3</b>	100	0.705	11.06	12.31	0.473	0.01
<b>SMA</b>	50	0.700	0.113	7.94	0.415	0.2

# Time-Domain Simulations

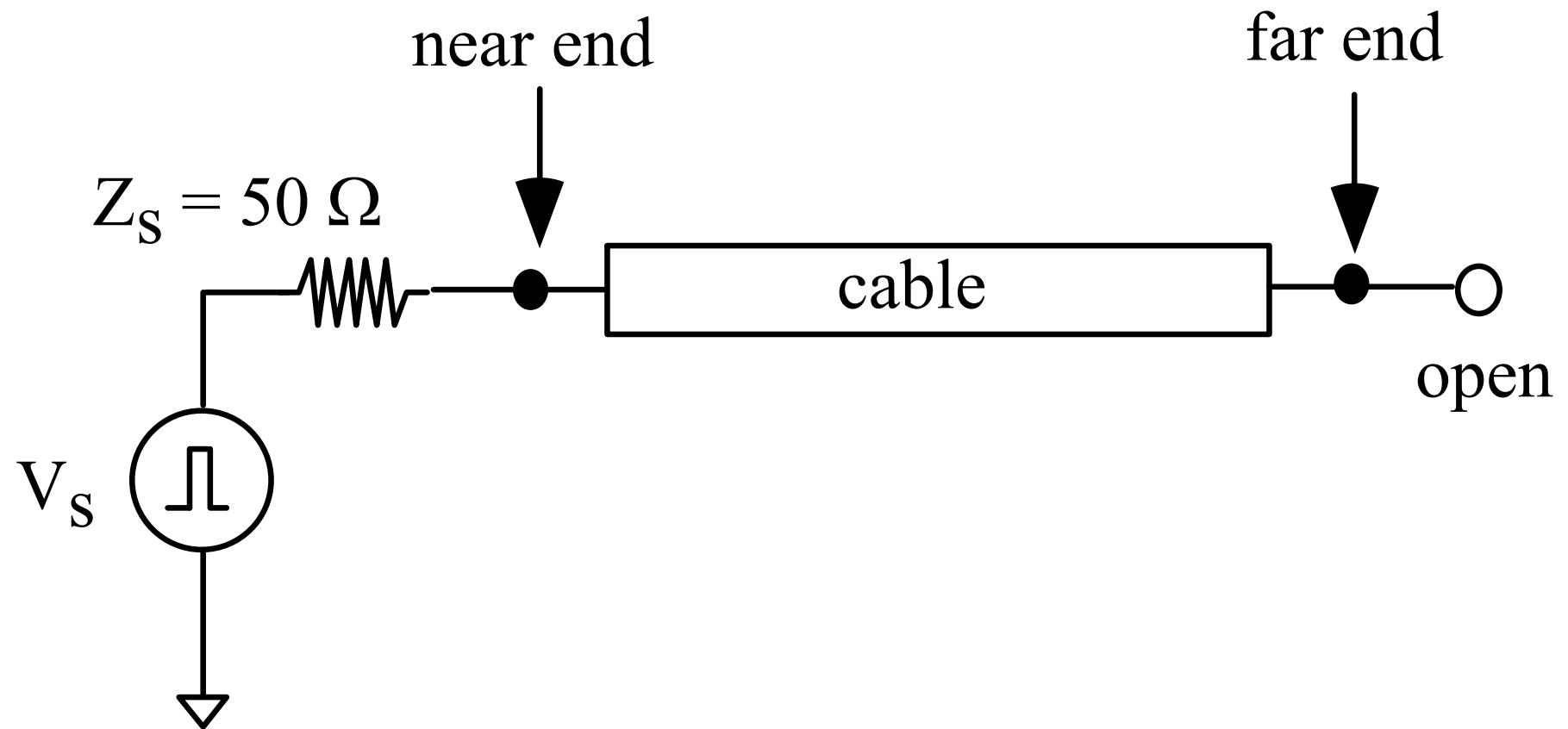

# Lossy Transmission Line



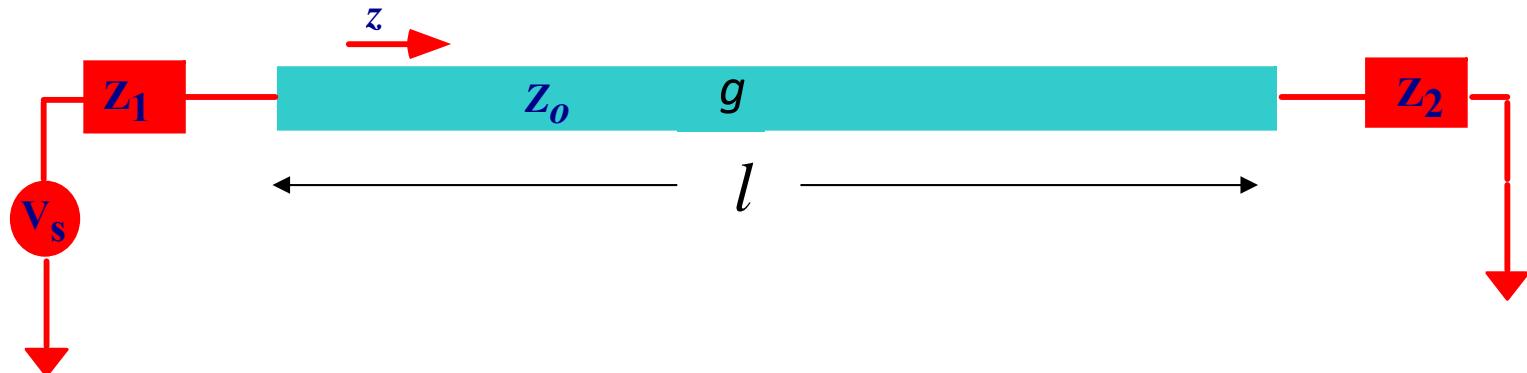


$$V(z) = A e^{-\alpha z} e^{-j\beta z} + B e^{+\alpha z} e^{+j\beta z}$$





$$I(z) = \frac{1}{Z_o} \left[ A e^{-\alpha z} e^{-j\beta z} - B e^{+\alpha z} e^{+j\beta z} \right]$$

$$Z_o = \sqrt{\frac{(R(\omega) + j\omega L)}{(G + j\omega C)}} \quad \gamma = \alpha + j\beta = \sqrt{(R(\omega) + j\omega L)(G + j\omega C)}$$





# Pulse Propagation (CAT-5)

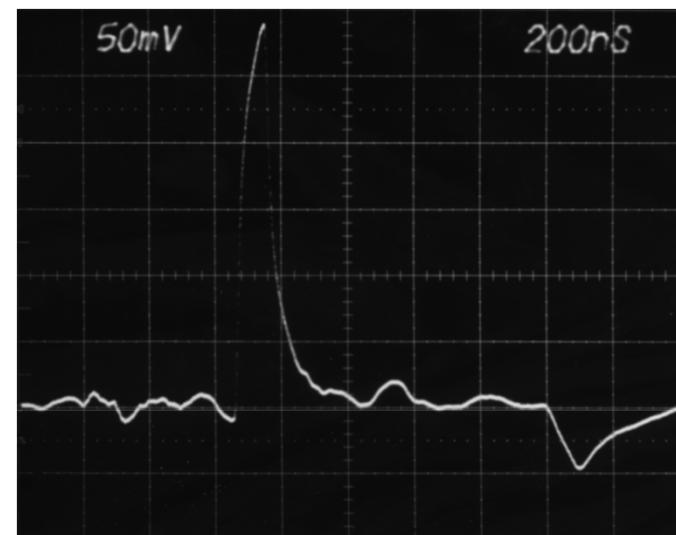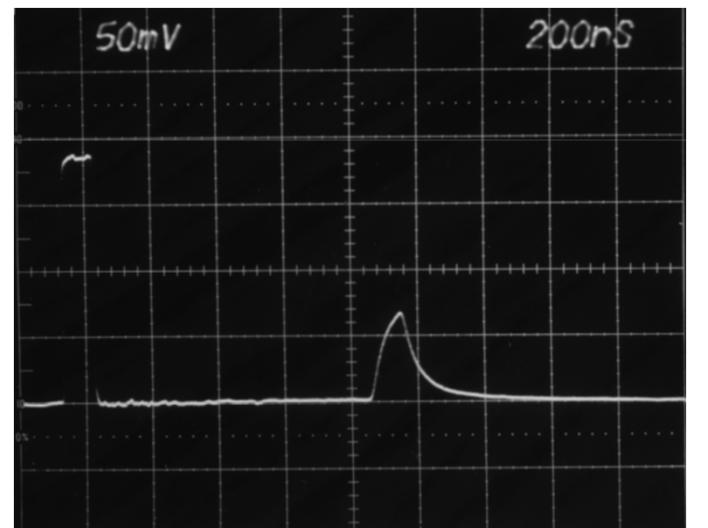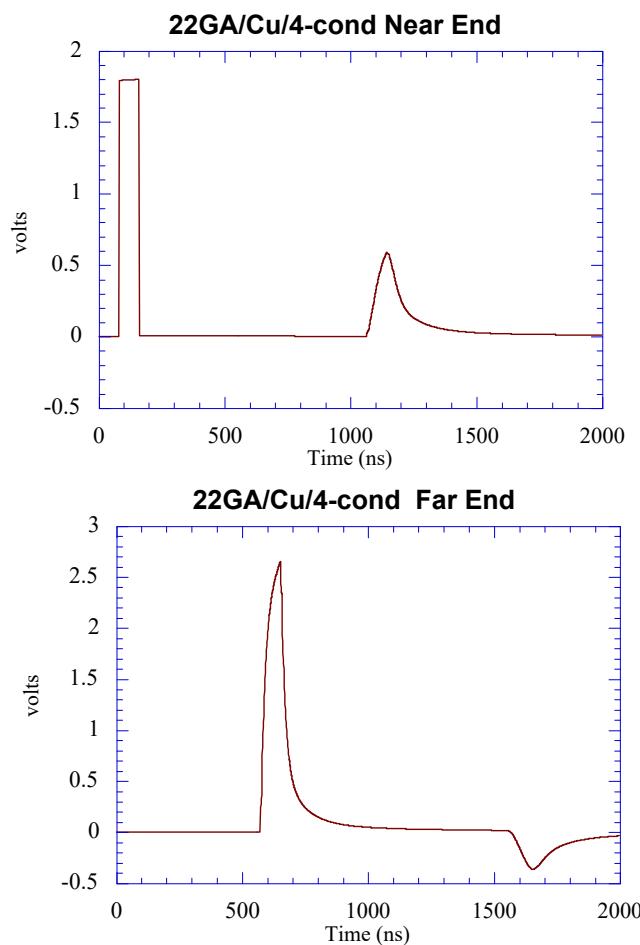


# Pulse Propagation (MP/CM)

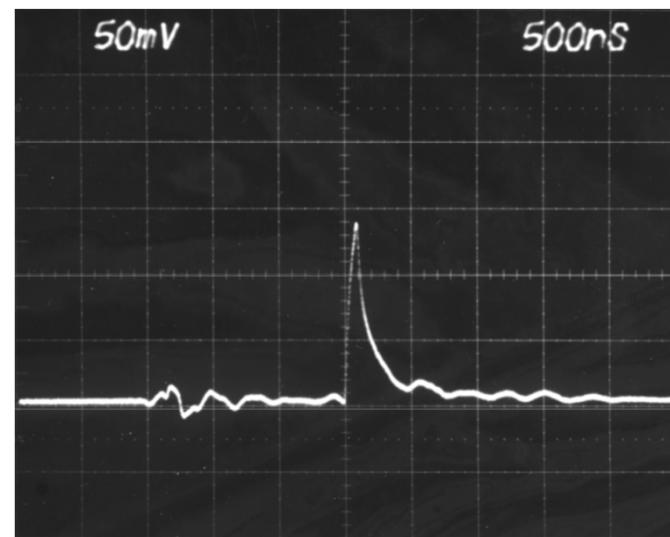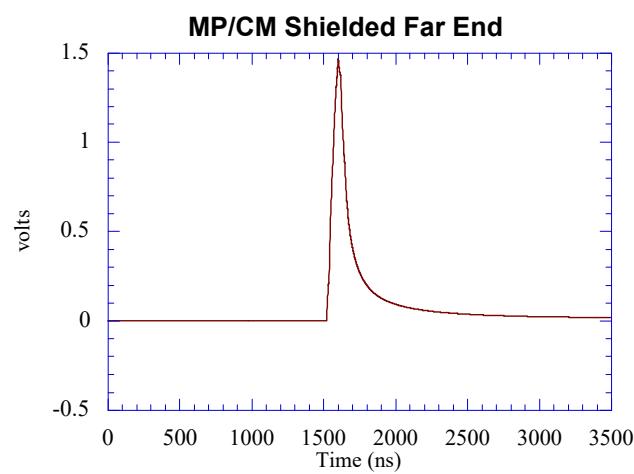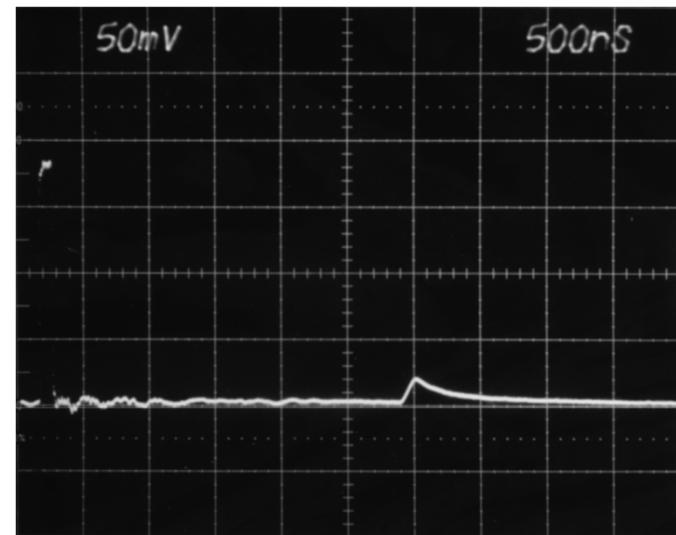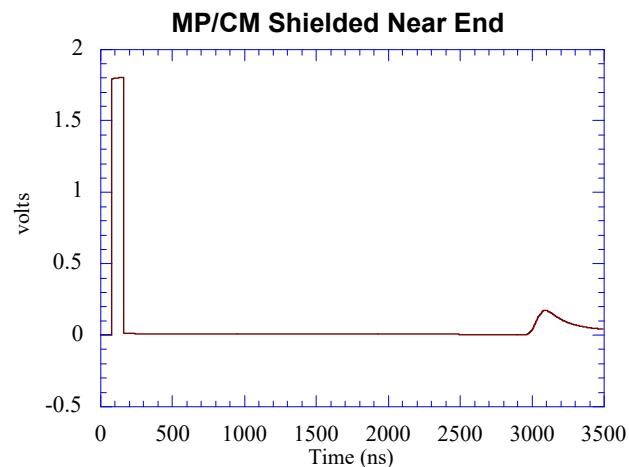

# Pulse Propagation (RG174)

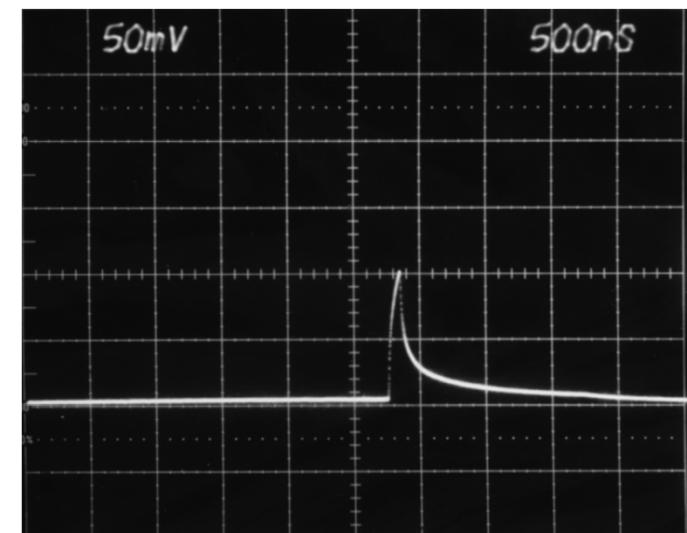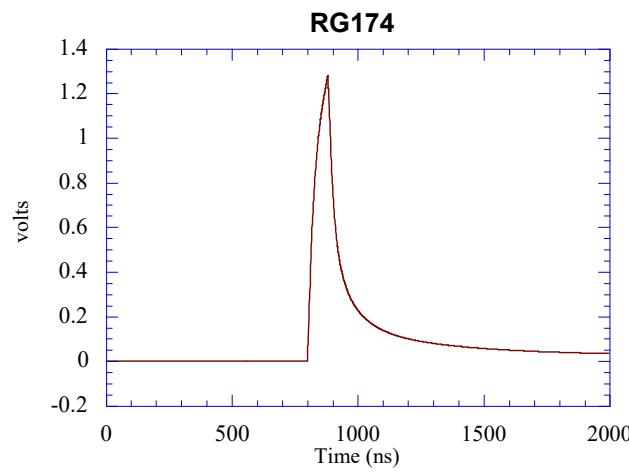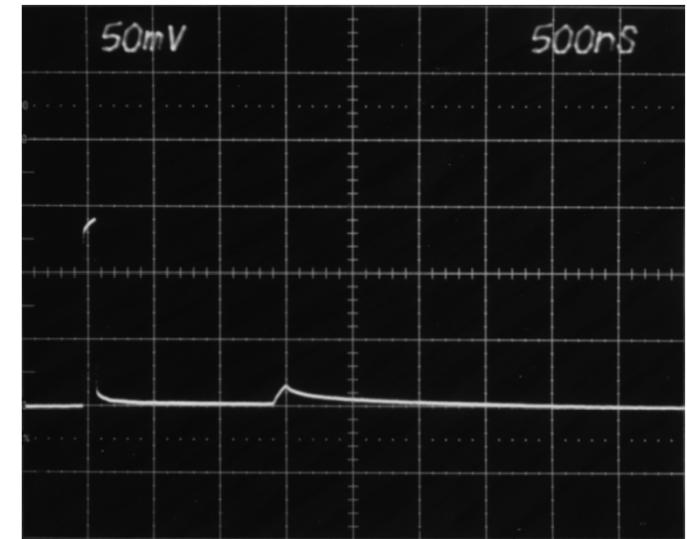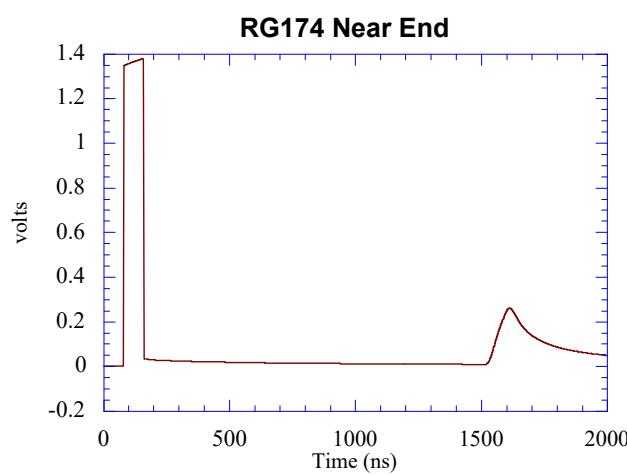


# Characterization of DIP Packages

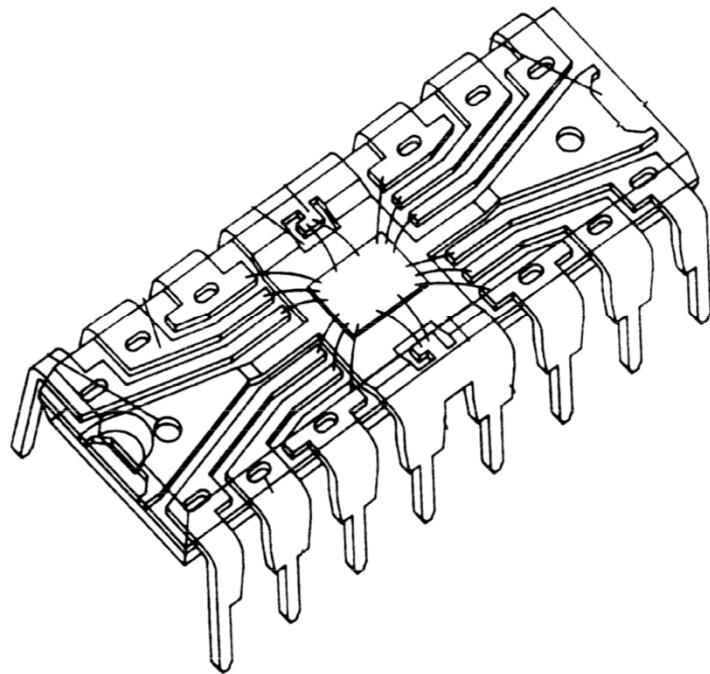

View of DIP Lead Frame



DIP Mounted on PCB with SMA

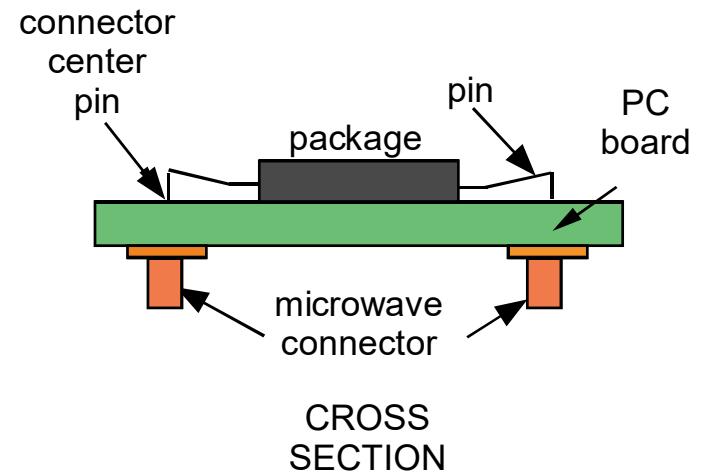

# Package Characterization Procedure





- **Devise Model for Package + Environment**
  - Obtain accurate model for topology
  - Determine frequency range for model
- **Calibrate ANA and Perform Measurements**
  - De-embed connector or use TRL
  - S Parameters can be converted
- **Optimize Model using Simulator**
  - ADS or SPICE
  - Select accurate optimization scheme

# Example – Topology & Model

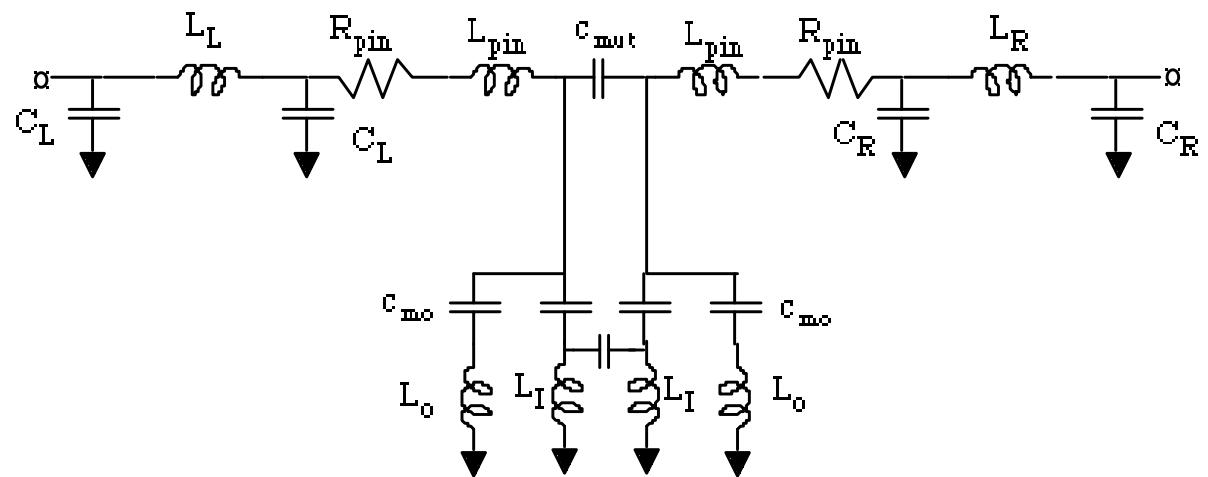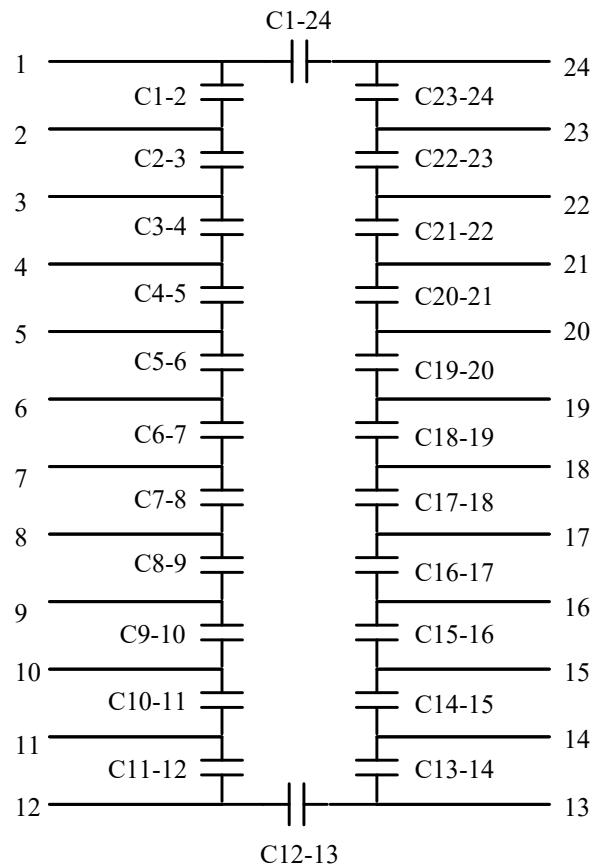


Circuit model for 2-port measurement Between 2 pins

# DIP Example – S-Parameters

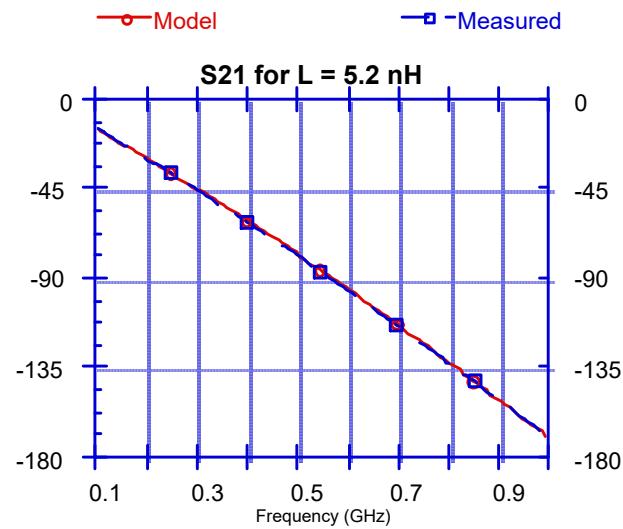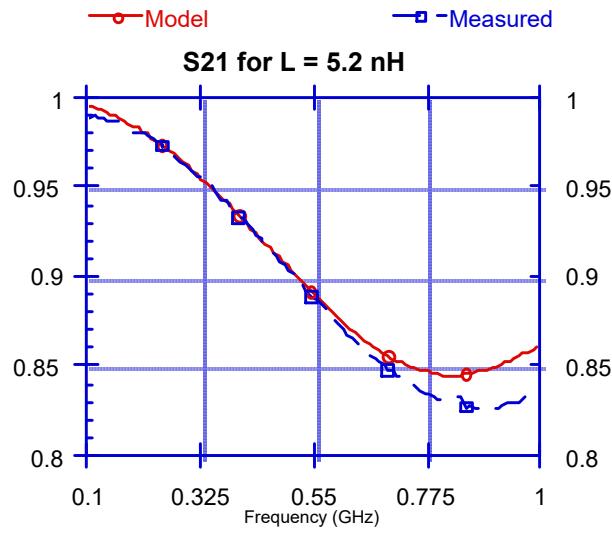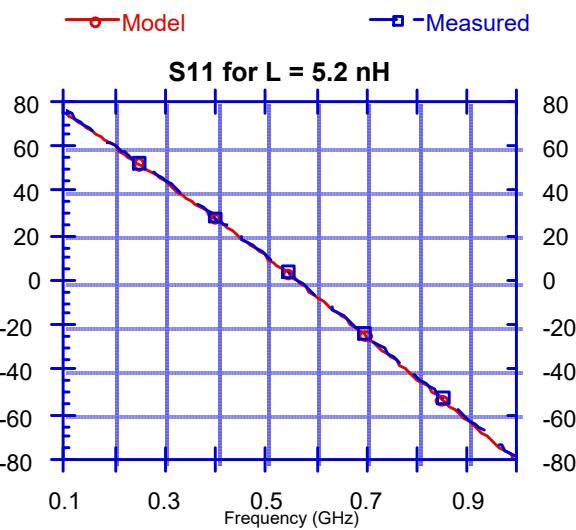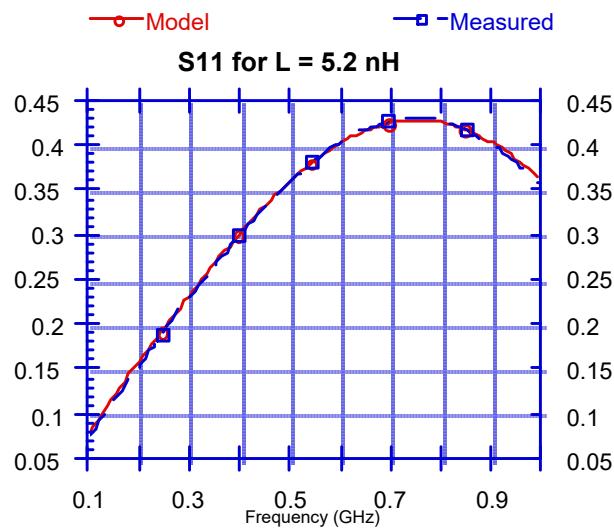

Model and Measured scattering parameters for pins 12-13 for the case were model inductance is assumed to be 5.2 nH.

# DIP Example – Inductance

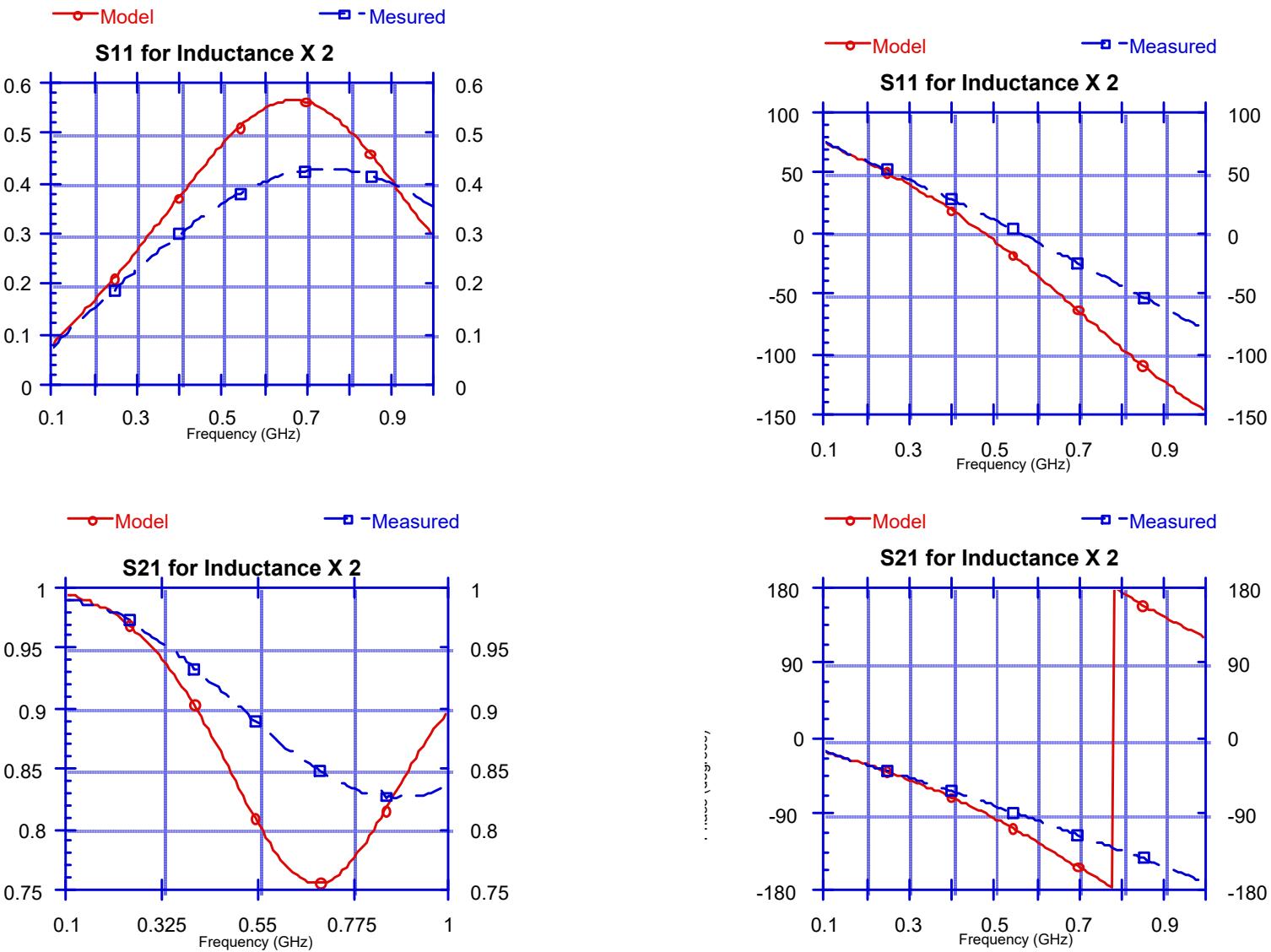

Model and Measured scattering parameters for pins 12-13 for the case were model inductance is assumed to be 10.4 nH.