

# ECE 451

# Advanced Microwave Measurements

## Amplifier Characterization

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jesa@illinois.edu

# Transistor Technology

Transistors are semiconductor devices with 3 terminals. They are used to amplify signals and get voltage, current or power gain

- **Three fundamental types**
  - Bipolar junction transistors (BJT)
  - Junction field effect transistors (JFET)
  - Metal-oxide semiconductor transistors (MOSFET)
- **Technologies**
  - Silicon
  - Compound Semiconductors (GaAs, InP, GaN)


# Models for Transistors

- **Polarity**


- NPN, PNP for BJT
- NMOS, PMOS for MOSFET
- CMOS

**NPN is favorites for BJT**

**NMOS is favorite for MOSFET**

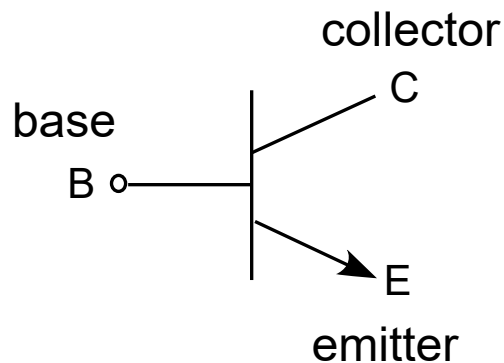

**NPN**

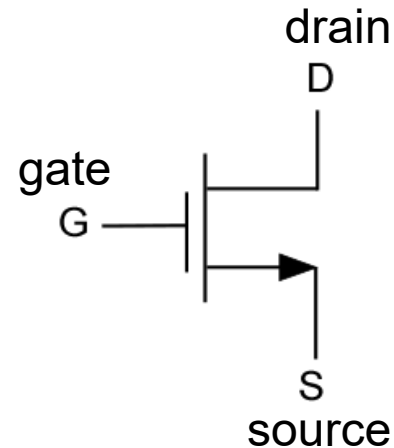


**NMOS**


# Transistor Models

- **Bipolar**
  - Ebers-Moll
  - Gummel-Poon
- **MOSFET**
  - Shichman-Hodges
  - BSIM

# MOSFET Amplifier

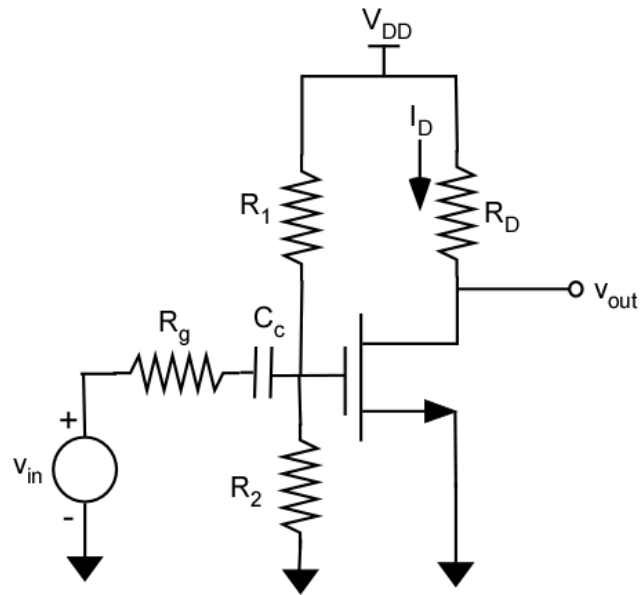


Common Source  
Topology

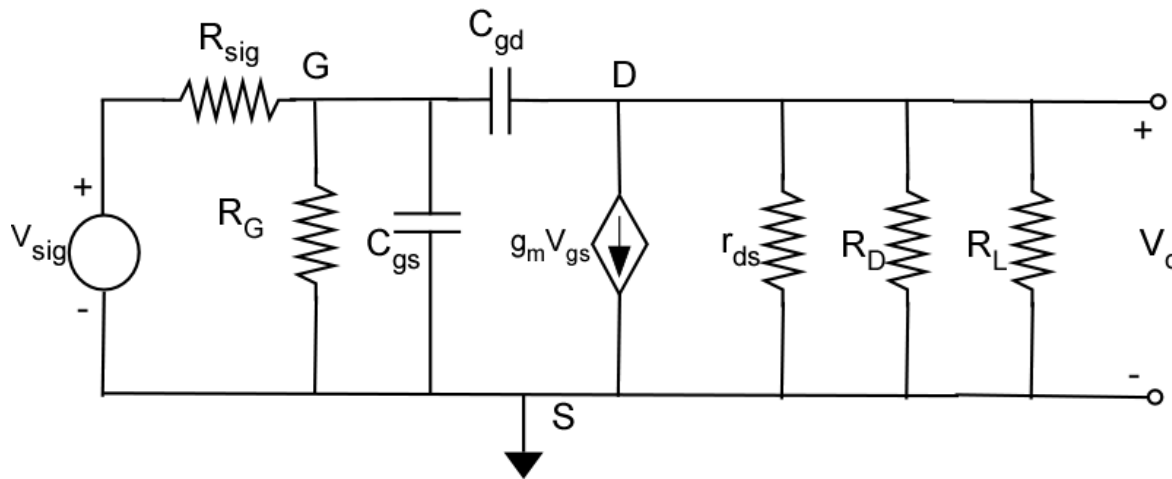


Small-Signal Model

# BJT Amplifier

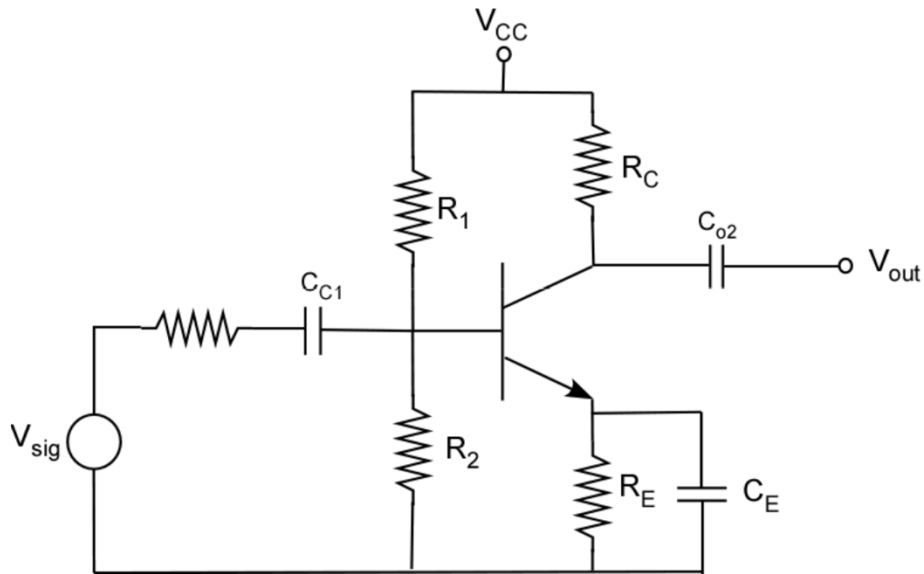


**Common Emitter  
Topology**

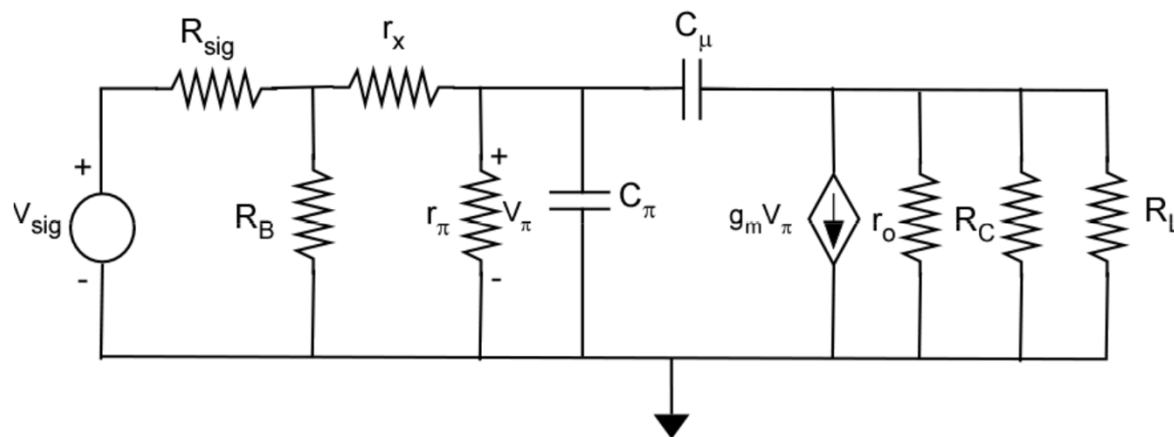

**Small-Signal Model**

# Amplifier Efficiency

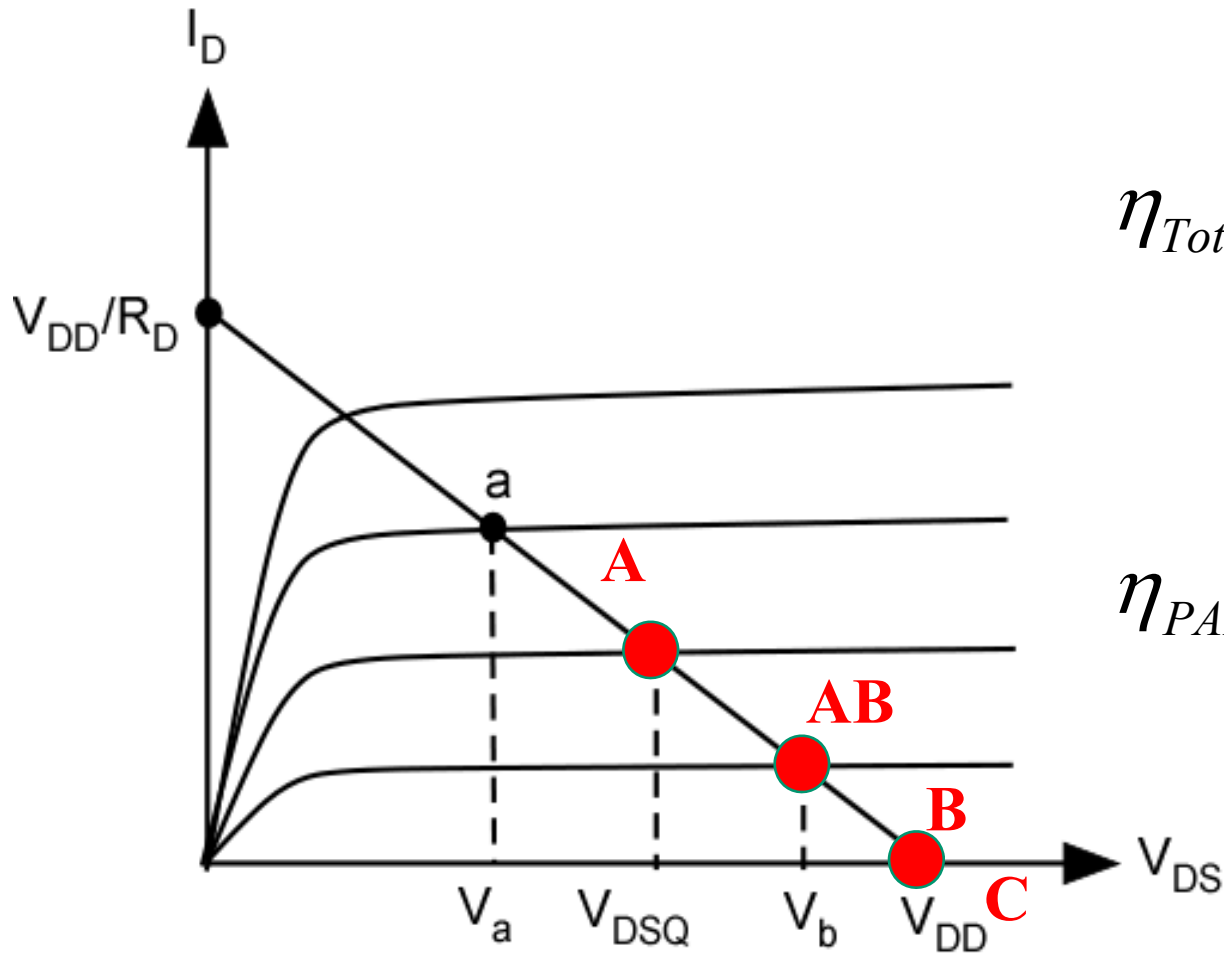

$$\eta_{Total} = \frac{P_{RF,out}}{P_{DC} + P_{RF,in}}$$

$$\eta_{PAE} = \frac{P_{RF,out} - P_{RF,in}}{P_{DC}}$$

# Amplifier Efficiency

For high-gain amplifiers,  $P_{RF,in} \ll P_{DC}$  and

$$\eta_{Total} \approx \eta_{PAE} \approx \eta = \frac{P_{RF,out}}{P_{DC}}$$

Efficiencies are typically between 25% and 50%


- **Class A amplifier**

- Maintain bias so that the transistor is in the middle of the linear range
- Efficiency is reduced because of DC current
- Best linearity
- Choice for small signal (small input) amplification


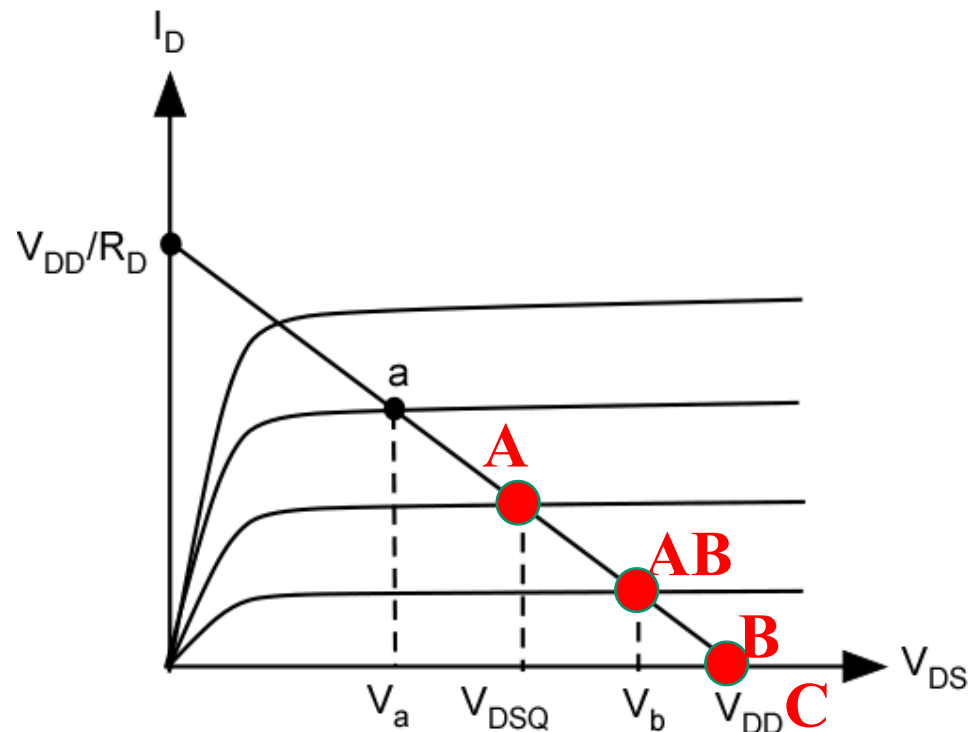
# Amplifier Efficiency


Efficiency is improved by reducing DC power and moving bias point further down the DC load line as in class B, AB and C.


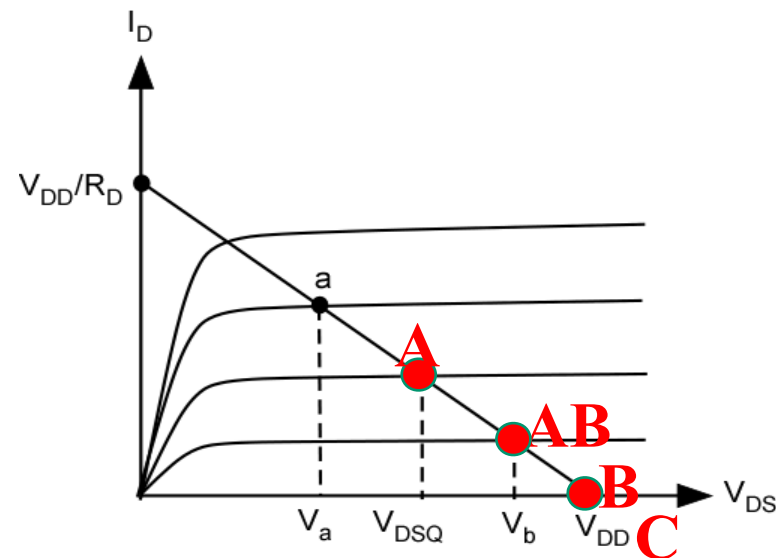
# Amplifier Efficiency


Class B, AB and C present impedance that is a function of the level of the RF signal.

Class B, AB and C are generally not used for broadband applications because of stability concerns



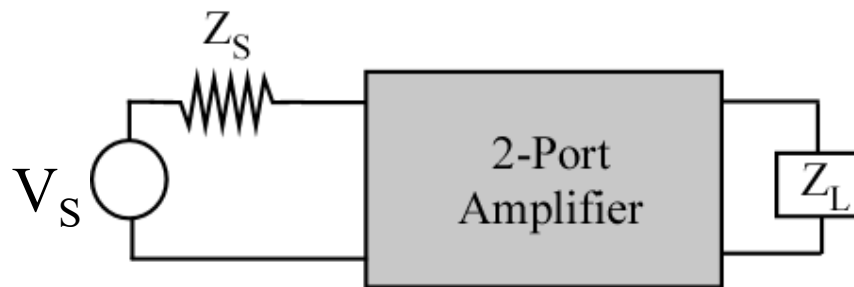
# Linear Amplifiers

The transducer power gain is defined as the power delivered to the load divided by the power available from the source.




$$P_{avs} = \frac{|b_s|^2}{1 - |\Gamma_s|^2}$$

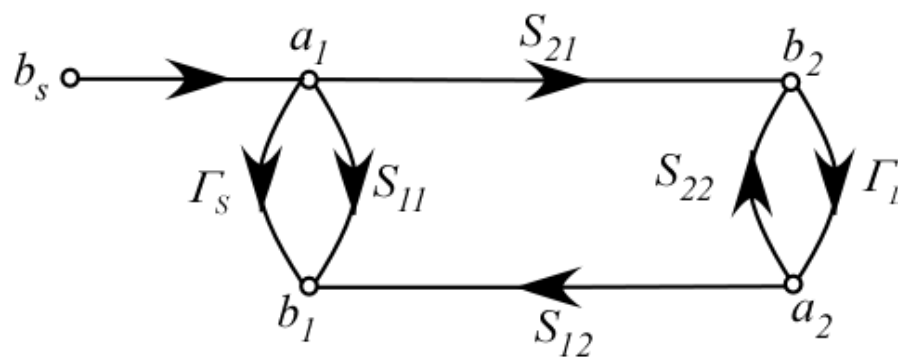

$$b_s = \frac{V_S \sqrt{Z_o}}{Z_S + Z_o}$$

# Linear Amplifiers

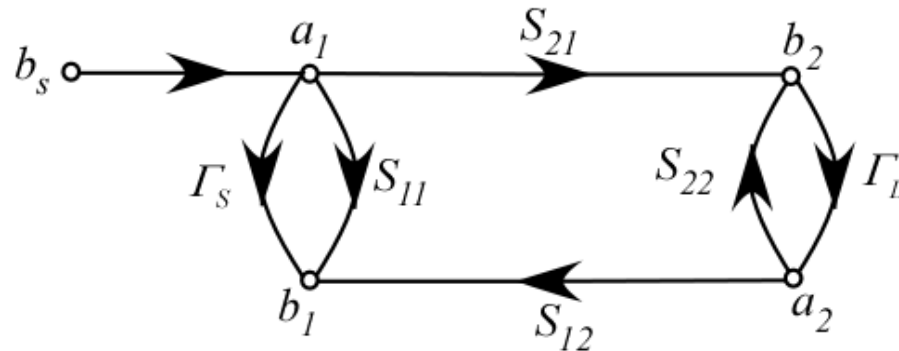

$$G_T = \frac{P_{del}}{P_{avs}} = \frac{|b_2|^2 (1 - |\Gamma_L|^2)}{|b_s|^2 / (1 - |\Gamma_S|^2)}$$

**Non-  
touching  
loop rule  
for power  
available**

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_S)(1 - S_{22}\Gamma_L) - S_{21}S_{12}\Gamma_S\Gamma_L|^2}$$


# Linear Amplifiers

If we assume that the network is unilateral, then we can neglect  $S_{12}$  and get the unilateral transducer gain for  $S_{12}=0$ .

$$G_{TU} = |S_{21}|^2 \frac{(1 - |\Gamma_S|^2)}{|1 - S_{11}\Gamma_S|^2} \frac{(1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2}$$


The first term ( $|S_{21}|^2$ ) depends on the transistor. The other 2 terms depend on the source and the load.

# Linear Amplifiers

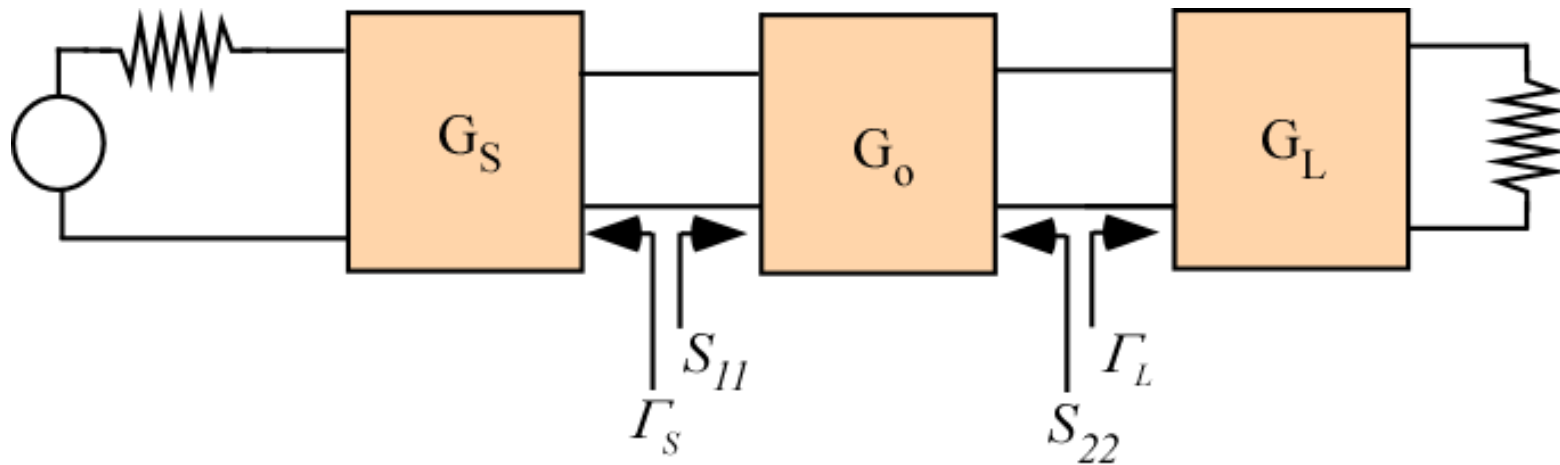


$G_S$  affects the degree of mismatch between the source and the input reflection coefficient of the two-port.

# Linear Amplifiers

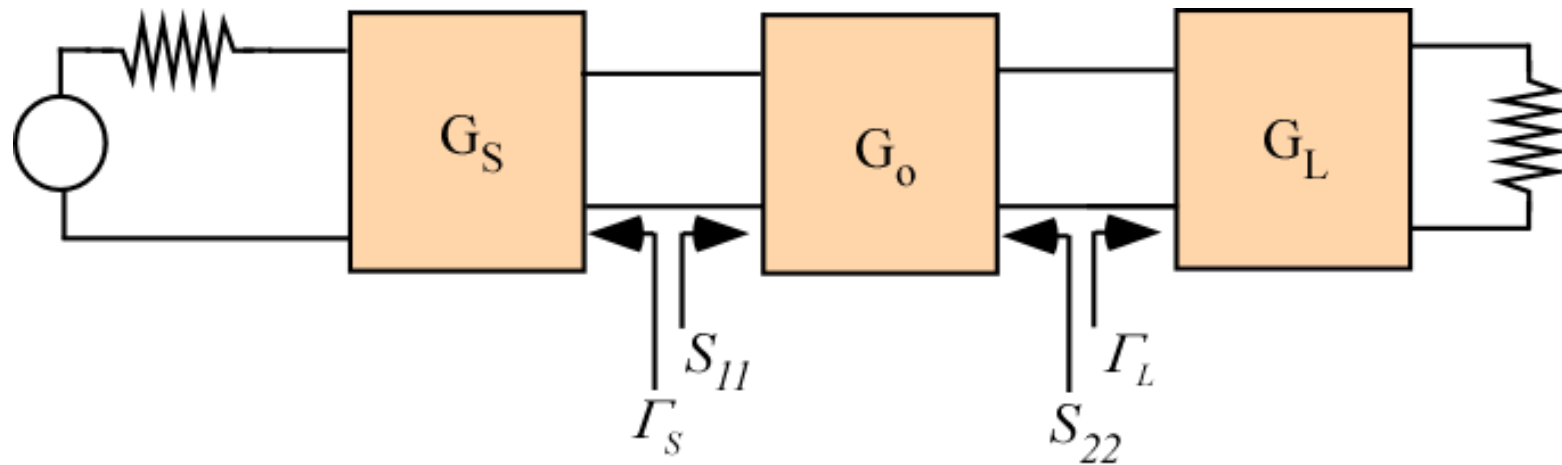

$G_L$  affects the degree of mismatch between the load and the output reflection coefficient of the 2-port.

# Linear Amplifiers

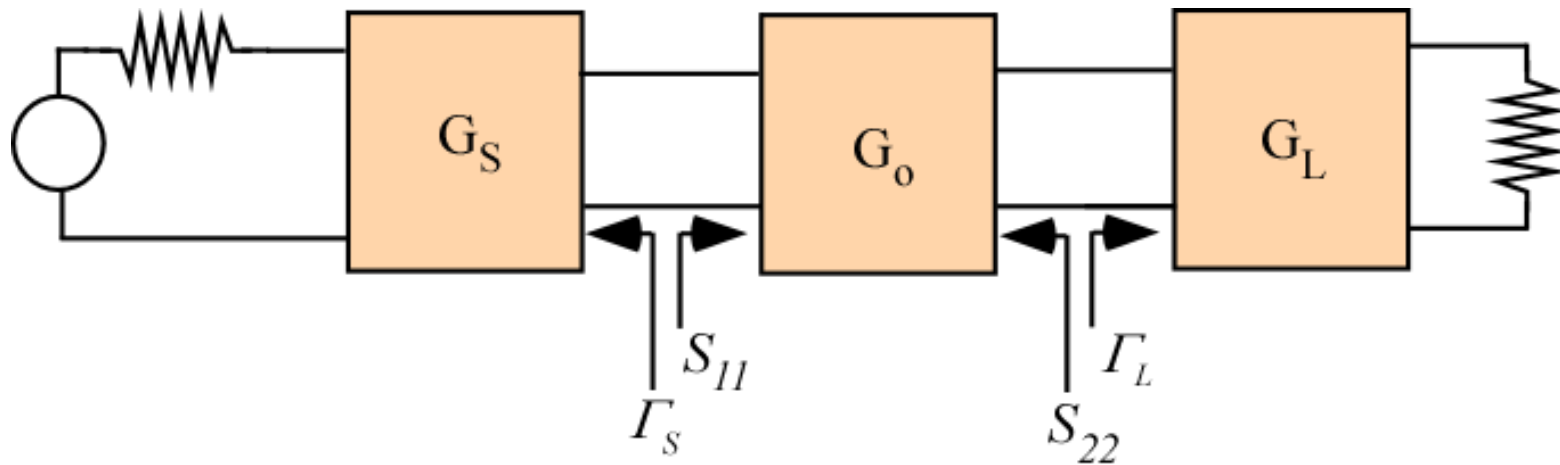


$G_o$  depends on the device and bias conditions




# Linear Amplifiers

Maximum unilateral transducer gain can be accomplished by choosing impedance matching networks such that.

$$\Gamma_S = S_{11}^* \qquad \Gamma_L = S_{22}^*$$
$$G_{UMAX} = \frac{1}{1 - |S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - |S_{22}|^2}$$

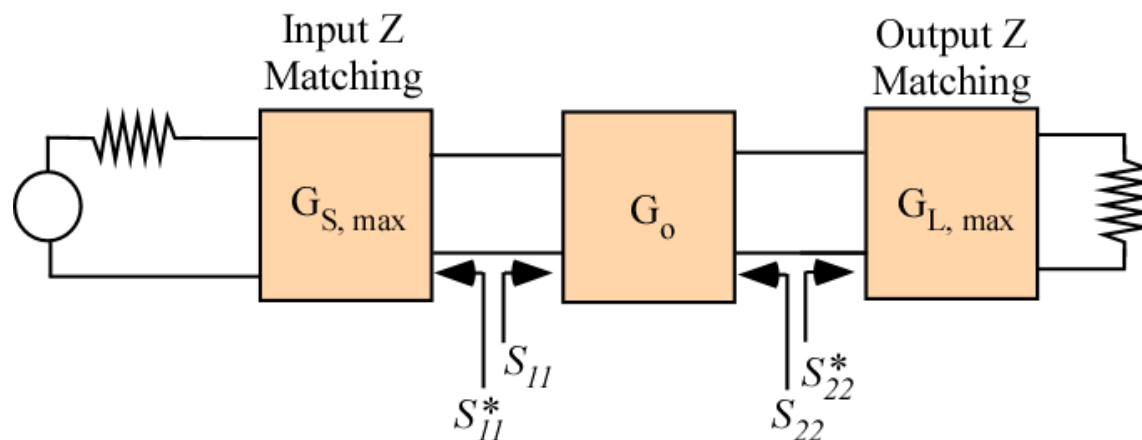

# Linear Amplifiers

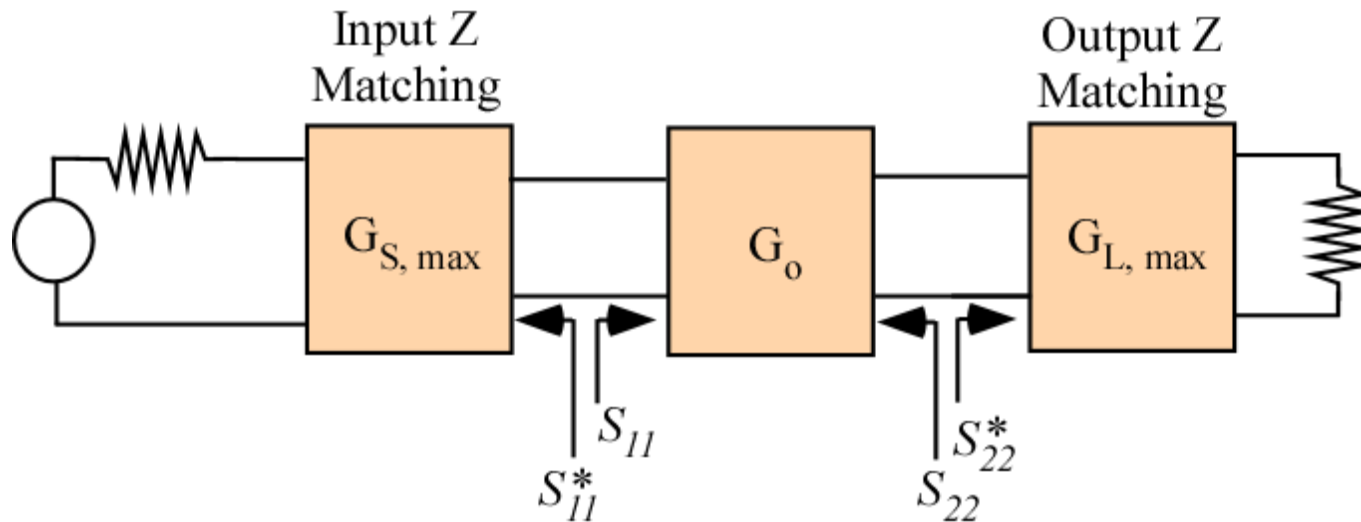


$$G_{UMAX} (dB) = G_{S_{\max}} (dB) + G_o (dB) + G_{L_{\max}} (dB)$$

**For  $\Gamma_S = S_{11}^*$ ,  $G_S$  is a maximum**

**For  $|\Gamma_S| = 1$ ,  $G_S$  is 0**

# Linear Amplifiers


For arbitrary values of  $G_S$  between these extremes, the solutions for  $|\Gamma_S|$  lies on a circle  
→ Gain circles

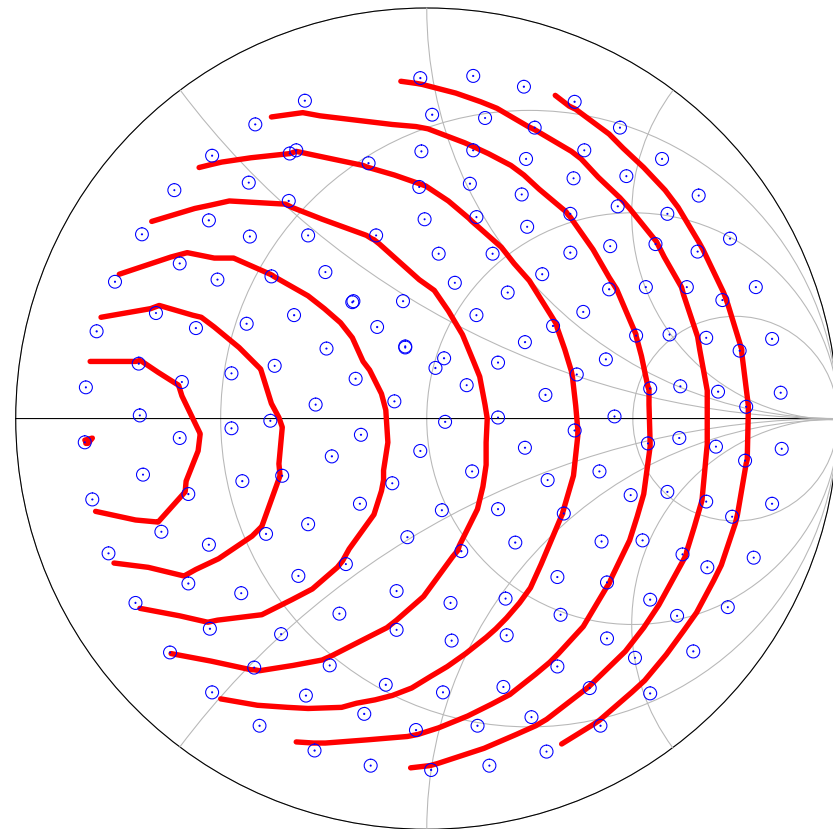


# Classification of Amplifiers

Class A - Amplifier is biased at current  $I_C$  greater than the amplitude of the signal. Transistor conducts for the entire cycle of the signal  $\rightarrow$  conduction angle =  $360^\circ$ .

**Class A**

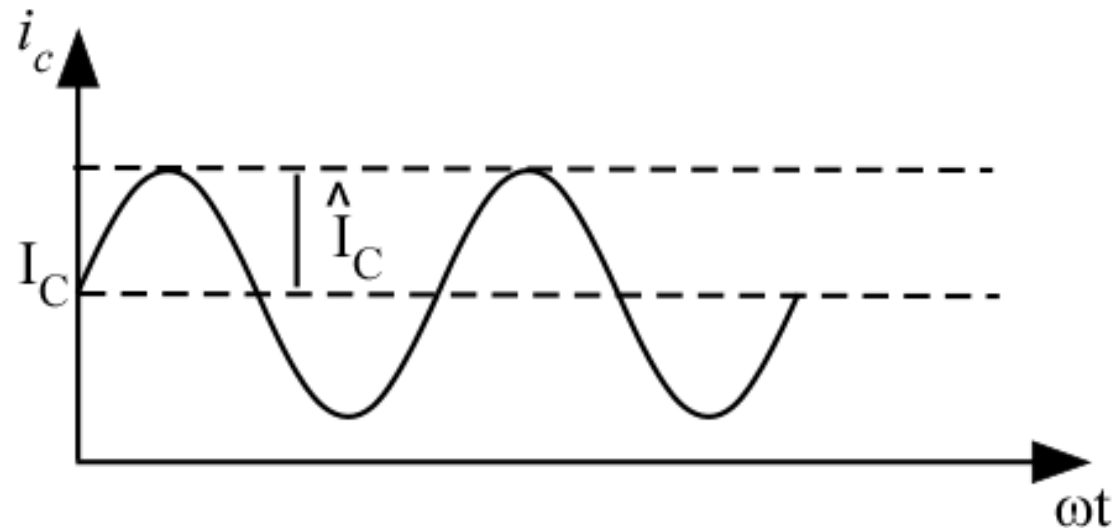

# Classification of Amplifiers

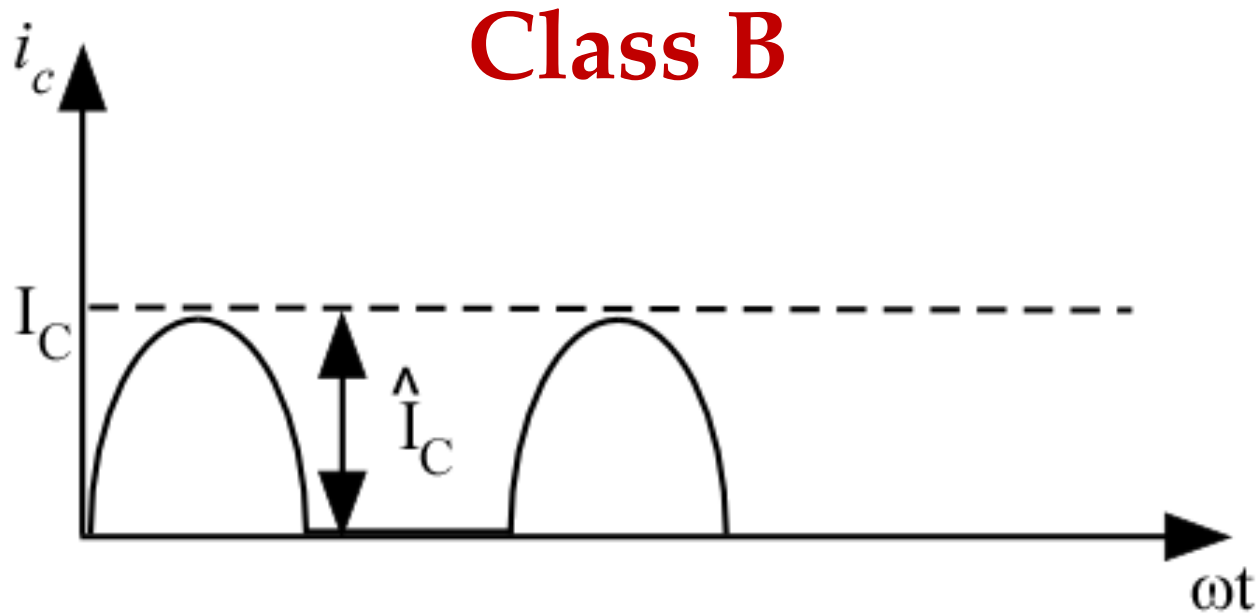

In class B stage, the transistor is biased for zero dc current


# Classification of Amplifiers

The amplifier conducts for only half of the cycle of the input sine wave. Conduction angle =  $180^\circ$  Negative halves supplied by another transistor operating in class B

An intermediate class between A and B is called class AB

AB involves biasing the transistor at a nonzero DC current much smaller than the peak current

# Classification of Amplifiers

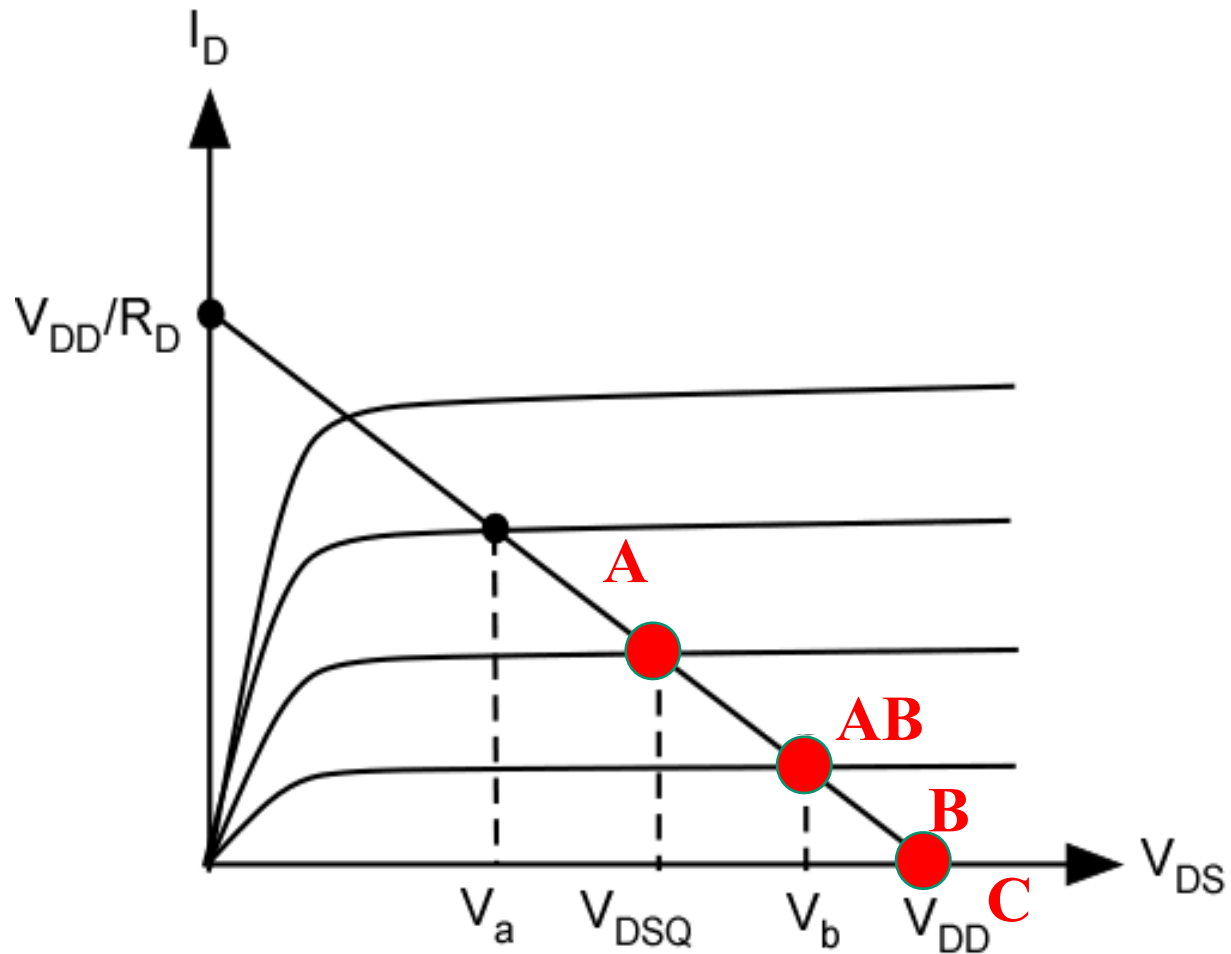


# Distortion and Nonlinearities

Distortion occurs when the output signal from an amplifier approaches the extremes of the load line and the output is no longer an exact replica of the input.

The ideal amplifier follows a linear relationship. Distortion leads to a deviation from this linear relationship




# Distortion and Nonlinearities

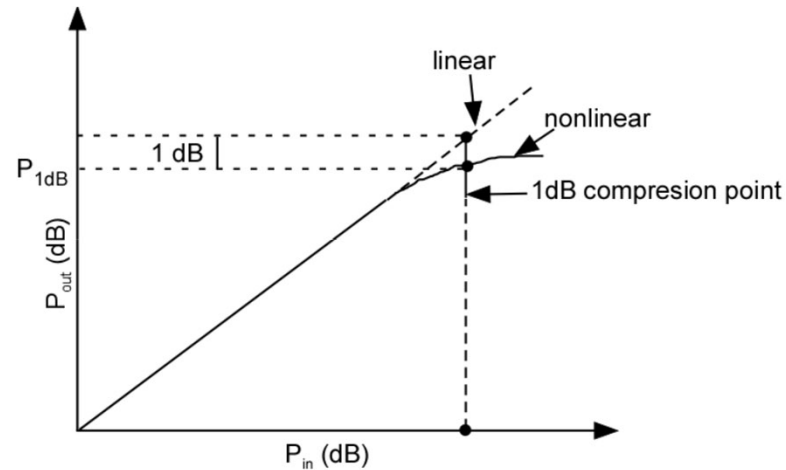


The *1dB compression point* is the point where the difference between the extrapolated linear response exceeds the actual gain by 1dB.  $P_{1dB}$  is the power output at the 1dB compression point and is the most important metric of distortion.

# Distortion and Nonlinearities

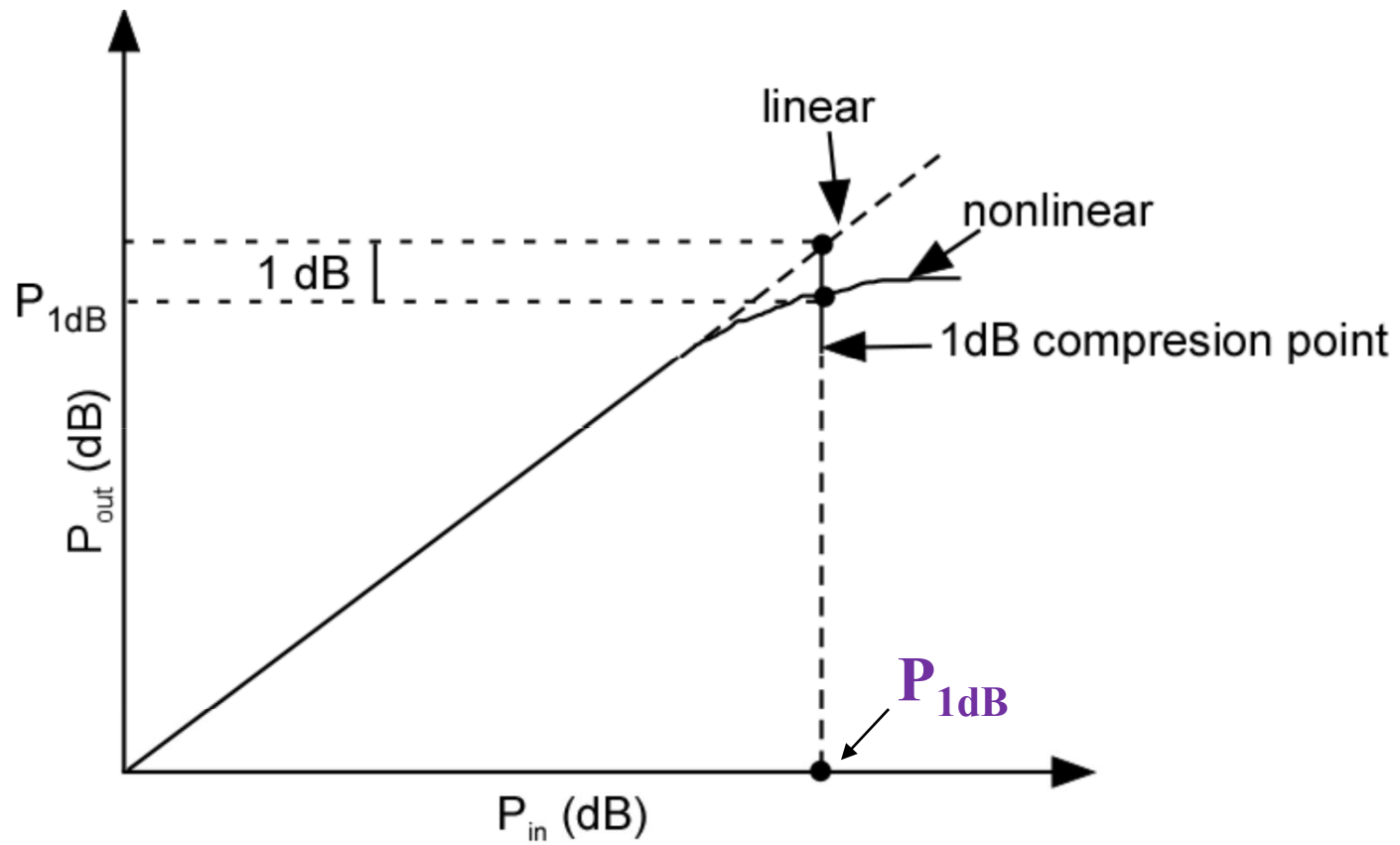

## AM-AM Distortion

# Distortion and Nonlinearities

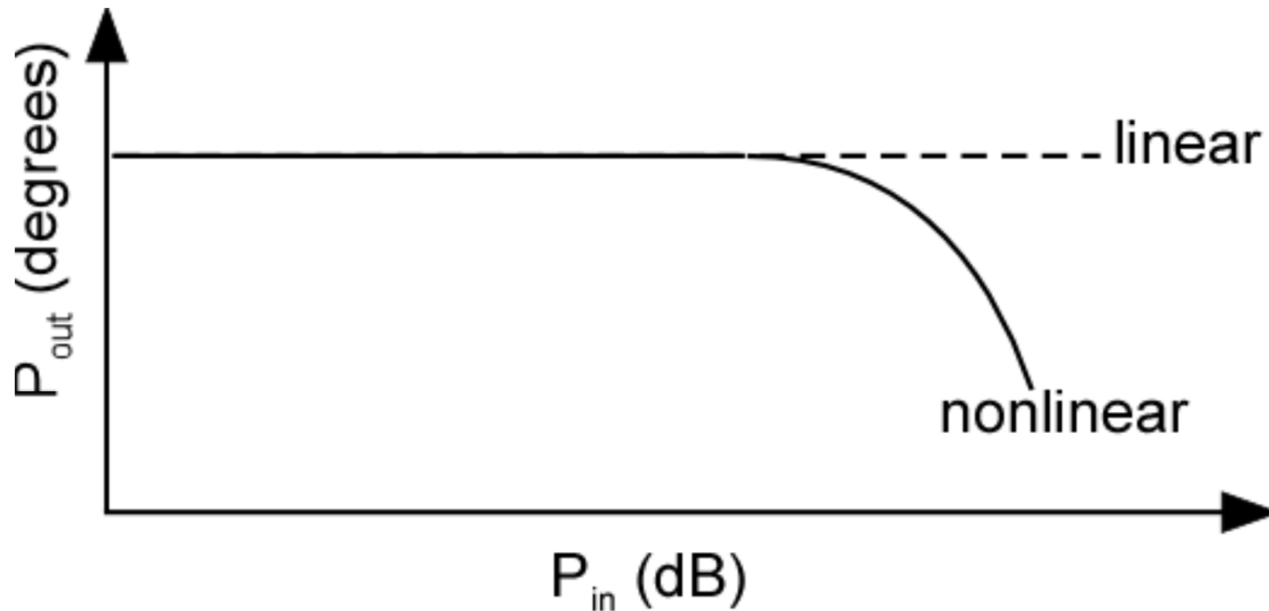

## AM-PM Distortion

# Distortion and Nonlinearities

AM-AM distortion is generally more significant

Distortion is a result of nonlinearities in the response of an amplifier. One possible model for the response is:

$$v_o = k_1 v_i + k_2 v_i^2 + k_3 v_i^3 + \dots$$

When the input signal is large enough the higher order terms become significant.


# Single-Tone Excitation

$$v_o = k_1 v_i + k_2 v_i^2 + k_3 v_i^3$$

$$v_i(t) = a_1 \cos \omega_1 t$$

$$v_o(t) = \frac{1}{2} k_2 a_1^2 + \left( k_1 a_1 + \frac{3}{4} k_3 a_1^2 \right) \cos \omega_1 t + \frac{1}{2} k_2 a_1^2 \cos 2\omega_1 t + \frac{1}{4} k_3 a_1^3 \cos 3\omega_1 t$$

# Single-Tone Excitation

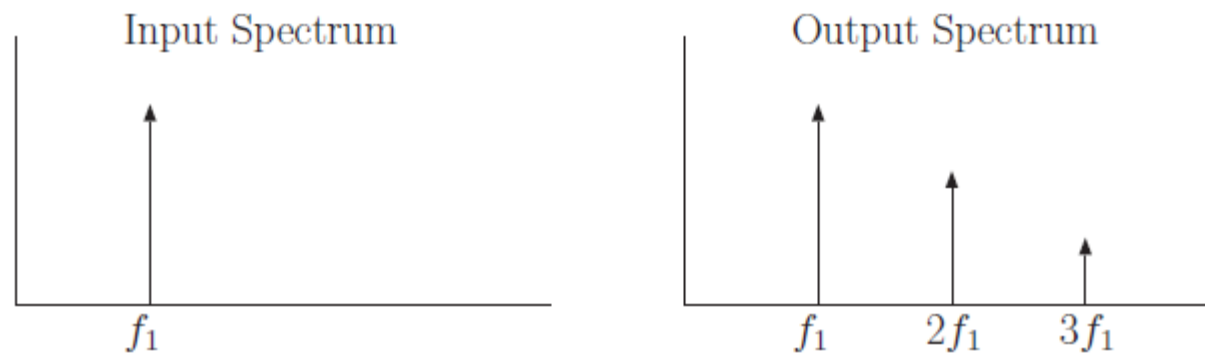

**Single-tone excitation produces harmonics of input frequency**

# Distortion and Nonlinearities

If the input is a sine wave, the output will contain harmonics of the input. That is the output will have frequency components that are integer multiples of the fundamental (CW) sine wave input signal

When the input signal is a two-tone signal (modulated signal), additional tones will appear at the output and we say that the distortion produces intermodulation products (IMP)

# Two-Tone Excitation


$$v_o = k_1 v_i + k_2 v_i^2 + k_3 v_i^3$$

$$v_i(t) = a_1 \cos \omega_1 t + a_2 \cos \omega_2 t$$

$$v_o(t) = k_1 [a_1 \cos \omega_1 t + a_2 \cos \omega_2 t] +$$
$$k_2 \left[ \frac{1}{2} (a_1^2 + a_2^2) + \frac{1}{2} a_1^2 \cos 2\omega_1 t + \frac{1}{2} a_2^2 \cos 2\omega_2 t \right. +$$
$$\left. + a_1 a_2 \cos(\omega_1 + \omega_2)t + a_1 a_2 \cos(\omega_1 - \omega_2)t \right] +$$
$$\frac{1}{4} k_3 \left[ \frac{1}{4} a_1^3 \cos 3\omega_1 t + \frac{1}{4} a_2^3 \cos 3\omega_2 t \right. +$$
$$\left. + \frac{3}{4} a_1 a_2^2 (\cos(2\omega_2 - \omega_1)t + \cos(2\omega_2 + \omega_1)) \right. +$$
$$\left. + \frac{3}{4} a_1^2 a_2 (\cos(2\omega_1 - \omega_2)t + \cos(2\omega_1 + \omega_2)) \right]$$



# Two-Tone Excitation

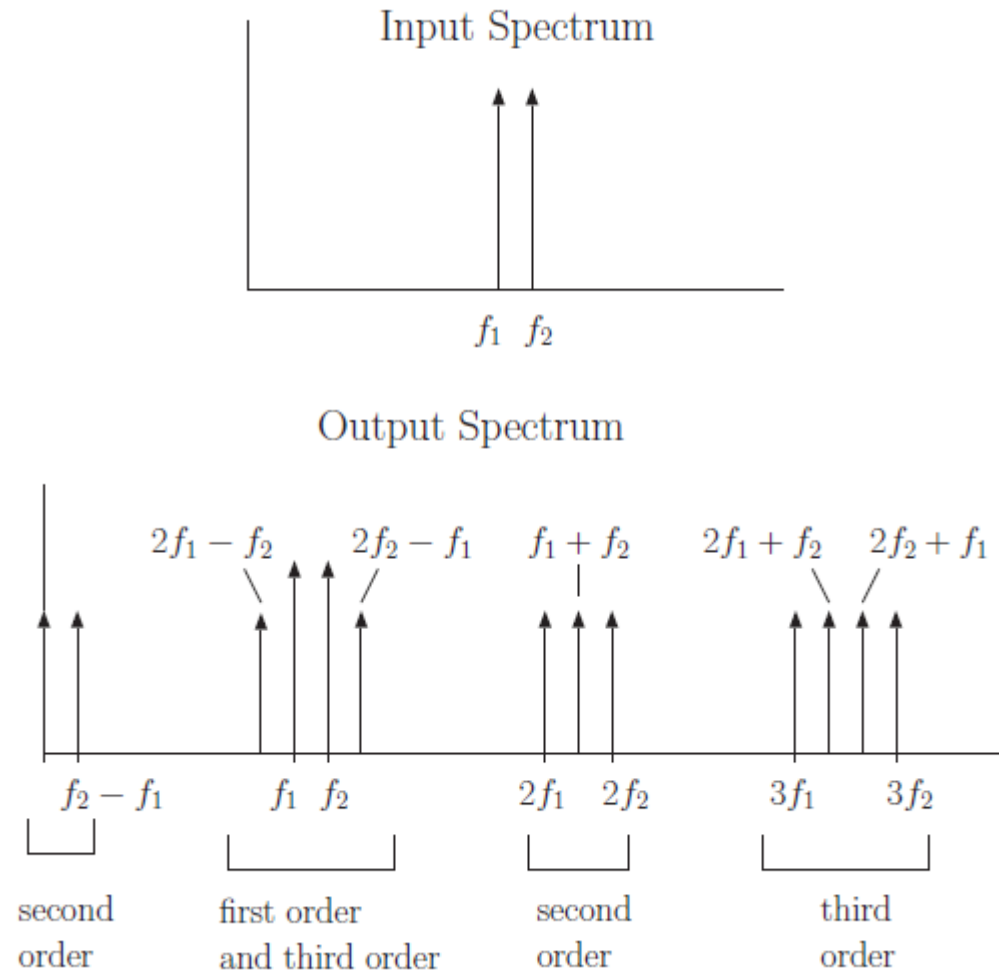


**Two-tone excitation produces intermodulation**

# Distortion and Nonlinearities

If  $f_1$  and  $f_2$  are the frequencies associated with the two signals, the output will have components at  $f_3$  and  $f_4$  where

$$f_3 = 2f_1 - f_2 \quad \text{and} \quad f_4 = 2f_2 - f_1$$

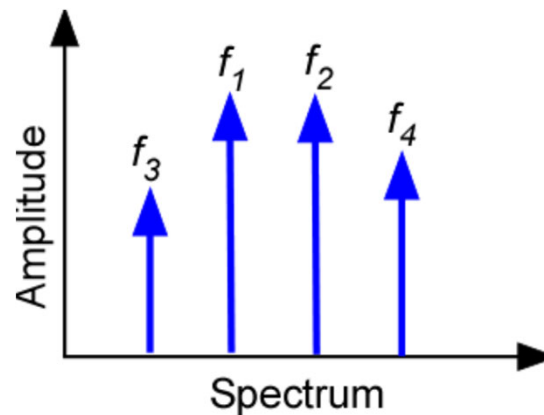
are known as the lower and upper IM3 respectively.


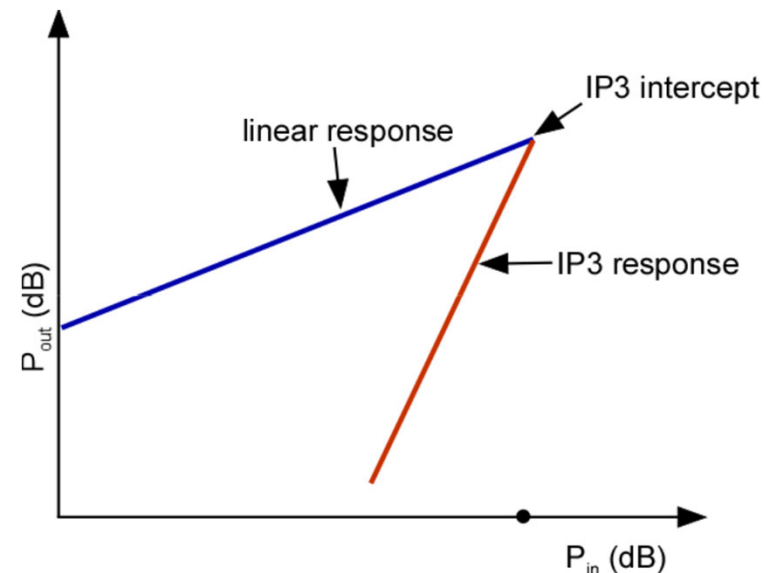
# Distortion and Intermodulation

At low power, before compression the fundamental has a response with 1:1 slope with respect to the input

The IP3 response varies as the *cube* of the level of input tones. The IP3 has a 3:1 logarithmic slope with respect to the input.




# Distortion and Intermodulation

The point of intersection of the extrapolated linear output (of power  $P_o$ ) and third order (IP3) of power  $P_{IP3}$  is called the third-order intercept point which is a key parameter

- Harmonics can be filtered out by filters
- Intermodulation distortion cannot be filtered out because they are in the main passband

# Distortion and Intermodulation

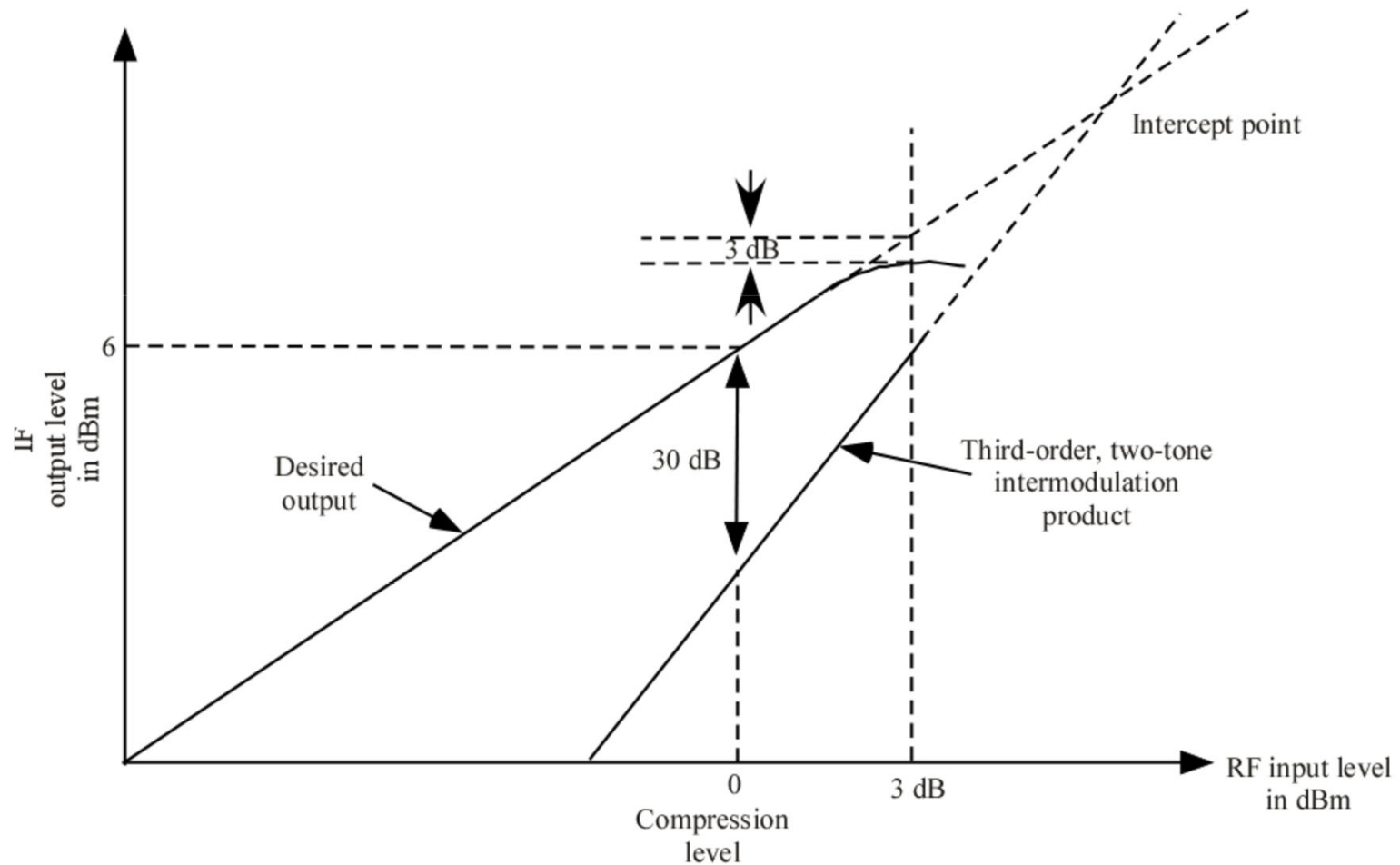



# Power Transistor Characterization

Because of nonlinearities, scattering parameters cannot be used to characterize power devices. Other techniques must be used.

- **Methods**
  - Load Pull
  - X-Parameters

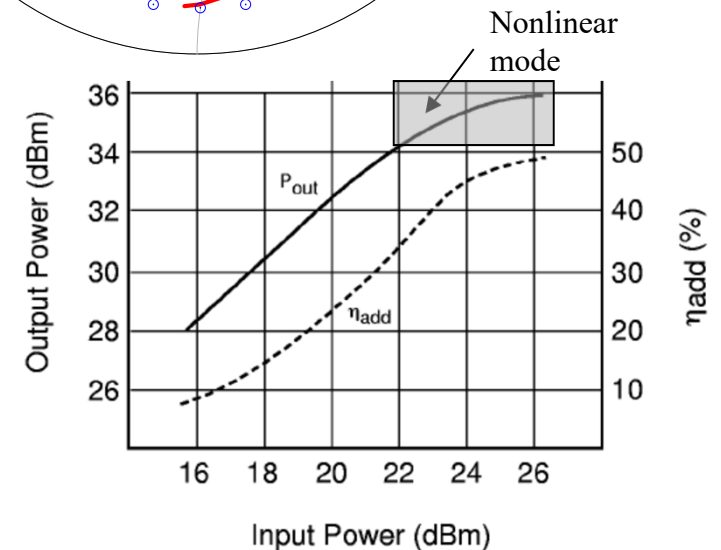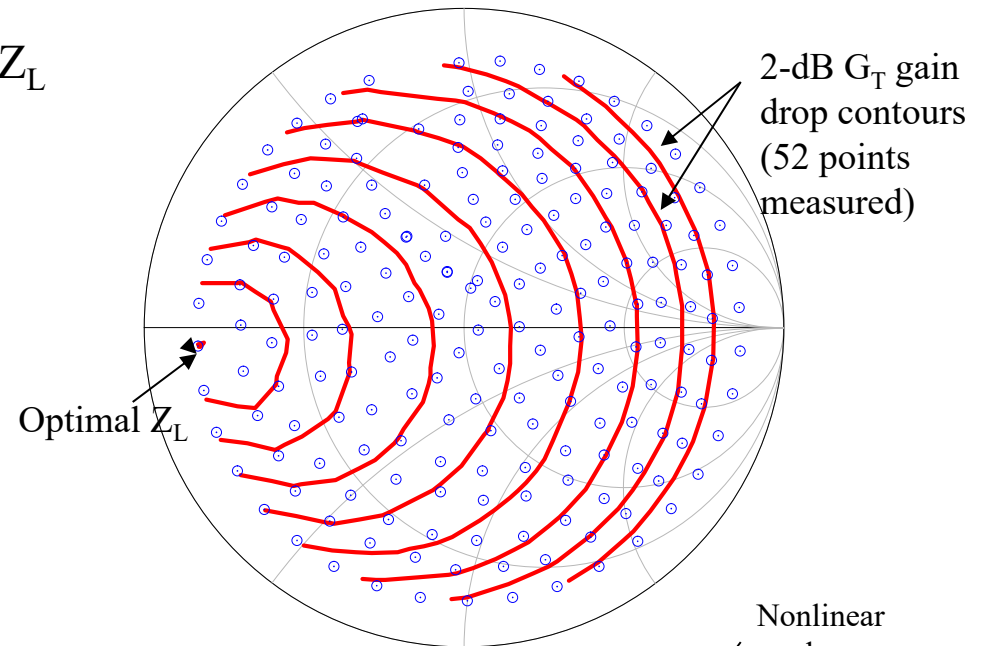
# Load-Pull Measurements

- Varying (“pulling”) load impedance  $Z_L$  seen by an active device under test
- Measuring performance metrics of DUT at each  $Z_L$  point:
  - Transducer Gain (as shown)
  - Power-added Efficiency
  - 1-dB Gain Compression Point
  - Noise Figure
  - ...
- Not needed for linear devices
  - Performance with any  $Z_L$  determined by measuring small-signal S-parameters
- Important for characterizing devices operating in large-signal (nonlinear) mode
  - Operating point (and thereby performance) may change for different loads


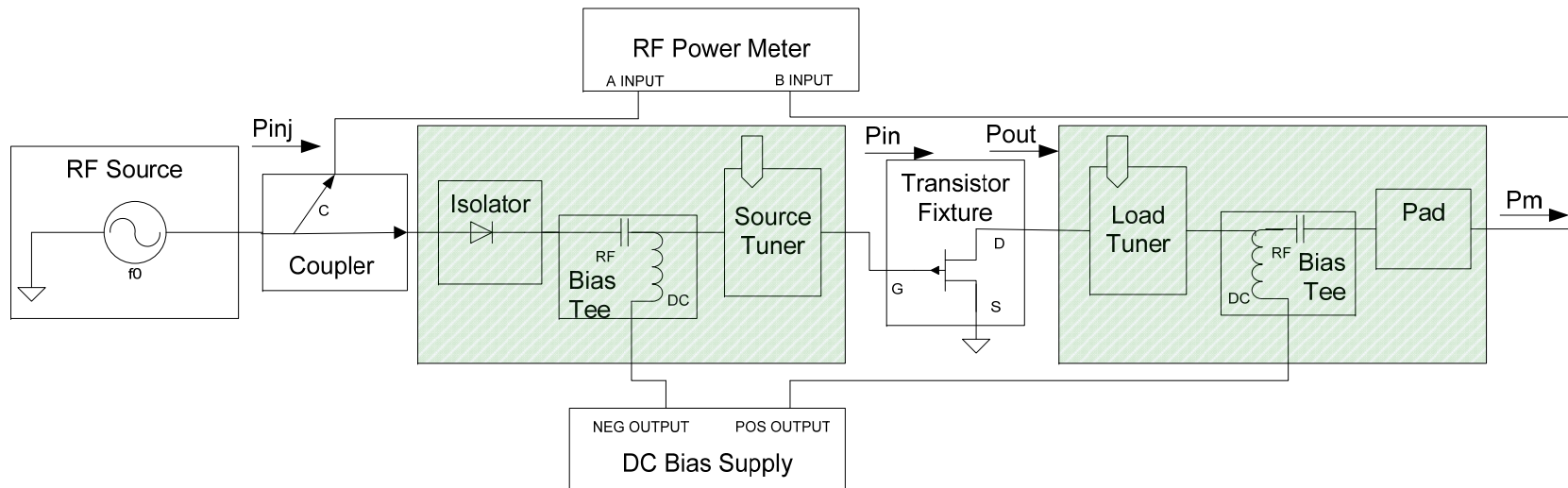
# Manual Load-Pull Setup

- First set up source tuner for maximum gain, then fix its position
- For each (X,Y) position of the load tuner:
  1. Measure injected power  $P_{inj}$ , delivered power  $P_m$
  2. Measure S-parameters of source and load circuitry (shaded boxes)
  3. Move the reference plane to the DUT input and output:
    - Calculate input and output power loss (due to mismatch) from measured S-parameters
    - Obtain  $P_{in}$ ,  $P_{out}$  by correcting  $P_{inj}$ ,  $P_m$  for power losses
  4. Solve for transducer gain  $G_T = P_{out}/P_{in}$



- Done at a constant input frequency  $f_0$  - harmonic measurements also possible
- Large number of points needed for each frequency
  - Measurements are usually automated