

# ECE 453

# Wireless Communication Systems


## Amplifiers

Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
jesa@Illinois.edu
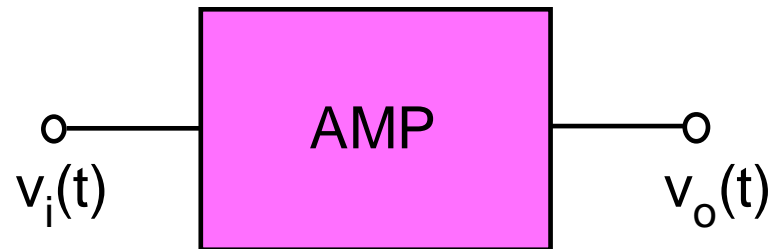
# Amplifiers

- **Definitions**

- Used to increase the amplitude of an input signal to a desired level
- This is a fundamental signal processing function
- Must be linear (free of distortion) – Shape of signal preserved




$v_o(t) = Av_i(t)$ , where  $A$  is the voltage gain

Voltage Gain:  $A_v = \frac{v_o}{v_i}$

Power Gain:  $A_p = \frac{\text{Load Power } (P_L)}{\text{Input Power } (P_I)}$
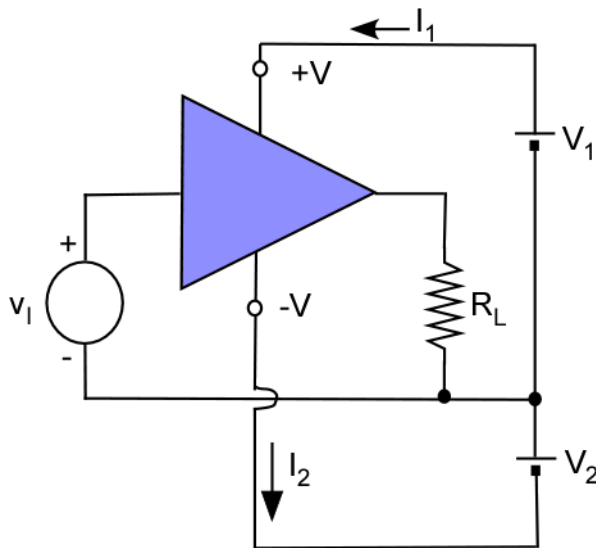
# Amplifiers

Since output associated with the signal is larger than the input signal, power must come from DC supply




$$P_{DC} = V_1 I_1 + V_2 I_2$$

$$P_{DC} + P_I = P_L + P_{dissipated}$$

$$\eta = \frac{P_L}{P_{DC}} \times 100 = \text{Power Efficiency}$$
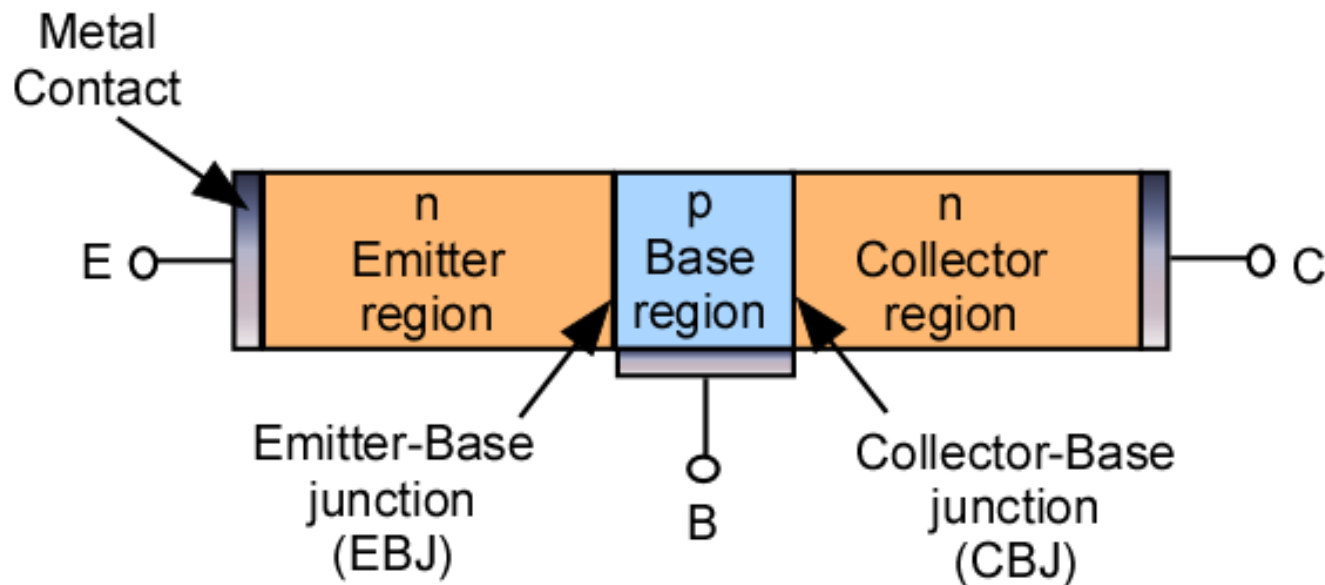
# Bipolar Junction Transistor


- **Bipolar Junction Transistor (BJT)**
  - First Introduced in 1948 (Bell labs)
  - Consists of 2 pn junctions
  - Has three terminals: emitter, base, collector




# BJT – Modes of Operation

Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Forw. Active	Forward	Reverse
Rev. Active	Reverse	Forward
Saturation	Forward	Forward


# Structure of BJT's

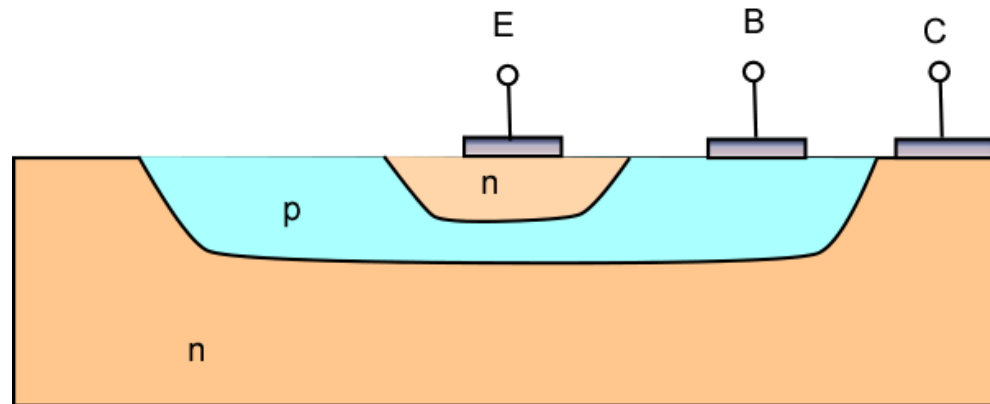


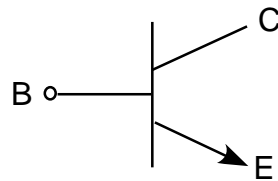
**Collector surrounds emitter region → electrons will be collected**




# BJT Transistor Polarities

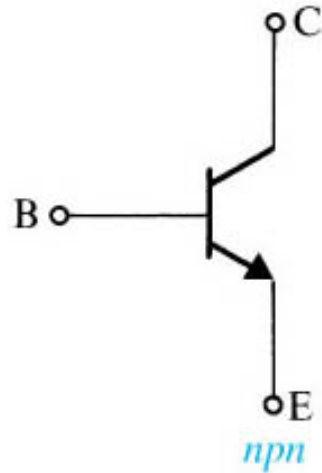

**NPN**

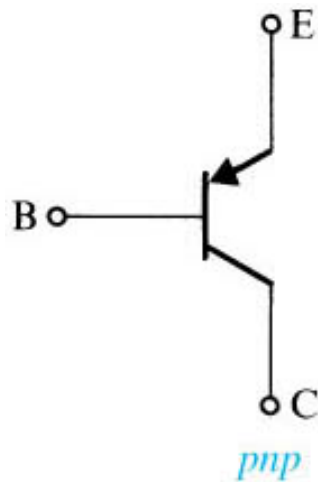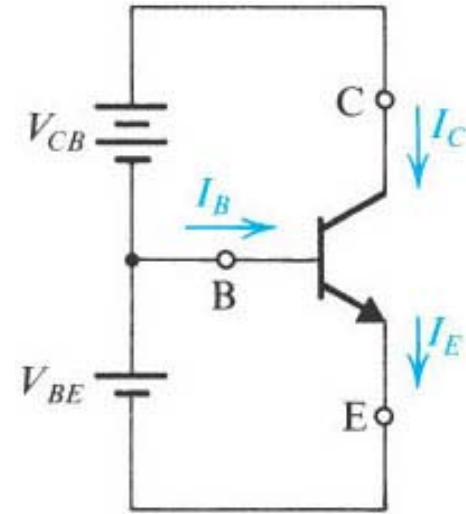


**PNP**

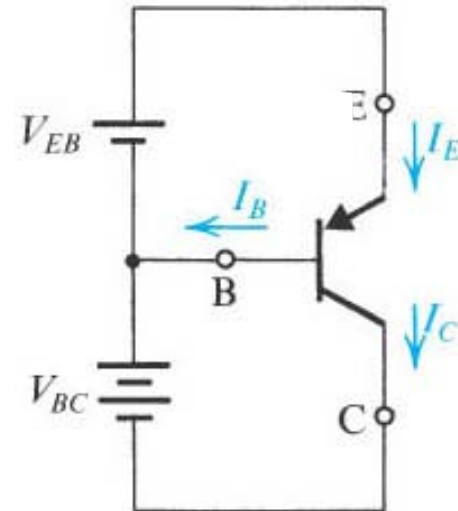

# Ebers-Moll Model

## NPN Transistor

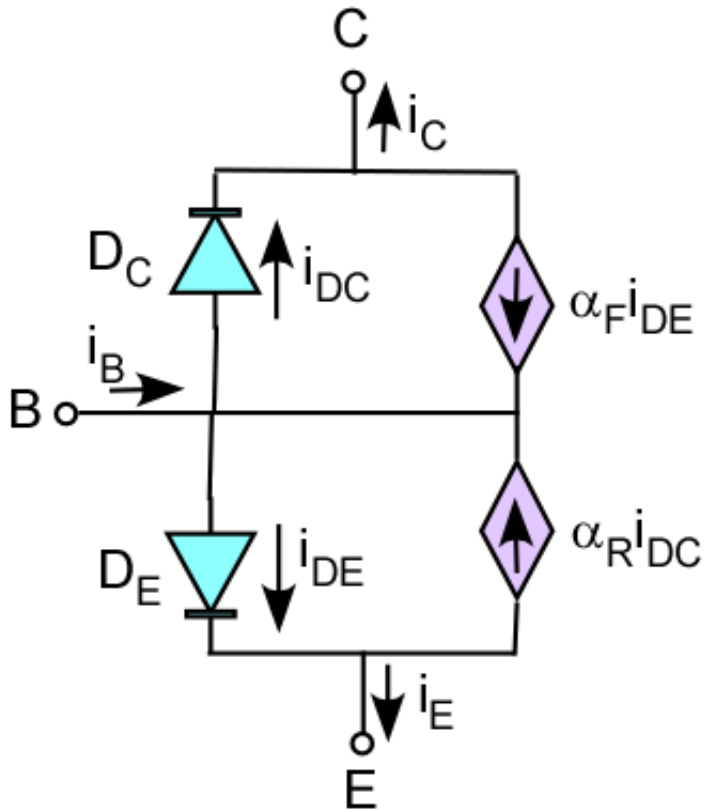

$$i_E = \left( \frac{I_S}{\alpha_F} \right) \left( e^{v_{BE}/V_T} - 1 \right) - I_S \left( e^{v_{BC}/V_T} - 1 \right)$$

$$i_C = I_S \left( e^{v_{BE}/V_T} - 1 \right) - \left( \frac{I_S}{\alpha_R} \right) \left( e^{v_{BC}/V_T} - 1 \right)$$

$$i_B = \left( \frac{I_S}{\beta_F} \right) \left( e^{v_{BE}/V_T} - 1 \right) + \left( \frac{I_S}{\beta_R} \right) \left( e^{v_{BC}/V_T} - 1 \right)$$


$$\beta_F = \frac{\alpha_F}{1 - \alpha_F}$$

$$\beta_R = \frac{\alpha_R}{1 - \alpha_R}$$

Describes BJT operation in all of its possible modes




# Biassing Bipolar Transistors

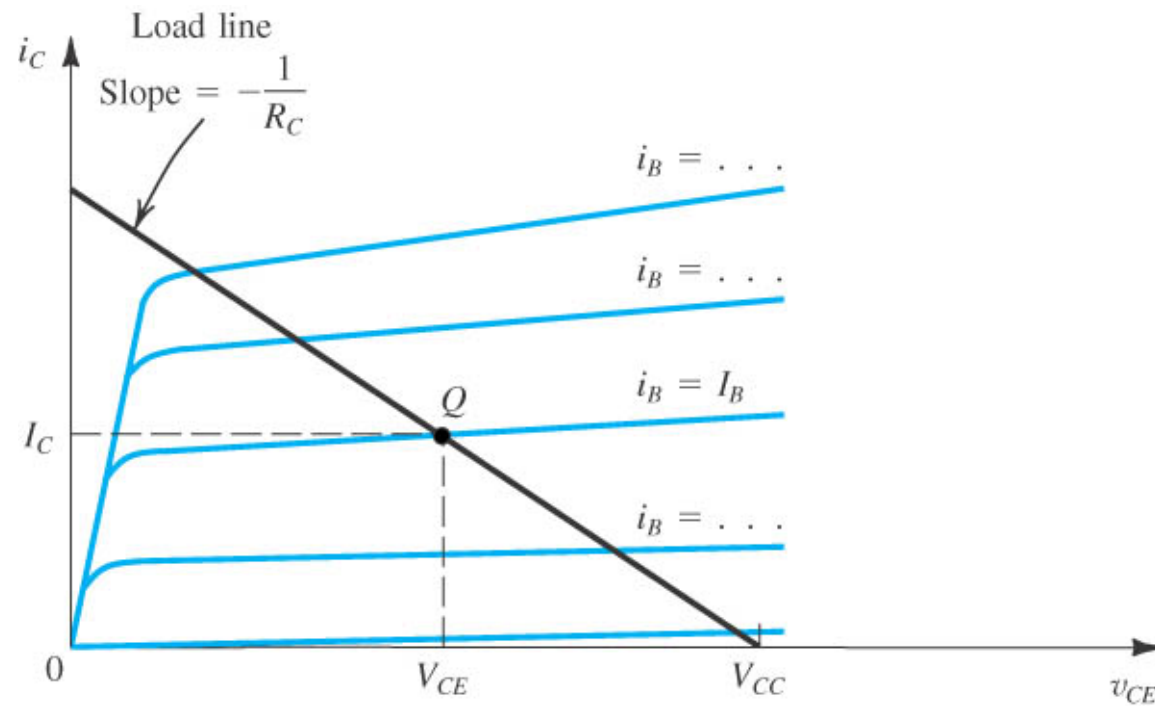
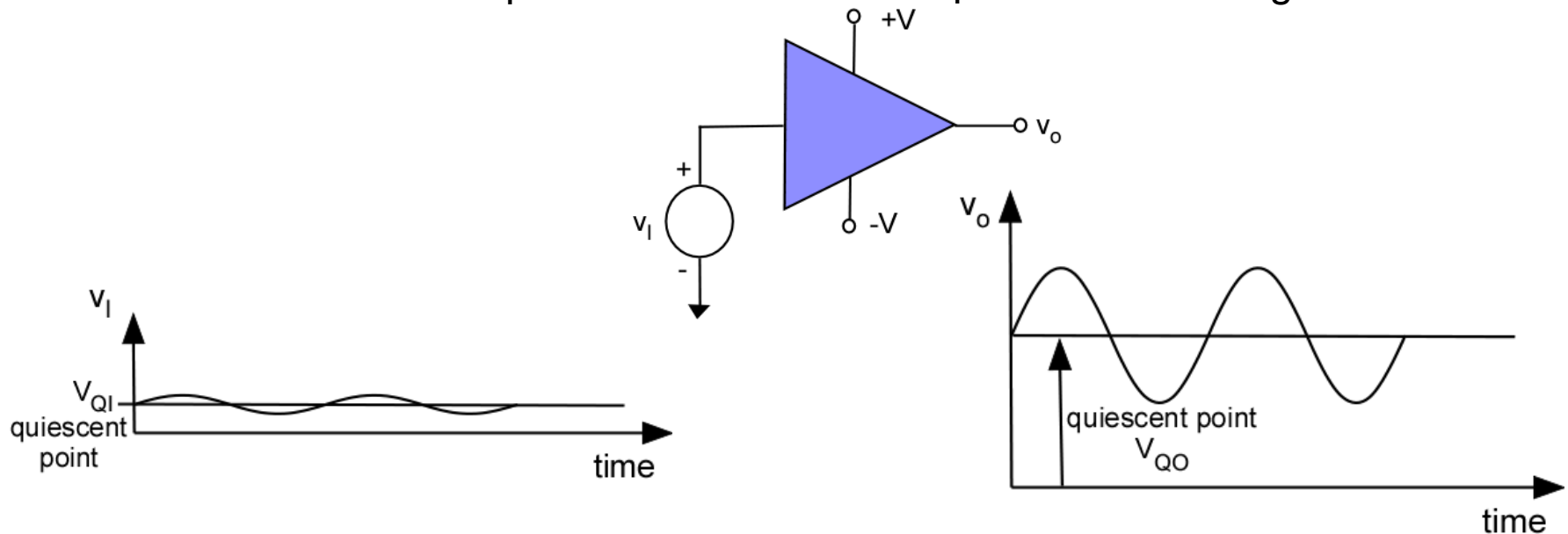
# Biassing of Amp

Bias will provide quiescent points for input and output about which variations will take place. Bias maintain amplifier in active region.



$$V_I(t) = V_{QI} + v_I(t)$$

$$V_o(t) = V_{QO} + v_o(t)$$

$$v_o(t) = A_v v_I(t)$$

$$A_v = \left. \frac{dv_o}{dv_I} \right|_{at Q}$$


**Amplifier characteristics are determined by bias point**

# Small-Signal Model

- **What is a small-signal incremental model?**
  - Equivalent circuit that only accounts for signal level fluctuations about the DC bias operating points
  - Fluctuations are assumed to be small enough so as not to drive the devices out of the proper range of operation
  - Assumed to be linear
  - Derives from superposition principle


# BJT Bias

## 2. Emitter Bias

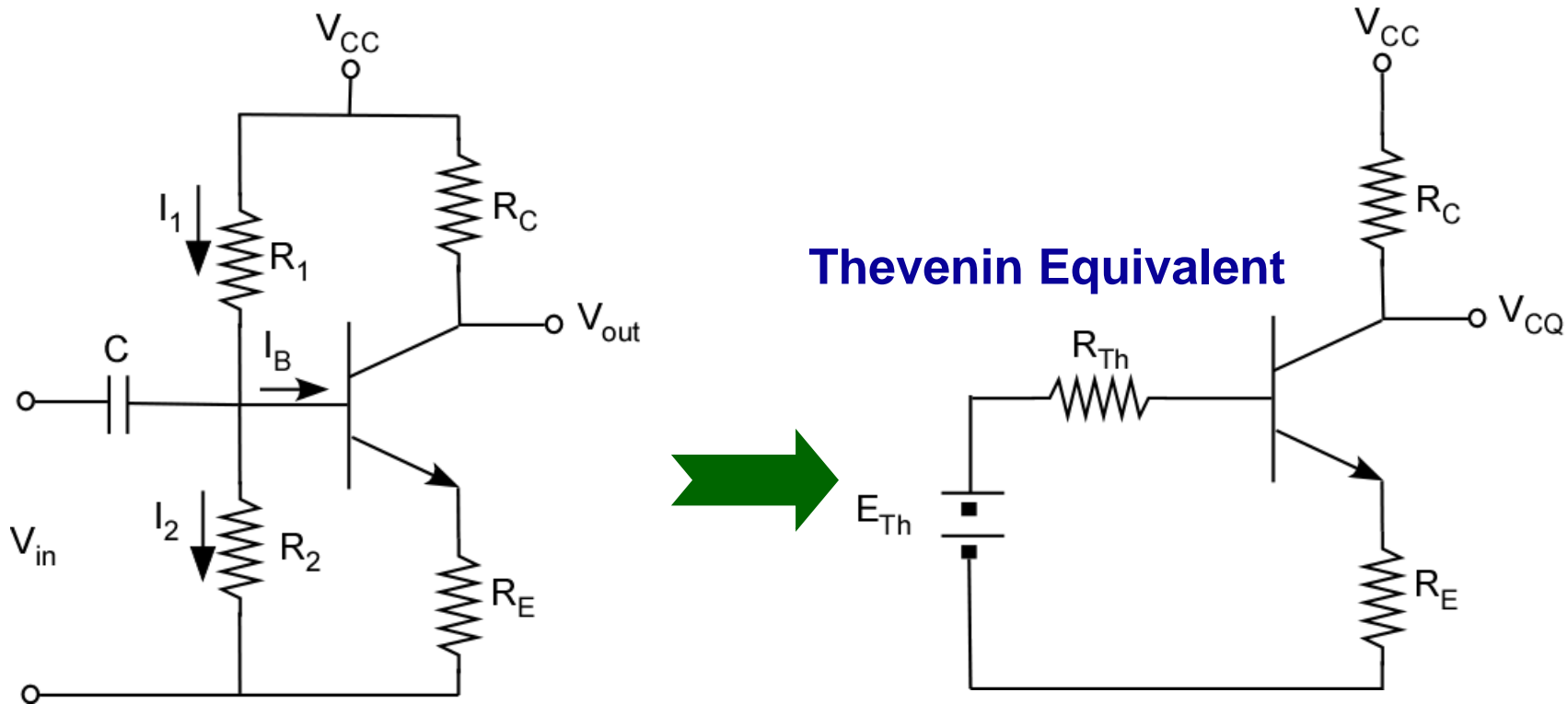

Provides good stability with respect to changes in  $\beta$  with temperature

# BJT Emitter Bias

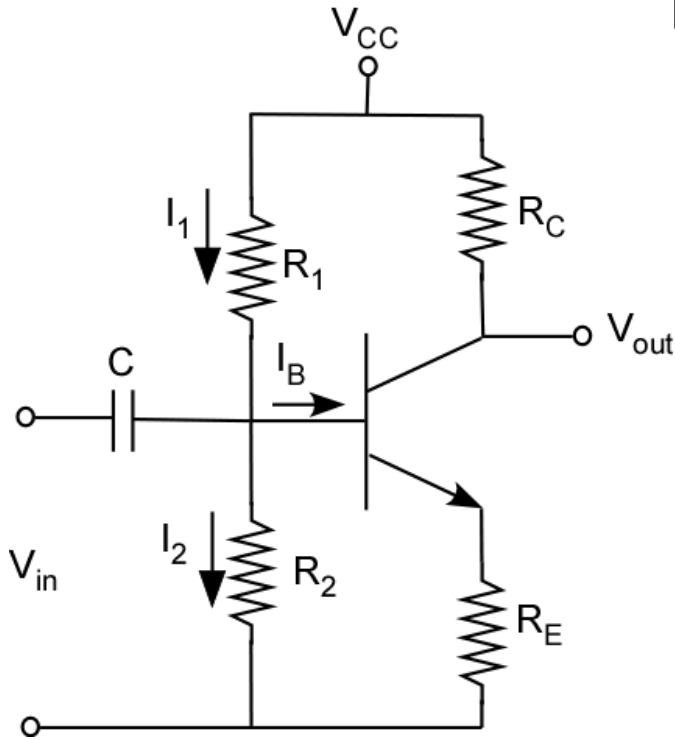

$$E_{th} = R_{th} I_B + V_{BE} + R_E I_E$$

$$I_E = I_B + I_C = (\beta + 1) I_B$$


$$E_{th} - V_{BE} = R_{th} I_B + R_E (\beta + 1) I_B$$

$$I_B = I_{BQ} = \frac{E_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$


$$E_{th} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$R_{th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

**Thevenin Equivalent**

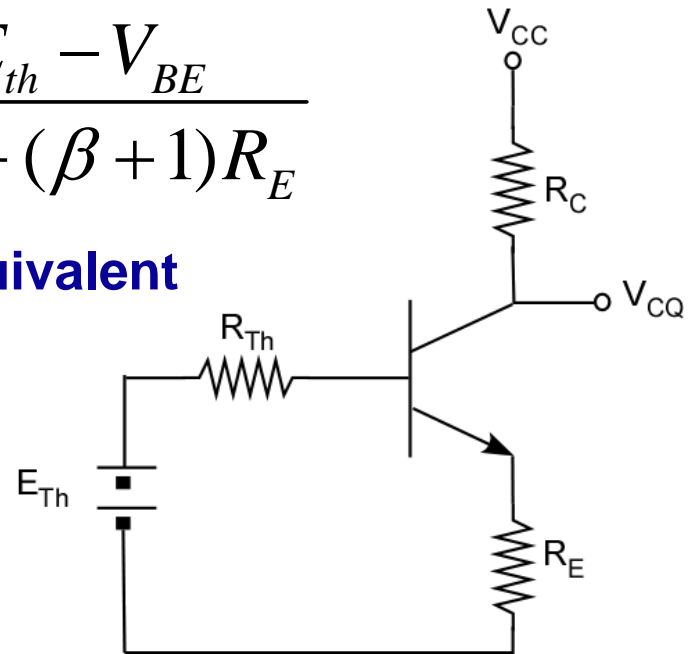
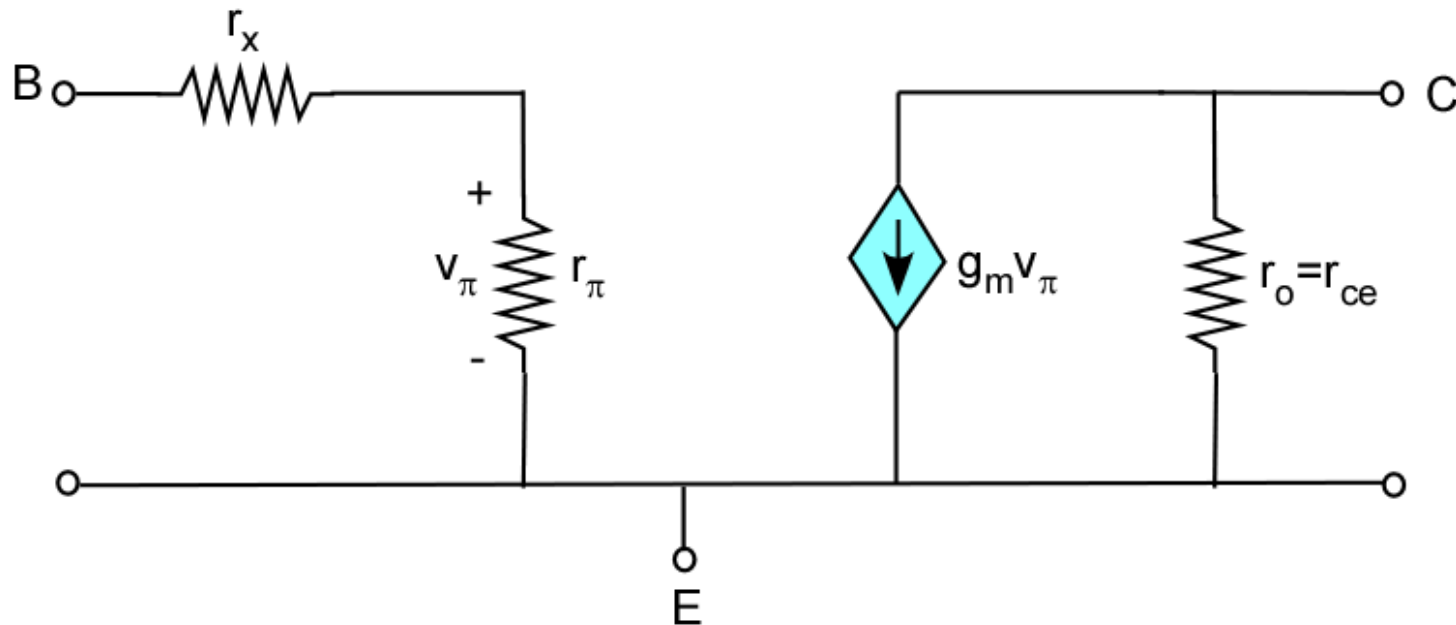
# Hybrid- $\pi$ Incremental Model for BJTs



$r_{\pi}$ : input resistance looking into the base

$r_x$ : parasitic series resistance looking into base – ohmic base resistance

$g_m$ : BJT transconductance

$r_o=r_{ce}$ : output collector resistance related to the Early effect

# Hybrid- $\pi$ Parameters

$$g_m = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{I_C = \text{constant}} = \frac{I_C}{V_T}$$

$r_\pi$  is defined as:  $r_\pi = \frac{v_\pi}{i_b}$

Since  $i_b = \frac{g_m v_\pi}{\beta}$  then  $r_\pi = \frac{\beta}{g_m}$

Can show that

$$r_\pi = (\beta + 1) r_e$$

$$g_m = \frac{\alpha}{r_e}$$


$$\beta = g_m r_\pi$$

$r_{ce} = r_o$  is associated with the Early effect

$$r_{ce} = r_o = \frac{|V_A|}{I_C} = \frac{|V_A|}{\beta I_B}$$

$$g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$$

# Common Emitter (CE) Amplifier

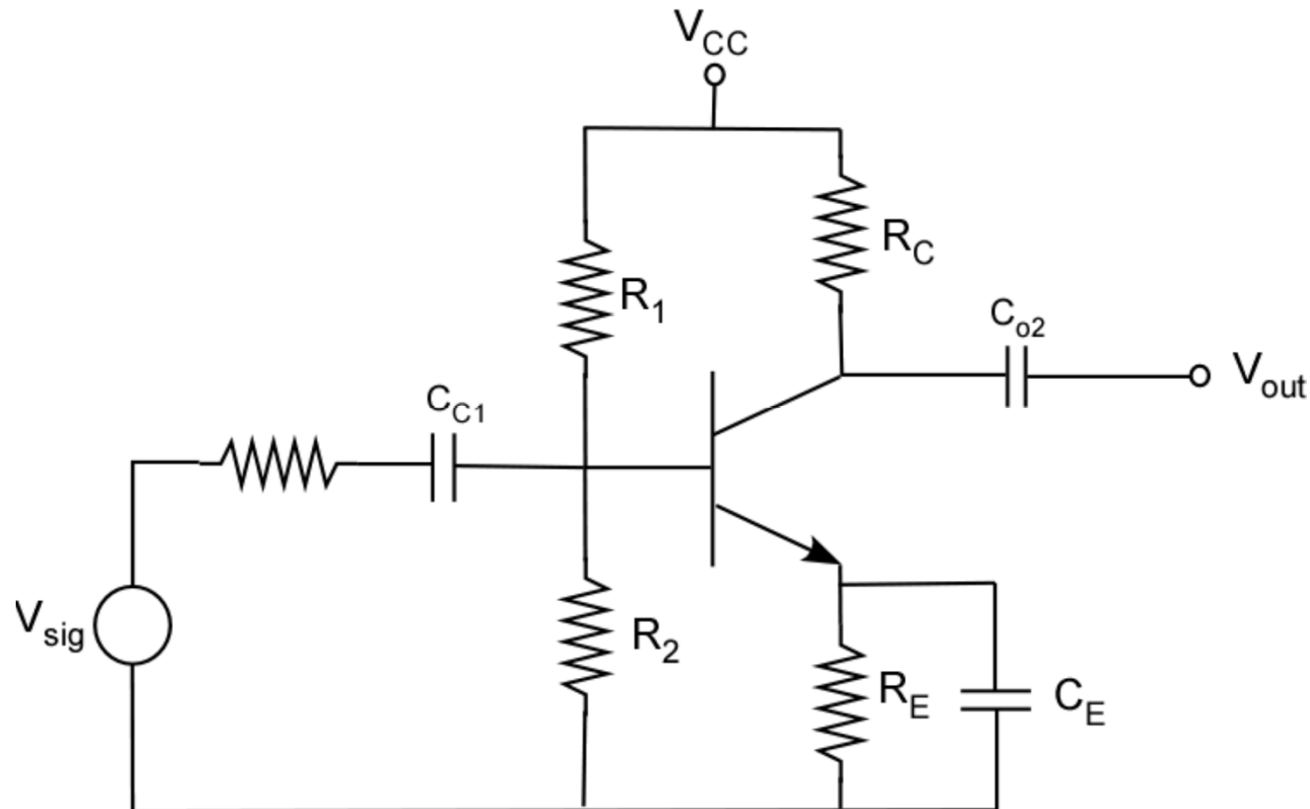


**Bias:** Choose  $R_1$  &  $R_2$  to set  $V_B \rightarrow V_E$  is then set. Choose  $R_E$  to set  $I_E \sim I_C$ .  
Quiescent point of  $V_{out}$  will be determined by  $R_C$ . Emitter is an AC short.



# Incremental Model for CE Amplifier

Hybrid- $\pi$  model (ignoring  $r_x$ )

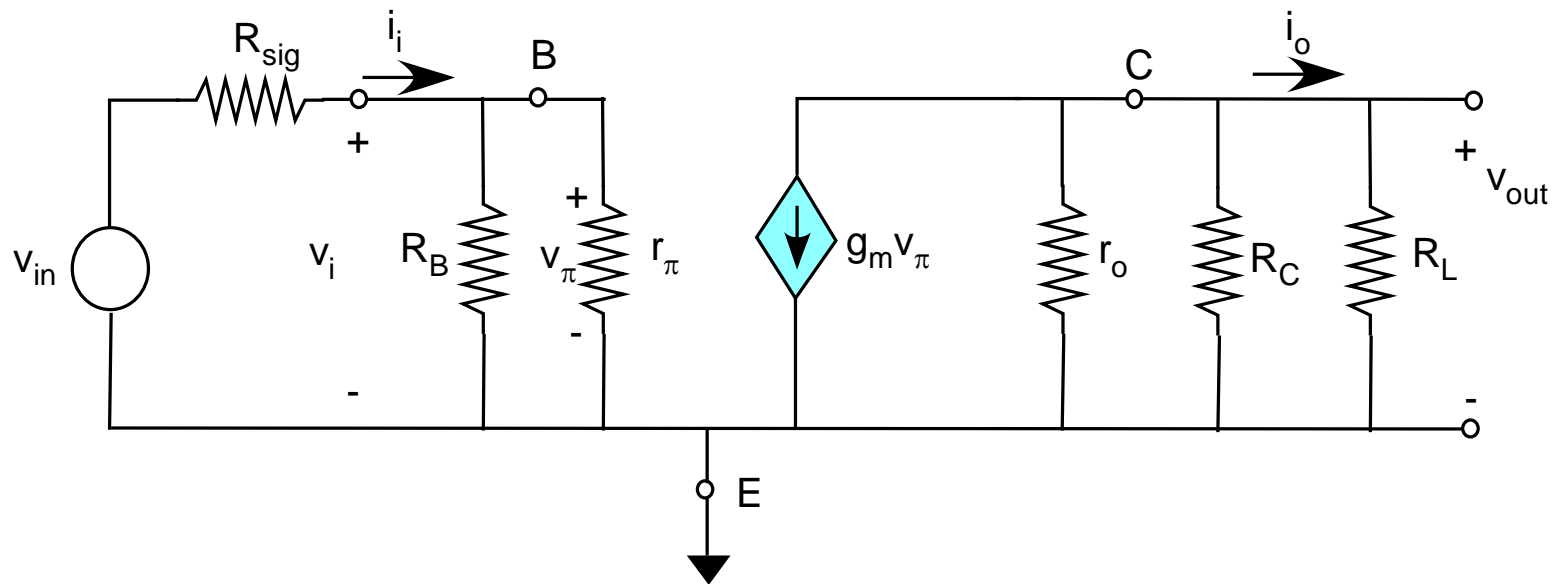

$$R_B = R_1 \parallel R_2$$

$$R_{in} = \frac{v_i}{i_i} = R_B \parallel r_\pi$$

*Sometimes  $R_B \gg r_\pi$  and  $R_{in} \approx r_\pi$*

# CE Amplifier

$$v_i = \frac{v_{sig} R_{in}}{R_{in} + R_{sig}} = \frac{v_{sig} R_B \parallel r_{\pi}}{(R_B \parallel r_{\pi}) + R_{sig}}$$

and if  $R_B \gg r_{\pi}$ ,  $v_i \simeq \frac{v_{sig} r_{\pi}}{r_{\pi} + R_{sig}}$

$$v_o = -g_m v_{sig} \frac{R_B \parallel r_{\pi} (r_o \parallel R_C \parallel R_L)}{(R_B \parallel r_{\pi}) + R_{sig}}$$

$$v_o = -g_m v_{\pi} (r_o \parallel R_C \parallel R_L)$$

$$v_i = v_{\pi}$$

$$A_v = \frac{v_o}{v_i} = -g_m (r_o \parallel R_C \parallel R_L)$$

gain from base to collector

# CE Amplifier

Open-circuit voltage gain:

$$A_{vo} = -g_m (r_o \parallel R_C)$$

In most cases  $r_o \gg R_C \Rightarrow A_{vo} = -g_m R_C$

$$G_v = -\frac{(R_B \parallel r_\pi)}{(R_B \parallel r_\pi) + R_{sig}} g_m (r_o \parallel R_C \parallel R_L)$$

and for the case where  $R_B \gg r_\pi$

$$G_v = -\frac{\beta (r_o \parallel R_C \parallel R_L)}{r_\pi + R_{sig}}$$

# CE Amplifier

## Output Impedance

$$R_{out} = R_C \parallel r_o$$



$$\text{If } r_o \gg R_C, R_{out} \simeq R_C$$

$$\text{from which } A_v = A_{vo} \left( \frac{R_L}{R_L + R_o} \right)$$

It can be seen that if  $R_{sig} \gg r_\pi$ , the gain will be highly dependent on  $\beta$ . This is not good because of  $\beta$  variations

$$\text{If } R_{sig} \ll r_\pi, G_v \simeq -g_m (R_C \parallel R_L \parallel r_o)$$

# Emitter Follower (Common Collector)

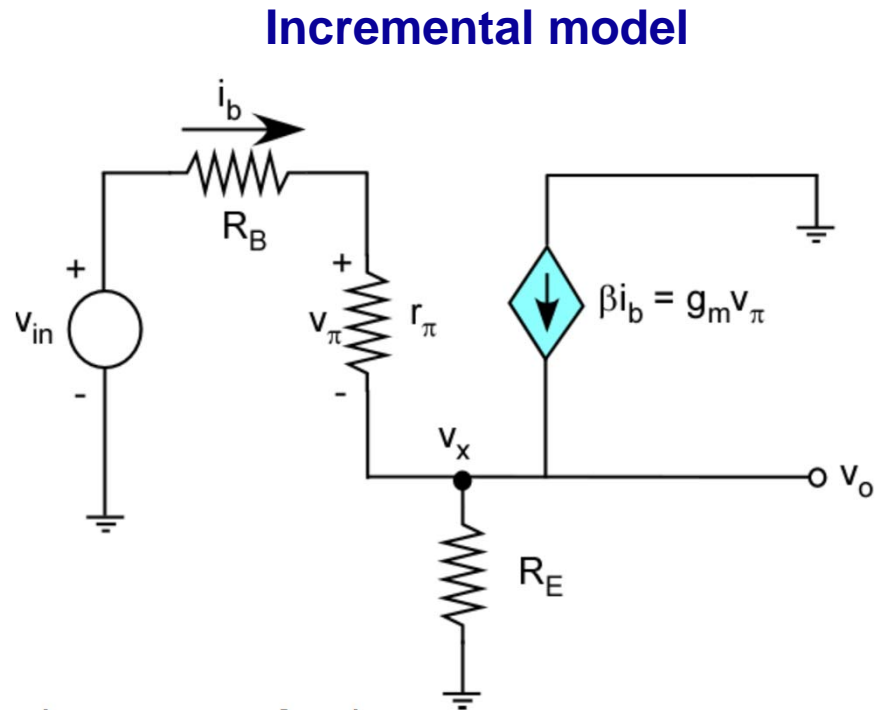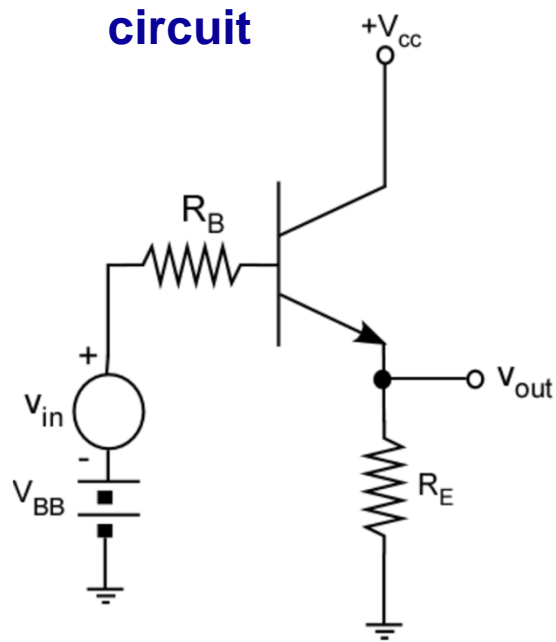

$$v_o = \left( g_m v_\pi + \frac{v_\pi}{r_\pi} \right) R_E = v_\pi \left( g_m + \frac{1}{r_\pi} \right) R_E$$

$$v_{in} = v_\pi + R_B i_b + v_o = v_\pi + v_\pi R_E \left( g_m + \frac{1}{r_\pi} \right) + \frac{v_\pi}{r_\pi} R_B$$

# Emitter Follower

$$v_{in} = v_{\pi} \left[ 1 + \frac{R_B}{r_{\pi}} + R_E \left( g_m + \frac{1}{r_{\pi}} \right) \right]$$


$$\frac{v_o}{v_{in}} = \frac{\left( g_m + \frac{1}{r_{\pi}} \right) R_E}{\left( g_m + \frac{1}{r_{\pi}} \right) R_E + 1 + \frac{R_B}{r_{\pi}}} = \frac{(g_m r_{\pi} + 1) R_E}{(g_m r_{\pi} + 1) R_E + r_{\pi} + R_B}$$

Using  $g_m r_{\pi} = \beta$

$$\frac{v_o}{v_{in}} = \frac{(\beta + 1) R_E}{(\beta + 1) R_E + r_{\pi} + R_B} \simeq 1$$

**Emitter follower has unity voltage gain**

# Emitter Follower – Input Impedance

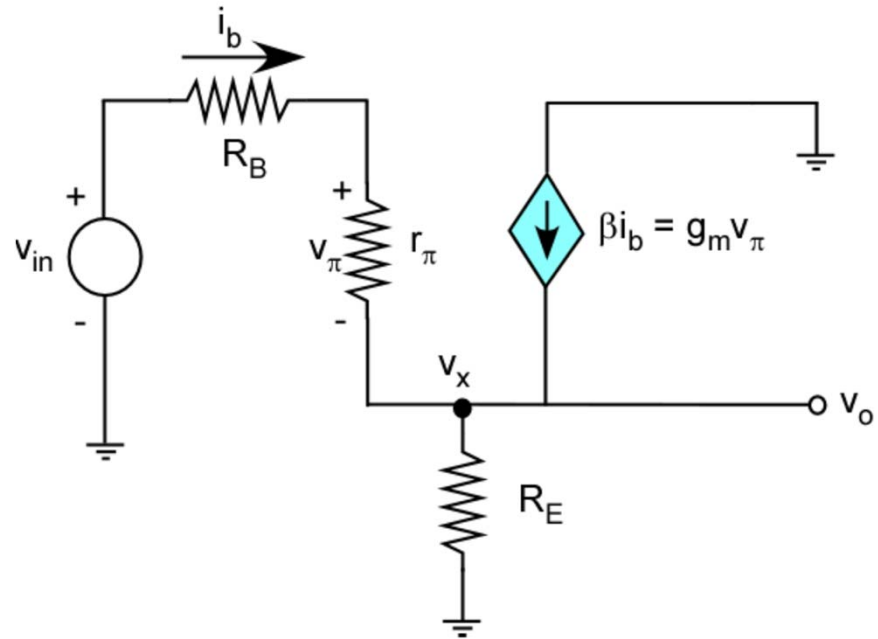

$$r_{in} = \frac{v_{in}}{i_b} = \frac{v_{\pi} \left[ 1 + R_B / r_{\pi} + R_E (g_m + 1 / r_{\pi}) \right]}{v_{\pi} / r_{\pi}}$$


$$r_{in} = r_{\pi} + R_B + R_E (\beta + 1)$$

# Emitter Follower – Output Impedance

$$i_B = -\frac{v_o}{r_\pi + R_B}$$

$$i_o = \frac{v_o}{R_E} - g_m v_\pi + \frac{v_o}{r_\pi + R_B} = \frac{v_o}{R_E} + \frac{g_m r_\pi v_o}{r_\pi + R_B} + \frac{v_o}{r_\pi + R_B}$$
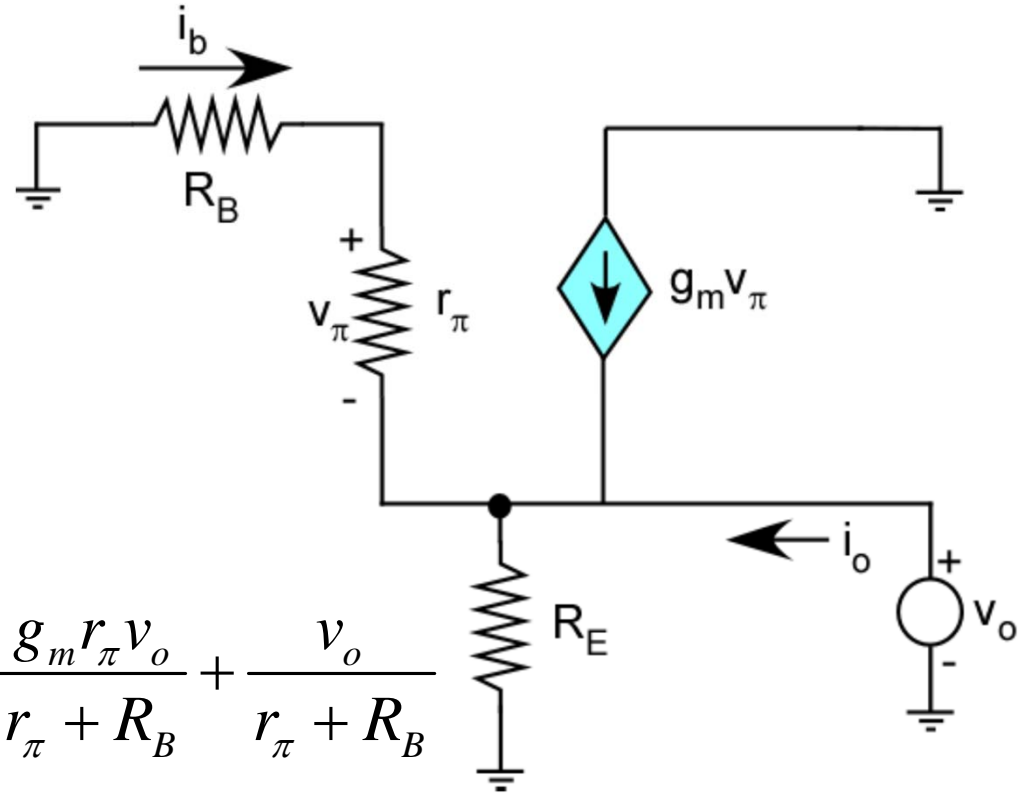
$$i_o = v_o \left[ \frac{1}{R_E} + \frac{g_m}{r_\pi + R_B} + \frac{1}{r_\pi + R_B} \right] = v_o \left[ r_\pi + R_B + R_E (\beta + 1) \right] \frac{1}{R_E (r_\pi + R_B)}$$





## Output Impedance (cont')

Using  $g_m r_\pi = \beta$


$$\frac{v_o}{i_o} = R_{out} = \frac{R_E (r_\pi + R_B)}{r_\pi + R_B + R_E (\beta + 1)} = \frac{R_E (r_\pi + R_B) / (\beta + 1)}{R_E + (r_\pi + R_B) / (\beta + 1)}$$

$$R_{out} = R_E \parallel (r_\pi + R_B) / (\beta + 1)$$

If we neglect  $R_B$

$$A'_{MB} = \frac{(\beta + 1)R_E}{r_\pi + (\beta + 1)R_E} \quad \text{and} \quad R'_{out} = R_E \parallel \frac{r_\pi}{\beta + 1}$$

# Common Base Configuration

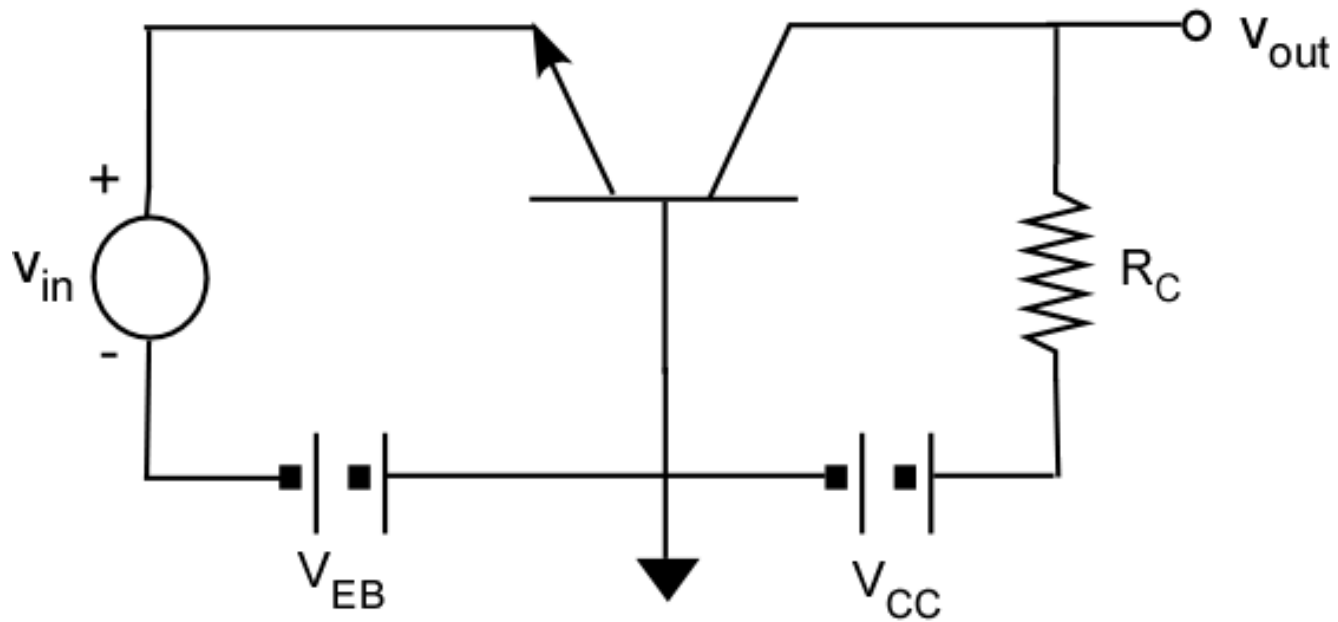

# Common Base Configuration


$$v_i = -v_\pi, \quad v_o = -g_m v_\pi R_C = g_m v_i R_C$$

$$\text{Voltage gain} = \frac{v_o}{v_i} = g_m R_C = \frac{\alpha R_C}{r_e}$$

$$\text{Current gain} = \frac{i_o}{i_i} = \frac{g_m v_\pi}{i_i} = \frac{-g_m v_\pi}{\left(g_m + \frac{1}{r_\pi}\right)(-v_\pi)} = \frac{\beta}{\beta + 1} = \alpha$$

$$R_{out} = R_C$$


$$r_{in} = \frac{r_\pi}{\beta + 1}$$

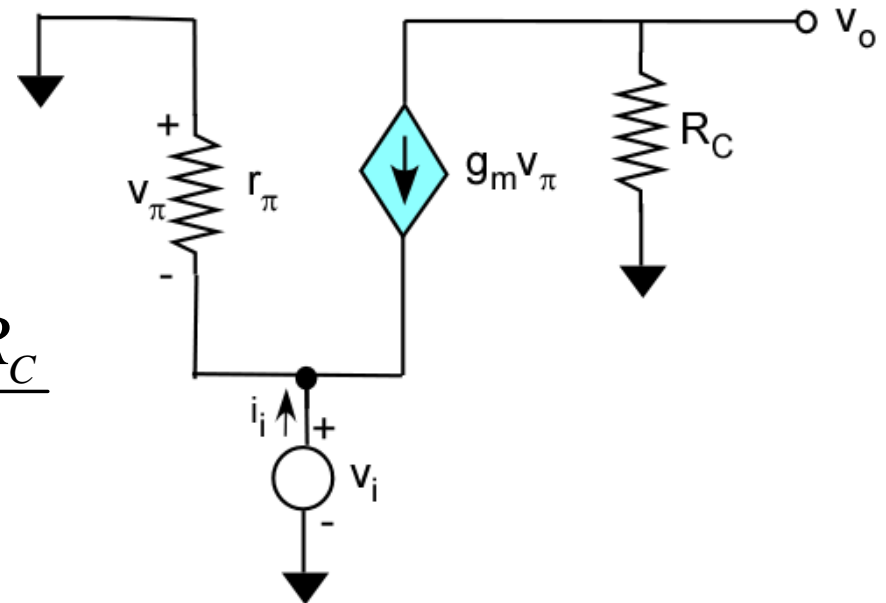

# BJT Topologies - Summary

	CE	CB	EF
$A_{vo}$	$-g_m R_C$	$g_m R_C$	1
$R_{in}$	$r_\pi$	$\frac{r_\pi}{\beta + 1}$	$r_\pi + R_E (\beta + 1)$
$R_{out}$	$R_C$	$R_C$	$R_E \parallel r_\pi / (\beta + 1)$

# Feedback – Basic Concept

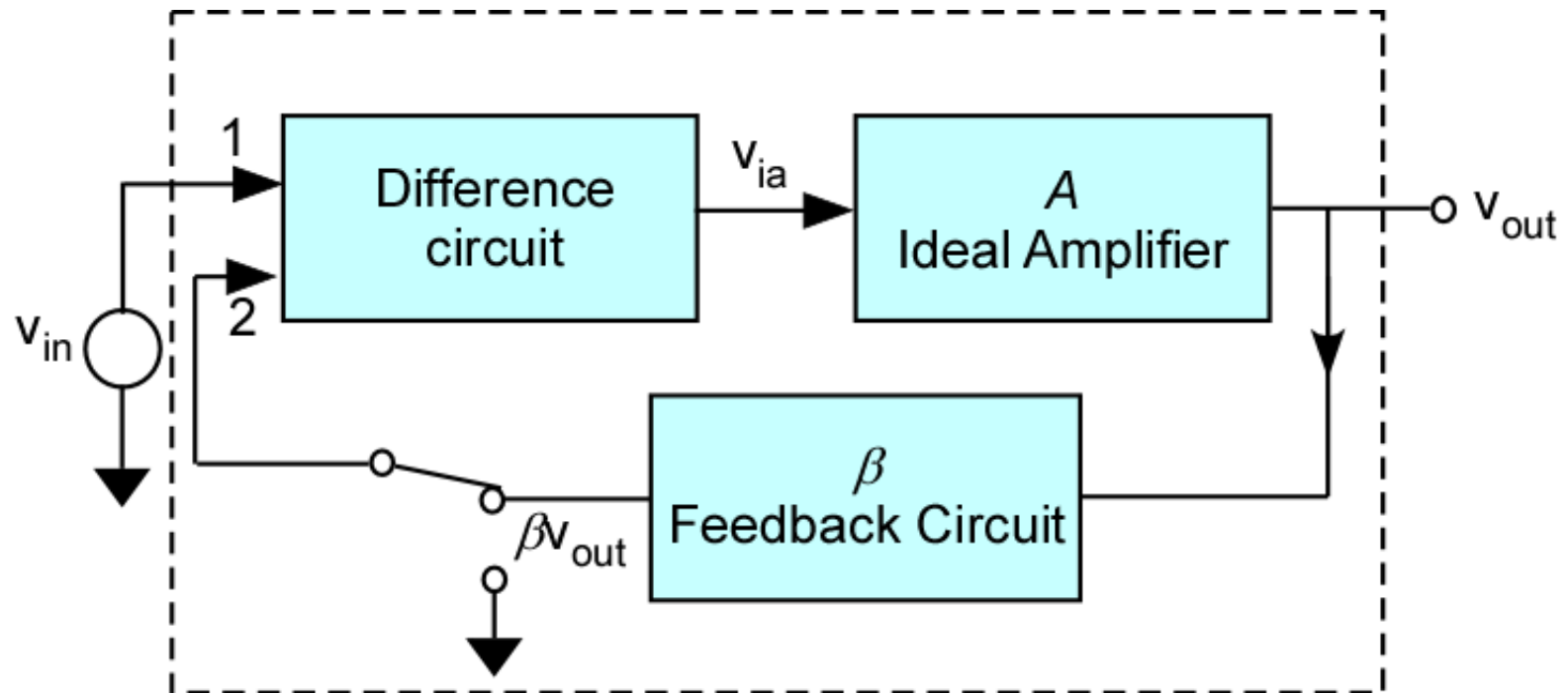

# Feedback and Frequency Dependence

1. The closed-loop transfer function is a function of frequency
2. The manner in which the loop gain varies with frequency determines the stability or instability of the feedback amplifier
3. The frequency at which the phase of the transfer function is equal to  $180^\circ$  will be unstable if the magnitude is greater than unity

# Feedback and Stability


$$A_f(s) = \frac{A(s)}{1 + A(s)\beta(s)}$$

$$A_f(j\omega) = \frac{A(j\omega)}{1 + A(j\omega)\beta(j\omega)}$$

**When loop gain  $A(j\omega)\beta(j\omega)$  has  $180^\circ$  phase, we have positive feedback**

# Nyquist Plot


- Radial distance is  $|A\beta|$
- Angle is phase of  $\phi$
- Intersects negative real axis at  $\omega_{180}$

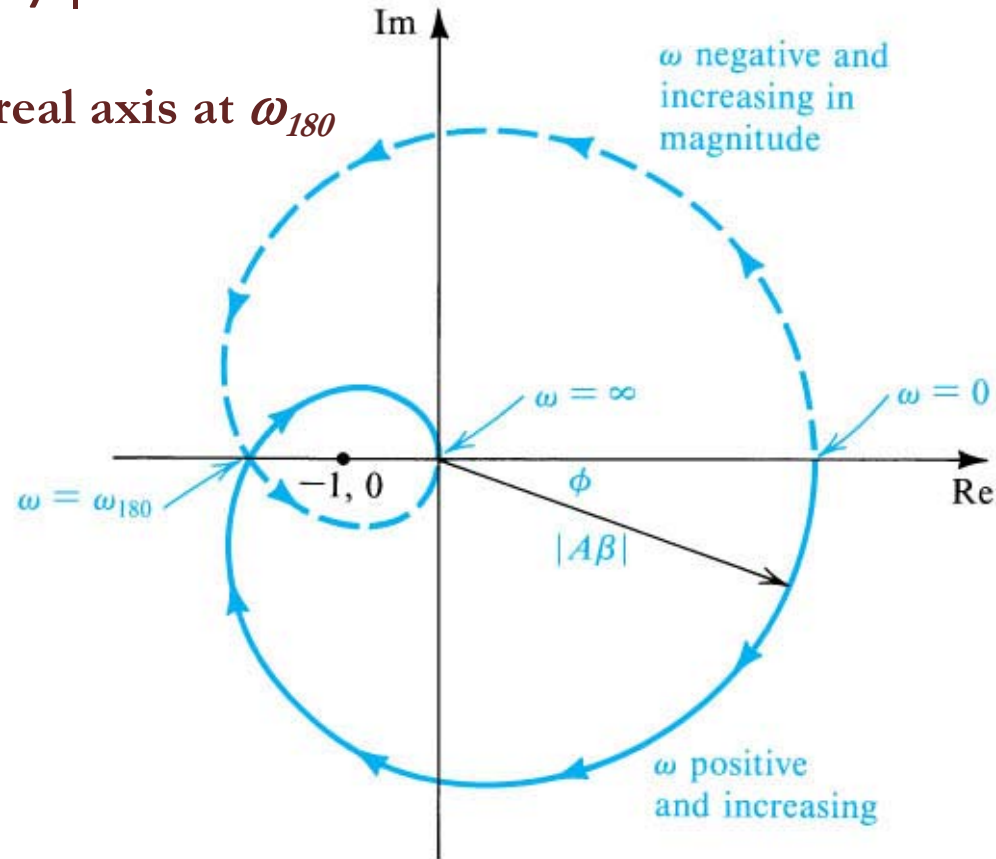


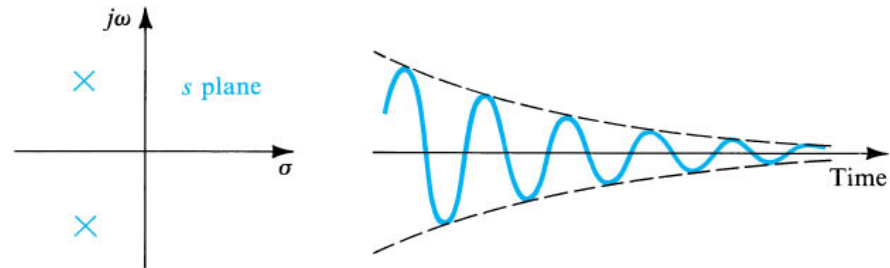
# Stability and Pole Location


$$v(t) = e^{\sigma_o t} \left[ e^{+j\omega t} + e^{-j\omega t} \right] = 2e^{\sigma_o t} \cos(\omega_n t)$$



(a)




(b)

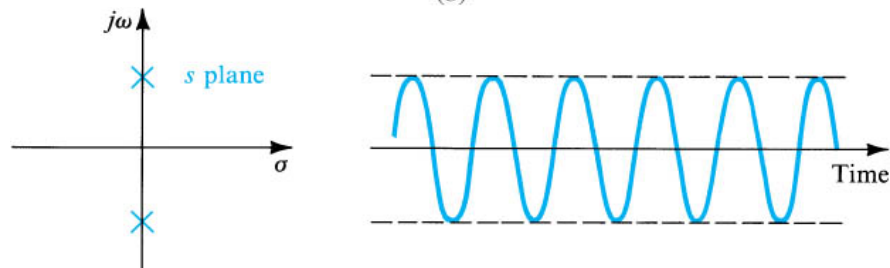

(c)

# Oscillator

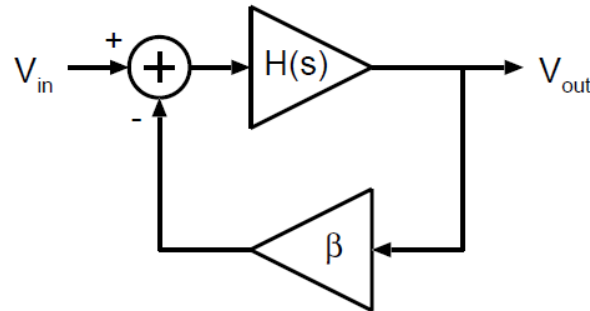

- Closed-Loop Transfer function:

$$-\frac{V_{out}}{V_{in}}(s) = \frac{H(s)}{1 + \beta H(s)}, \text{ where } s = j\omega$$

- Barkhausen's criteria for oscillation:

$$- |\beta H(j\omega_0)| = 1$$

$$- \arg(\beta H(j\omega_0)) = -180^\circ.$$

- $\omega_0$  = oscillation-frequency.