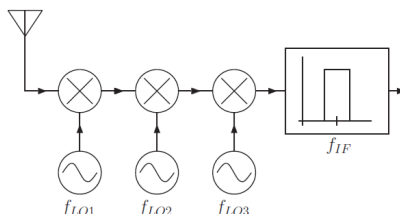


### Solutions

1. Consider a triple-conversion receiver with three ideal mixers in cascade. There are no filters between the mixers. The local-oscillator frequencies are  $f_{LO1} = 1250$  MHz,  $f_{LO2} = 1370$  MHz, and  $f_{LO3} = 185$  MHz. The only filter is the final IF filter, which is ideal and centered at  $f_{IF} = 12.5$  MHz.



- (a) Find all positive input frequencies that can produce an output exactly at 12.5 MHz after the third mixer.
  - (b) If a fourth unfiltered conversion stage were added, how many input-frequency solutions would normally exist, assuming no accidental degeneracies?
2. The transfer function for a regenerative amplifier is:

$$T(\omega) = \frac{GF(\omega)}{1 - AGF(\omega)}$$

where  $A$  and  $G$  are positive real constants and  $AG < 1$ . Suppose that the filter is implemented with a single series or parallel  $RLC$  resonant circuit, in which case the frequency response function of the filter,  $F(\omega)$ , will have the form:

$$F(\omega) = \frac{1}{1 + jQ\left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega}\right)},$$

where the factor  $Q$  is a dimensionless constant that controls the bandwidth of the filter.

- (a) Find an expression for the bandwidth of  $F(\omega)$  at attenuation level decibels — the “ $-\alpha$  dB bandwidth” — where  $\alpha$  is the attenuation expressed in dB. Denote this bandwidth by  $\Delta f_{-\alpha dB}$  and express your result in terms of the power ratio  $r = 10^{\alpha/10}$ , the parameter  $Q$ , and the center frequency  $f_o = \omega_o/2\pi$ . Note that  $|F(2\pi f)|$  is a bandpass function with peak at  $f = f_o$ . The  $-\alpha$  dB bandwidth is defined to be the separation between the two frequencies  $f_1$  and  $f_2$  that satisfy  $f_1 > 0, f_2 > 0$  and  $|F(2\pi f_1)| = |F(2\pi f_2)| = |F(2\pi f_o)| / \sqrt{r}$ .
- (b) Using your answer to part a, write down the expression for the  $-3$  dB bandwidth of  $F(\omega)$ . We will use this result often during the rest of the semester.

- (c) Find an expression for the  $-3\text{ dB}$  bandwidth of  $T(\omega)$ . Make sure that your result reduces to the result found in part a when  $A \rightarrow 0$ . Discuss how the magnitude of the loop gain ( $AG$ ) affects the peak gain of  $T(\omega)$  and the bandwidth of  $T(\omega)$ .
- (d) Comment on how the product of the peak gain and bandwidth of  $T(\omega)$  (the *gain-bandwidth product*) depends on the feedback gain parameter,  $A$ .
- (e) Find an expression for the *shape factor* (SF) of the regenerative amplifier's frequency response,  $T(\omega)$ , where

$$SF = \frac{\Delta f_{-30\text{dB}}}{\Delta f_{-3\text{dB}}}.$$

We already know that the gain of the system is increased and the bandwidth is decreased if we let the loop gain ( $AG$ ) approach 1 from below. How does the shape factor of  $T(\omega)$  change as the loop gain approaches 1? (Note - a good channel selection filter will have a shape factor smaller than 2. A really good channel selection filter might have shape factor of 1.2 or even smaller.)

- (f) Find the numerical values of the shape factor of  $T(\omega)$  when  $A = 0$  and when  $A$  is chosen to make  $AG = 0.99$ .