

ECE 453

Wireless Communication Systems

Noise

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

Noise



Random fluctuations of voltage and current

Properties

- Establishes minimum detectable signal
- Sets bounds on range of signals that can be processed
- Comes in different types (thermal, flicker, shot)
- Has frequency and time-domain characteristics
- Not fully understood

Noise from a Resistor

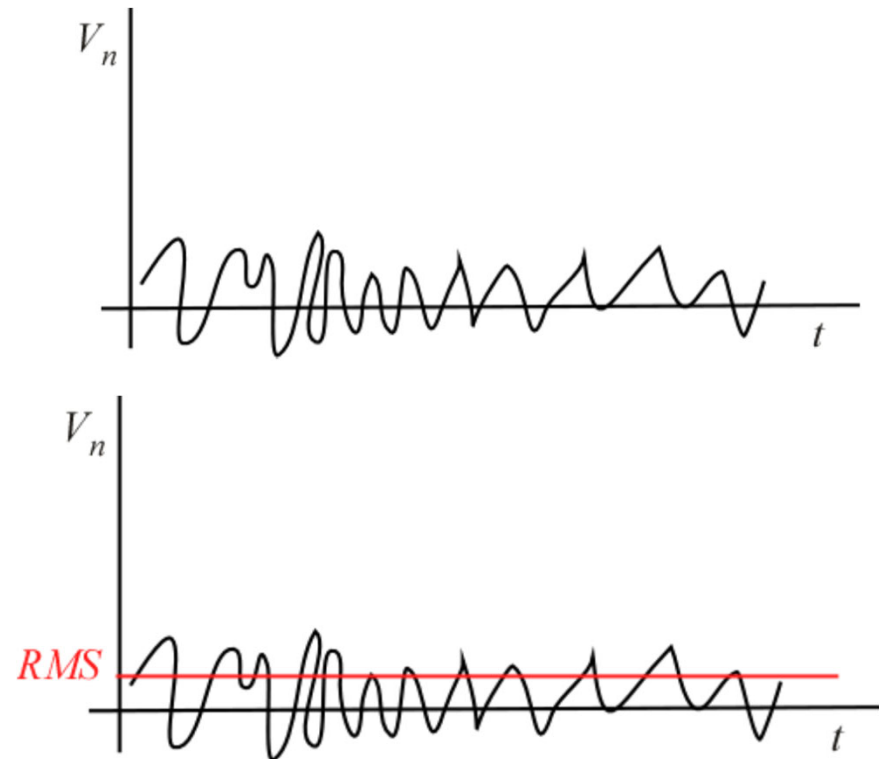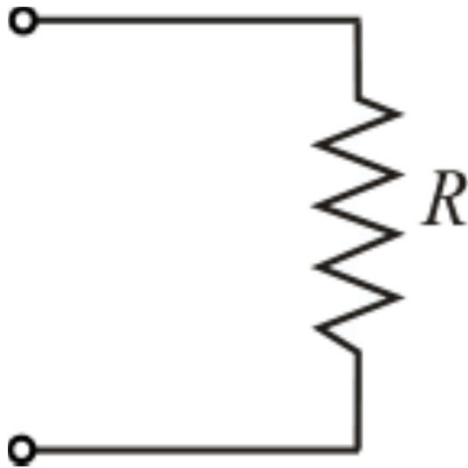Random fluctuations of charge carriers in a conductor will produce thermal noise



At room temperature a resistor has available noise power ~ -174 dBm in 1 Hz of bandwidth

Nyquist Noise Formula

The spectral density of noise voltage at the terminals of a resistor is given by

$$S_n(f) = 4R \frac{hf}{e^{hf/kT} - 1} \text{ (Volts}^2 \text{ / Hz)}$$

f = frequency in Hz

h = Plank's constant = 6.62×10^{-34} joules-sec

k = Boltzman's constant = 1.38×10^{-23} joules/°K

T = absolute temperature °K

R = resistance in ohms

Noise from a Resistor


If $f \ll kT/h$, then S_n can be approximated as:

$$S_n = 4kTR \text{ (Volts}^2 \text{ / Hz)}$$

Noise voltage at the terminals of a resistor is given by

$$V_n^2 = 4kTBR$$

B = bandwidth in Hz

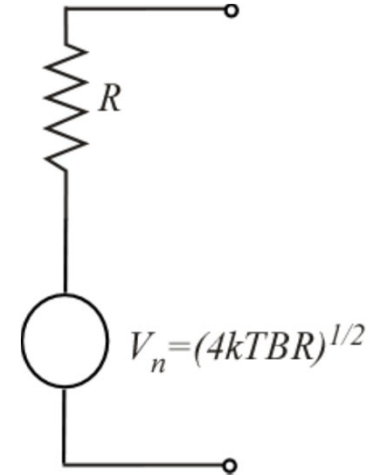

Noise from a Resistor

AC Voltmeter


Input resistance = 10 M Ω

Bandwidth = 40 MHz

$$V_n^2 = 4 \times 1.38 \times 10^{-23} \times 300 \times 4 \times 10^6 \times 10^7$$

$$V_n^2 = 66.24 \times 10^{-8}$$
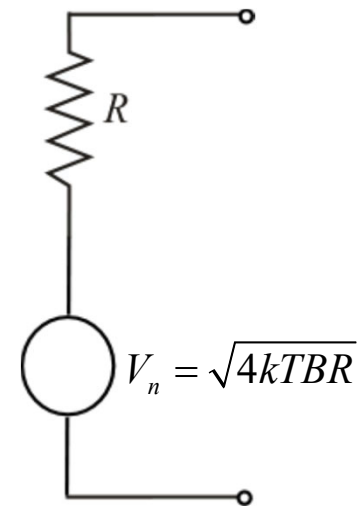
$$V_n \approx 8 \times 10^{-4} = 0.8 \text{ mV}$$



Resistors in Series

$$V_{n1}^2 = \frac{1}{T} \int_0^T v_{n1}^2(t) dt$$


$$V_{n2}^2 = \frac{1}{T} \int_0^T v_{n2}^2(t) dt$$

$$V_{nT}^2 = \frac{1}{T} \int_0^T [v_{n1}(t) + v_{n2}(t)]^2 dt$$


$$V_{nT}^2 = \frac{1}{T} \int_0^T v_{n1}^2(t) dt + \frac{1}{T} \int_0^T 2v_{n1}(t)v_{n2}(t) dt + \frac{1}{T} \int_0^T v_{n2}^2(t) dt$$

0 if v_{n1} and v_{n2} are uncorrelated
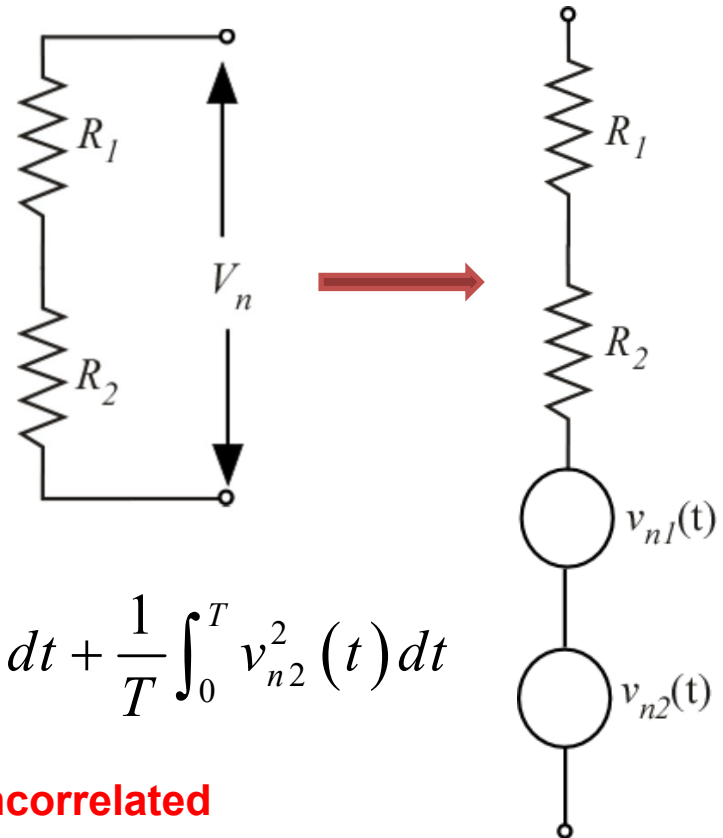
$$V_{nT}^2 = V_{n1}^2 + V_{n2}^2 = 4kTBR_1 + 4kTBR_2$$




Resistors in Series


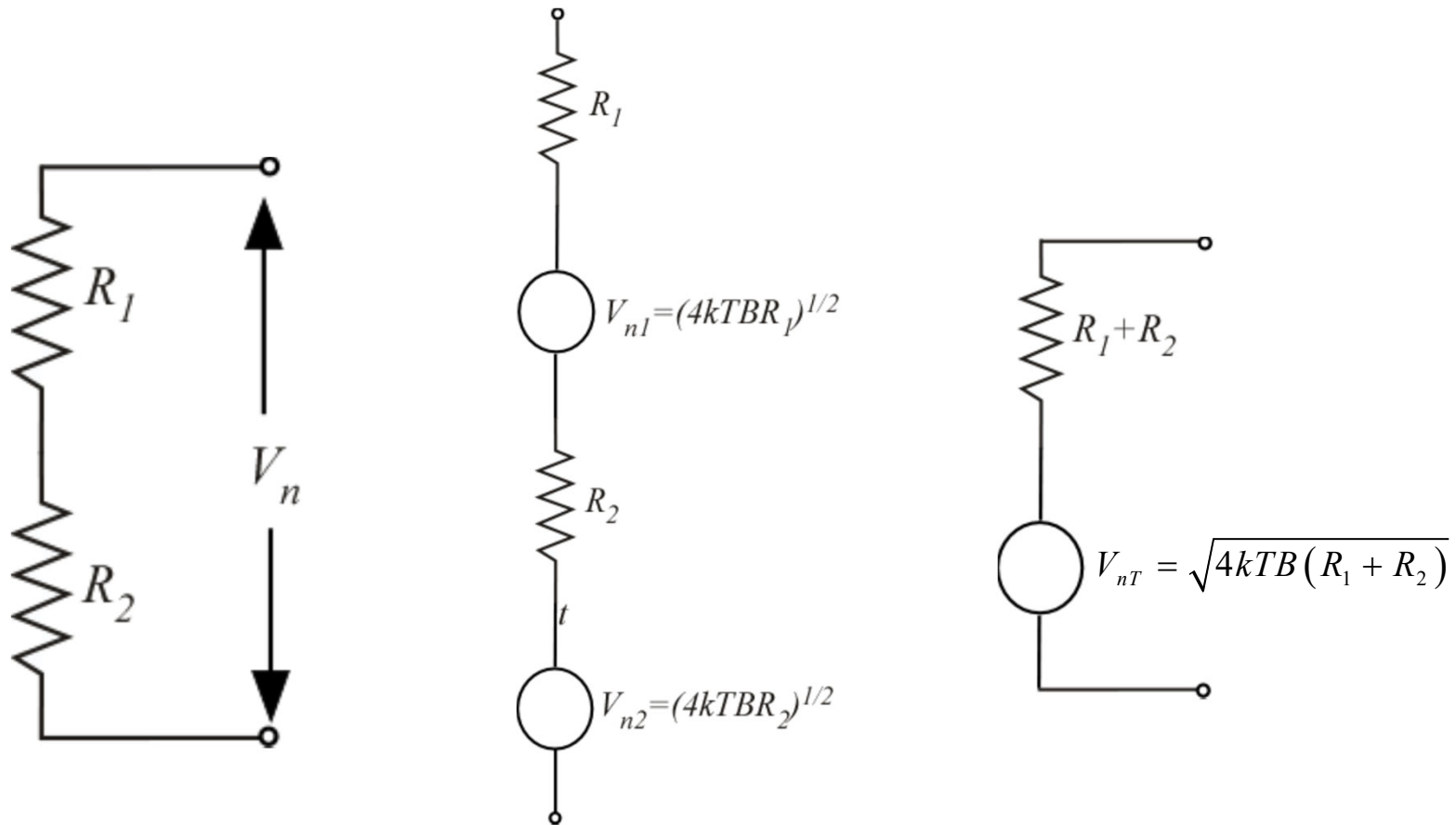


$$V_{nT}^2 = V_{n1}^2 + V_{n2}^2 \text{ for 2 uncorrelated noise sources}$$

Effective Value of Noise Sources

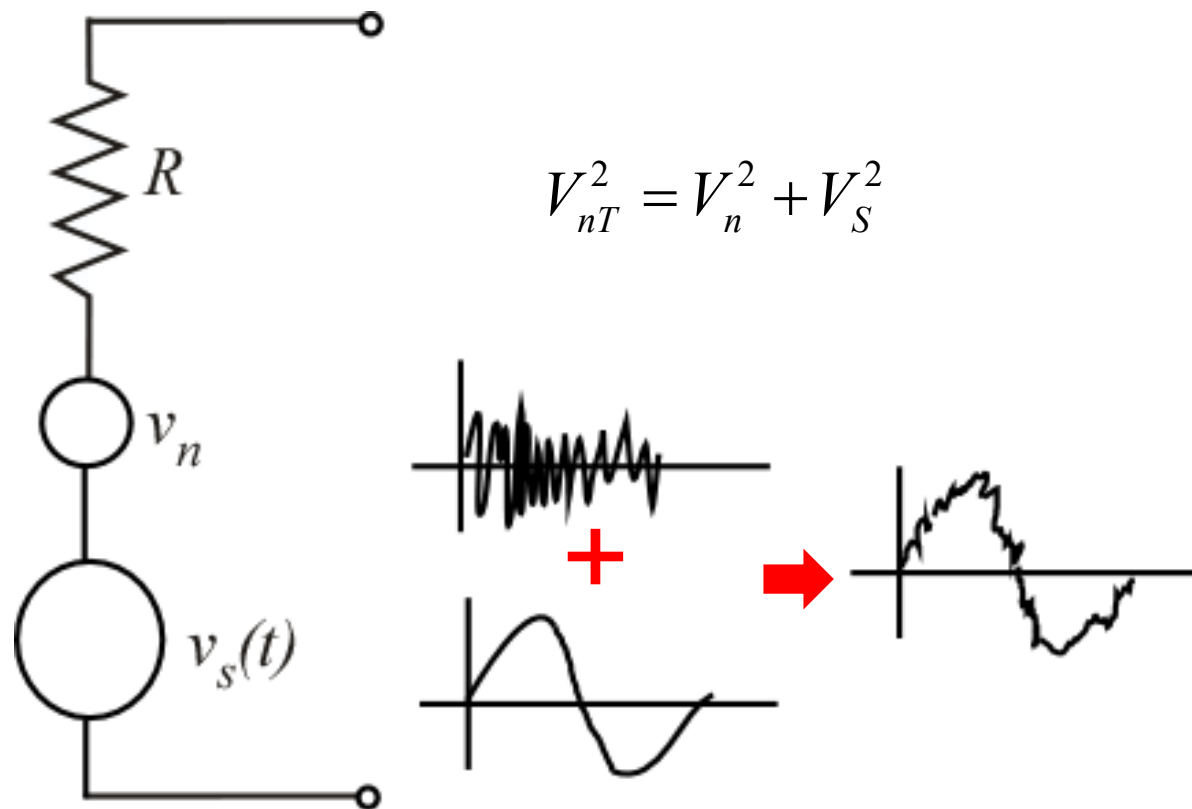

Bandwidth

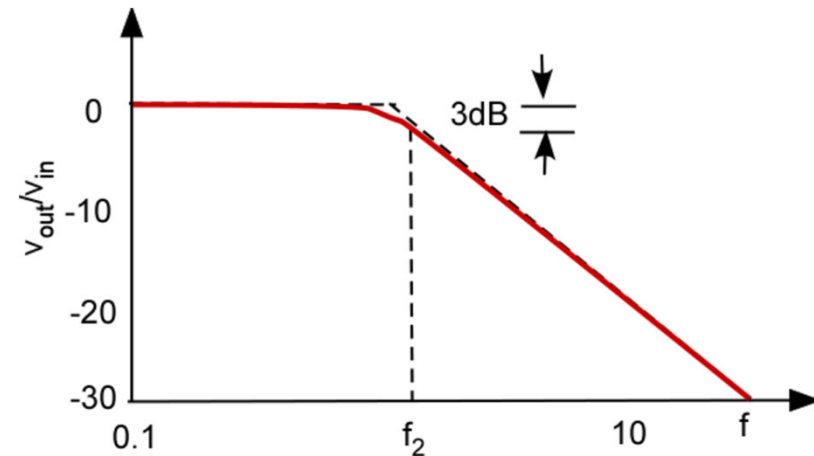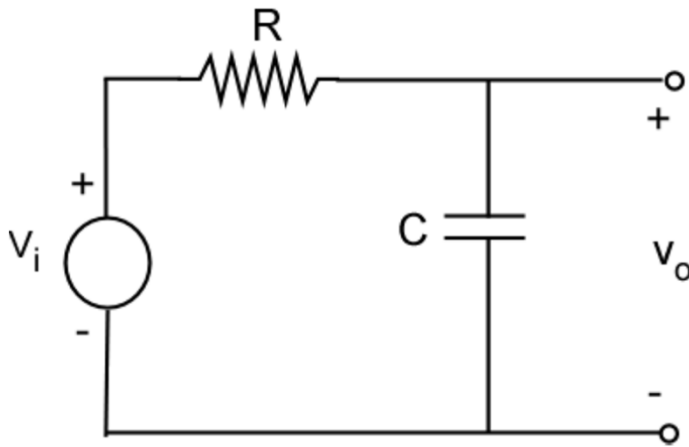


$$\frac{V_o}{V_{in}} = \frac{1}{1 + j\omega RC}$$

The output voltage drops to 0.707 of its low-frequency value when $\omega RC = 1$


The half-power frequency is given by $2\pi f_2 RC = 1$

$$\rightarrow f_2 = 1/2\pi RC$$

Noise from a Circuit

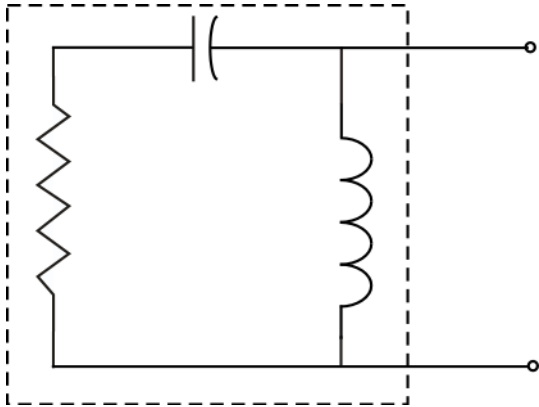


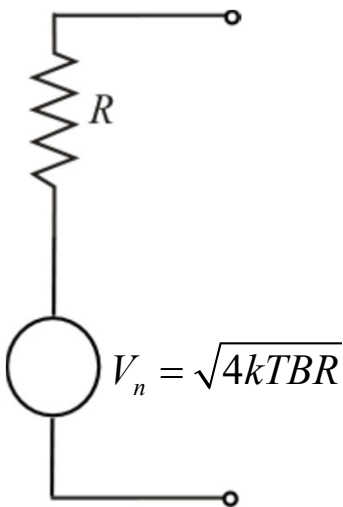
$$V_n^2 = 4kT \left[\int_0^\infty R(f) df = BR \right]$$



$R(f)$ is the real part of the impedance at each frequency

Noise from a Circuit

For an RC circuit

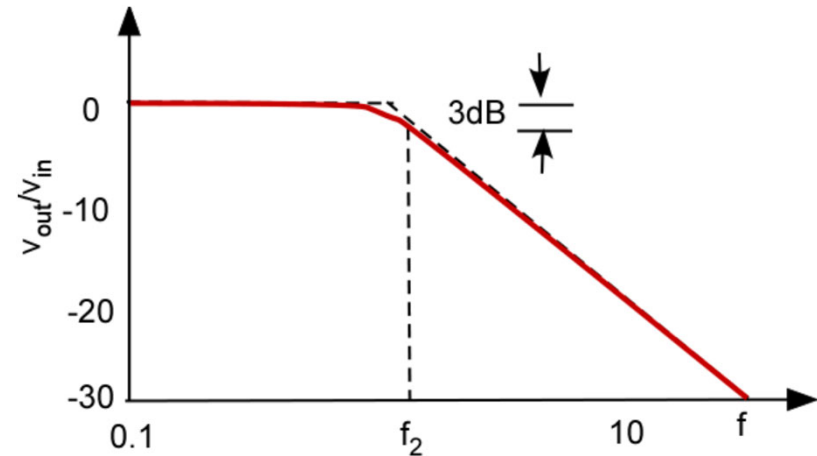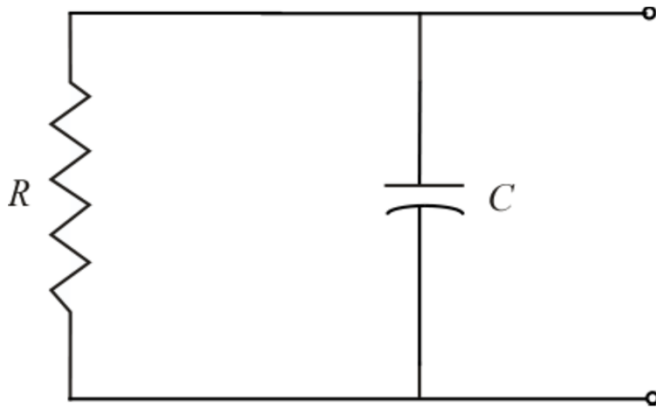

For coherent signals, the bandwidth of an RC circuit is

$$f_2 = \frac{1}{2\pi RC}$$


$|Z|$ is $0.707R$ when $\omega_2 R = 1/R \rightarrow 2\pi f_2 = 1/RC$

RC Circuit

The noise from the RC circuit is given by

$$V_n^2 = 4kT \int_0^\infty R(f) df$$
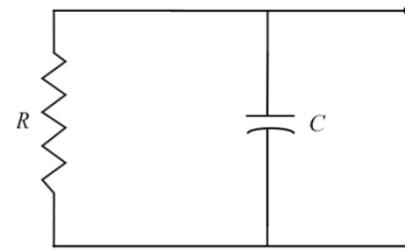
$$R(f) = \operatorname{Re}(Z) = \frac{G}{G^2 + \omega^2 C^2}$$



$$Z = \frac{G - j\omega C}{G + j\omega C}$$

In terms of $\omega_2 = 1/RC$, $R(f) = \frac{1}{R \left[\frac{1}{R^2} + \frac{\omega^2}{\omega_2^2 R^2} \right]}$

$$R(f) = \frac{R}{\left[1 + \frac{\omega^2}{\omega_2^2} \right]}$$

RC Circuit


The noise from the RC circuit is given by

$$V_n^2 = 4kT \int_0^\infty R(f) df = \frac{4kT}{2\pi} \int_0^\infty \frac{R}{1 + \frac{\omega^2}{\omega_2^2}} d\omega$$

Using $\int \frac{dx}{a^2 + b^2 x^2} = \frac{1}{ab} \tan^{-1} \frac{bx}{a}$

$$V_n^2 = \frac{4kTR}{2\pi} \omega_2 \frac{\pi}{2} = 4kTRf_2 \frac{\pi}{2}$$

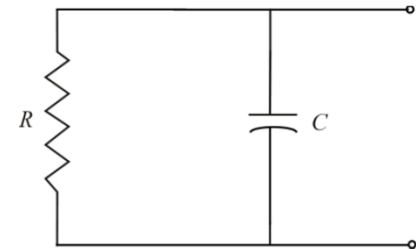The coherent signal bandwidth is from 0 to f_2



RC Circuit


For an RC circuit,

$$V_n^2 = \frac{4kTR}{2\pi} \omega_2 \frac{\pi}{2} = 4kTRf_2 \frac{\pi}{2}$$

where $f_2 = \frac{1}{2\pi RC}$


Consequently,
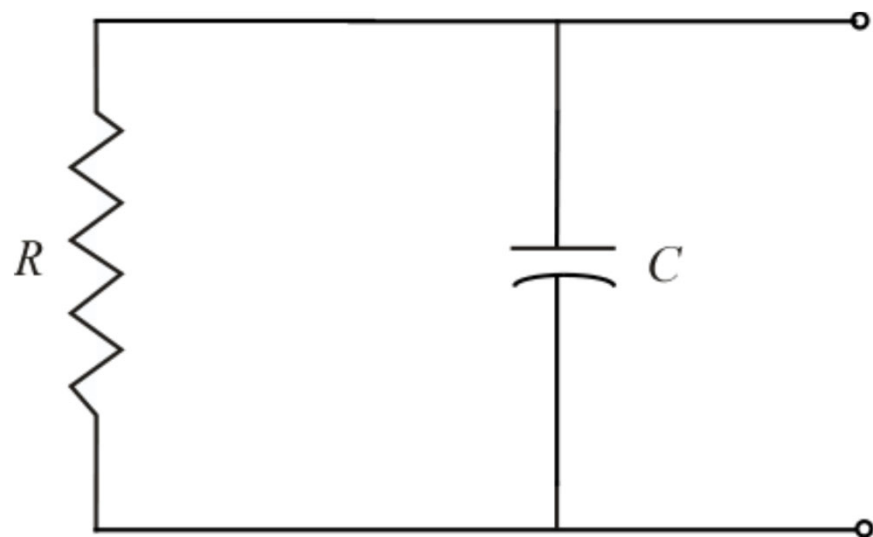
$$V_n^2 = 4kTR \frac{\pi}{2\pi RC2} = \frac{kT}{C}$$



Independent of resistance!

Noise Factor

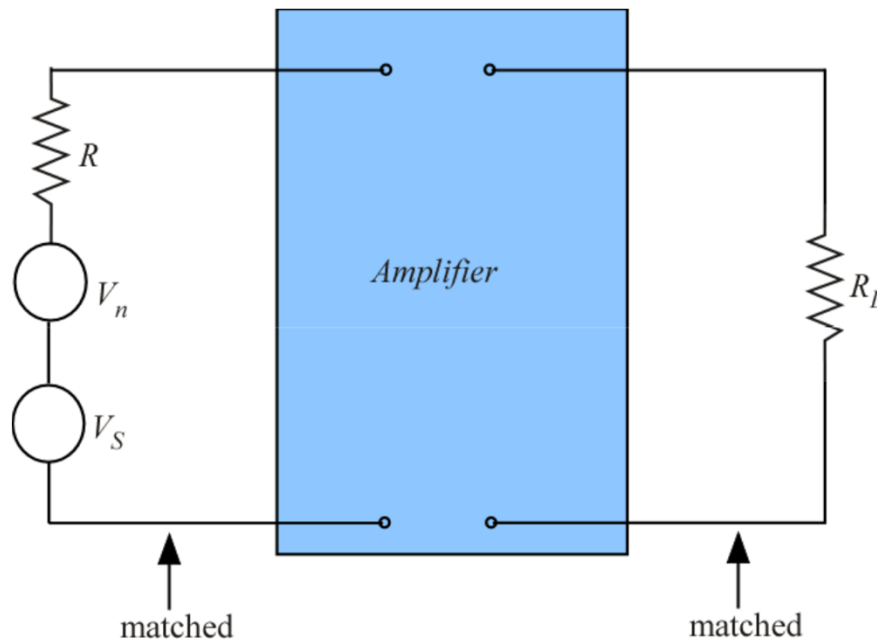

The noise at the input N_{in} is given by

$$N_{in} = \frac{V_n^2}{R_{in}} = \frac{4kTBR}{(2)^2 R} = kTB$$


S_{in} – Signal power into the amplifier

N_{in} – Noise power into the amplifier

S_o – Signal power at the output

N_o – Noise power at the output

Noise Factor

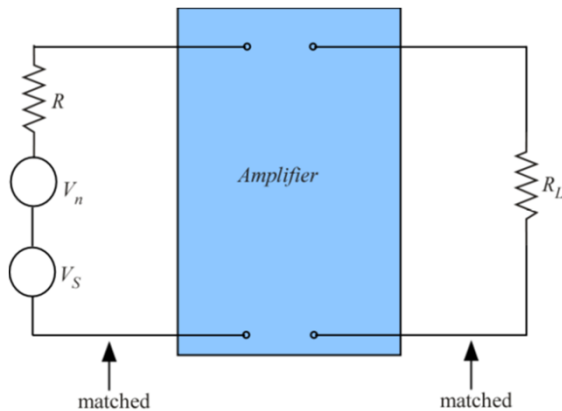

Let N_{int} be the noise power generated in the amplifier referenced to the amplifier input

The total noise power at the amplifier output is:

$$N_o = N_{in} G + N_{int} G$$

where G is the power gain. We define the noise factor as:

$$\text{Noise Factor} = F = \frac{S_{in} / N_{in}}{S_o / N_o} > 1 \quad \text{if noise is generated by the amplifier}$$

Noise Figure

$$F = \frac{S_{in} / N_{in}}{S_o / N_o} = \frac{S_{in}}{N_{in}} \times \frac{N_o}{S_o} = \frac{S_{in}}{N_{in}} \times \frac{N_o}{S_{in} G}$$

$$F = \frac{N_o}{kTBG} = \frac{N_{in} G + N_{int} G}{kTBG}$$

$$F(kTB) = kTB + N_{int}$$

$$N_{int} = (F - 1)kTB$$

The **Noise Figure** is the noise factor expressed in decibels


$$NF = 10 \log(F)$$

Noise Figure

$$F = \frac{S_{in} / N_{in}}{S_o / N_o} = \frac{S_{in}}{S_o} \times \frac{N_o}{N_{in}} = \frac{1}{G} \times \left[\frac{(N_{in} + N_{int})G}{N_{in}} \right]$$

$$F = \frac{1}{G} \times \left[\frac{(kTB + N_{int})G}{kTB} \right]$$

$N_{in} = kTB$ if matched

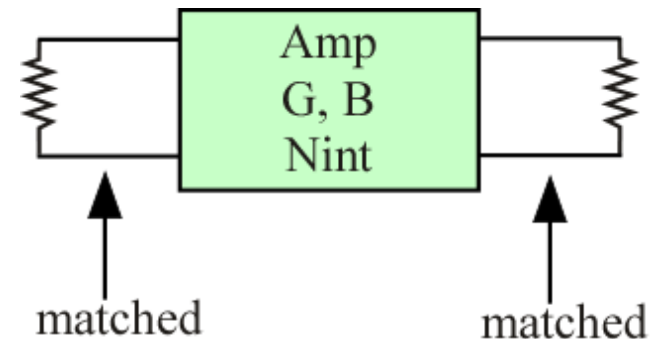

To have a standard value for F , we use $T = 290^\circ$ for the temperature of the resistor giving the N_{in}

$$F(G)kTB = (kTB + N_{int})G$$

$$(F - 1)kTB = N_{int}$$

Noise Figure - Example

Receiver

$NF=9$ dB, $BW=3$ kHz, $R_o = 500 \Omega$, $R_{in} = 50 \Omega$, $G = 10^8$

$$NF = 10 \log_{10} \frac{S_{in} / N_{in}}{S_o / N_o}$$

What input signal voltage do we need to get $S_o/N_o = 10$?

$$S_o = GS_{in} \quad N_o = GN_o|_{in}$$

$$N_o = kTBG + N_{int}G = kTBG + (F - 1)kTBG$$

$$N_o|_{in} = F(kTB) = 8 \times 1.38 \times 10^{-23} \times 290 \times 3 \times 10^3 = 9.936 \times 10^{-17} \text{ watts}$$


Noise Figure - Example

For $S_o/N_o = 10$, we need

$$S_{in} = 10N_o|_{in} = \frac{V_{in}^2}{R_{in}} = \frac{V_{in}^2}{50\Omega} = 10 \times 9.93 \times 10^{-17} \text{ watts}$$

$$V_{in} = 0.223 \mu\text{V}$$

Cascaded Stages

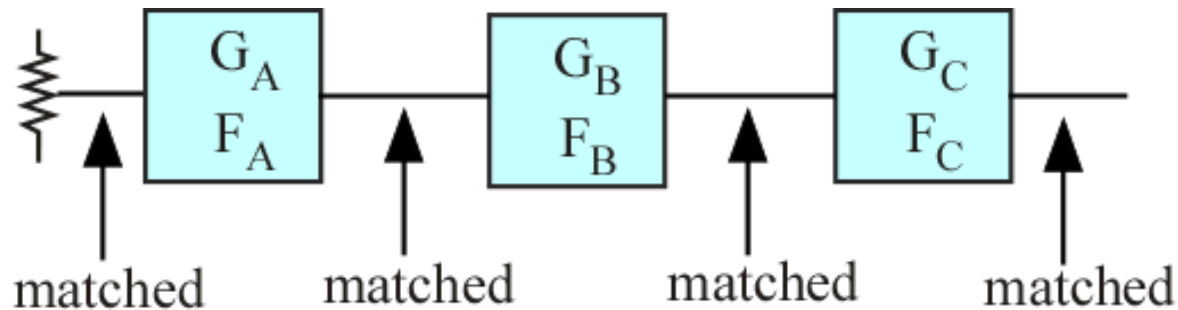


What is the overall Noise Factor?

$$N_{output} = kTBG_A G_B G_C + (F_A - 1)kTBG_A G_B G_C \\ + (F_B - 1)kTBG_B G_C + (F_C - 1)kTBG_C$$

F of 3 stages

$$F = \frac{N_o}{GN_{in}} = \frac{N_o}{kTBG_A G_B G_C} \\ = 1 + (F_A - 1) + \frac{(F_B - 1)}{G_A} + \frac{(F_C - 1)}{G_A G_B}$$

Cascaded Stages

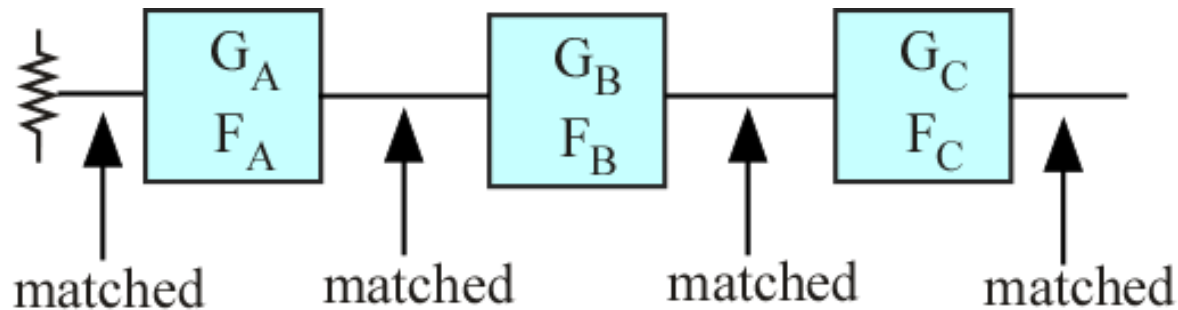


Noise Factor of 3 stages

$$F = F_A + \frac{(F_B - 1)}{G_A} + \frac{(F_C - 1)}{G_A G_B}$$

Frii's formula for m cascaded stages

$$F^T = F_1 + \sum_{n=2}^m \frac{F_n - 1}{\prod_{i=2}^n G_{i-1}}$$

Antenna

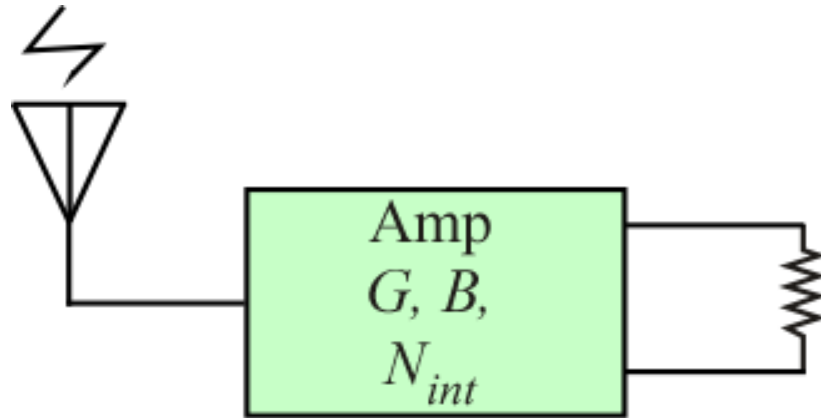

$$N_o = N_{int} G + N_A G$$


noise from antenna

We can write:

$$N_A = kT_A B$$

T_A = equivalent temperature of the antenna

Antenna

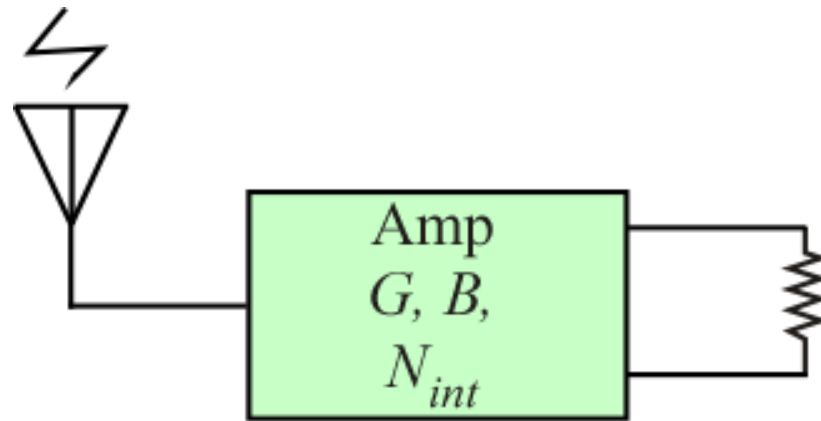

200- Ω antenna exhibiting an rms noise voltage of 0.1 μV with $B=10^4$ Hz

$$V^2 = 4kT_A RB$$

$$T_A = \frac{V^2}{4kRB} = \frac{10^{-14}}{1.38 \times 10^{-23} \times 200 \times 10^4} = 90.6\text{K}$$

Noise equivalent to that of a 200- Ω resistor at temperature of 90.6K

Antenna

Antenna temperatures

- T_A looking at earth = 300 K
- T_A looking at the moon = 450 K
- T_A looking at the sun = 3000 K

$$N_o = kT_{eq}BG$$

where T_{eq} is the temperature of the system referred to the input of the amplifier

$$N_o = kT_A BG + N_{int} G$$

$$kT_{eq}BG = kT_A BG + (F - 1)kT_{stan}BG$$

Antenna

$$T_{eq} = T_A + \underbrace{(NF - 1)T_{290}BG}_{T_{rec}}$$

$$F = \frac{S_{in} / N_{int}}{S_o / N_o}$$


For $F = 1$, the amplifier is noiseless and $T_{rec} = 0$

Cable

RG8v cable given 3dB loss per 100 ft at 200 MHz

Cable

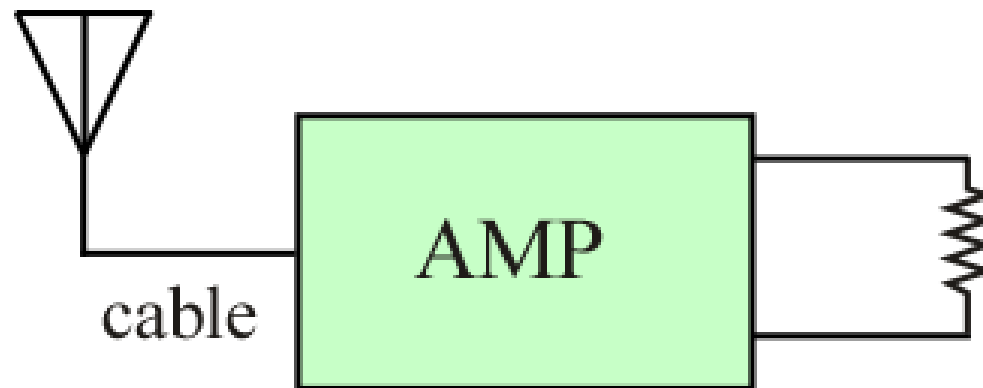- Attenuates signal
- Attenuates noise from antenna
- Generates noise




Cable

Let $L =$ loss factor of cable $L = \frac{P_{in}}{P_{out}}$

For 6-dB loss $L = 4$

N into the amplifier $= kT_{cable}B$

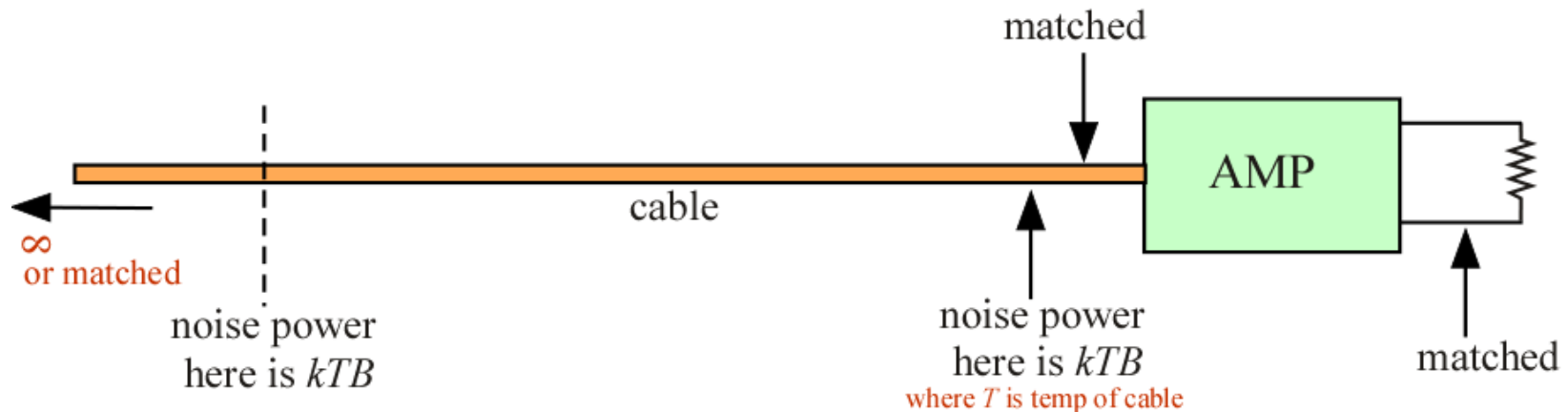Also, N into the amplifier $= \frac{kT_{cable}B}{L} +$ Noise generated in the finite length of cable




Cable

Let $L =$ loss factor of cable $L = \frac{P_{in}}{P_{out}}$

For 6-dB loss $L = 4$

N into the amplifier $= kT_{cable}B$

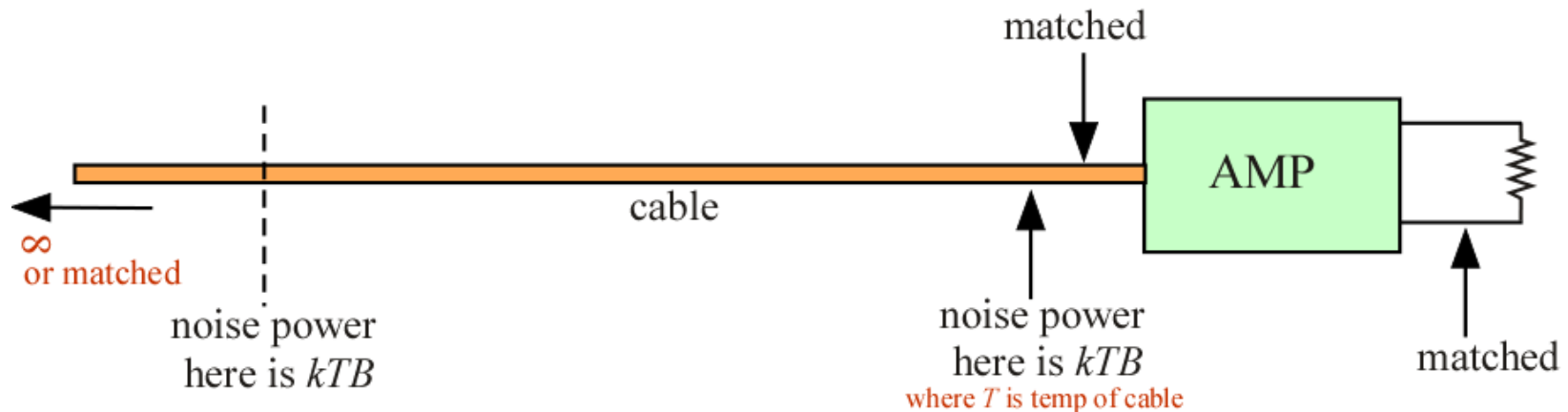Also, N into the amplifier $= \frac{kT_{cable}B}{L} +$ Noise generated in the finite length of cable



Cable

$$\text{Noise generated in the finite length of cable} = kT_{cable}B - \frac{kT_{cable}B}{L} = kT_{cable} \left[1 - \frac{1}{L} \right] B$$

The equivalent noise temperature of a finite

$$\text{length of cable} = T_{cable} \left[1 - \frac{1}{L} \right]$$

- For a short cable $L = 1$ and T_{eq} of cable = 0
- For a very long cable $L \rightarrow inf$ and T_{eq} of cable = T_{cable}

$$\underbrace{T_{system}}_{\text{referred to amp input}} = \frac{T_A}{L} + T_{cable} \left[1 - \frac{1}{L} \right] + T_{amp}$$

$$N_o|_{input} = kT_{system}B$$