


# ECE 453

# Wireless Communication Systems

## Network Parameters


Jose E. Schutt-Aine  
Electrical & Computer Engineering  
University of Illinois  
[jesa@illinois.edu](mailto:jesa@illinois.edu)

# Transfer Function Representation

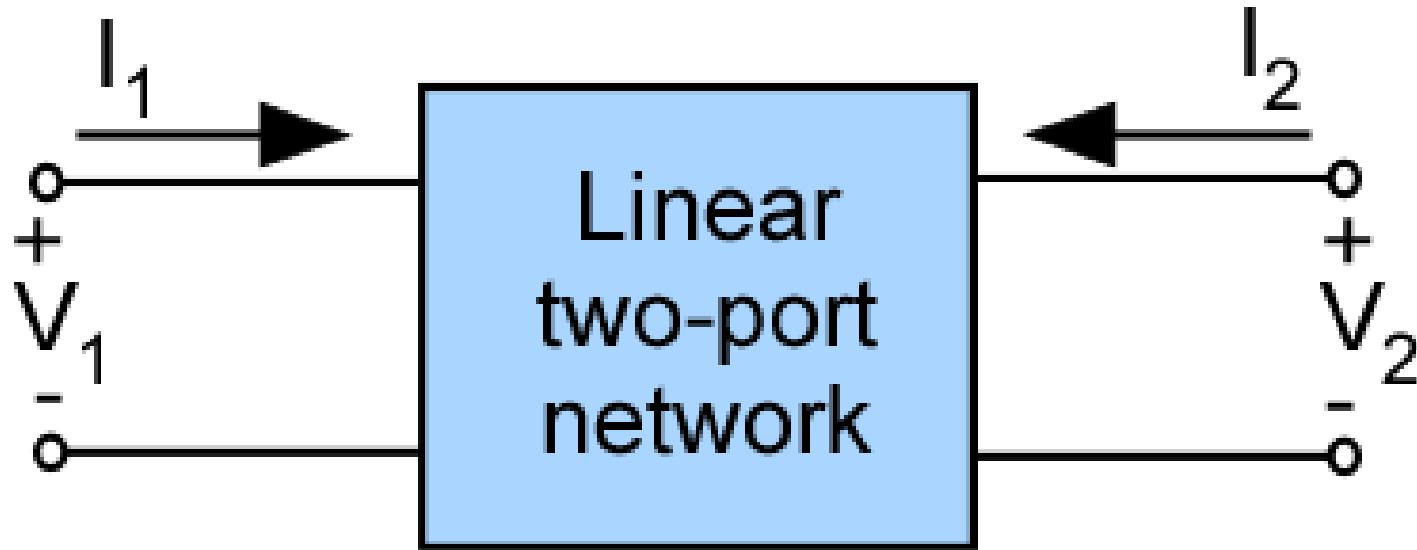

Use a two-terminal representation of system for input and output


# Y-parameter Representation

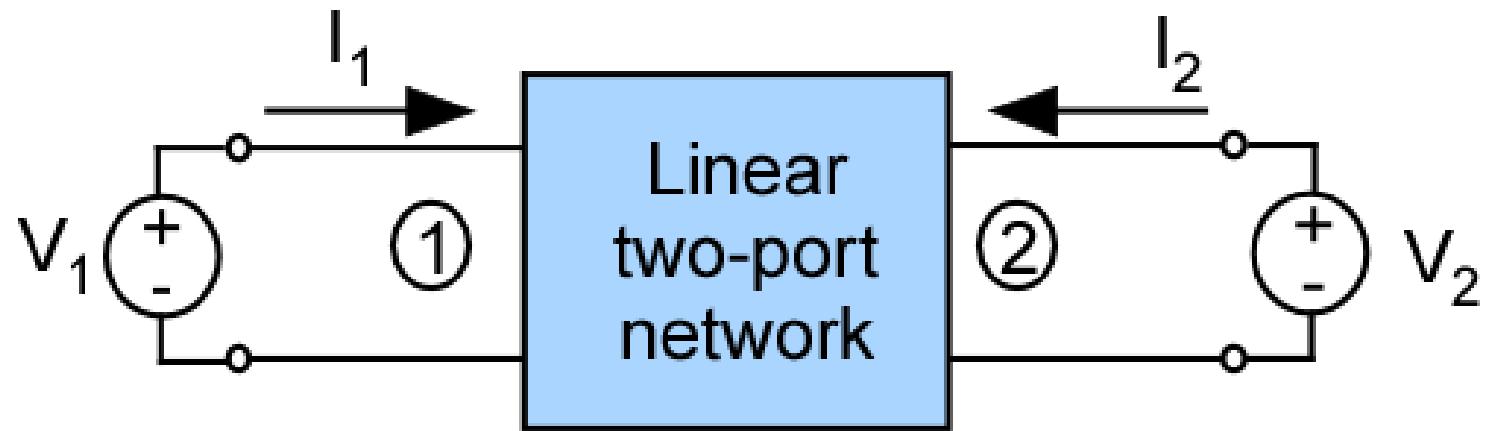

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

# Y Parameter Calculations

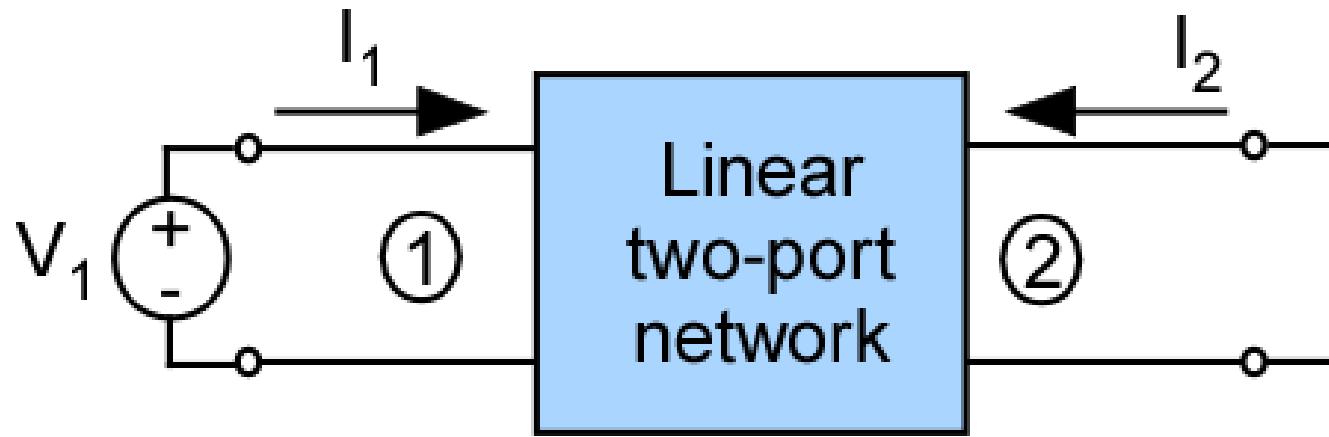


$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

To make  $V_2=0$ , place a short at port 2


# Z Parameters

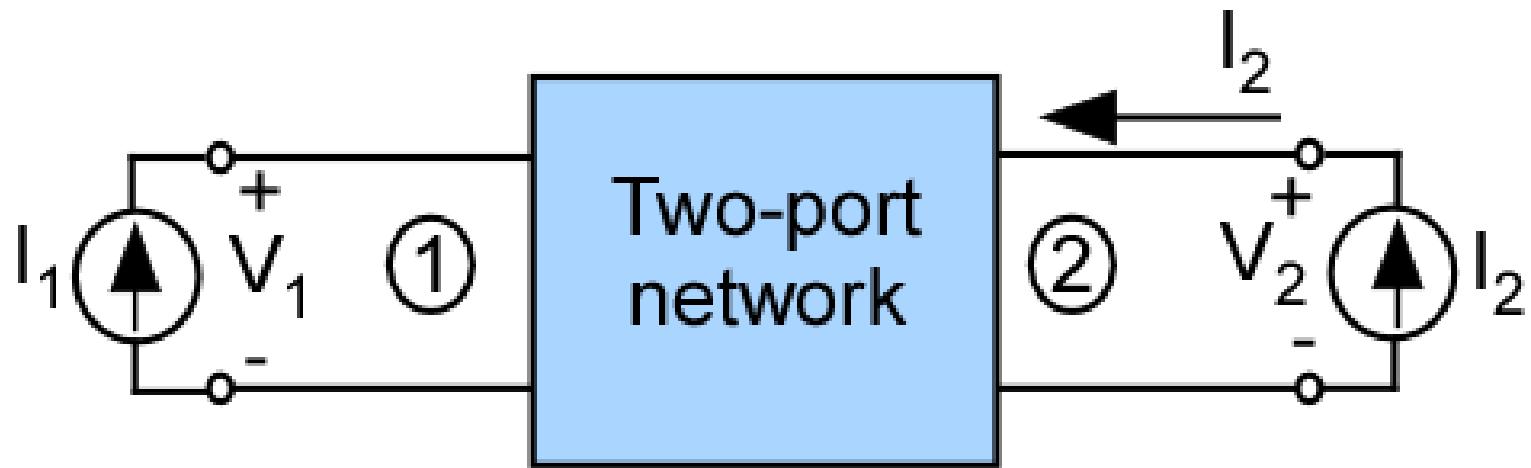

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

# Z-parameter Calculations

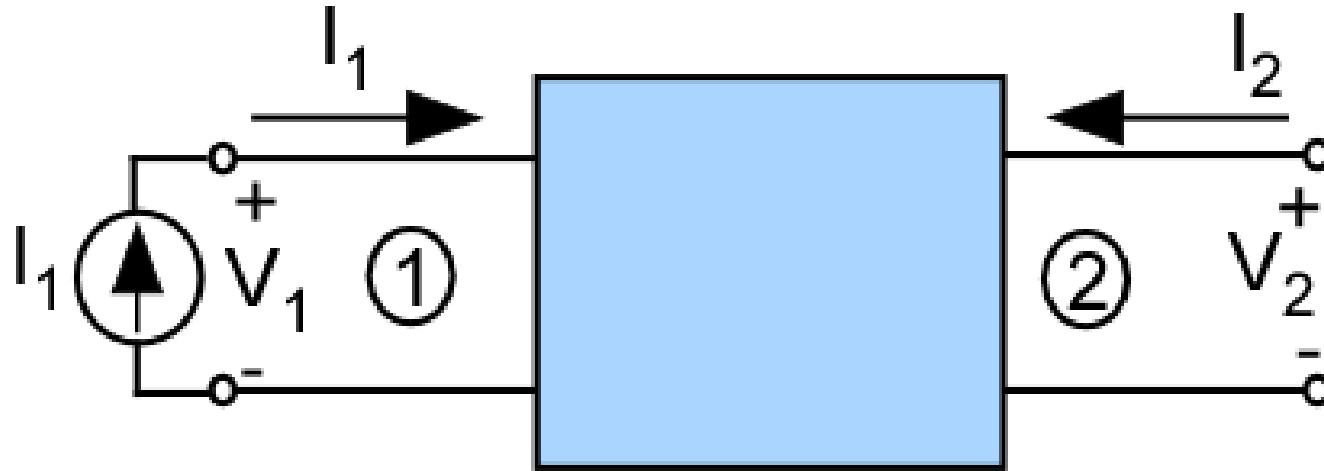


$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

To make  $I_2=0$ , place an open at port 2


# H Parameters

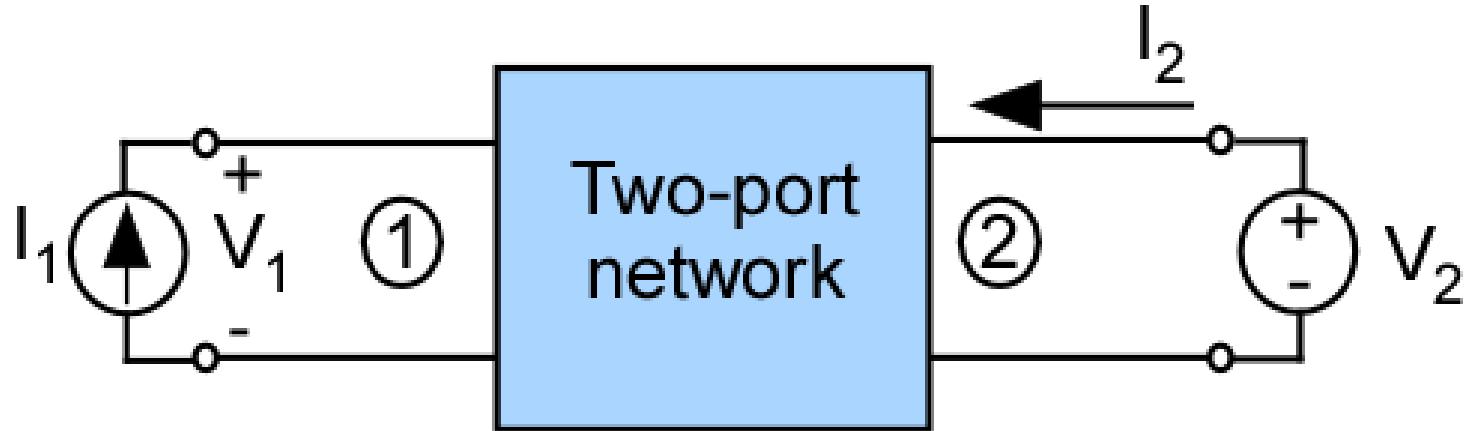

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$


# H Parameter Calculations

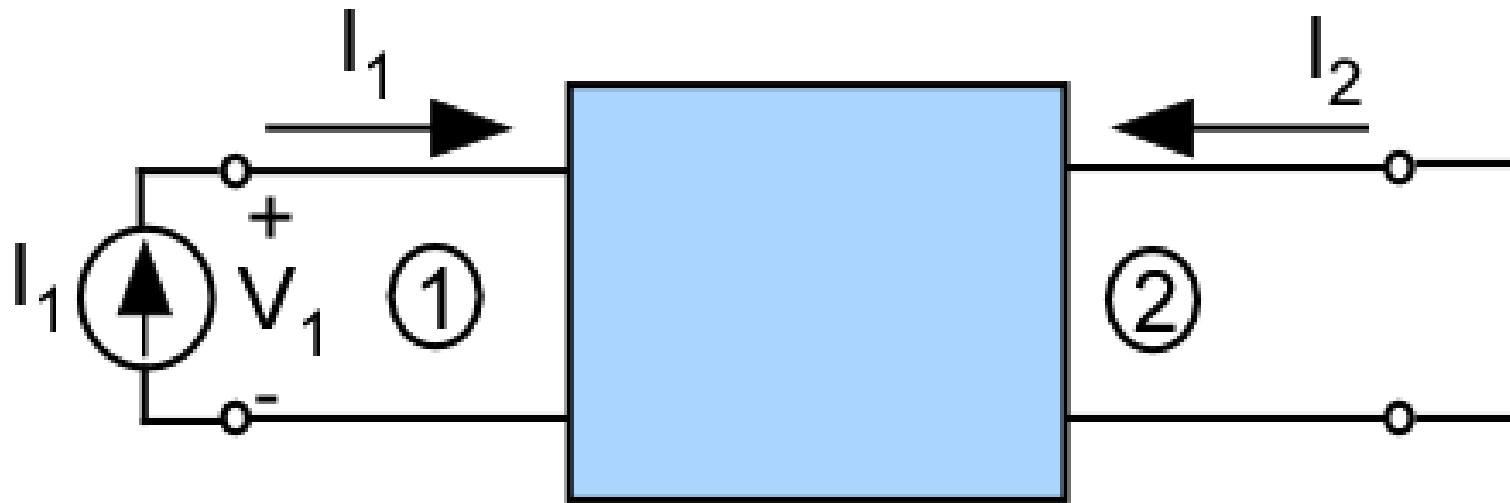

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$
$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

To make  $V_2=0$ , place a short at port 2


# G Parameters

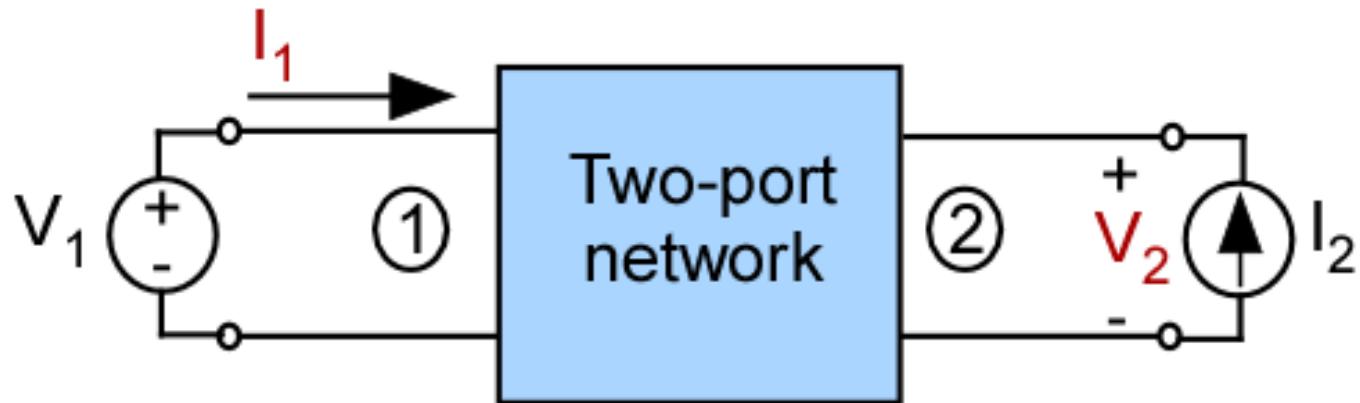

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$


# G-Parameter Calculations

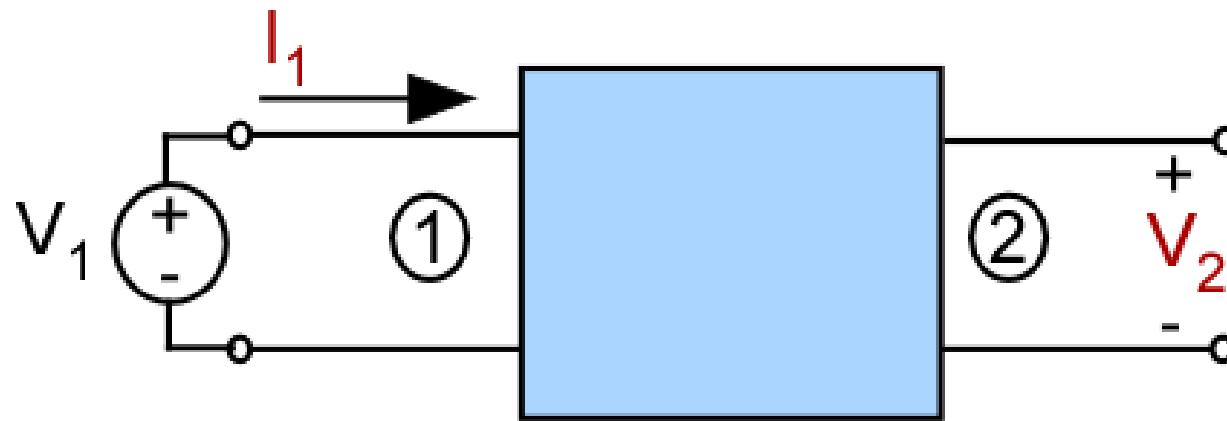

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$
$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

To make  $I_2 = 0$ , place an open at port 2

# Y-Parameters of TL

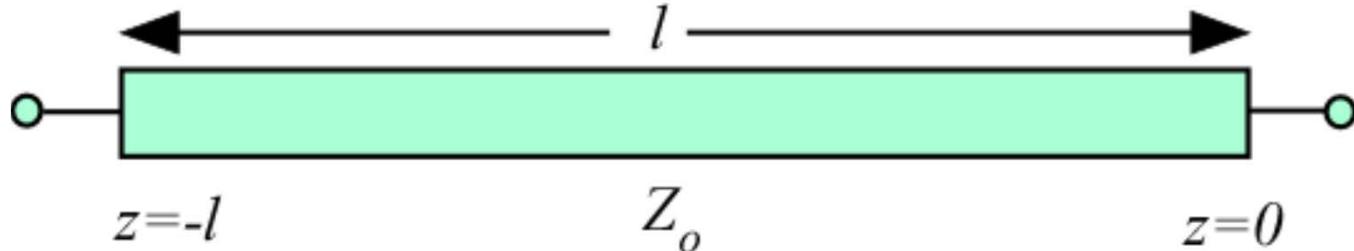


Find the Y-parameters of a lossless transmission line with propagation constant  $\beta$  and characteristic impedance  $Z_o$  (admittance  $Y_o$ )

$$V(z) = V_+ e^{-j\beta z} + V_- e^{+j\beta z}$$

$$I(z) = Y_o (V_+ e^{-j\beta z} - V_- e^{+j\beta z})$$

Let port 1 be at  $z = -l$  and port 2 at  $z = 0$

# Y-Parameters of TL

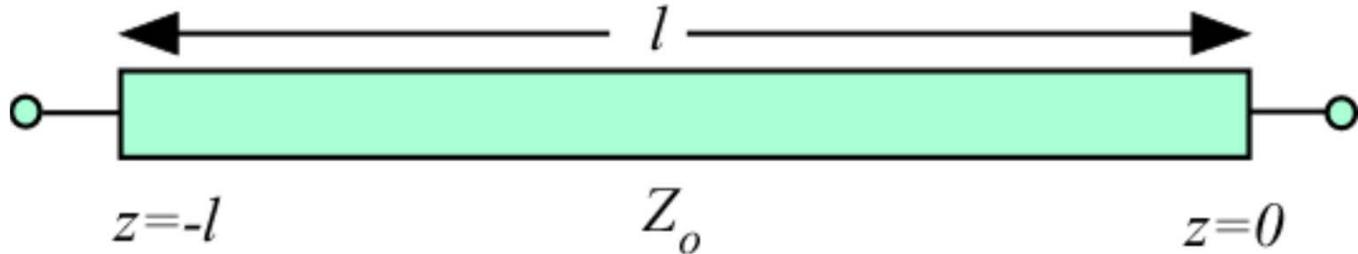

at port 1

$$V_1 = V_+ e^{+j\beta l} + V_- e^{-j\beta l}$$

$$I_1 = Y_o (V_+ e^{+j\beta l} - V_- e^{-j\beta l})$$


at port 2 ( $z = 0$ )

$$V_2 = V_+ + V_-$$

$$I_2 = -Y_o (V_+ - V_-)$$

$$V_+ = \frac{V_2 - Z_o I_2}{2} \quad \text{and} \quad V_- = \frac{V_2 + Z_o I_2}{2}$$

# Y-Parameters of TL

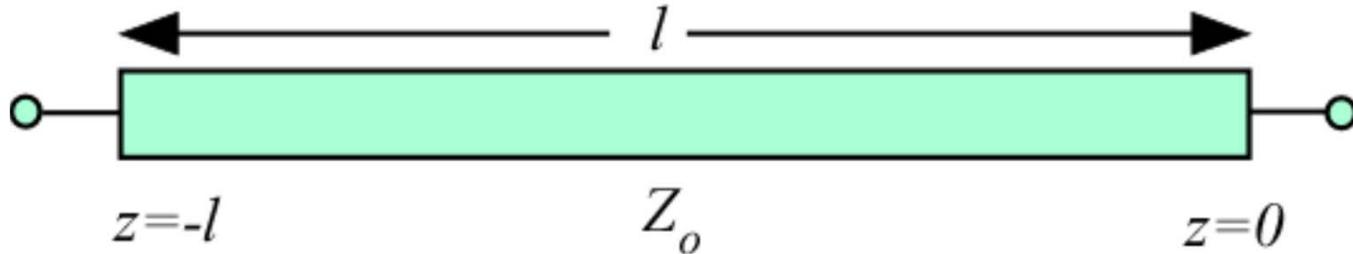

So that

$$V_1 = \left( \frac{V_2 - Z_o I_2}{2} \right) e^{+j\beta l} + \left( \frac{V_2 + Z_o I_2}{2} \right) e^{-j\beta l}$$


$$I_1 = Y_o \left( \frac{V_2 - Z_o I_2}{2} \right) e^{+j\beta l} - Y_o \left( \frac{V_2 + Z_o I_2}{2} \right) e^{-j\beta l}$$

and

$$V_1 = V_2 \cos \beta l - Z_o I_2 j \sin \beta l$$

$$I_1 = +Y_o V_2 j \sin \beta l - I_2 \cos \beta l$$

# Y-Parameters of TL

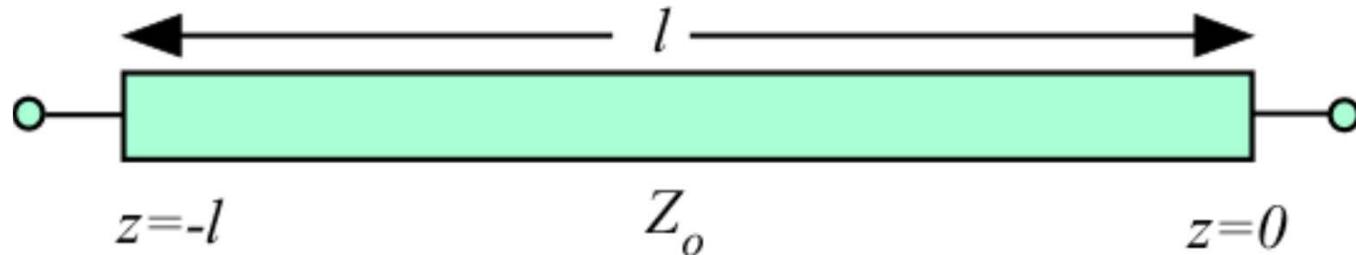

Using definitions for  $Y_{11}$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{-I_2 \cos \beta l}{-jZ_o I_2 \sin \beta l} = \frac{-jY_o \cos \beta l}{\sin \beta l}$$


and

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{-I_2}{-jZ_o I_2 \sin \beta l} = \frac{+jY_o}{\sin \beta l}$$

$$Y_{22} = Y_{11} \text{ by symmetry}$$

$$Y_{12} = Y_{21} \text{ by reciprocity}$$

# TWO-PORT NETWORK REPRESENTATION

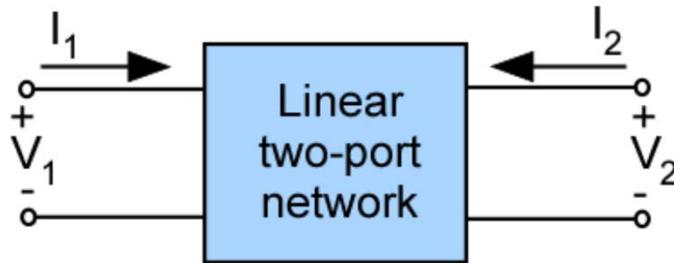

## Z Parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$


## Y Parameters

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$


- At microwave frequencies, it is more difficult to measure total voltages and currents.
- Short and open circuits are difficult to achieve at high frequencies.
- Most active devices are not short- or open-circuit stable.

# Two-Ports in Parallel

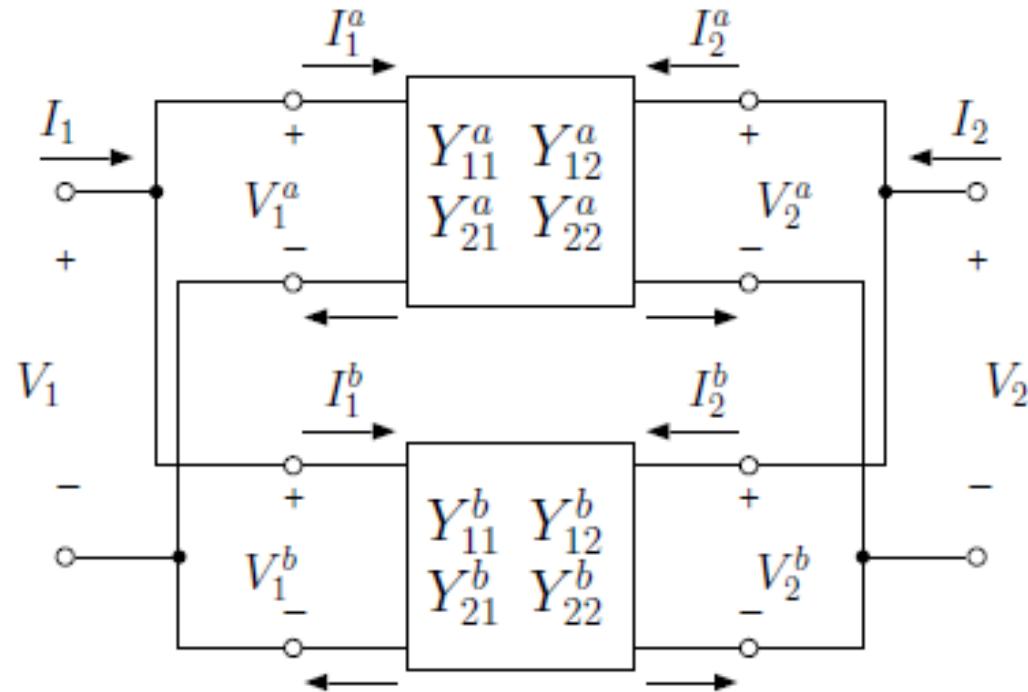


$$\mathbf{Y} = \mathbf{Y}^a + \mathbf{Y}^b$$

# Two-Ports in Series

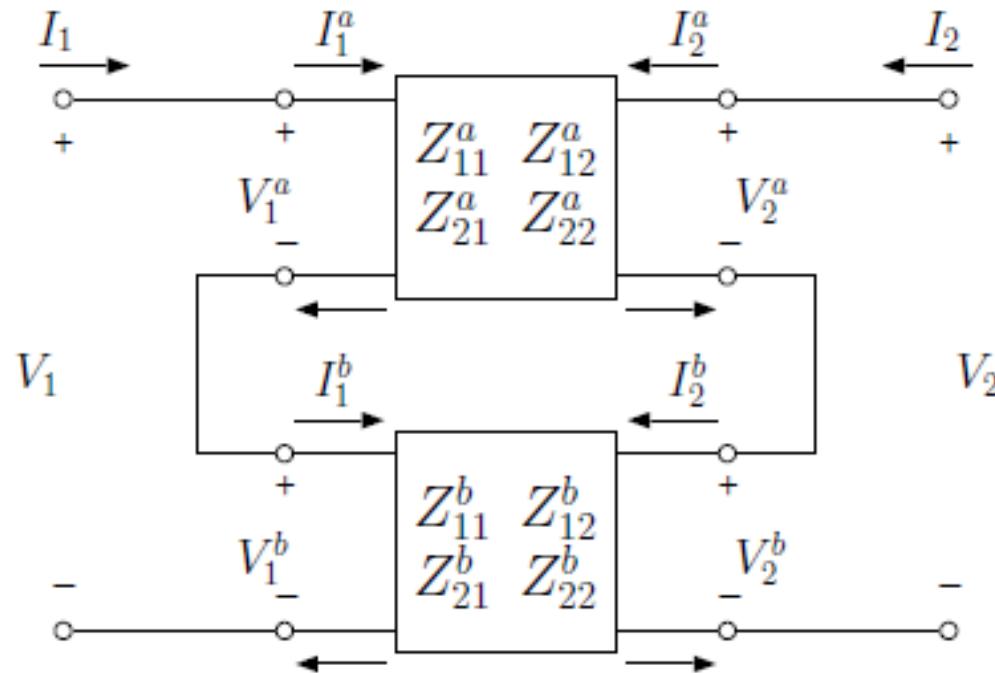

$$\mathbf{Z} = \mathbf{Z}^a + \mathbf{Z}^b$$

# ABCD -Parameters

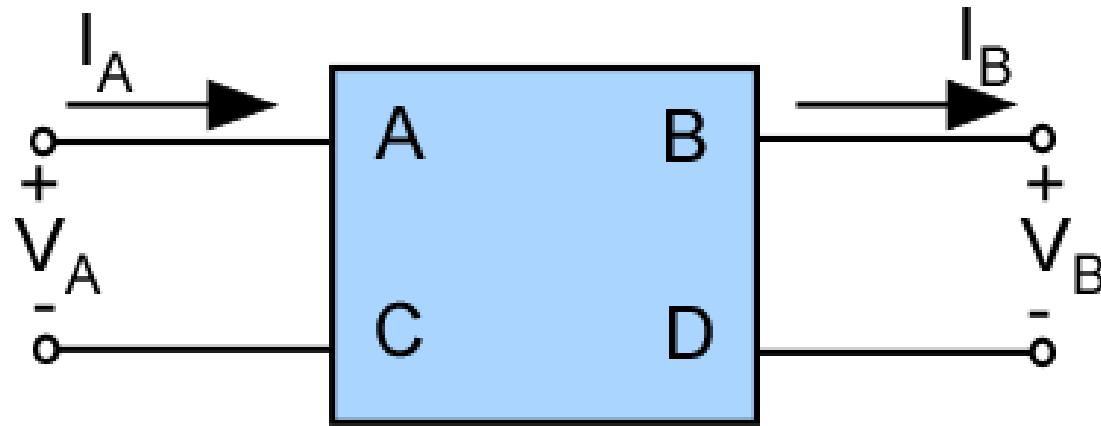

$$V_A = AV_B + BI_B$$

$$I_A = CV_B + DI_B$$



# ABCD -Parameters

$$V_A = V_1$$

$$V_B = V_2$$

$$I_A = I_1$$


$$I_B = -I_2$$

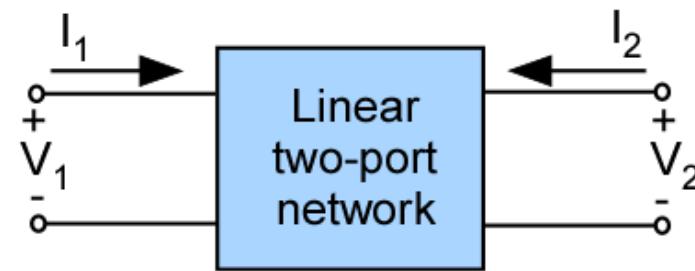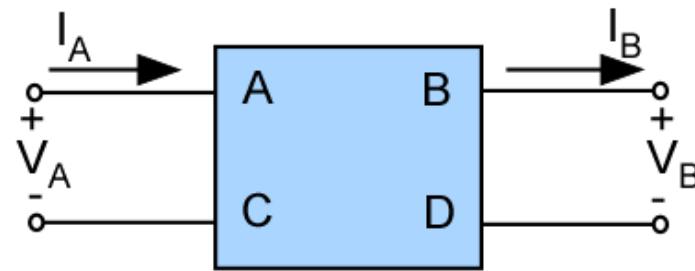

Relationship with Z parameters is obtained by first expressing ABCD parameters in terms of Z parameters

# ABCD -Parameters


From

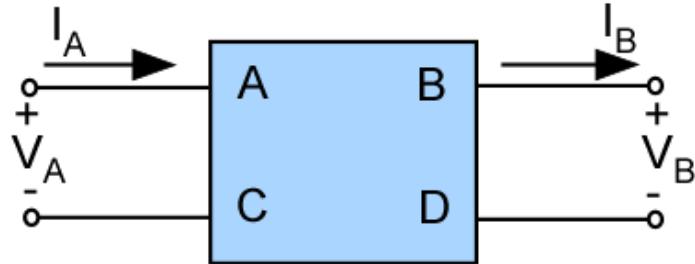

$$V_A = Z_{11}I_A - Z_{12}I_B$$

$$V_B = Z_{21}I_A - Z_{22}I_B$$

We get

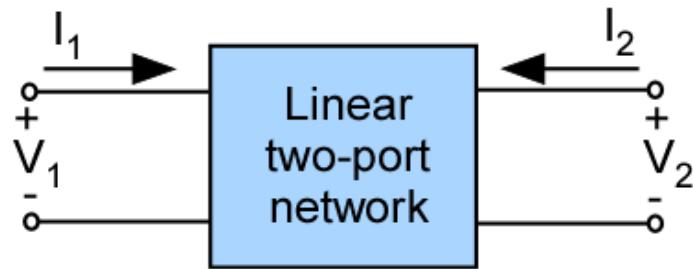


$$A = \frac{Z_{11}}{Z_{21}} \quad B = \frac{\Delta}{Z_{21}}$$

$$C = \frac{1}{Z_{21}} \quad D = \frac{Z_{22}}{Z_{21}}$$


$$\Delta = Z_{11}Z_{22} - Z_{12}Z_{21}$$

# ABCD -Parameters

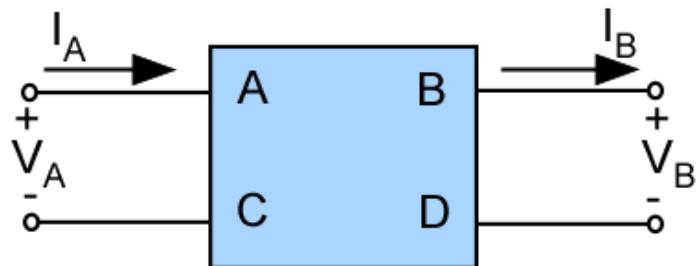

$$Z_{11} = \frac{A}{C}$$

$$Z_{12} = \frac{(AD - BC)}{C}$$

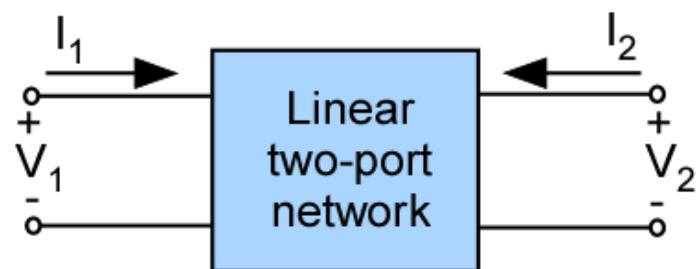

$$Z_{21} = \frac{1}{C}$$

$$Z_{22} = \frac{D}{C}$$



For a reciprocal network,  $Z_{21} = Z_{12}$ , therefore

$$AD - BC = 1$$



Reciprocity condition  
for ABCD parameters

# ABCD -Parameters

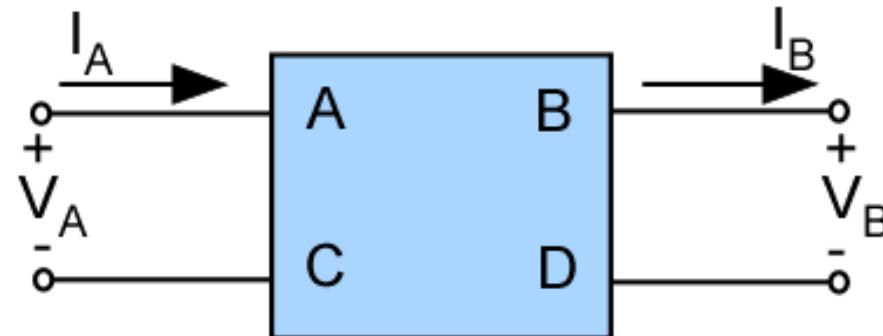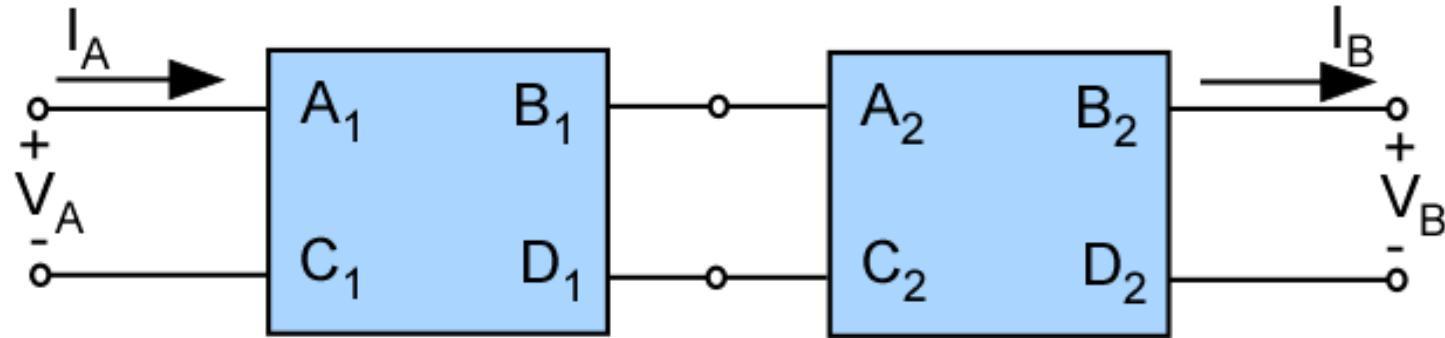

When cascading two-ports, it is best to use ABCD parameters. Put voltage and currents in cascadable form with the input variables in terms of the output variables

$$\text{ABCD} = (\text{ABCD})_1 \cdot (\text{ABCD})_2$$