

ECE 546

Lecture 11

MOS Amplifiers


Spring 2018

Jose E. Schutt-Aine
Electrical & Computer Engineering
University of Illinois
jesa@illinois.edu

Amplifiers

- **Definitions**

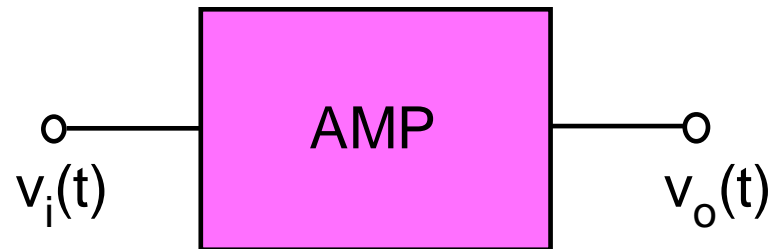- Used to increase the amplitude of an input signal to a desired level
- This is a fundamental signal processing function
- Must be linear (free of distortion) – Shape of signal preserved



$v_o(t) = Av_i(t)$, where A is the voltage gain

$$\text{Voltage Gain: } A_v = \frac{v_o}{v_i}$$

$$\text{Power Gain: } A_p = \frac{\text{Load Power } (P_L)}{\text{Input Power } (P_I)}$$

Amplifiers

$$A_p = \frac{v_o i_o}{v_I i_I}$$

$$\text{Current Gain: } A_i = \frac{i_o}{i_i}$$

$$\text{Note: } A_p = A_v A_i$$

Expressing gain in dB (decibels)


$$\text{Voltage gain in dB} = 20 \log |A_v|$$

$$\text{Current gain in dB} = 20 \log |A_i|$$

$$\text{Power gain in dB} = 10 \log |A_p|$$

Amplifiers

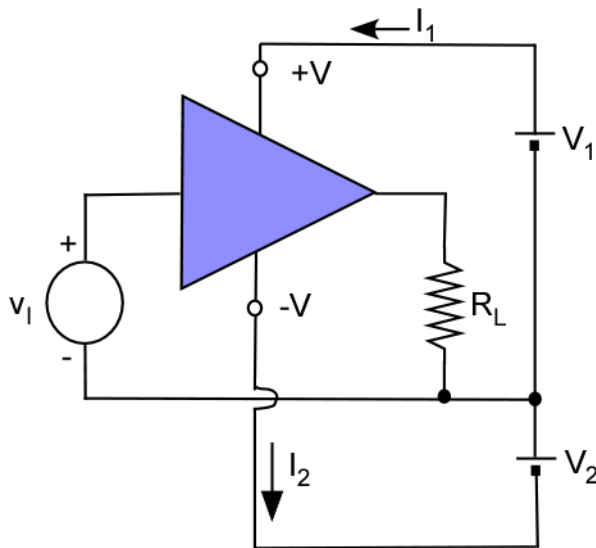Since output associated with the signal is larger than the input signal, power must come from DC supply




$$P_{DC} = V_1 I_1 + V_2 I_2$$

$$P_{DC} + P_I = P_L + P_{dissipated}$$

$$\eta = \frac{P_L}{P_{DC}} \times 100 = \text{Power Efficiency}$$

Biassing of Amp

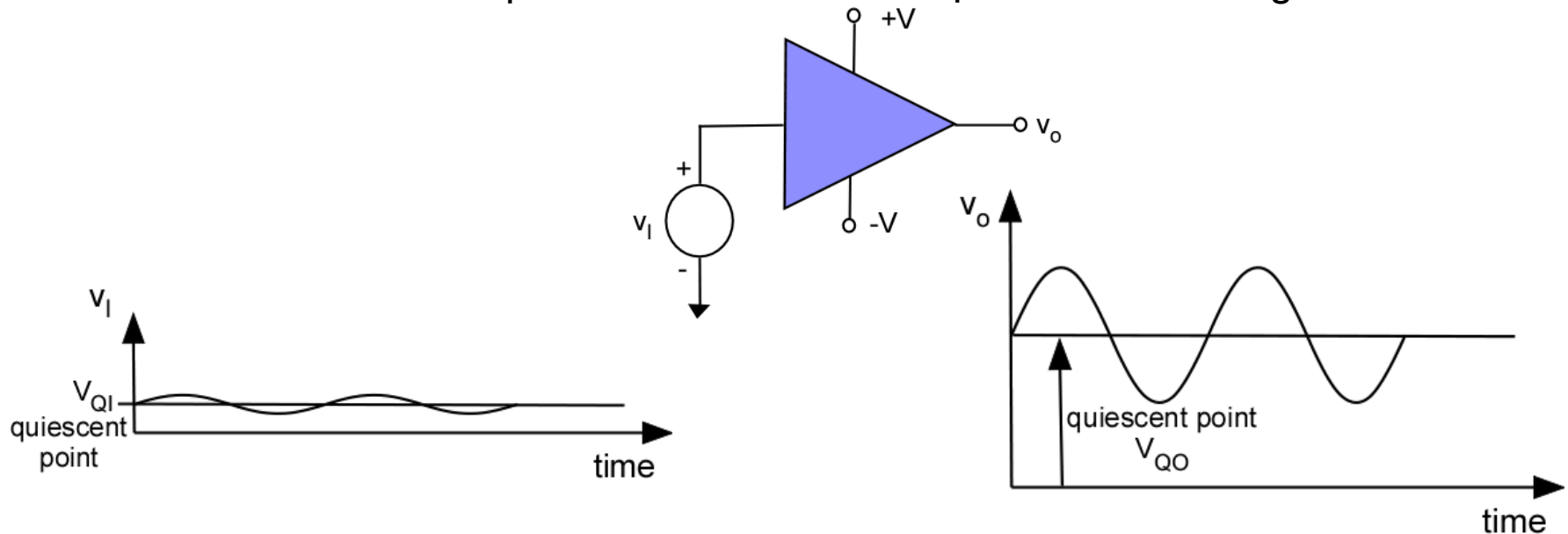Bias will provide quiescent points for input and output about which variations will take place. Bias maintain amplifier in active region.



$$V_I(t) = V_{QI} + v_I(t)$$

$$V_o(t) = V_{QO} + v_o(t)$$

$$v_o(t) = A_v v_I(t)$$

$$A_v = \left. \frac{dv_o}{dv_I} \right|_{at Q}$$

Amplifier characteristics are determined by bias point

Small-Signal Model

- **What is a small-signal incremental model?**
 - Equivalent circuit that only accounts for signal level fluctuations about the DC bias operating points
 - Fluctuations are assumed to be small enough so as not to drive the devices out of the proper range of operation
 - Assumed to be linear
 - Derives from superposition principle


Biasing of MOS Transistors

- **Bias Characteristics**


- Operation in saturation region
- Stable and predictable drain current

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

Single-Supply MOS Bias

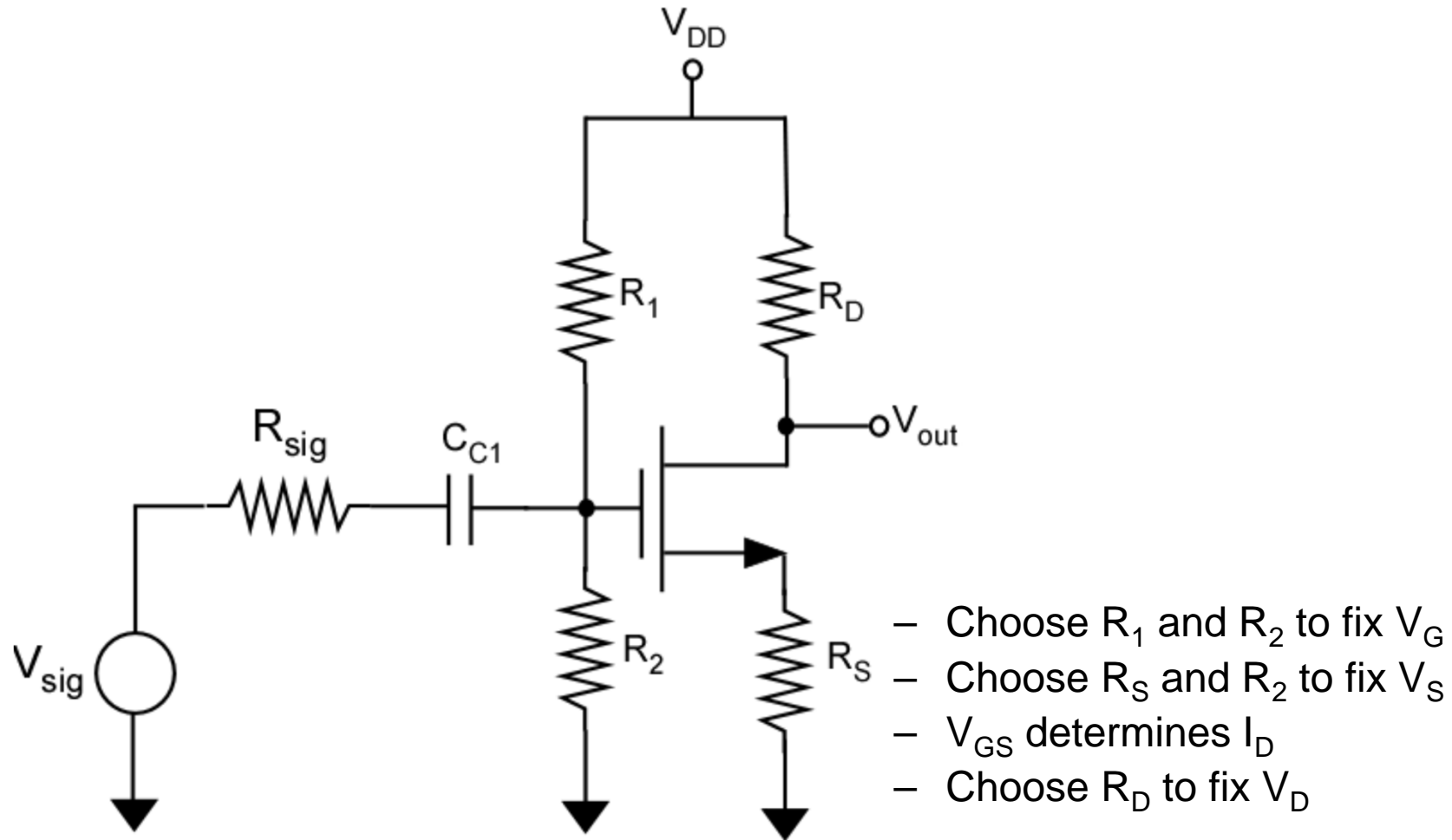


Common Source MOSFET Amplifier

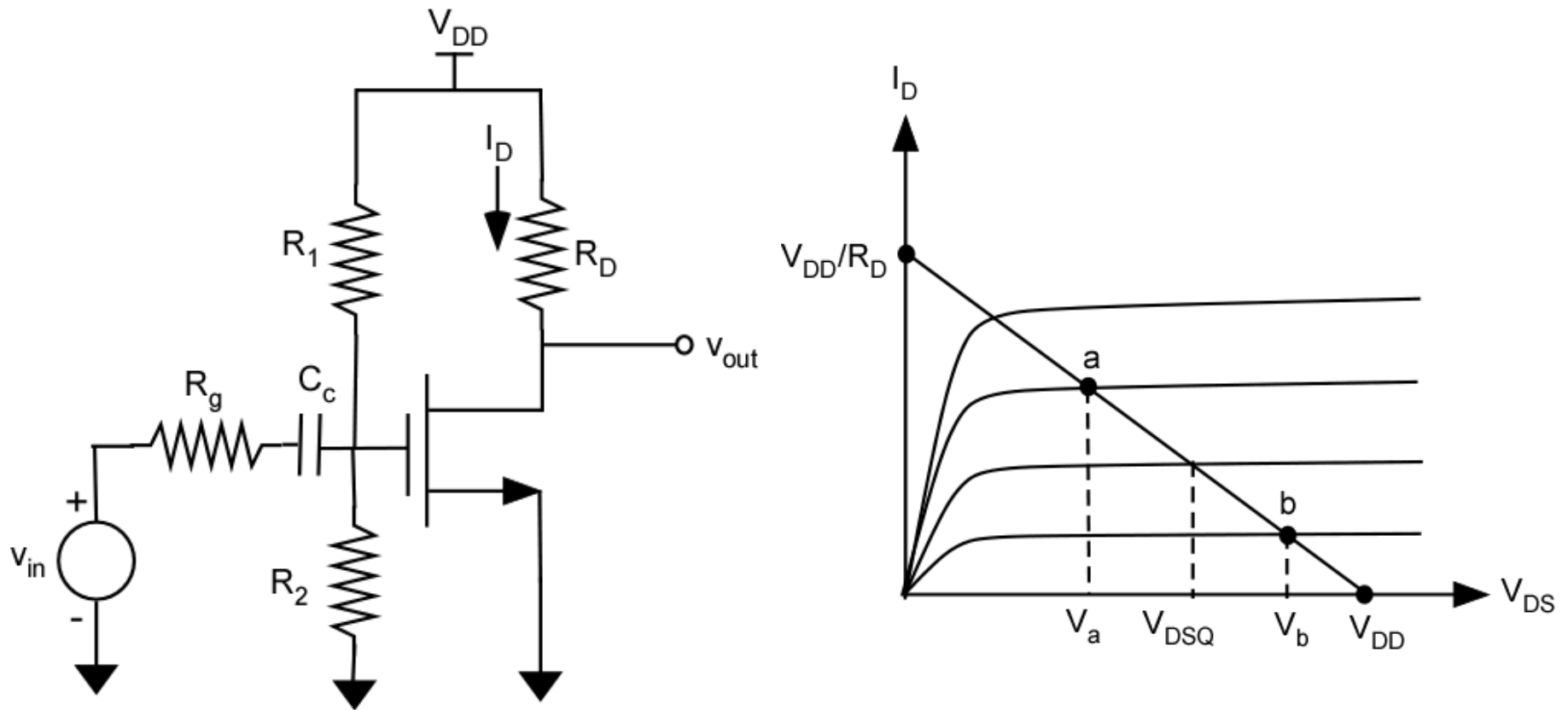

Bias is to keep MOS in saturation region

Common Source MOSFET Amplifier

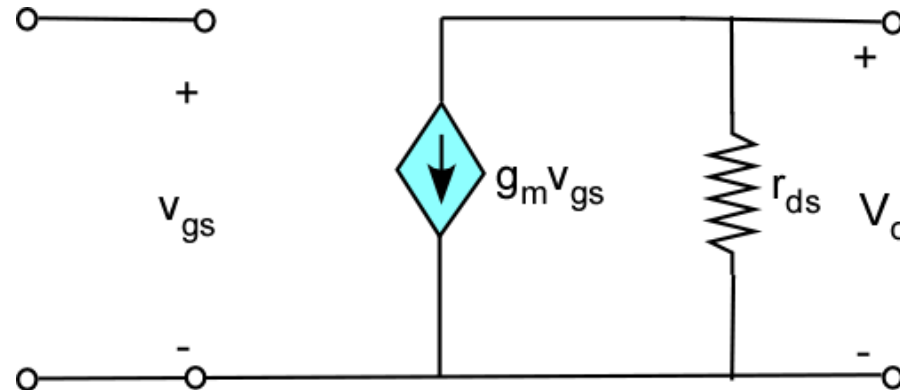Small-Signal Equivalent Circuit for MOS (device only)



$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_T)^2$$

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{GS}=V_{GSQ}} = \frac{2I_D}{V_{eff}}$$

where $V_{GS} - V_T = V_{eff}$

Which leads to

$$g_m = \sqrt{2k_n'} \sqrt{W/L} \sqrt{I_D}$$

g_m is proportional to $= \sqrt{W/L}$

MOSFET Output Impedance

To calculate r_{ds} , account for λ


$$r_{ds} = \left. \frac{\partial V_{DS}}{\partial I_D} \right|_{V_{GS}=V_{GSQ}} = \frac{1}{\lambda \mu \frac{W}{2L} C_{ox} [V_{GS} - V_T]^2} = \frac{1}{\lambda I_{DP}}$$

$$I_{DP} = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_T)^2$$

r_{ds} , accounts for channel width modulation resistance.

Midband Frequency Gain

Incremental model for complete amplifier

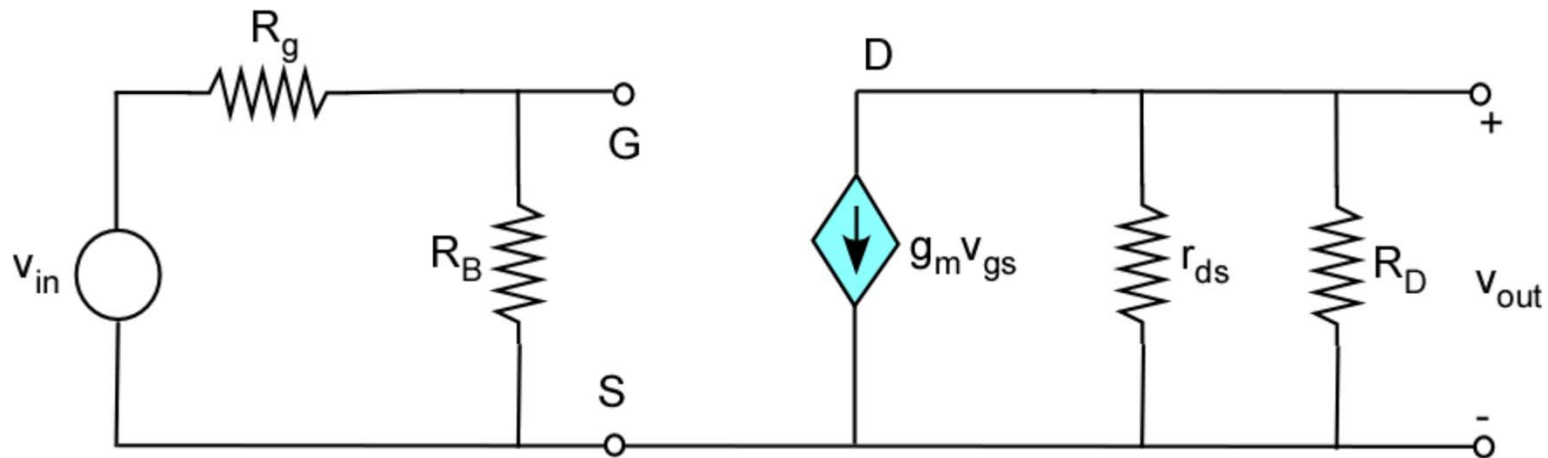


$$A_{MB} = \frac{v_{out}}{v_{in}} = -\frac{R_B}{R_B + R_g} g_m \frac{r_{ds} R_D}{r_{ds} + R_D}$$

Example

For the circuit shown, $k=75 \mu\text{A}/\text{V}^2$, $V_T=1 \text{ V}$, $\lambda=0$

(a) Find V_{DQ} , V_{SQ}

(b) Find the midband gain

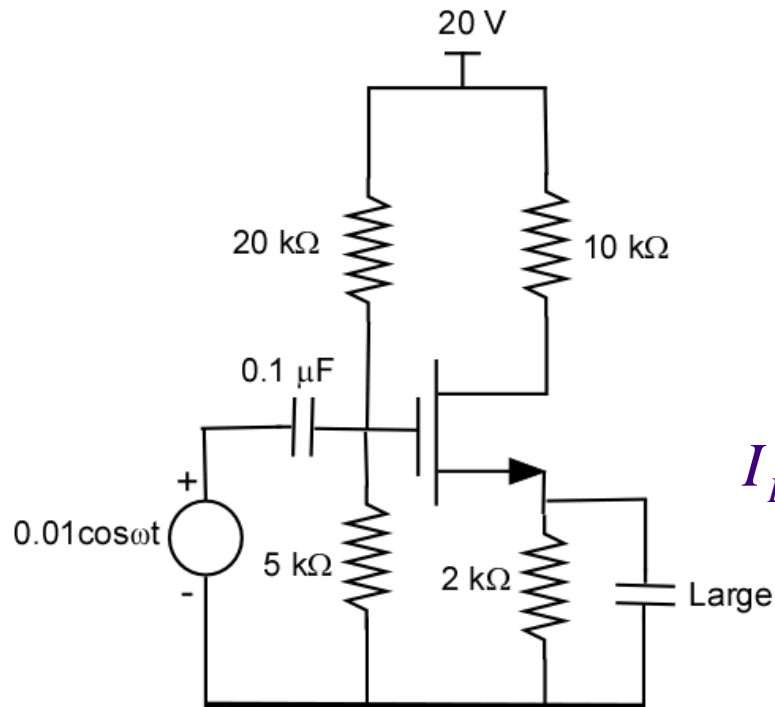

$$V_{GQ} = V_{DD} \frac{R_2}{R_1 + R_2} = \frac{20 \times 5}{25} = 4 \text{ V}$$

$$V_{GSQ} = V_{GQ} - V_{SQ} = 4 - 2I_{DQ}$$

$$I_{DQ} = K [V_{GSQ} - V_T]^2 = 0.075 [4 - 2I_{DQ} - 1]^2$$

$$I_{DQ} = 0.075(9 - 12I_{DQ} + 4I_{DQ}^2)$$

$$4I_{DQ}^2 - 12I_{DQ} + 9 = 13.3I_{DQ} \Rightarrow I_{DQ}^2 - 6.33I_{DQ} + 2.25 = 0$$

Example (Cont')

$$I_{DQ} = 3.167 \pm \frac{\sqrt{6.33^2 - 9}}{2} = 0.378 \text{ mA or } 5.953 \text{ mA}$$

reject since voltage drop across R_D will be too large

$$I_{DQ} = 0.378 \text{ mA}$$

$$V_{DQ} = V_{DD} - R_D I_{DQ} = 20 - 10 \times 0.378 = 16.22 \text{ V}$$

$$V_{SQ} = R_S I_{DQ} = 2 \times 0.378 = 0.756 \text{ V}$$

$$V_{DQ} = 16.22 \text{ V}$$

$$V_{SQ} = 0.756 \text{ V}$$


Example (Cont')

$$g_m = \sqrt{2k'_n \frac{W}{L} I_{DQ}} = \sqrt{4 \times 0.075 \times 0.378} = 0.337$$

$$A_{MB} = -g_m R_D = -0.337 \times 10 = -3.37$$

$$A_{MB} = -3.37$$

Low-Pass Circuit

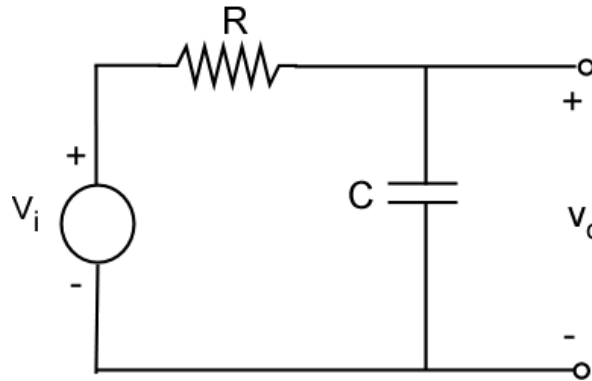


In frequency domain:
$$V_o = \frac{V_i}{R + \frac{1}{j\omega C}} \cdot \frac{1}{j\omega C}$$

$$V_o = \frac{V_i}{1 + j\omega RC} \Rightarrow A_v = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$

$$A_v = \frac{1}{1 + j\omega RC} = \frac{1}{1 + jf / f_2}$$



Low-Pass Circuit
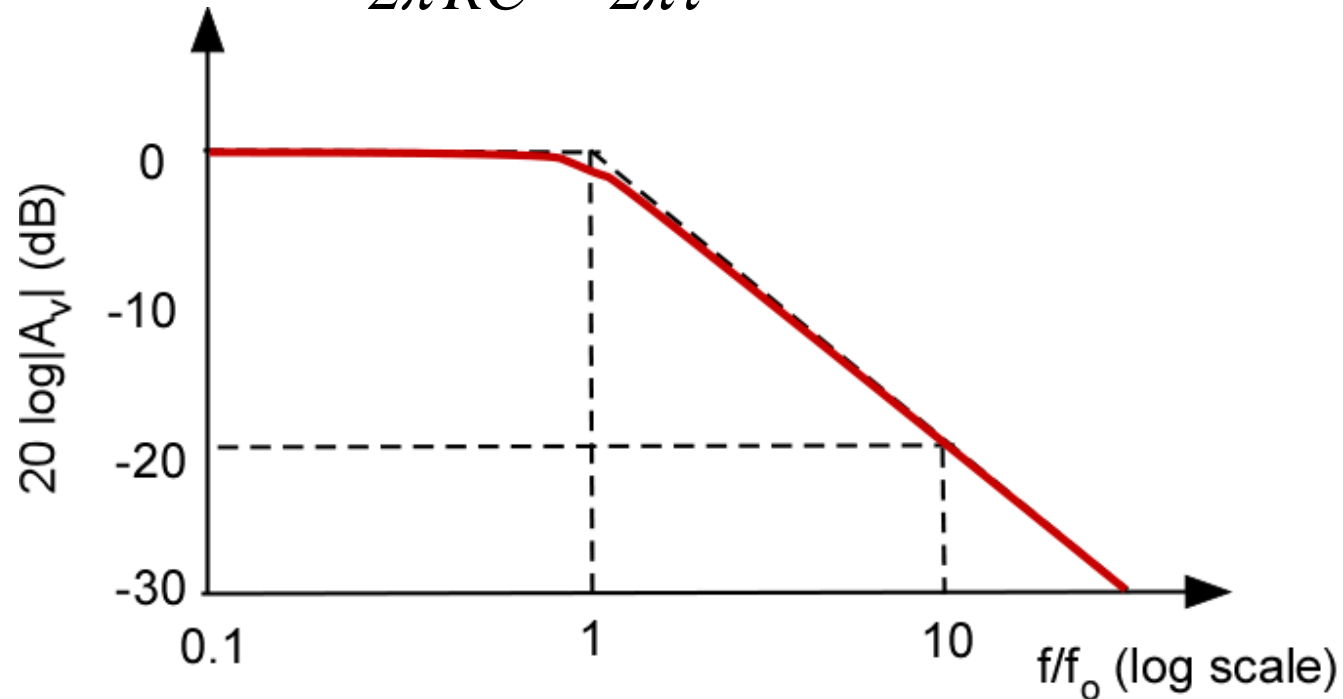
$$f_2 = \frac{1}{2\pi RC} = \frac{1}{2\pi\tau}$$



$$\tau = 2\pi RC = \text{time constant}$$

High-Pass Circuit

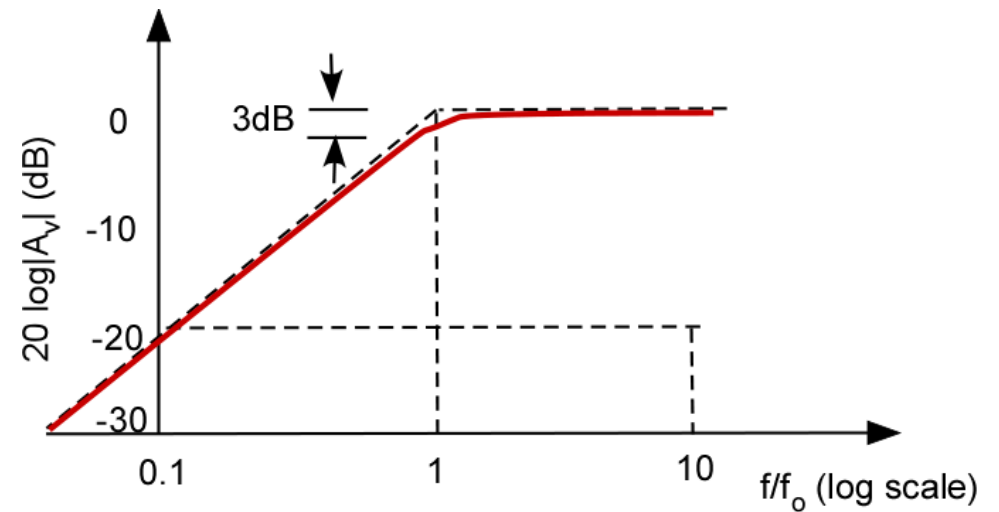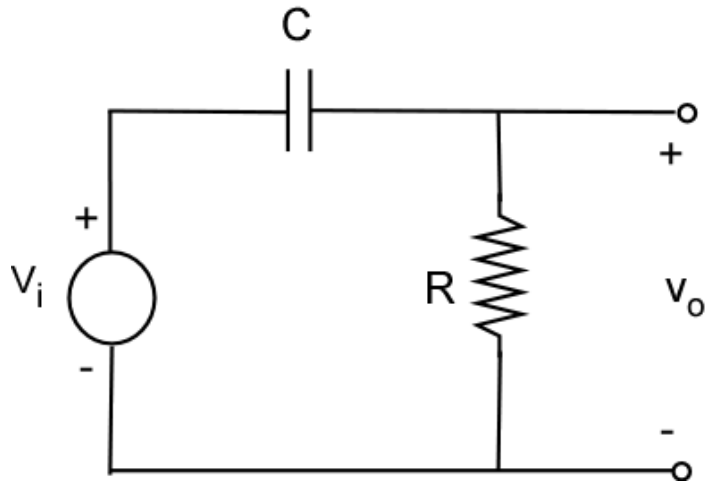

$$V_o = \frac{V_i R}{R + \frac{1}{j\omega C}} = \frac{V_i}{1 + \frac{1}{j\omega RC}}$$



$$A_v = \frac{V_o}{V_i} = \frac{1}{1 - j \frac{1}{2\pi f RC}} = \frac{1}{1 - j f_2 / f}$$

$$f_2 = \frac{1}{2\pi RC}$$

Model for general Amplifying Element


C_{c1} and C_{c2} are coupling capacitors (large) $\rightarrow \mu\text{F}$

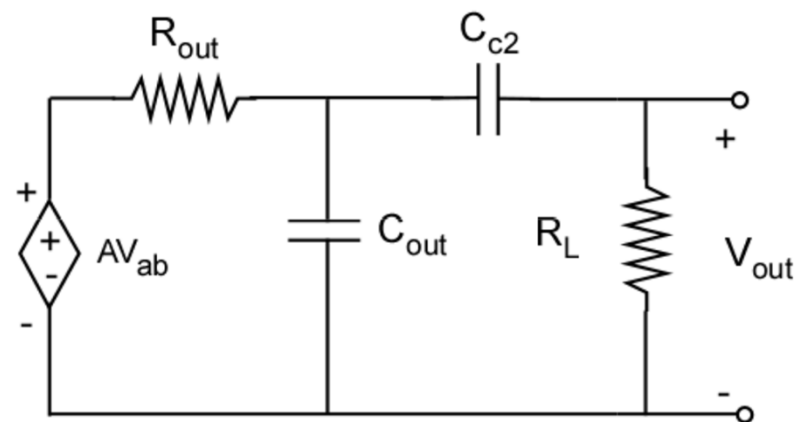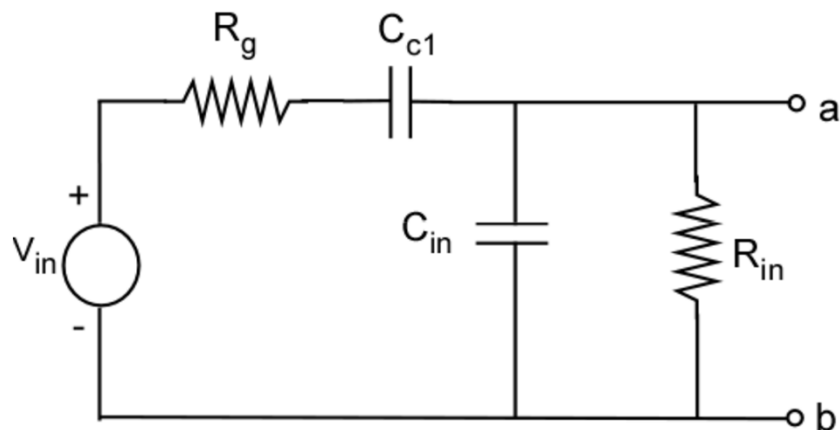C_{in} and C_{out} are parasitic capacitors (small) $\rightarrow \text{pF}$



Midband Frequencies

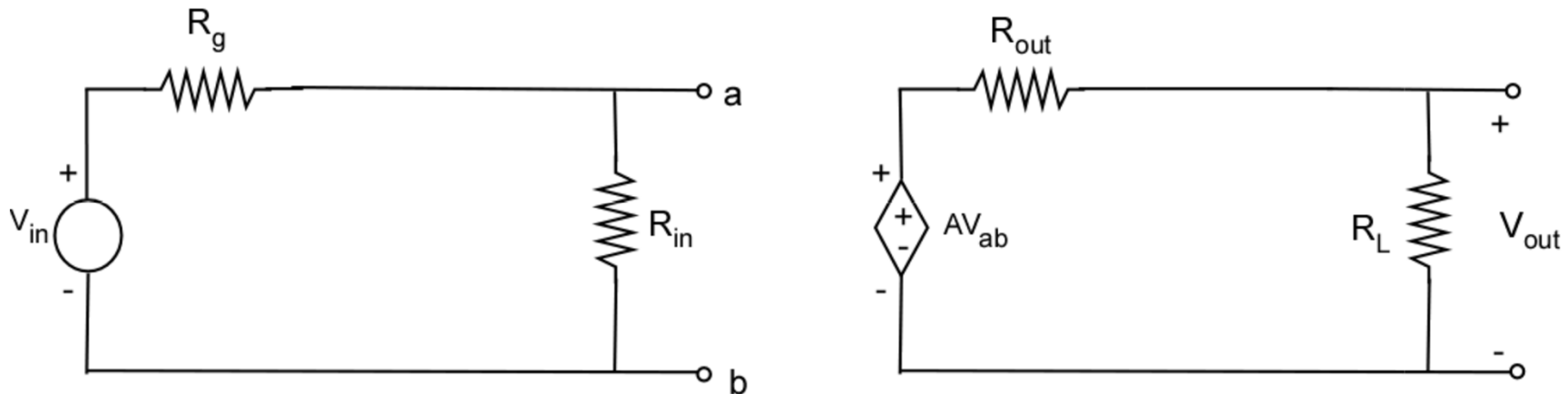
- Coupling capacitors are short circuits
- Parasitic capacitors are open circuits



$$A_{MB} = \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_g + R_{in}} A \frac{R_L}{R_{out} + R_L}$$

Low Frequency Model

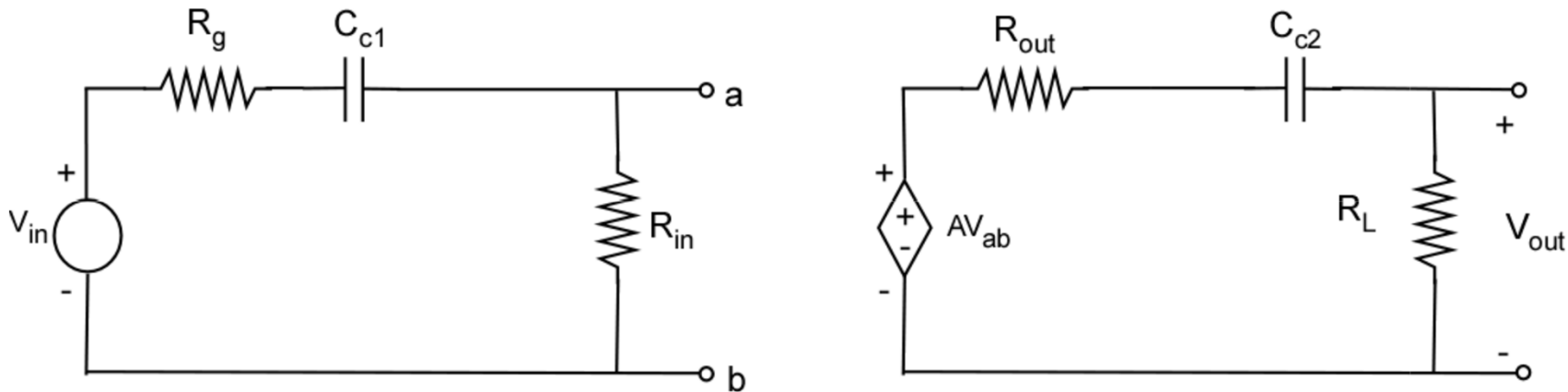
- Coupling capacitors are present
- Parasitic capacitors are open circuits



$$v_{ab} = \frac{v_{in} R_{in}}{R_g + R_{in} + \frac{1}{j\omega C_{c1}}} = \frac{v_{in} j\omega C_{c1} R_{in}}{1 + j\omega C_{c1} (R_g + R_{in})}$$

$$v_{ab} = v_{in} \frac{R_{in}}{R_g + R_{in}} \cdot \frac{j\omega C_{c1} (R_g + R_{in})}{\left[1 + j\omega C_{c1} (R_g + R_{in}) \right]}$$

MOSFET High-Frequency Model

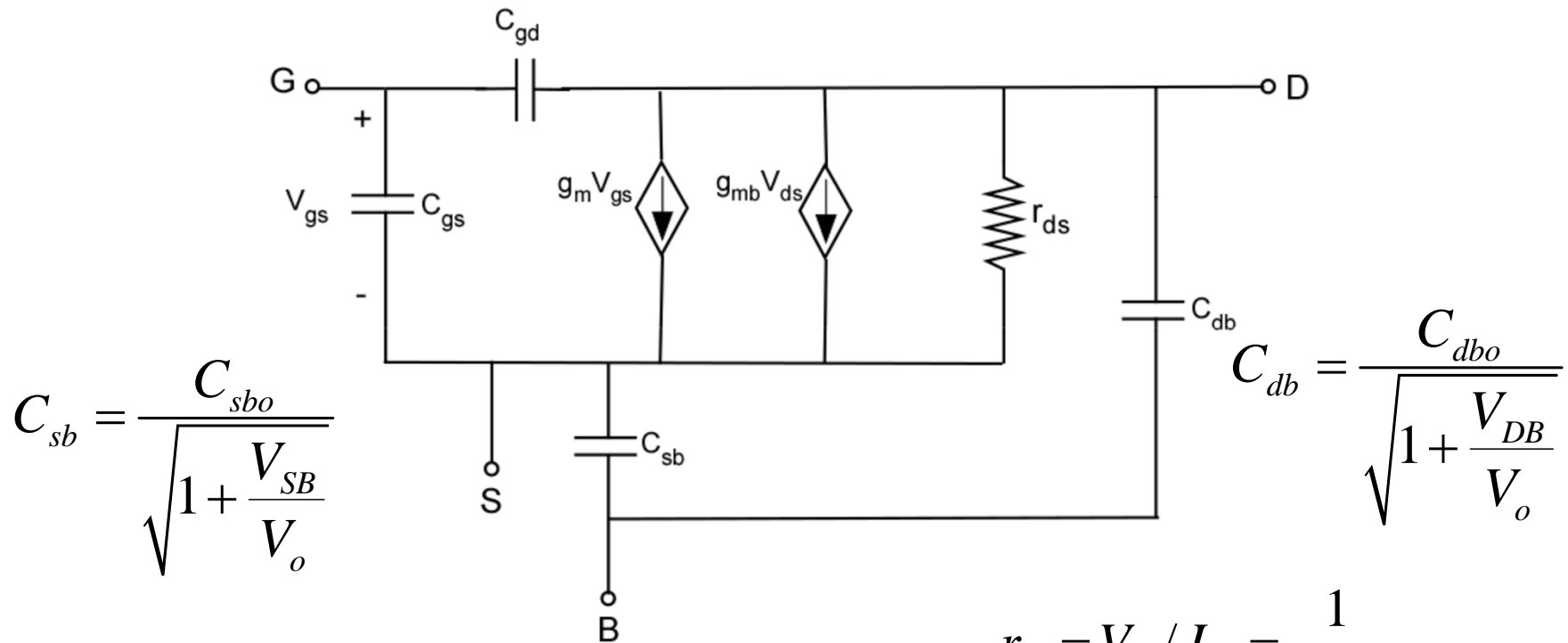

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}}$$

$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DB}}{V_o}}}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{eff} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{eff}}$$



$$g_{mb} = \chi g_m = \frac{\gamma}{2\sqrt{2\phi_F + V_{sb}}} g_m$$

$$r_{ds} = V_A / I_D = \frac{1}{\lambda I_D}$$

$$C_{gs} = \frac{2}{3} W L C_{ox} + W L_{ov} C_{ox}$$


$$C_{gd} = W L_{ov} C_{ox}$$

CS - Three Frequency Bands

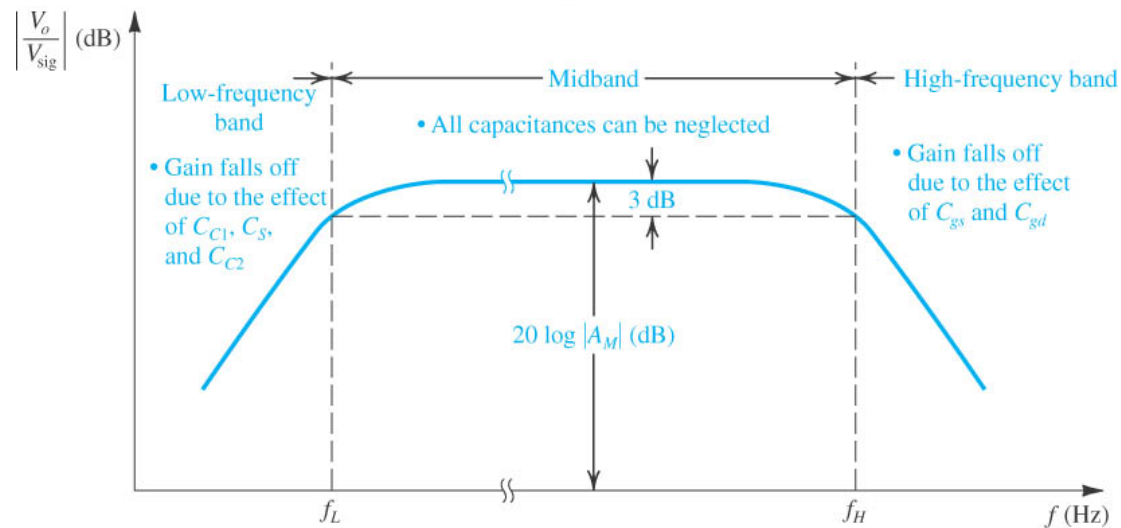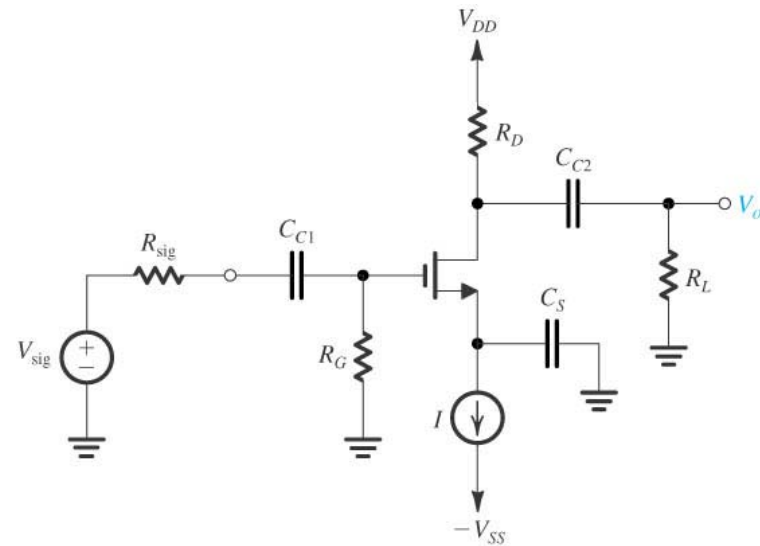

Unity-Gain Frequency f_T

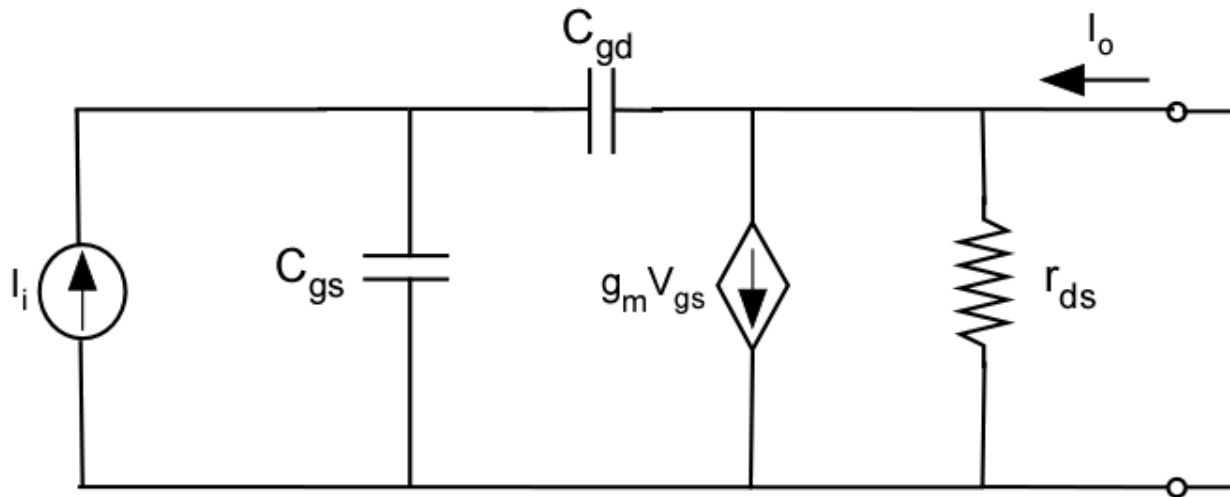f_T is defined as the frequency at which the short-circuit current gain of the common source configuration becomes unity



Define:
 $s = j\omega$

(neglect $sC_{gd}V_{gs}$ since C_{gd} is small)

$$I_o = g_m V_{gs} - sC_{gd} V_{gs} \qquad \frac{I_o}{I_i} = \frac{g_m}{s(C_{gs} + C_{gd})}$$

$$I_o \approx g_m V_{gs} \qquad V_{gs} = \frac{I_i}{s(C_{gs} + C_{gd})}$$


Calculating f_T

For $s=j\omega$, magnitude of current gain becomes unity at


$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}} \Rightarrow f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$f_T \sim 100$ MHz for 5- μm CMOS, $f_T \sim$ several GHz for 0.13 μm CMOS

CS - High-Frequency Response

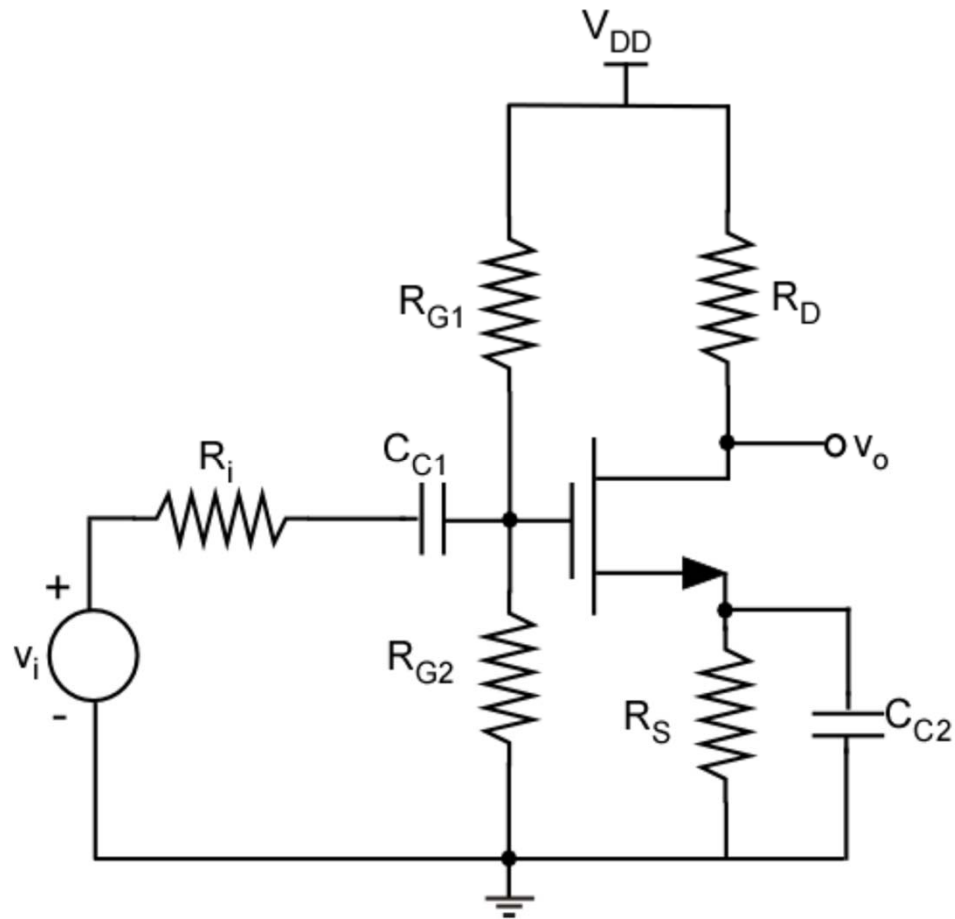

CS – Miller Effect – Exact Analysis

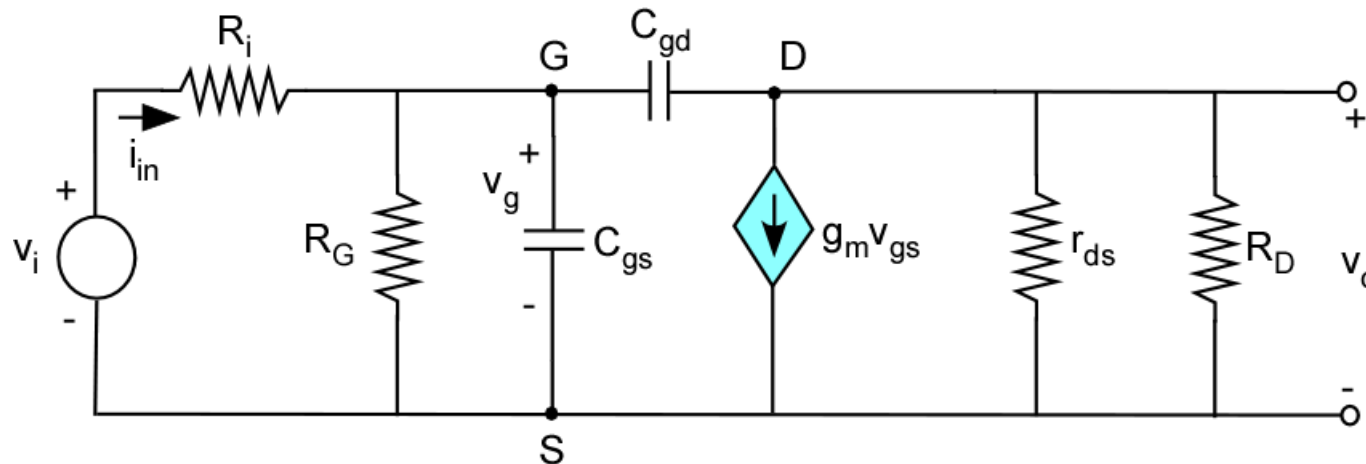

$$G_i = \frac{1}{R_i} \quad G_D = \frac{1}{R_D} \quad G_g = \frac{1}{R_g} \quad g_{ds} = \frac{1}{r_{ds}}$$

$$R'_D = R_D \parallel r_{ds} = \frac{1}{G_D + g_{ds}}$$

$$\frac{v_o}{v_i} = - \frac{G_i R'_D (g_m - s C_{gd})}{G_i + G_g + s [C_{gs} + C_{gd}] + s C_{gd} R'_D [G_i + G_g] + s C_{gd} g_m R'_D + s^2 C_{gd} C_{gs} R'_D}$$

CS – Miller Effect – Exact Analysis

We neglect the terms in s^2 since

$$\left|s^2 C_{gd} C_{gs} R'_D\right| \ll \left|s C_{gd} g_m R'_D\right| \quad \text{or} \quad \left|s C_{gs}\right| \ll \left|g_m\right|$$

$$\frac{v_o}{v_i} = - \frac{G_i R'_D (g_m - s C_{gd})}{G_i + G_g + s \left[C_{gs} + \underbrace{C_{gd} (1 + g_m R'_D)}_{\text{Miller}} + C_{gd} R'_D (G_i + G_g) \right]}$$

If we multiply through by $R_i = \frac{1}{G_i}$

CS – Miller Effect – Exact Analysis

$$\frac{v_o}{v_i} = - \frac{R'_D (g_m - sC_{gd})}{1 + R_i G_g + s \left\{ R_i \left[C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D (1 + R_s G_g) \right\}}$$

From which we extract the 3-dB frequency point

$$f_H = \frac{1 + R_i G_g}{2\pi \left\{ R_i \left[C_{gs} + C_{gd} (1 + g_m R'_D) \right] + C_{gd} R'_D (1 + R_i G_g) \right\}}$$

CS – Miller Effect – Exact Analysis

If G_g is negligible

$$f_H = \frac{1}{2\pi \left\{ R_i \left[C_{gs} + C_{gd} \left(1 + g_m R'_D \right) \right] + C_{gd} R'_D \right\}}$$

If $R_i = 0$

$$f_H = \frac{1}{2\pi C_{gd} R'_D}$$

Transfer Function Representation

In general, the transfer function of an amplifier can be expressed as

$$F_H(s) = a_m \frac{(s - Z_1)(s - Z_2) \dots (s - Z_m)}{(s - P_1)(s - P_2) \dots (s - P_m)}$$

Z_1, Z_2, \dots, Z_m are the **zeros** of the transfer function

P_1, P_2, \dots, P_m are the **poles** of the transfer function

s is a complex number $s = \sigma + j\omega$

3dB Frequency Determination

$$A(s) \equiv A_M F_H(s)$$

- Designer is interested in midband operation
- However needs to know upper 3-dB frequency
- In many cases some conditions are met:
 - Zeros are infinity or at very high frequencies
 - One of the poles (ω_{P1}) is at much lower frequency than other poles (→ dominant pole)
- If the conditions are met then $F_H(s)$ can be approximated by:

$$F_H(s) \equiv \frac{1}{1 + s / \omega_{P1}} \quad \text{and we have} \quad \omega_H \cong \omega_{P1}$$

3dB Frequency Determination

If the lowest frequency pole is at least 4 times away from the nearest pole or zero, it is a **dominant pole**

If there is no dominant pole, the 3-dB frequency ω_H can be approximated by:

$$\omega_H \cong 1 / \sqrt{\left(\frac{1}{\omega_{P1}^2} + \frac{1}{\omega_{P2}^2} + \dots \right) - 2 \left(\frac{1}{\omega_{Z1}^2} + \frac{1}{\omega_{Z2}^2} + \dots \right)}$$

Open-Circuit Time Constants

$$F_H(s) = \frac{1 + a_1s + a_2s^2 + \dots + a_ns^n}{1 + b_1s + b_2s^2 + \dots + b_ns^n}$$

The coefficients a and b are related to the frequencies of the zeros and poles respectively.

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \dots + \frac{1}{\omega_{pn}}$$

b_1 can be obtained by summing the individual time constants of the circuit using the *open-circuit time constant method*

Open-Circuit Time Constant Method

- The time constant of each capacitor in the circuit is evaluated. It is the product of the capacitance and the resistance seen across its terminals with:
 - All other internal capacitors open circuited
 - All independent voltage sources short circuited
 - All independent current sources opened
- The value of b_1 is computed by summing the individual time constants

$$b_1 = \sum_{i=1}^n C_i R_{i_o}$$

Open-Circuit Time Constant Method

- An approximation can be made by using the value of b_1 to determine the 3dB upper frequency point ω_H
- If the zeros are not dominant and if one of the poles P_1 is dominant, then

$$b_1 = \frac{1}{\omega_{P1}}$$

Assuming that the 3-dB frequency will be approximately equal to ω_{P1}

$$\omega_H = \frac{1}{b_1} = \frac{1}{\sum_i C_i R_{io}}$$

Bandwidth of Multistage Amplifier

- The poles of a multistage amplifier are difficult to obtain analytically
- An approximate value for the 3dB upper frequency point ω_{3dB} can be obtained by assigning an open circuit time constant τ_{i0} to each capacitor C_i


Bandwidth of Multistage Amplifier

- The time constant τ_{i0} is the product of the capacitance and the resistance seen across its terminals with:
 - All other internal capacitors open circuited
 - All independent voltage sources short circuited
 - All independent current sources opened
- The upper 3dB frequency point ω_{3dB} is then found by using :

$$\omega_{3dB} = \frac{1}{\sum \tau_{i0}}$$

MOSFET Amp Bandwidth

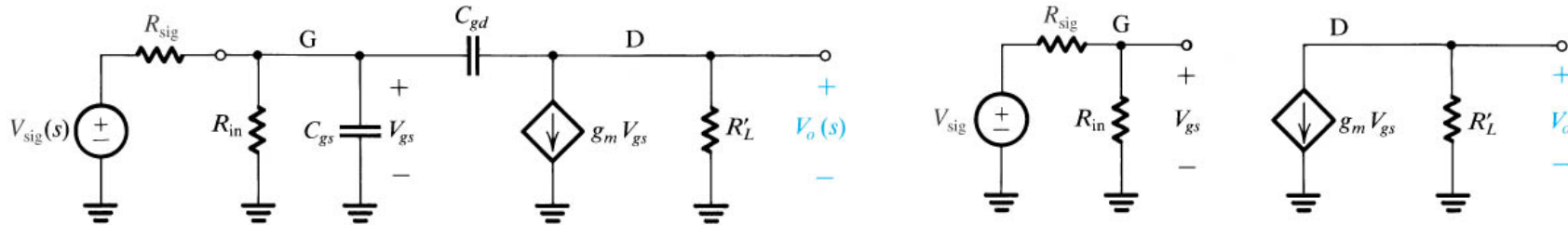
MOSFET amplifier has $R_{sig} = 100 \text{ k}\Omega$, $C_{gs} = C_{gd} = 1 \text{ pF}$, $g_m = 4 \text{ mA/V}$ and $R_L' = 3.33 \text{ k}\Omega$. Find midband voltage gain and 3-dB frequency.



$$A_M = \frac{V_o}{V_{sig}} = -\frac{R_{in}}{R_{in} + R_{sig}} (g_m R_L') = -\frac{420}{420 + 100} \times 4 \times 3.33 = -10.8$$

MOSFET Amp Analysis

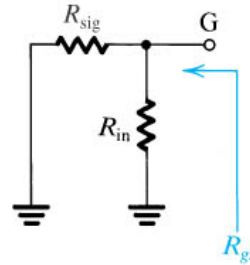To determine the 3-dB frequency, we first evaluate the time constant associated with C_{gs} . First, we determine the resistance R_{gs} seen by C_{gs} . The capacitance C_{gd} is removed and V_{sig} is short-circuited




$$R_{gs} = R_{in} \parallel R_{sig} = 420 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 80.8 \text{ k}\Omega$$

The time constant associated with C_{gs} is

$$\tau_{gs} = C_{gs} R_{gs} = 1 \times 10^{-12} \times 80.8 \times 10^3 = 80.8 \text{ ns}$$

MOSFET Amp Analysis

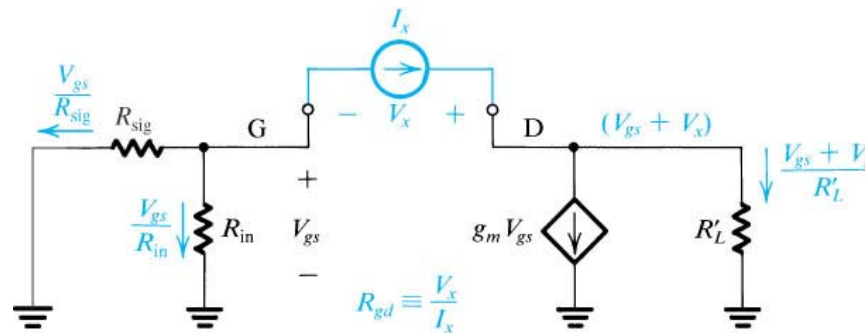The resistance R_{gd} seen by C_{gd} is found by setting $C_{gs} = 0$ and short-circuiting V_{sig}



$$I_x = -\frac{V_{gs}}{R_{in}} - \frac{V_{gs}}{R_{sig}}$$

$$V_{gs} = -I_x R'$$

$$R' = R_{in} \parallel R_{sig}$$

$$I_x = g_m V_{gs} + \frac{V_{gs} + V_x}{R'_L}$$

$$R_{gd} = \frac{V_x}{I_x} = R' + R'_L + g_m R'_L R'$$

MOSFET Amp Analysis

The open-circuit time constant of C_{gd} is

$$\tau_{gd} = C_{gd} R_{gd} = 1 \times 10^{-12} \times 1.16 \times 10^6 = 1160 \text{ ns}$$

The upper 3-dB frequency ω_H can now be determined from

$$\omega_H = \frac{1}{\tau_{gs} + \tau_{gd}} = \frac{1}{(80.8 + 1160) \times 10^{-9}} = 806 \text{ krad / s}$$

$$f_H = \frac{\omega_H}{2\pi} = 128.3 \text{ kHz}$$