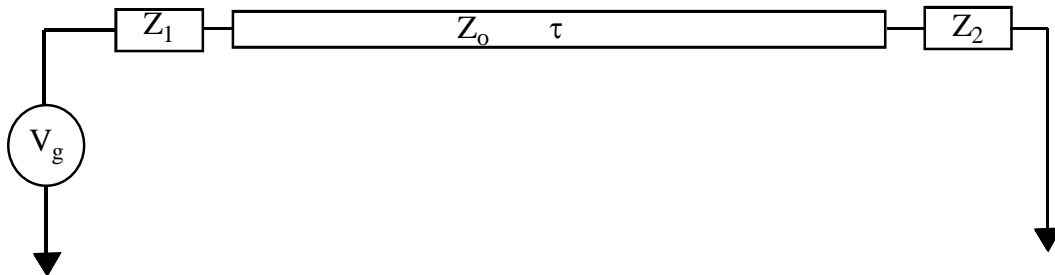


ECE 546 HOMEWORK No 3 Due Wednesday, February 17, 2016

1. Write a program that simulates the response (voltage at near and far ends) of a lossless transmission line terminated with linear resistive loads. Test your program using the example shown below . Use $Z_0 = 75 \Omega$, $\tau = 2.37 \text{ ns}$, $Z_1 = 50 \Omega$, $Z_2 = 1 \text{ K}\Omega$. Optimize your code to minimize run time. Show plots of the pulse response at the near and far ends of the line. Give a listing of your program.



The pulse characteristics for $V_g(t)$ are as shown in the figure below, with


time delay: $t_d = 1 \text{ ns}$


rise time: $t_r = 1 \text{ ns}$

fall time: $t_f = 1 \text{ ns}$

pulse width: $t_w = 20 \text{ ns}$

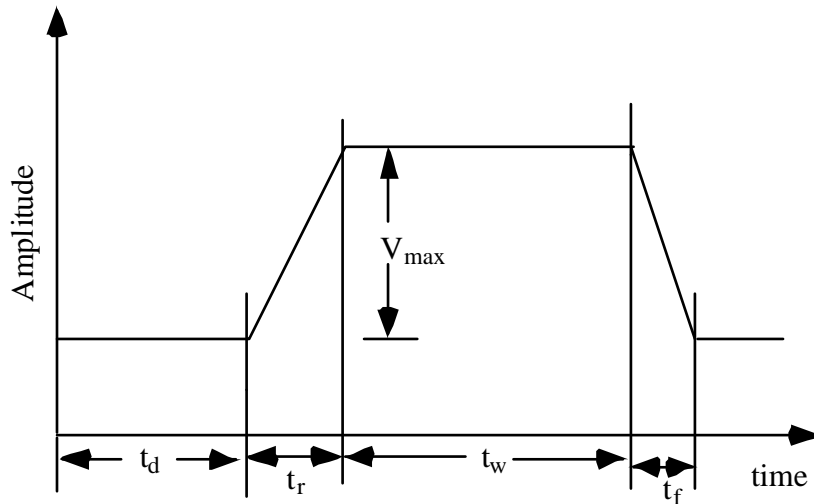pulse amplitude: $V_{\text{max}} = 4 \text{ volts}$



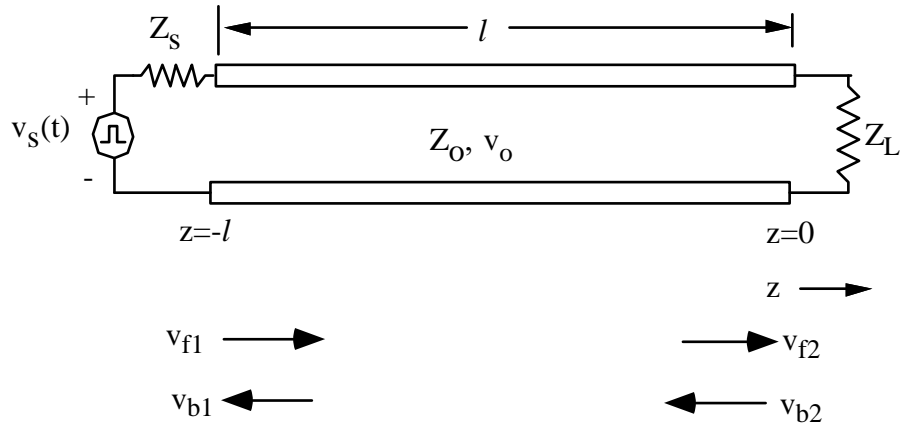

Use the following equations:

$$v_{f1}(t) = \Gamma_1 v_{b2}(t - \tau) + T_1 v_s(t) \quad v_{b2}(t) = \Gamma_2 v_{f1}(t - \tau)$$

$$v_{f2}(t) = v_{f1}(t - \tau) \quad v_{b1}(t) = v_{b2}(t - \tau)$$

$$v_1(t) = v_{f1}(t) + v_{b1}(t) \quad v_2(t) = v_{f2}(t) + v_{b2}(t)$$

$\tau = l/v$ time delay

$$\Gamma_1 = \frac{Z_s - Z_0}{Z_s + Z_0}$$

$$\Gamma_2 = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$T_1 = \frac{Z_0}{Z_s + Z_0}$$

