


1. Write a code to simulate the response of a lossy twisted-pair 100-meter cable terminated with linear resistive loads. Test your program using the example shown below. Use  $Z_1 = 50 \Omega$  and  $Z_2 = 10 \text{ K}\Omega$ .

The parameters of the cable are  $L = 145 \text{ nH/m}$ ,  $C = 14 \text{ pf/m}$ . The skin effect resistance is:  $R_o = 5.0 \Omega / m - \sqrt{\text{GHz}}$ . Show near and far end plots for two different loss models:

(a)  $Z(f) = R_o \sqrt{f} + jL\omega$

(b)  $Z(f) = R_o \sqrt{f} + jR_o \sqrt{f} + jL\omega$

Which model is correct? Why?

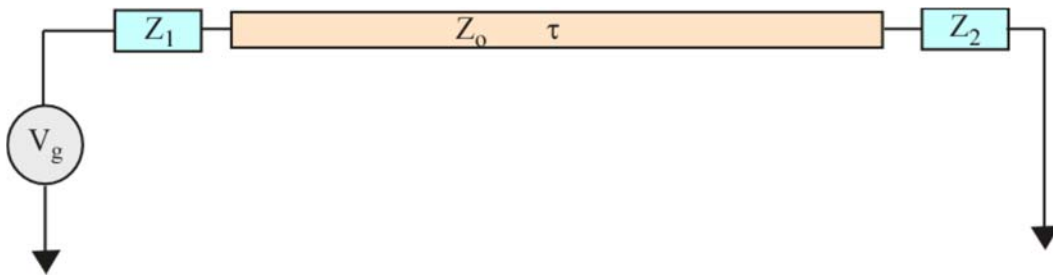

The pulse characteristics for  $V_g(t)$  are as shown in the figure below, with time delay:  $t_d = 5 \text{ ns}$ , rise time:  $t_r = 2 \text{ ns}$ , fall time:  $t_f = 2 \text{ ns}$ , pulse width:  $t_w = 20 \text{ ns}$ , pulse amplitude:  $V_{\text{max}} = 1 \text{ volt}$

